

Lecture 32

1st Order Transients – 3 of 5

extensions and examples



Other Stuff

- Time invariance; for switch at $t = t_0$



$$x(t) = x(\infty) + (x(t_0) - x_\infty)e^{-(t-t_0)/\tau} + x_\infty$$

- Unit step function

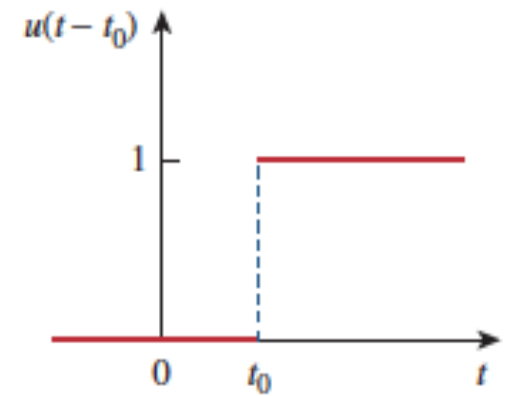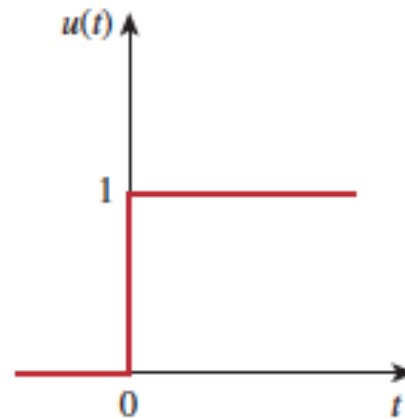
$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$




might replace the switch

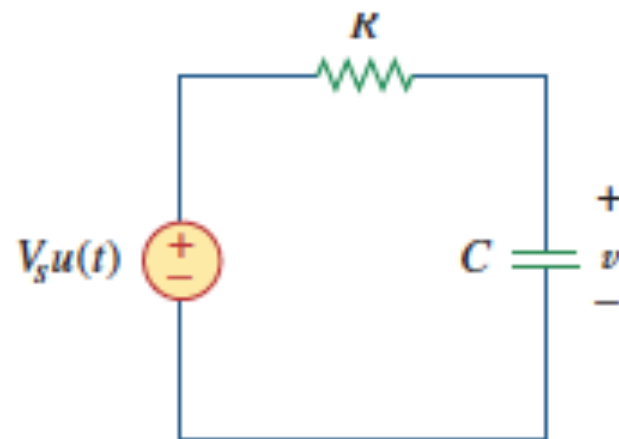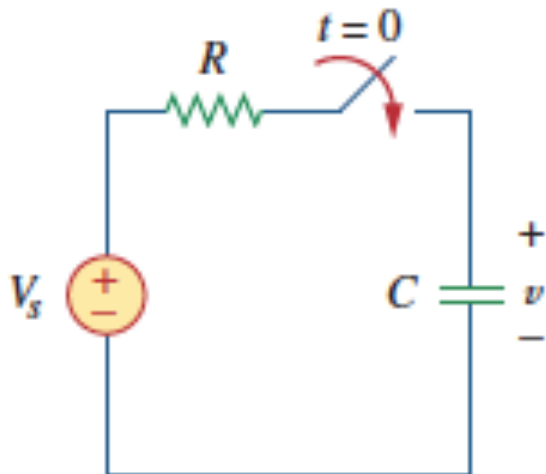

Example: note the 4 seconds

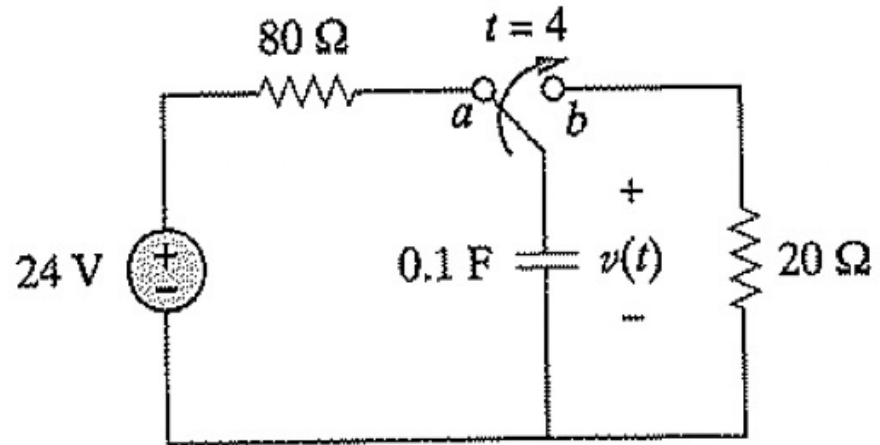

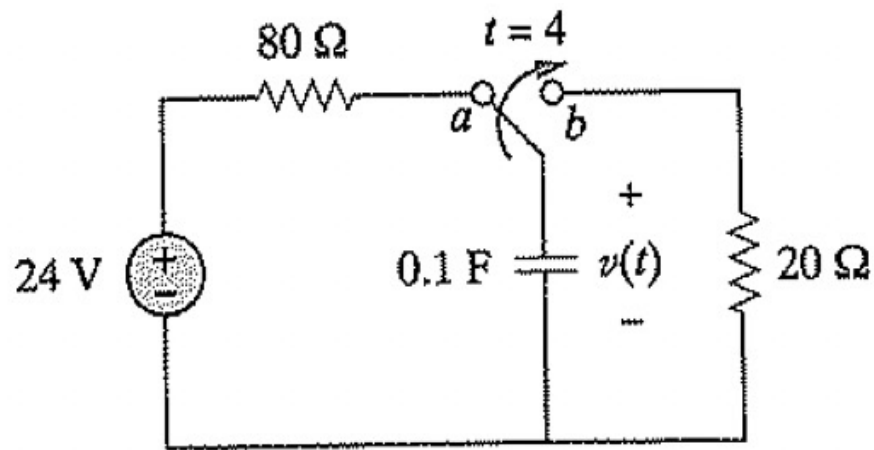

$a \rightarrow b$:

$$v(4) = 24 \text{ V}$$

$$v_{\infty} = 0 \text{ V}$$

$$R_{Th} = 20 \Omega$$


$b \rightarrow a$:


$$v(4) = 0 \text{ V}$$

$$v_{\infty} = 24 \text{ V}$$

$$R_{Th} = 80 \Omega$$

Example: switch opens

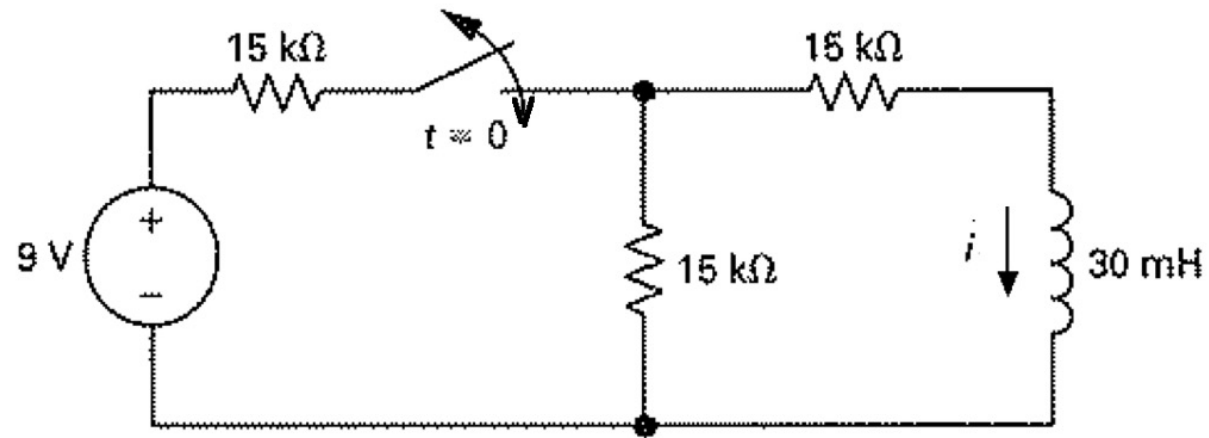

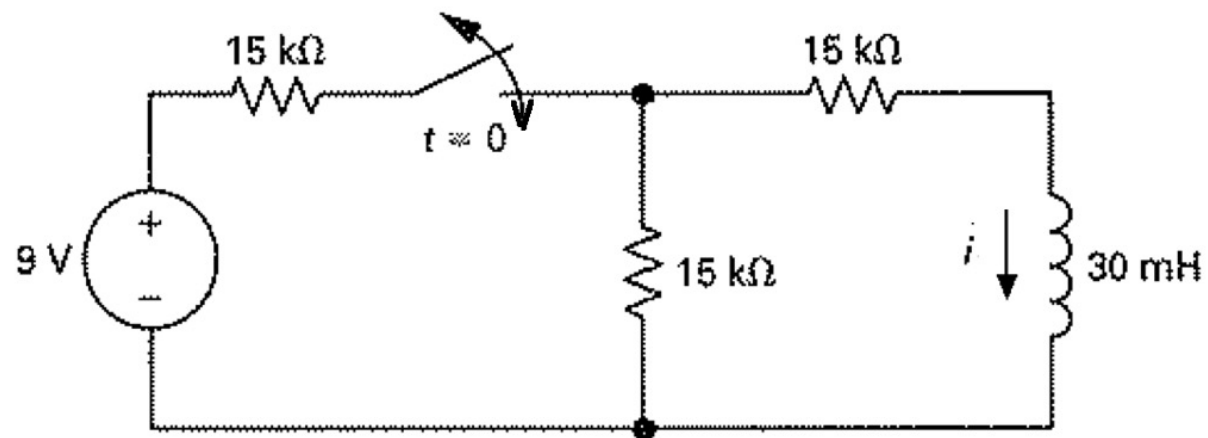


Opening at zero:

$$i_0 = 0.2 \text{ mA}$$

$$i_\infty = 0 \text{ mA}$$

$$R_{Th} = 30 \text{ k}\Omega$$

Example: switch closes

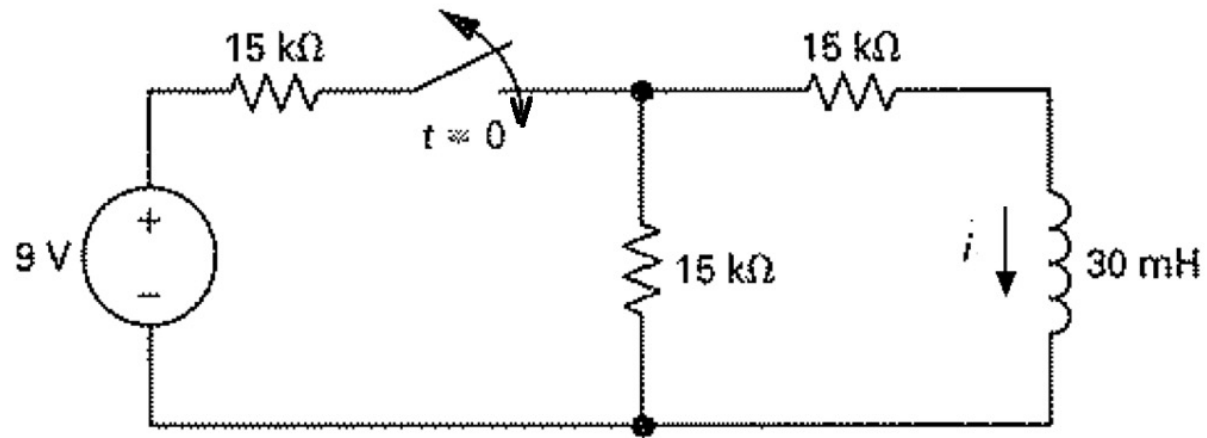


Closing at zero:


$$i_0 = 0 \text{ mA}$$

$$i = 0.2 \text{ mA}$$

$$R_{Th} = 22.5 \text{ k}\Omega$$


Example: switch moves from a to b

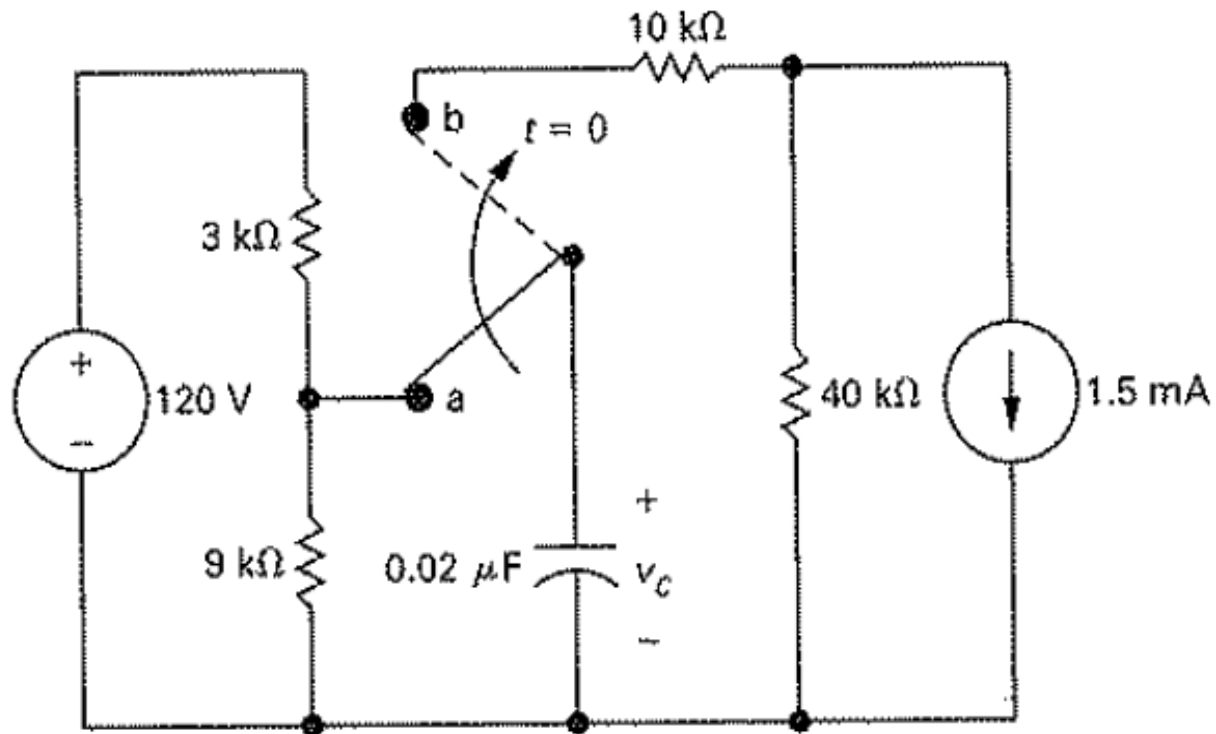


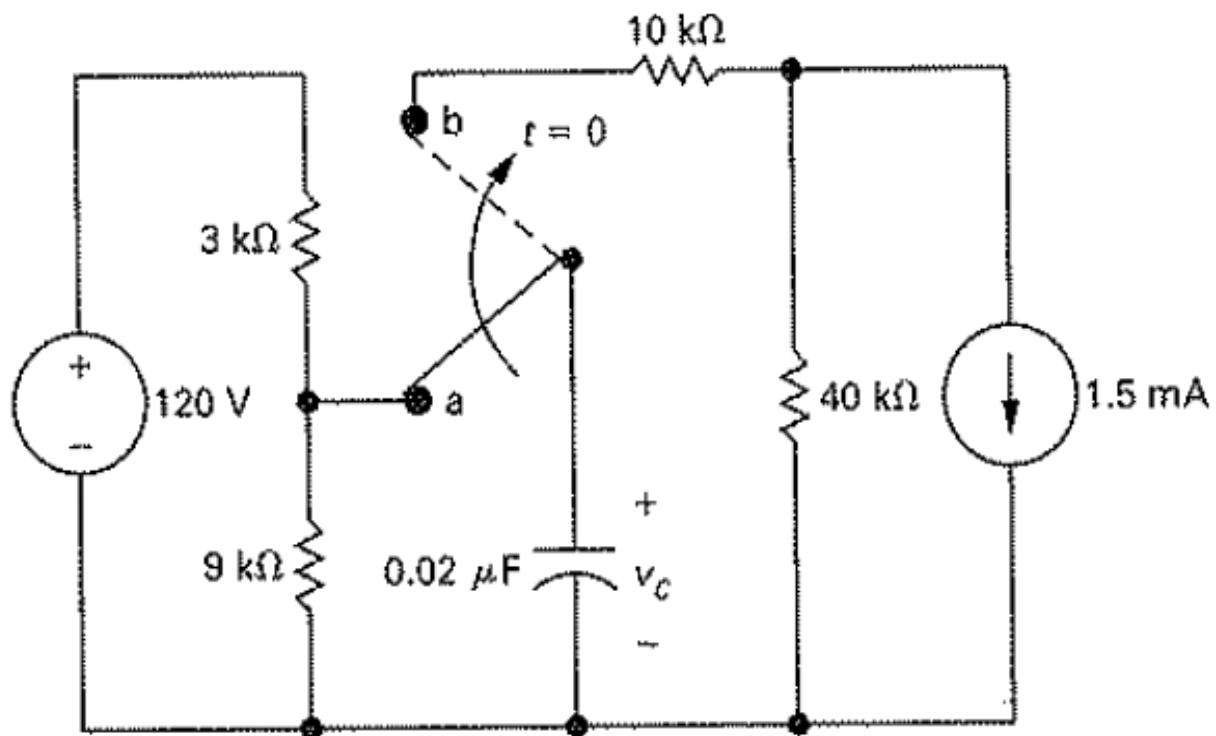

$$\begin{aligned}
 v_0 &= 90 \text{ V} \\
 v_\infty &= -60 \text{ V} \\
 R_{Th} &= 50 \text{ k}\Omega
 \end{aligned}$$


Practice problem: find $i(t)$

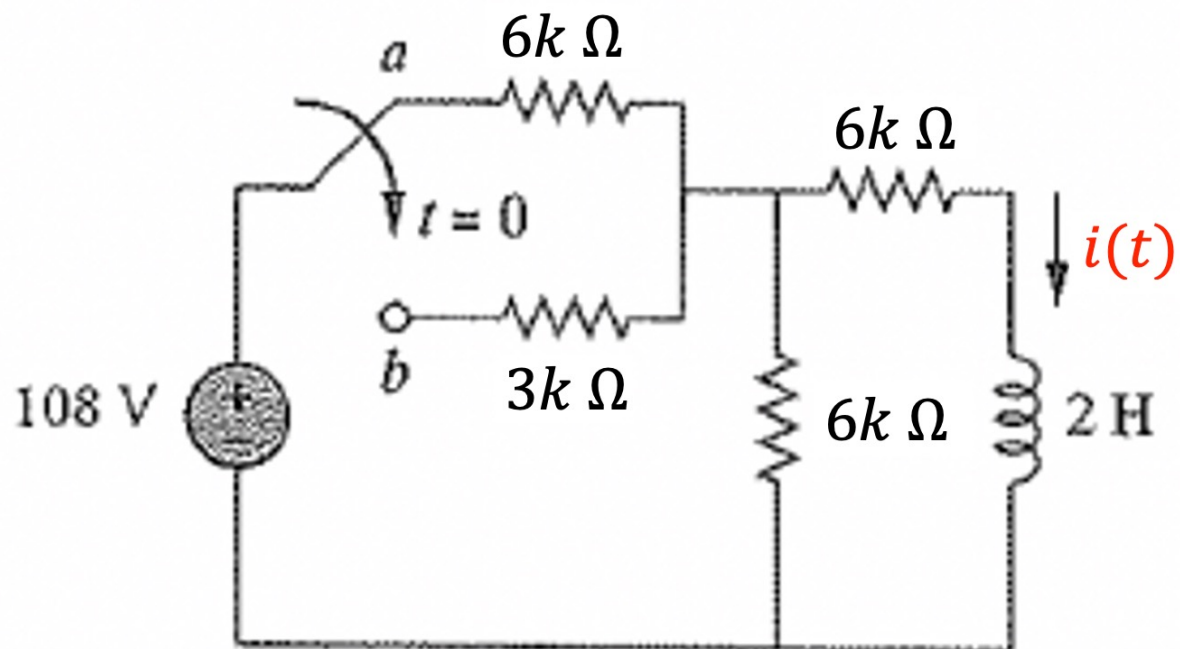


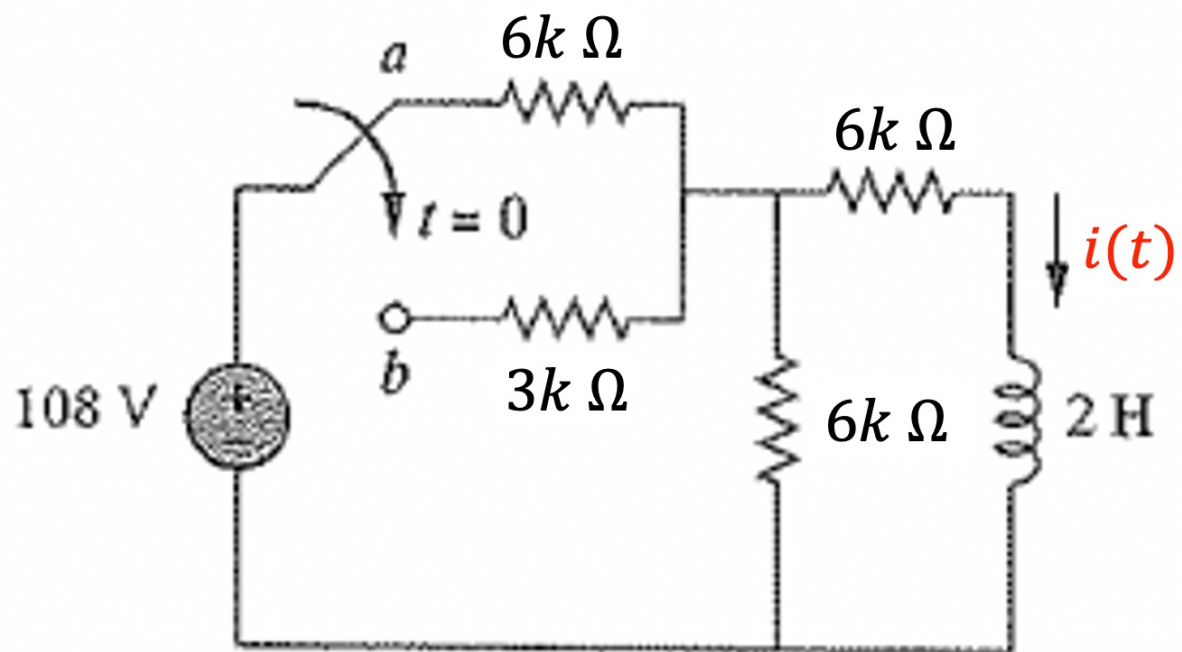

$$i(t) = -3 e^{-4000t} + 9\text{ mA}$$

Practice problem:

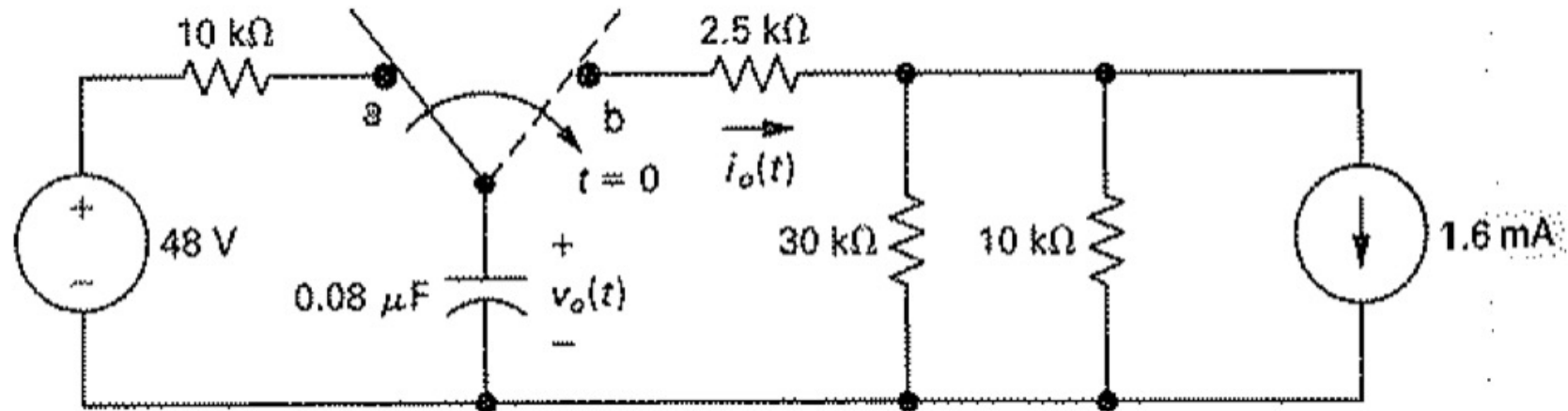


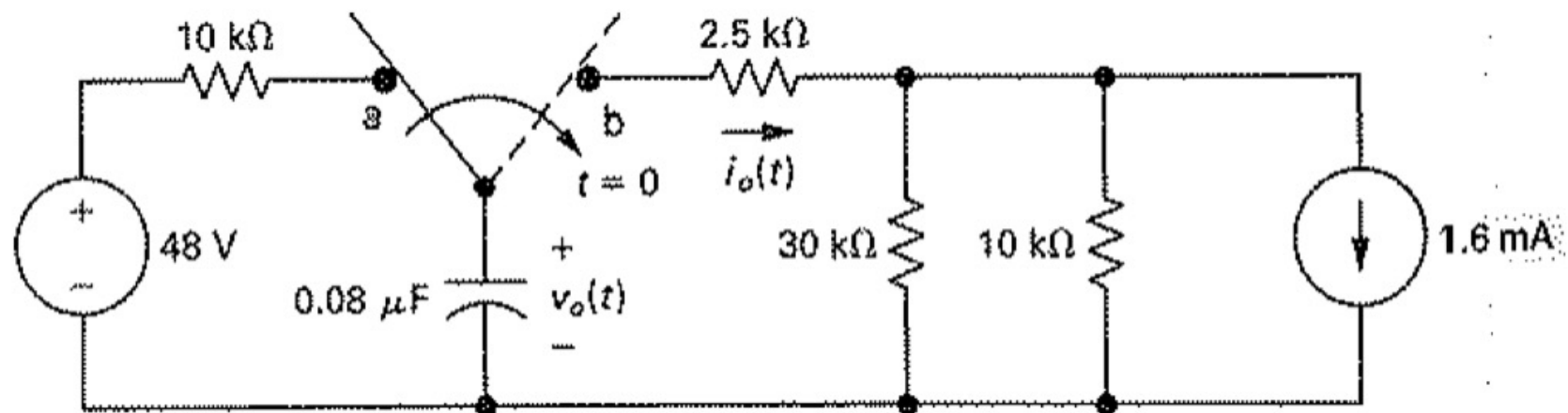

$$v(t) = 60 e^{-125t} - 12\text{ V}$$


$$v(t) = 12 e^{-t} - 24 \text{ V}$$

Practice problem:

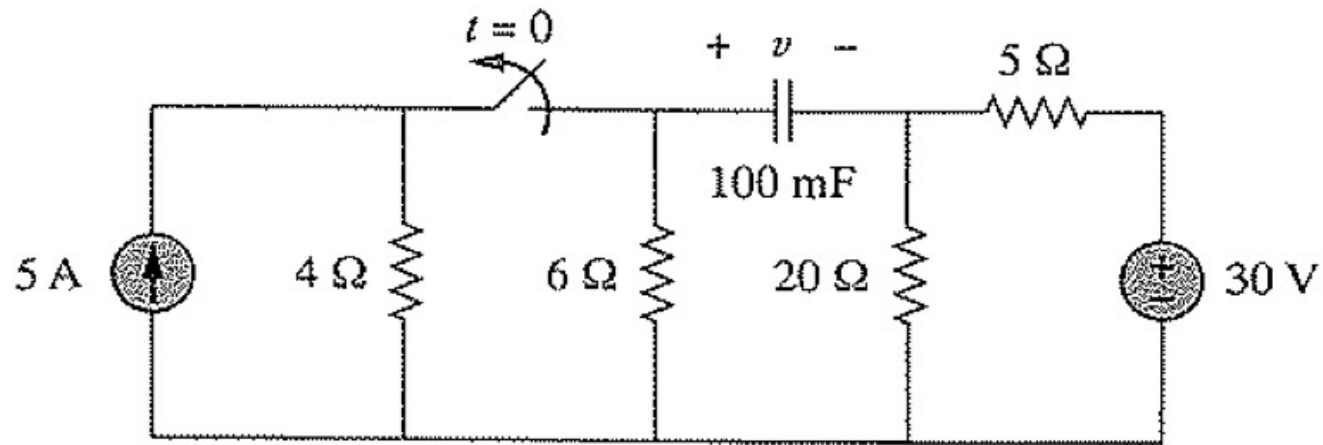

$$v(t) = -6e^{-t/21} + 10 \text{ V}$$

Practice problem:

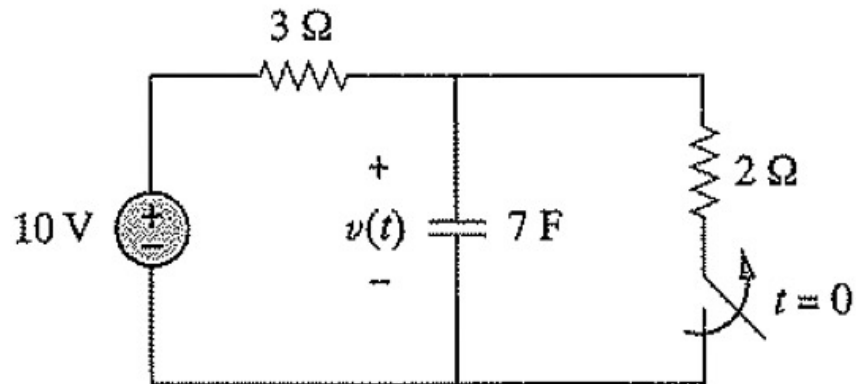

Practice problem:

$$v(0) = 28 \text{ V}$$

$$v_{\infty} = 14.0 \text{ V}$$

$$R = 54.8 \Omega$$

