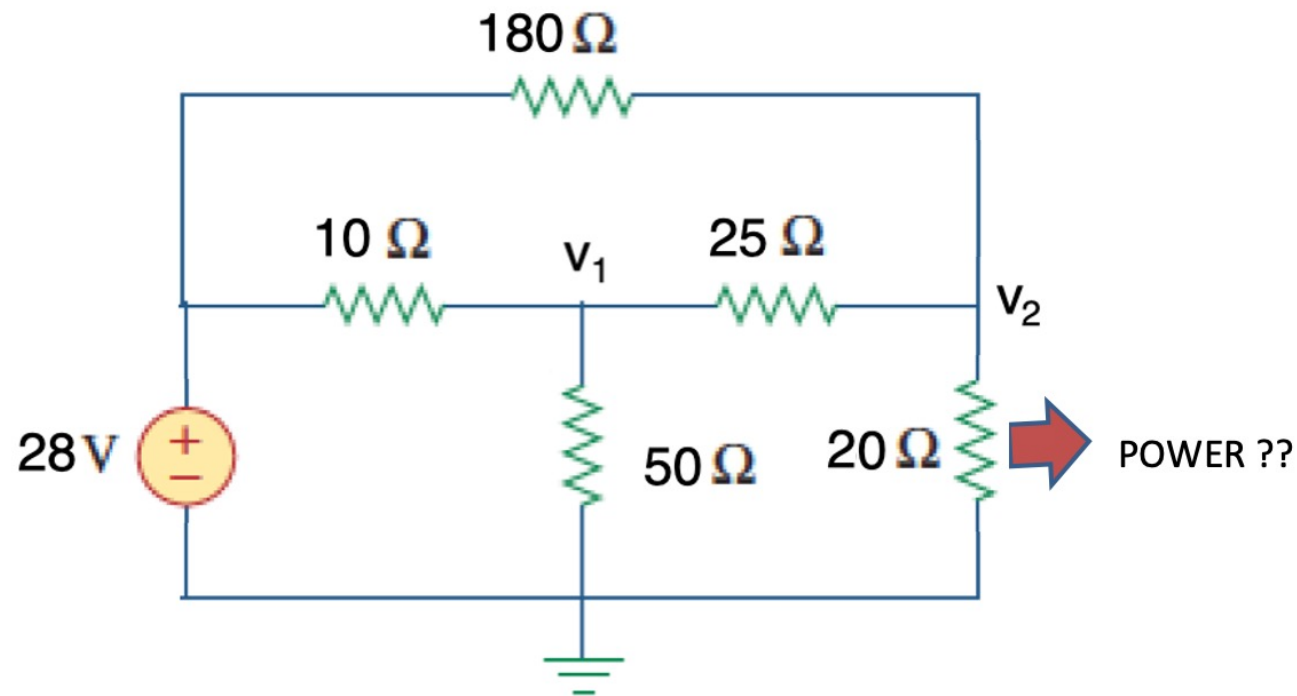


Lecture 27

Theorems – 4 of 6


maximum power transfer

Power Transfer




- How much power is dissipated in the 20 Ω resistor?
 - Method: node analysis $\rightarrow v_2 = 10 \text{ V}$
 - Power calculation $P = \frac{v_2^2}{20} = \frac{10^2}{20} = 5 \text{ W}$

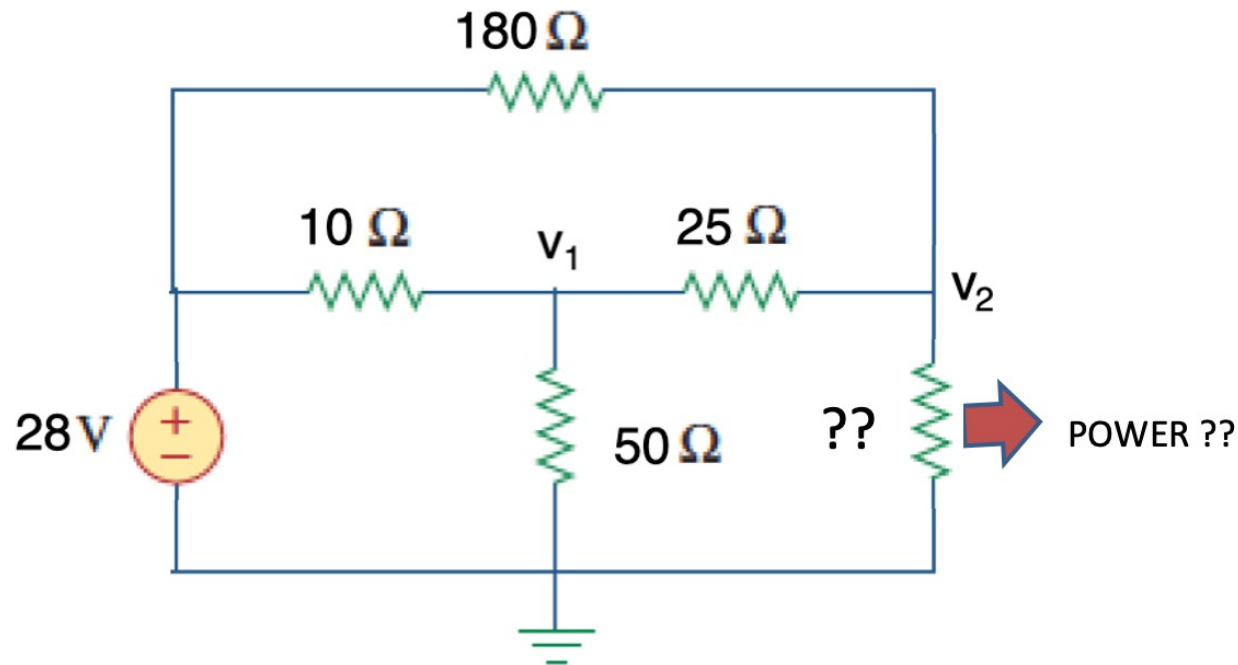- Question – if the resistance was larger/smaller than $20\ \Omega$ could it take more power from the circuit?



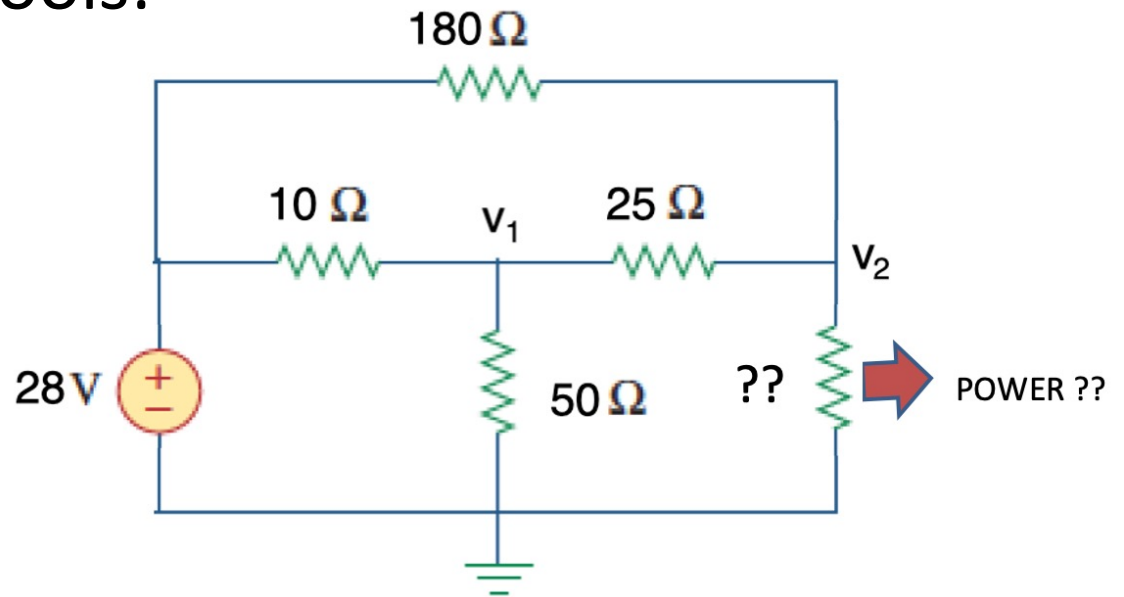- Approach 1 – solve for power in terms of R
 - MatLab symbolic tools:



%% setup problem

`syms v1 v2 R`

`[s1,s2] = solve(v1/50+(v1-28)/10+(v1-v2)/25==0, ...`

`v2/R+(v2-v1)/25+(v2-28)/180==0,v1,v2)`

`pow = s2^2/R;`

%% check for R = 20 ohms

`subs(s2,R,20)`

`subs(pow,R,20)`

`ans =`

`10`

`ans =`

`5`


- Optimize

% optimize over R

`dpow = diff(pow,R);`

`Rstar = solve(dpow)`

`eval(subs(pow,R,Rstar))`

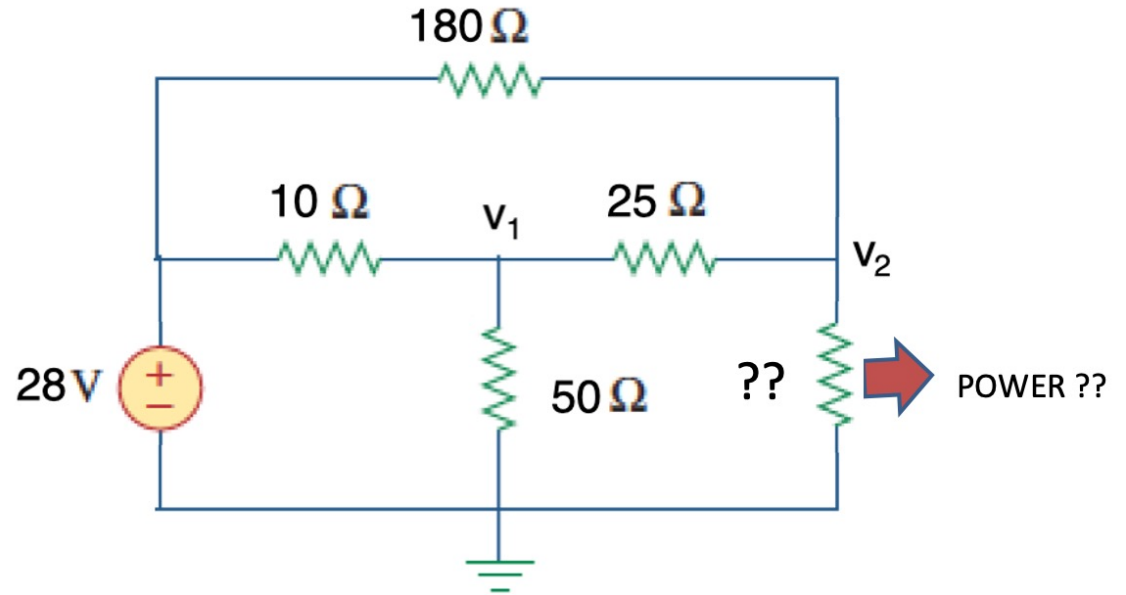

`Rstar =`

`225/8`

`ans =`



`5.1467e+00`

$$R^* = \frac{225}{8} = 28.1 \, \Omega$$

$$P_{max} = 5.15 \, W$$

- What's going on?


$$P = \frac{148225 R}{4 (8R + 225)^2}$$

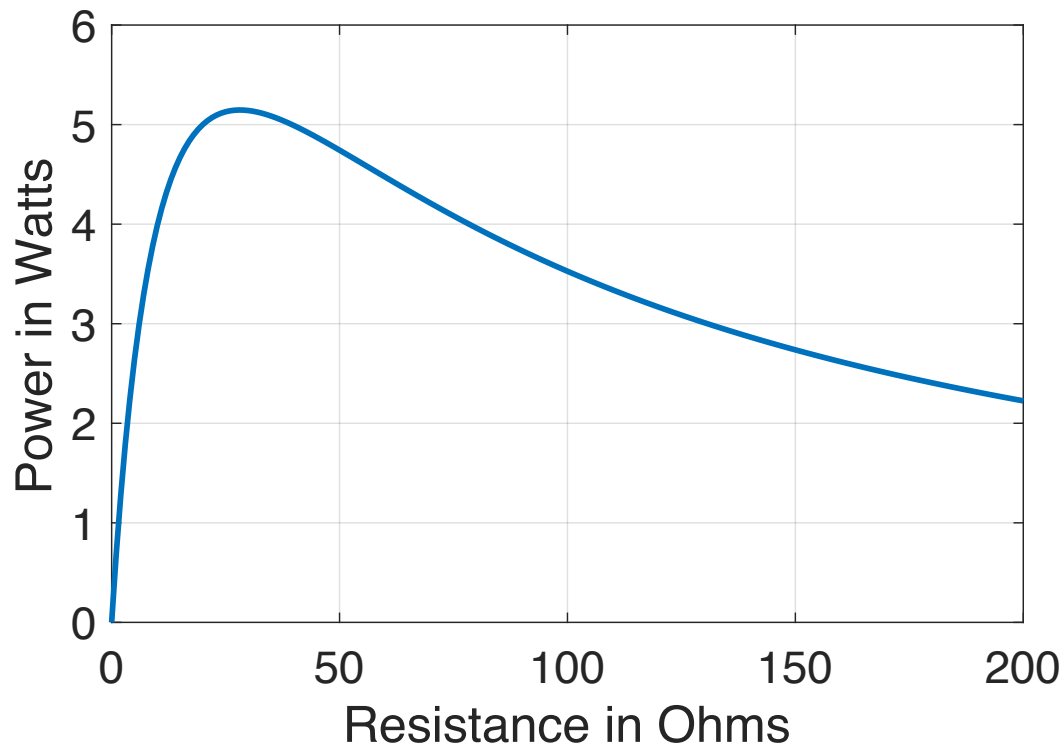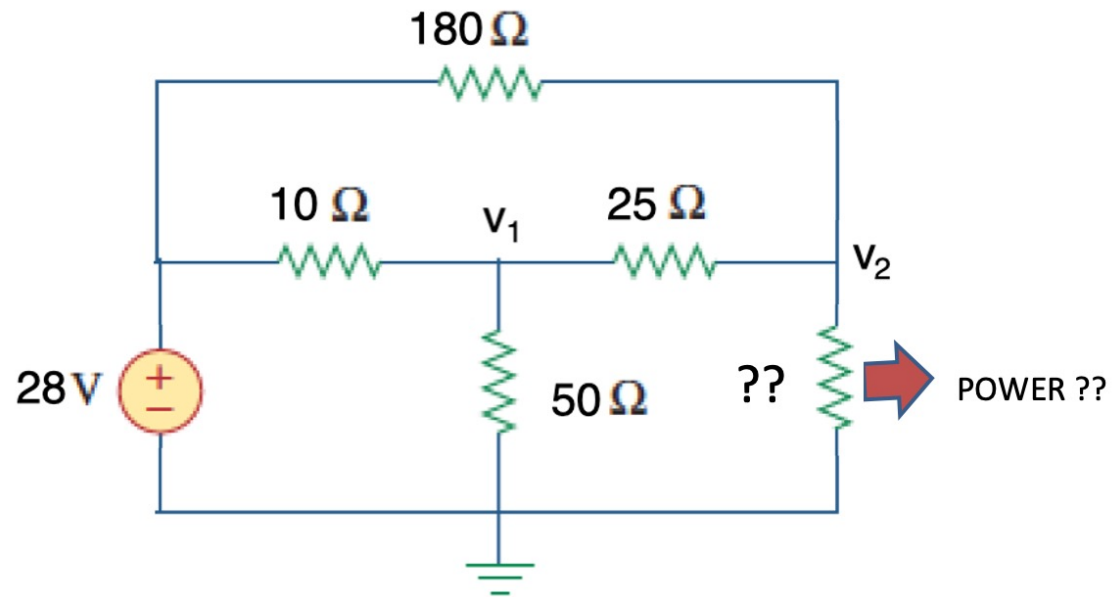



```
Rv = 0:200;
Pv = subs(pow,Rv);
plot(Rv,Pv)
```

Maximum Power Transfer

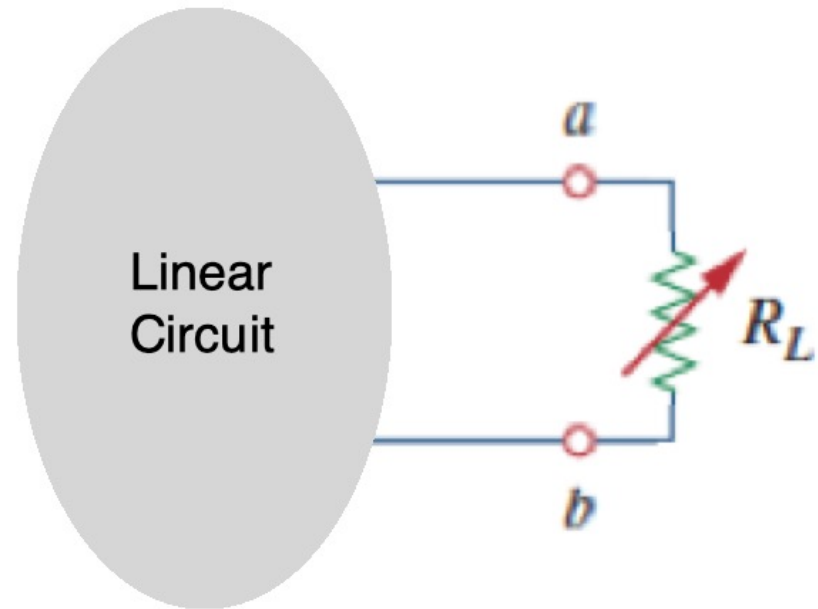- Consider connecting a “load” resistance, R_L , across two points of a circuit
- What happens as it varies?
 - Current
 - Voltage
 - Power



- Use the Thevenin model

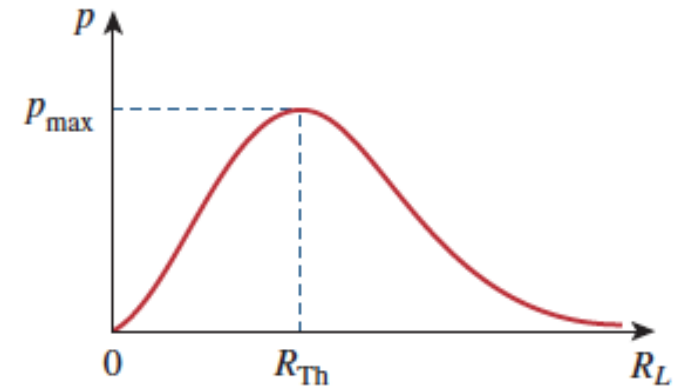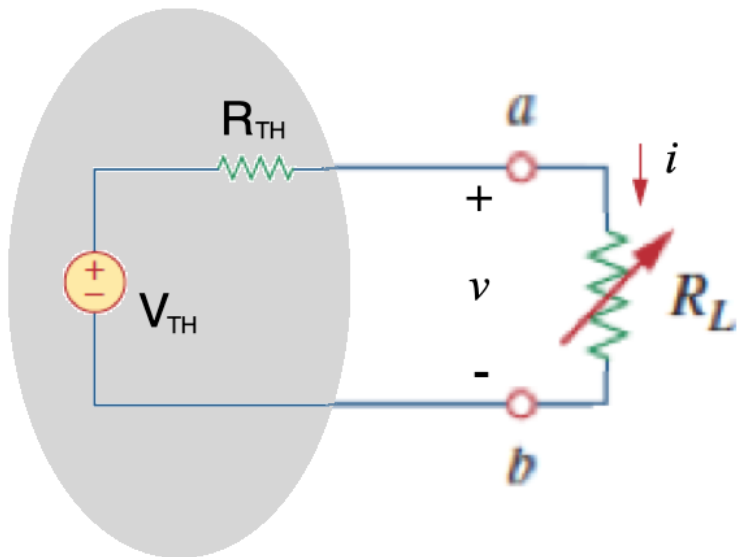


$$v = \frac{R_L}{R_L + R_{th}} v_{th}$$

$$p = \frac{v^2}{R_L} = \frac{R_L}{(R_L + R_{th})^2} v_{th}^2$$


- $\frac{\partial p}{\partial R_L} = 0$ yields a max of $P_{max} = \frac{V_{th}^2}{4R_{th}}$ when $R_L = R_{th}$


Example: find a load resistance to dissipate maximum power

$20\ \Omega, 20\ W$

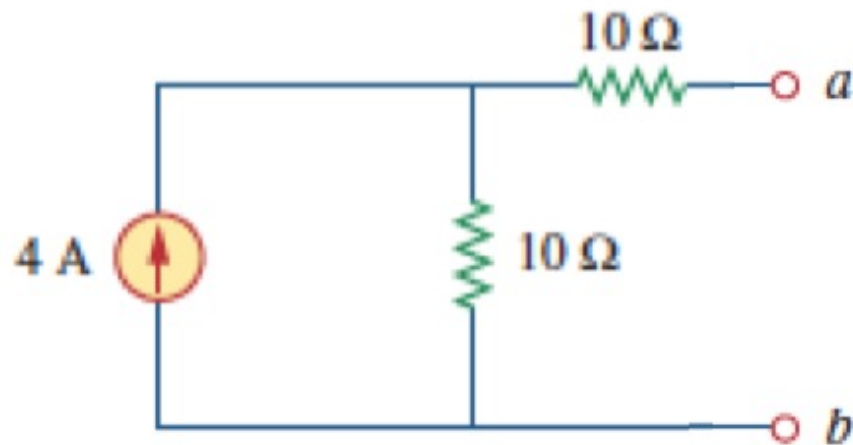

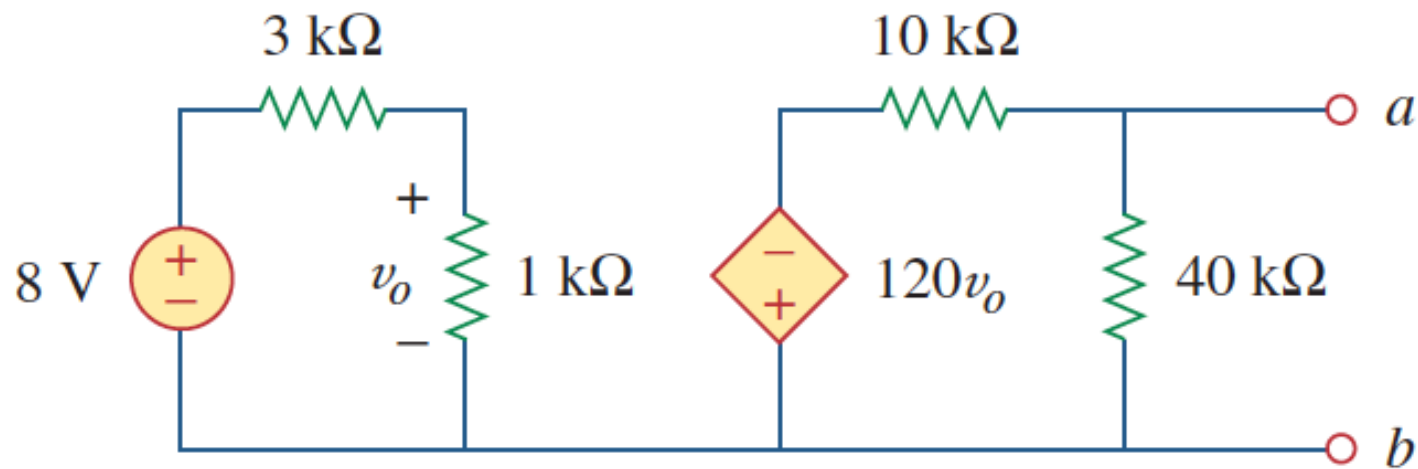
Example: find the load that dissipates maximum power



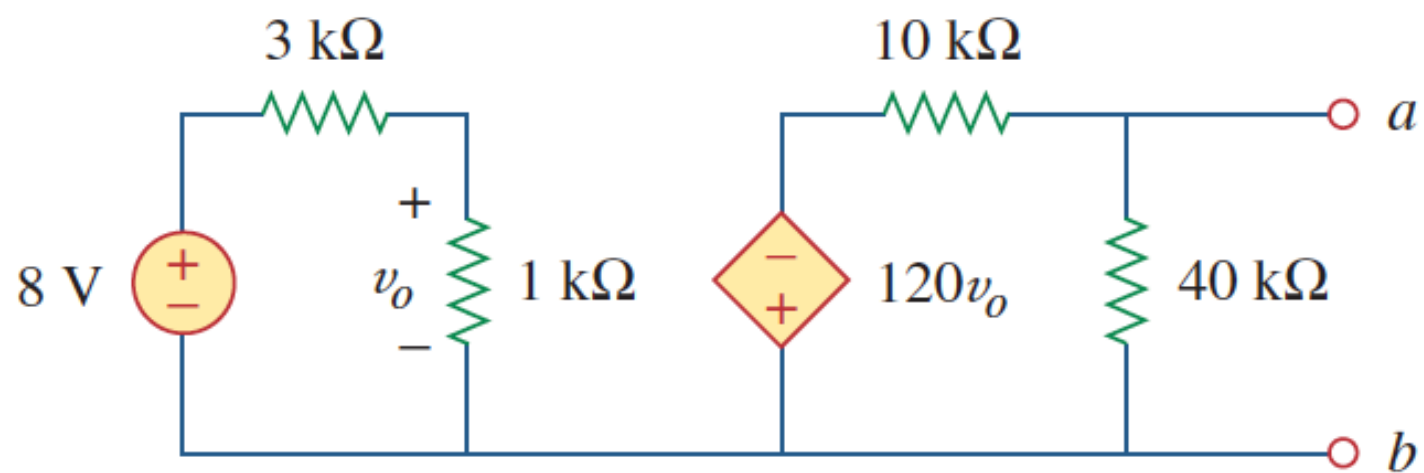


$8\text{ k}\Omega$

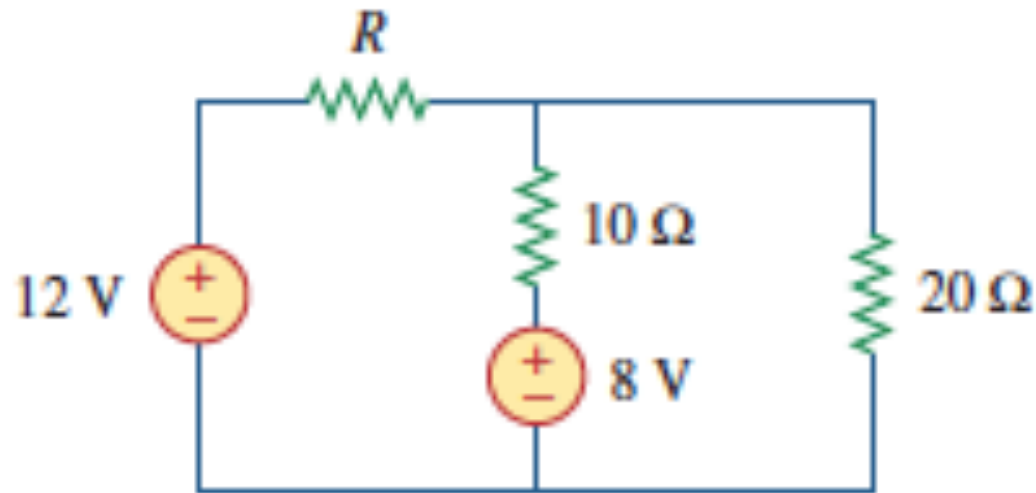Example (trick): find R to maximum the power delivered to the $10\ \Omega$ resistor




$$1.6 \, \Omega, \frac{5}{8} \, W$$

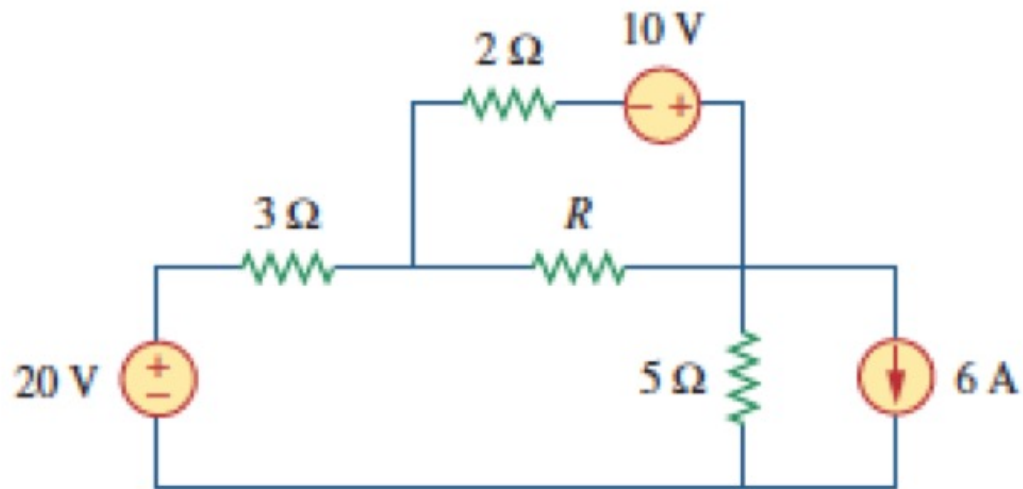Practice problem: maximize the power to R




3 k Ω , 468 mW

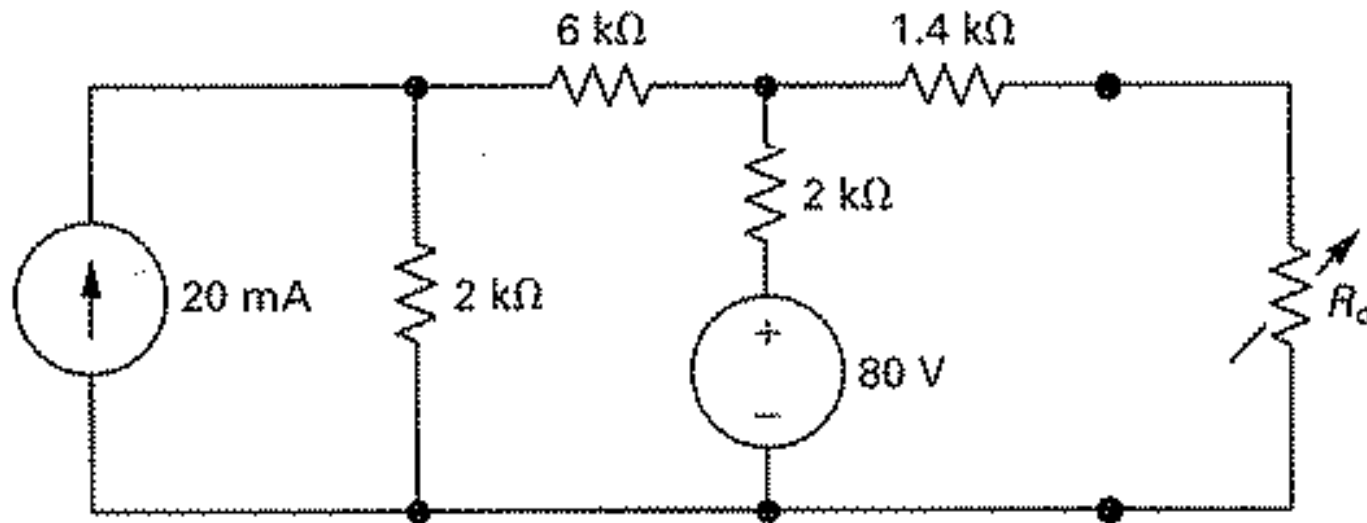Practice problem: maximize the power to R_o



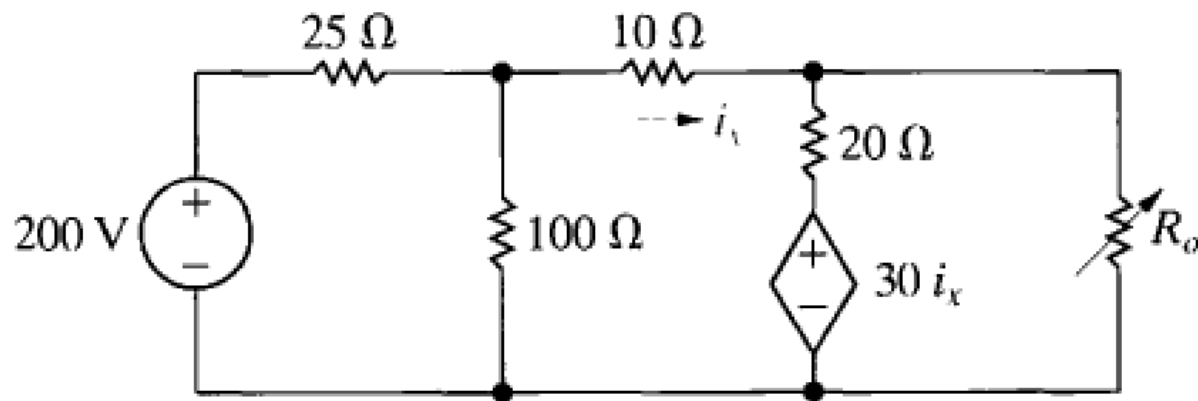
7.5 Ω , 333 W

Practice problem: maximize the power to R_o



$3\ \Omega, 1.2\ \text{kW}$

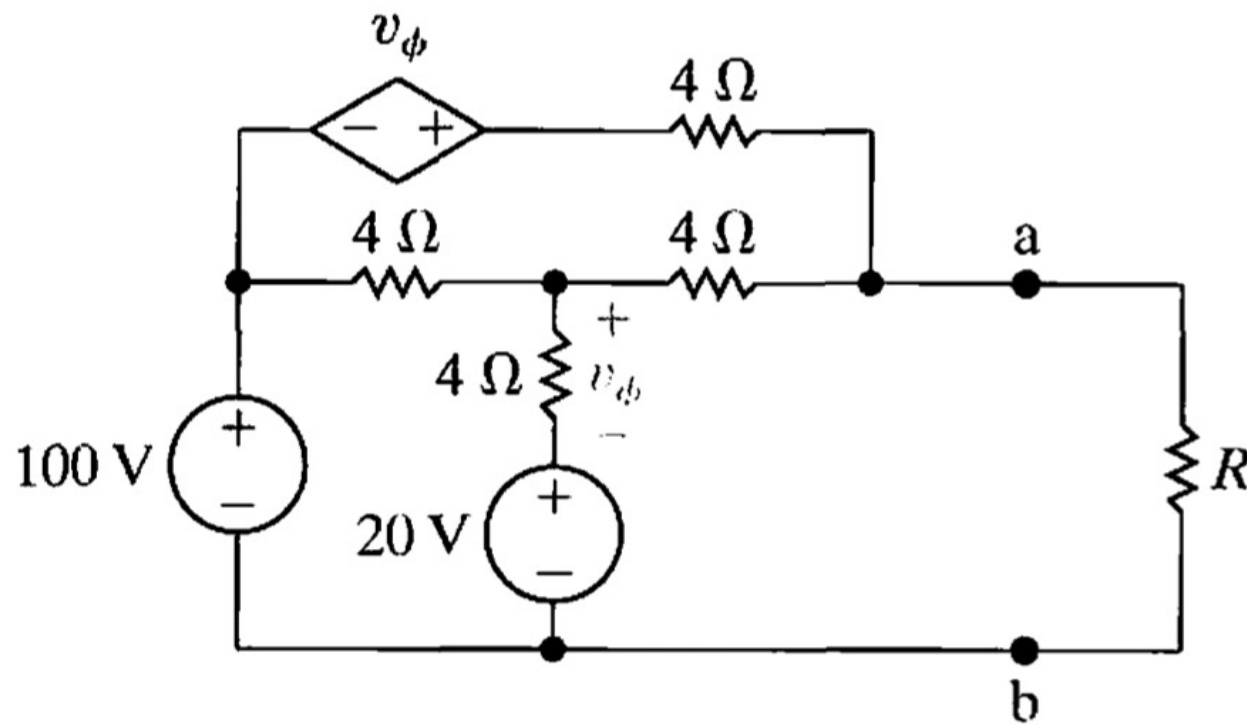Practice problem: maximize the power to R



$4\text{ k}\Omega, 9\text{ mW}$

Practice problem: maximize the power to R_L

