


# Lecture 11

## Node Analysis – 4 of 7

dependent sources


# Extension #3 – dependent sources


- Consider:

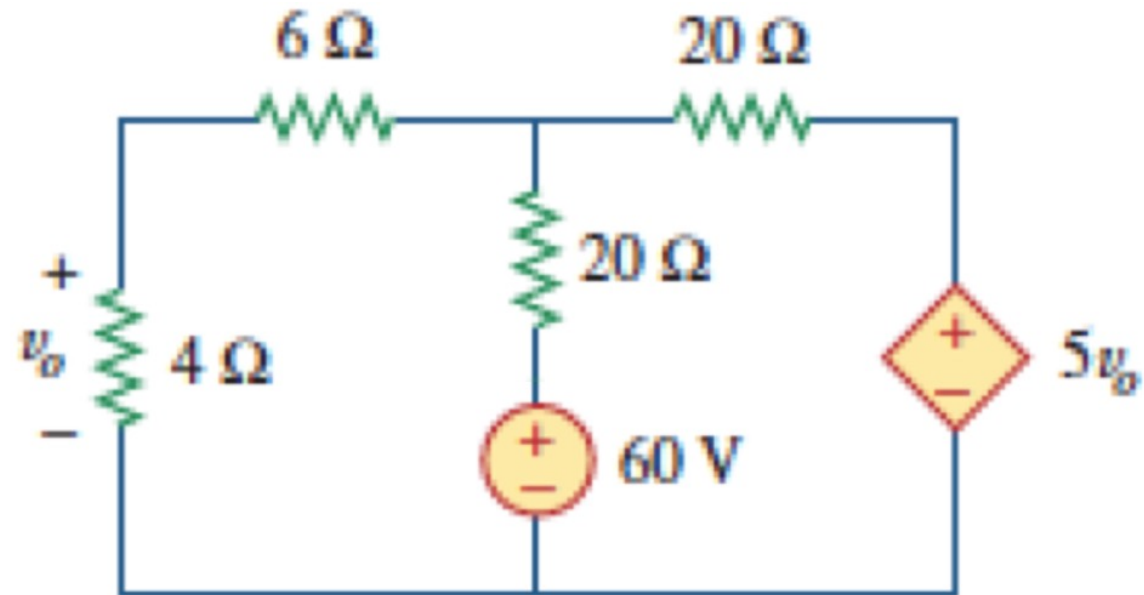

- Write node equations as usual,
- Add an equation “defining” the controlling variable in terms of the node voltages

Example (solved on next slide)

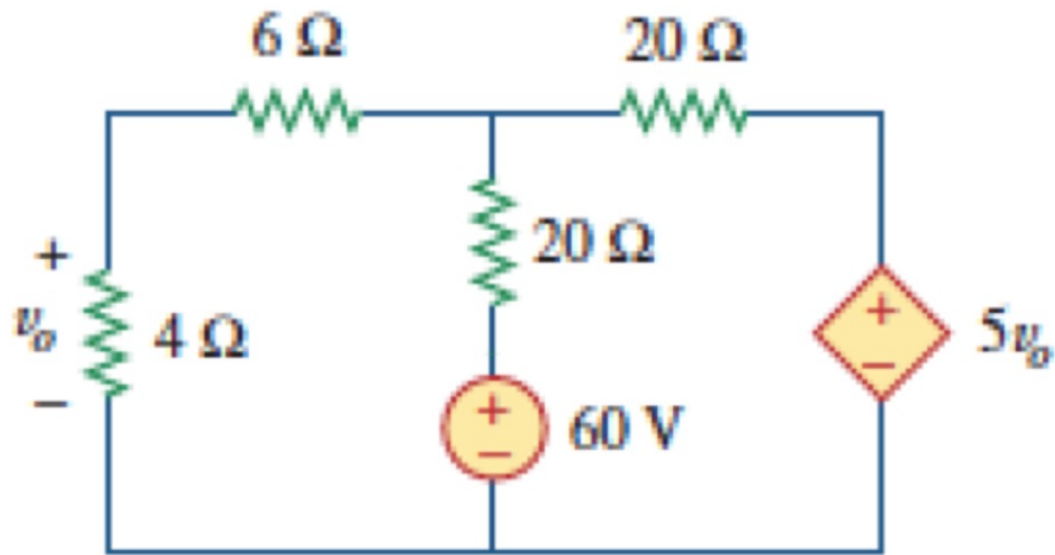

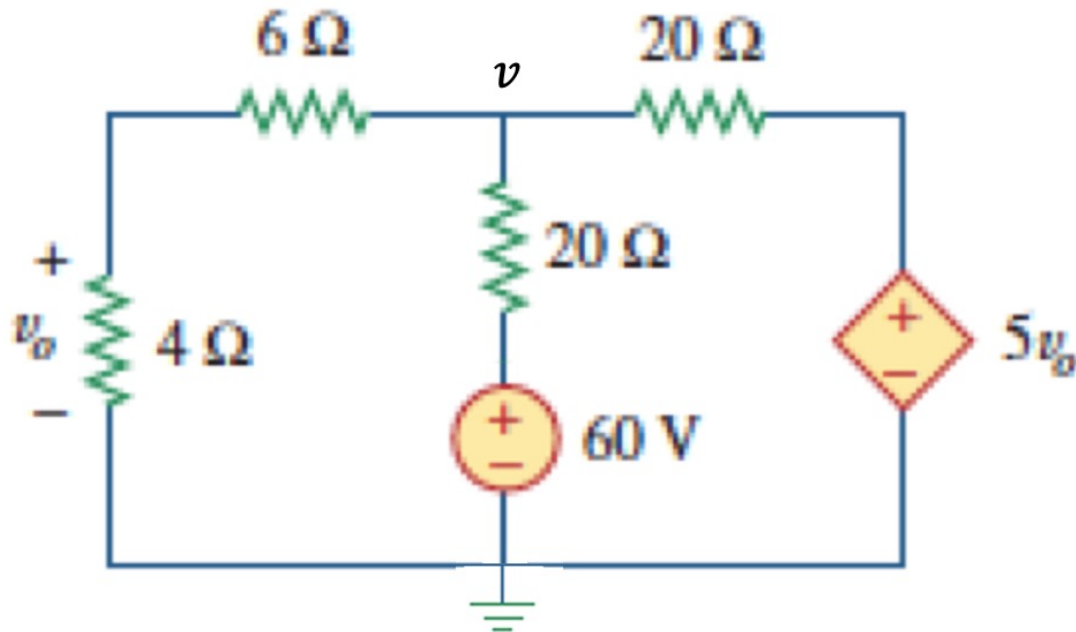

Node equation:

$$\frac{v}{10} + \frac{v - 60}{20} + \frac{v - 5v_o}{20} = 0$$

Relate  $v_o$  to the node:

$$v_o = \frac{4}{10} v$$


$$4v - 5v_o = 60$$

$$4v - 5 \frac{4}{10} v = 60$$


$$v = 30 \text{ volts}$$

$$V_o = 10\text{ V}$$

**Example:** find  $V_o$

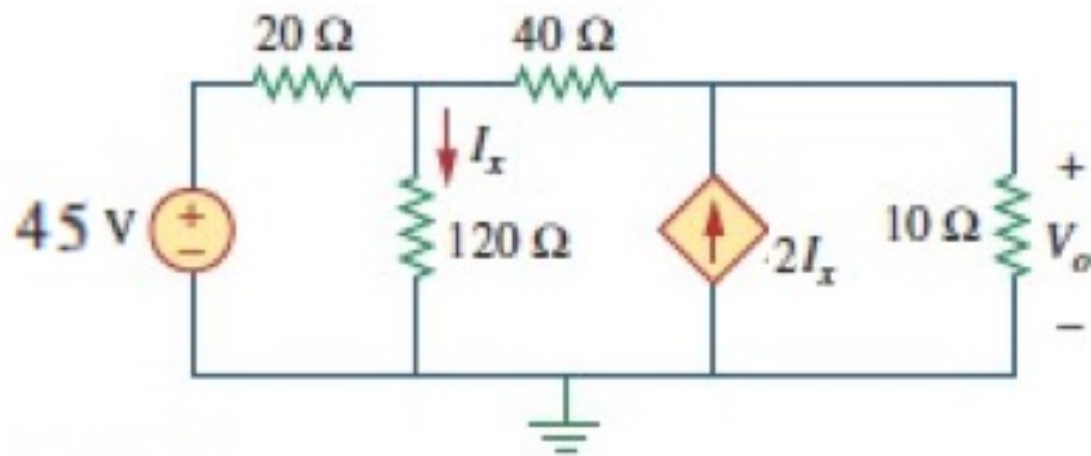


**Example:**

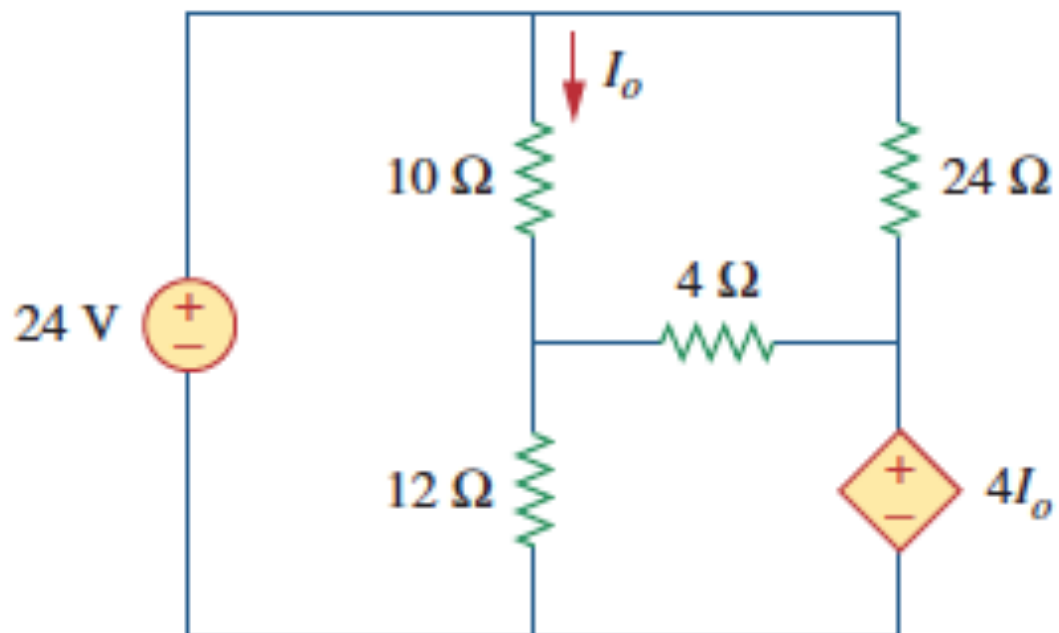

$$\begin{aligned}v_L &= 9 \text{ V}, \\i_o &= 1.5 \text{ A} \\v_R &= 6 \text{ V}\end{aligned}$$


$$P = -36 \text{ W}$$

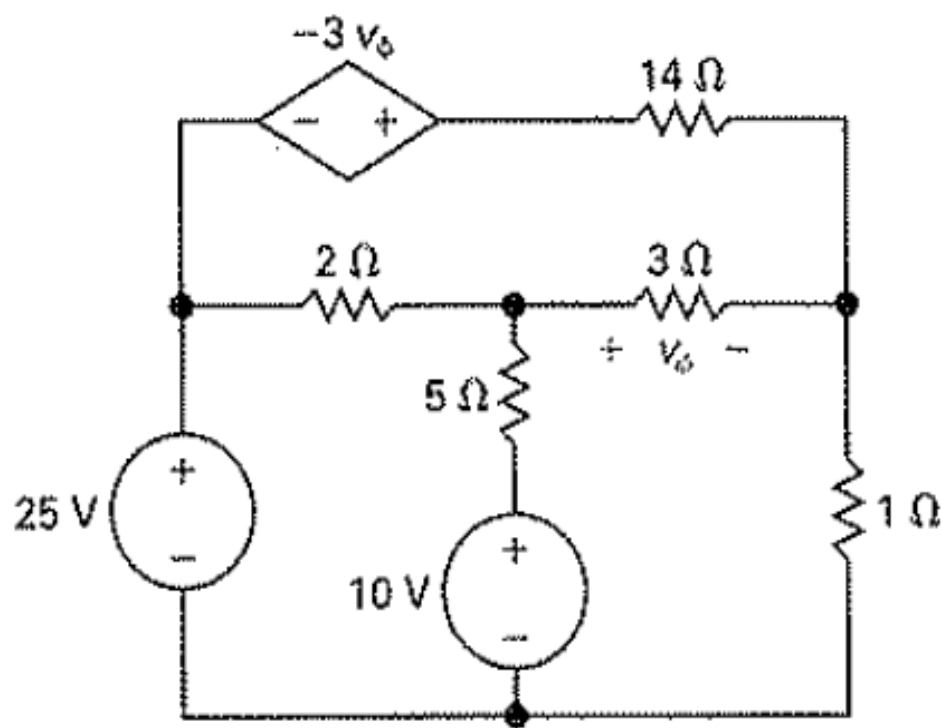**Example:** find the power of the dependent source



$$i_0 = 11.25 \text{ A}$$


**Practice problem:** find  $i_0$

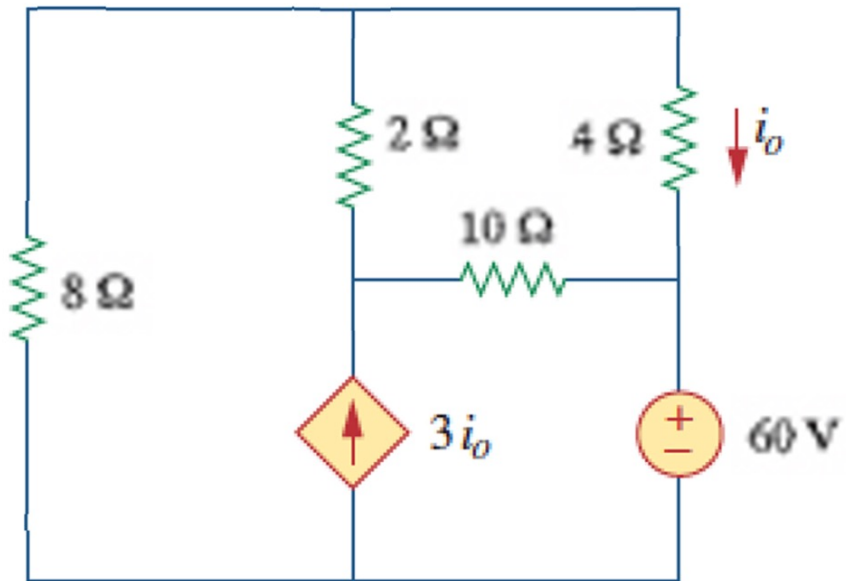




$$v_o = -50\text{ V}$$

**Practice problem:** find  $v_o$

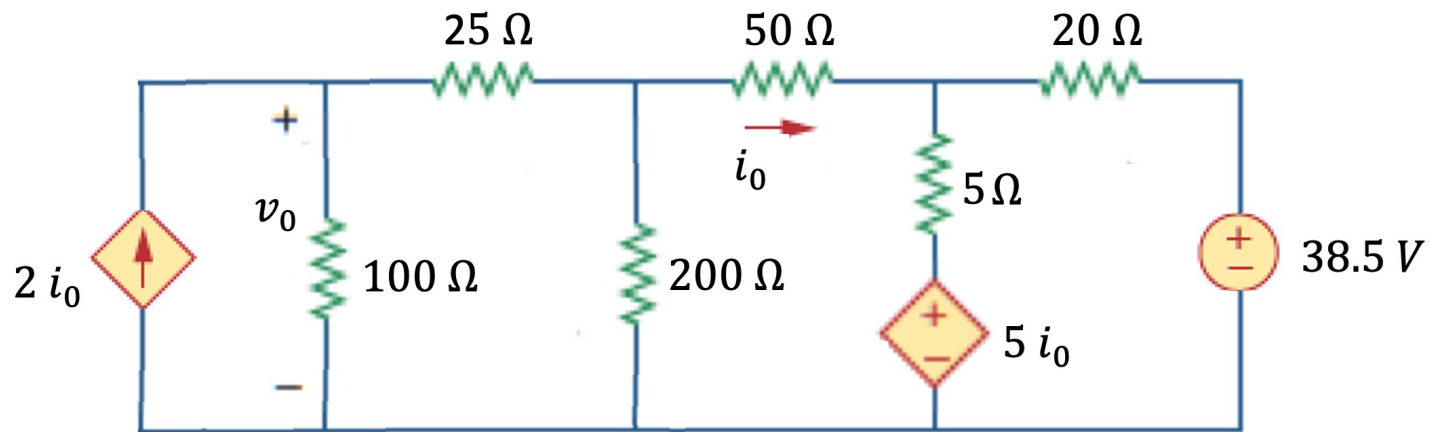

## Practice Problem:

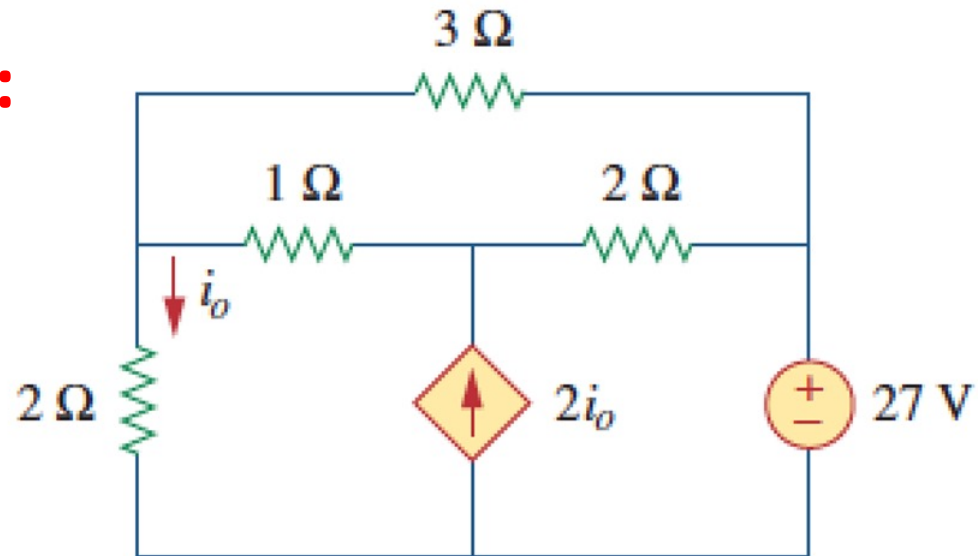

$$v_L = 36\text{ V}$$
$$v_R = 57\text{ V}$$

$$I_0 = 7.5 \text{ A}$$

**Practice problem:** find  $I_0$

