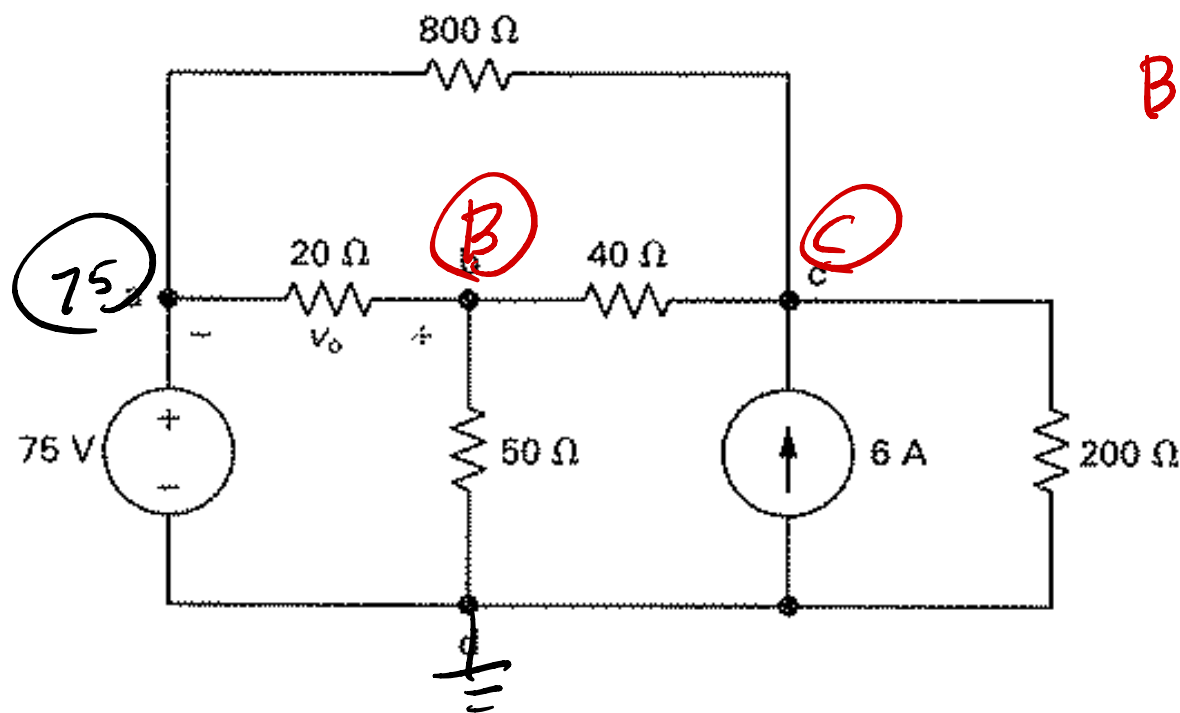


# Lecture 13

## Node Analysis – 6 of 7

examples

**Example:** find  $v_o$




1- labels

2- KCL

B: 
$$\frac{B-75}{20} + \frac{B}{50} + \frac{B-C}{40} = 0$$

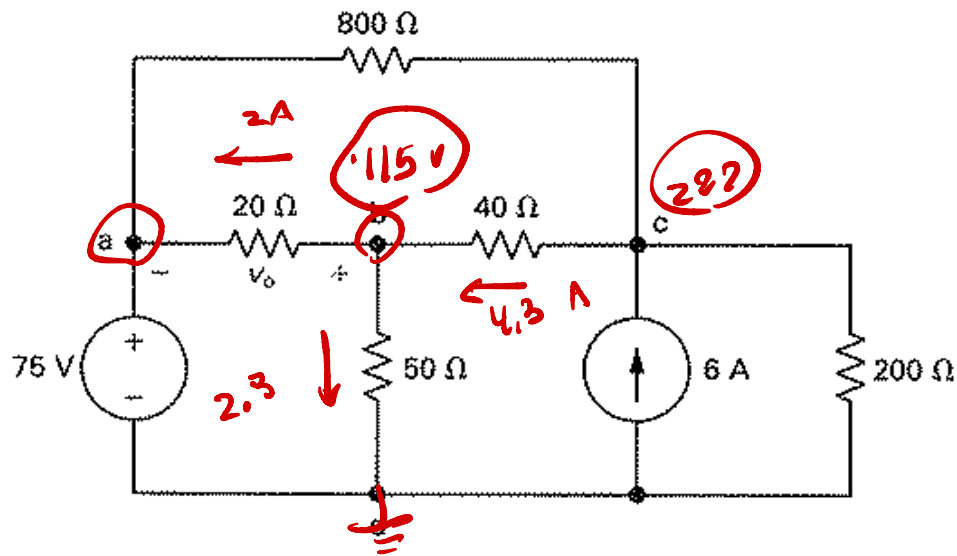
C: 
$$\frac{C-75}{800} + \frac{C}{200} - 6 + \frac{C-B}{40} = 0$$



$$\frac{172}{207}$$

$$v_o = 40 \text{ V}$$

**Example:** find  $i_0$

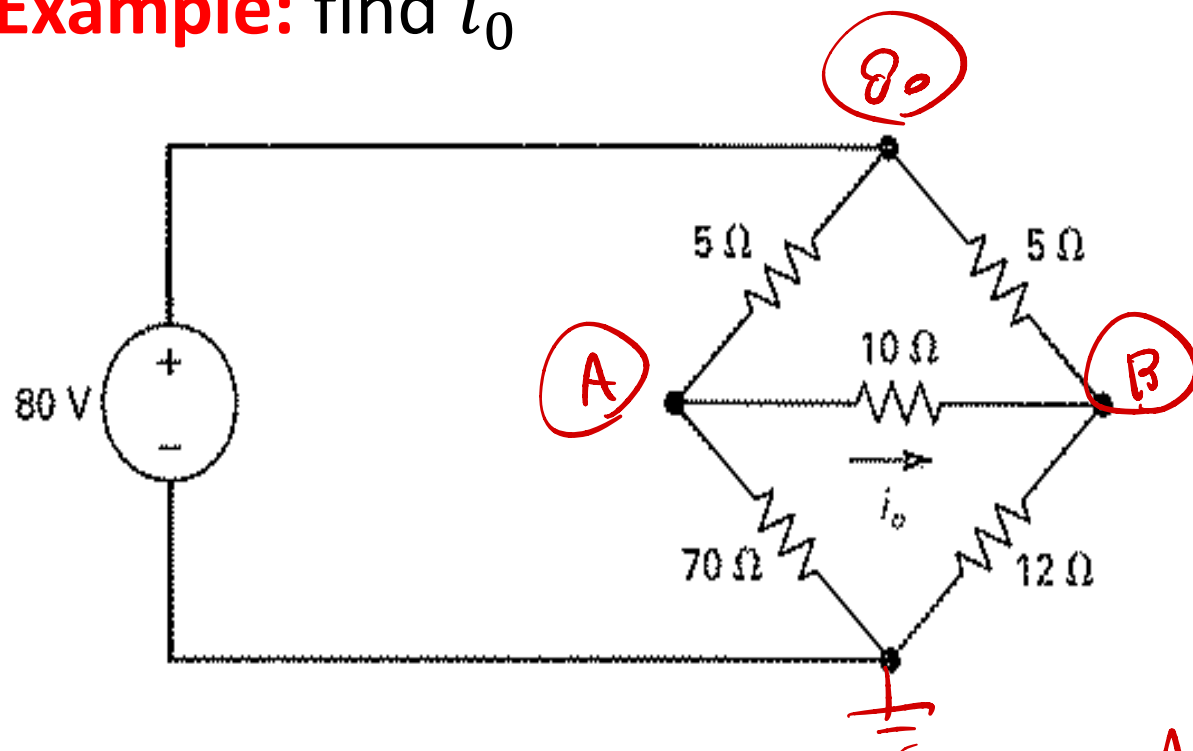

1 - label  $A \rightarrow B$

2 - KCL


$$A: \frac{A - 80}{5} + \frac{A}{70} + \frac{A - B}{10} = 0$$

$$B: \frac{B - 80}{5} + \frac{B}{12} + \frac{B - A}{10} = 0$$

$$A = \underline{\hspace{2cm}}$$


$$B = \underline{\hspace{2cm}}$$

$$\hat{v}_0 = \frac{A - B}{10}$$

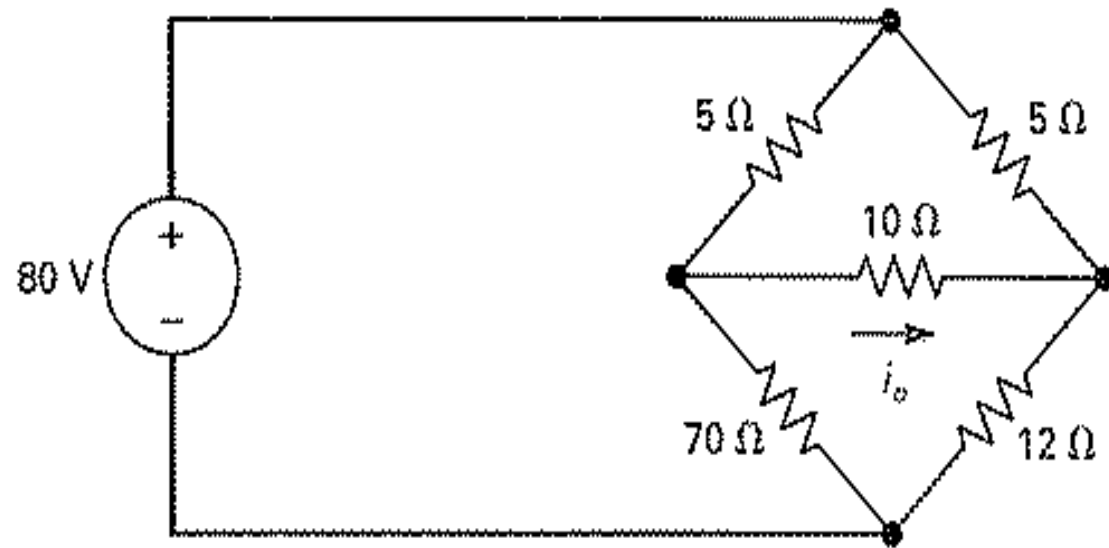

$$i_o = 1 \text{ A}$$

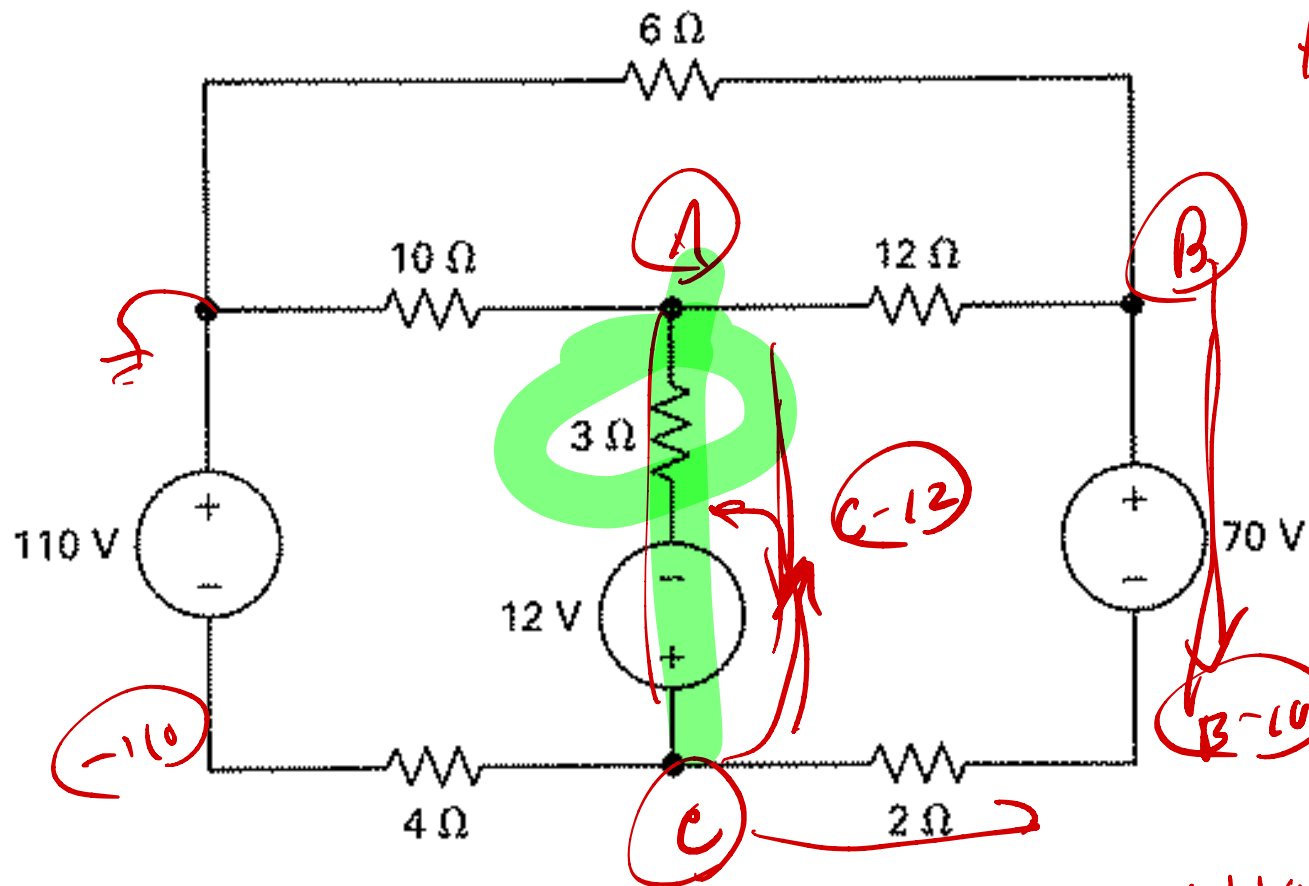**Example:** find the power of the 10  $\Omega$  resistor



$$A: \frac{A}{10} + \frac{A-B}{12}$$


$$+ \frac{A-C+12}{3} = 0$$

$$B: \frac{B-A}{12} + \frac{B-70-C}{2}$$

$$+ \frac{B}{6} = 0$$

$$C: \frac{C+110}{4} + \frac{C-12-A}{3}$$


$$+ \frac{C-(B-70)}{2} = 0$$

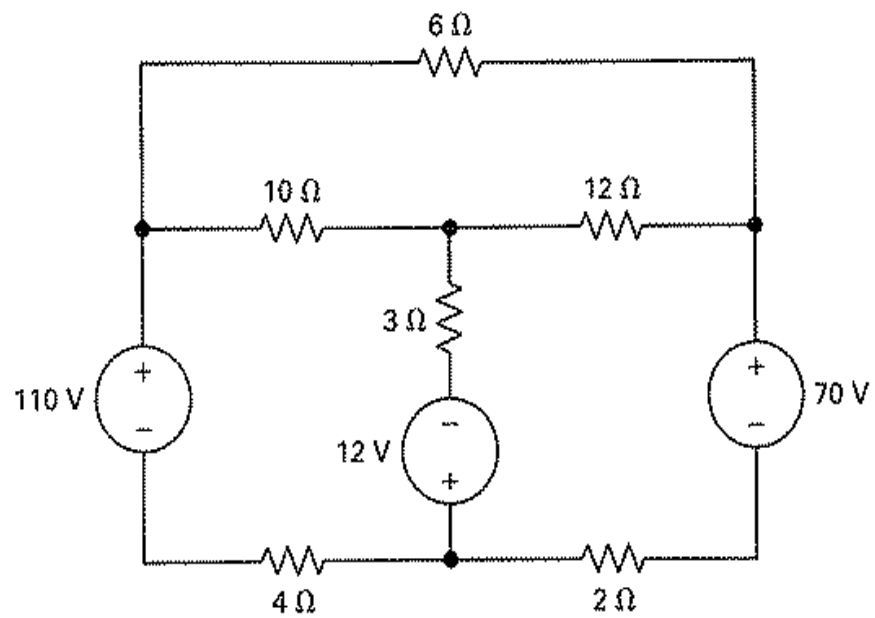

$$P = 360 \text{ W}$$

$$v = 30 \text{ V}$$

**Example:** find  $v$

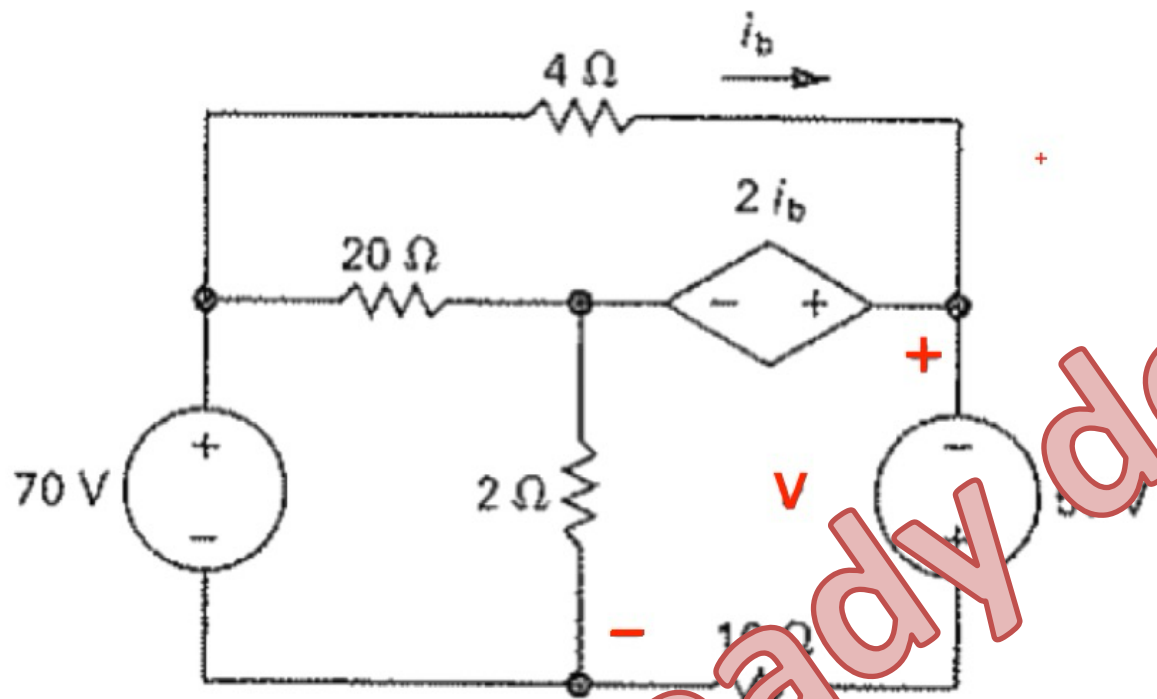




2. For the circuit shown below, find  $v_1$ . How much power is supplied by the current source?

$$P = v \cdot i = (-v_1)(3)$$

1- label with supernode

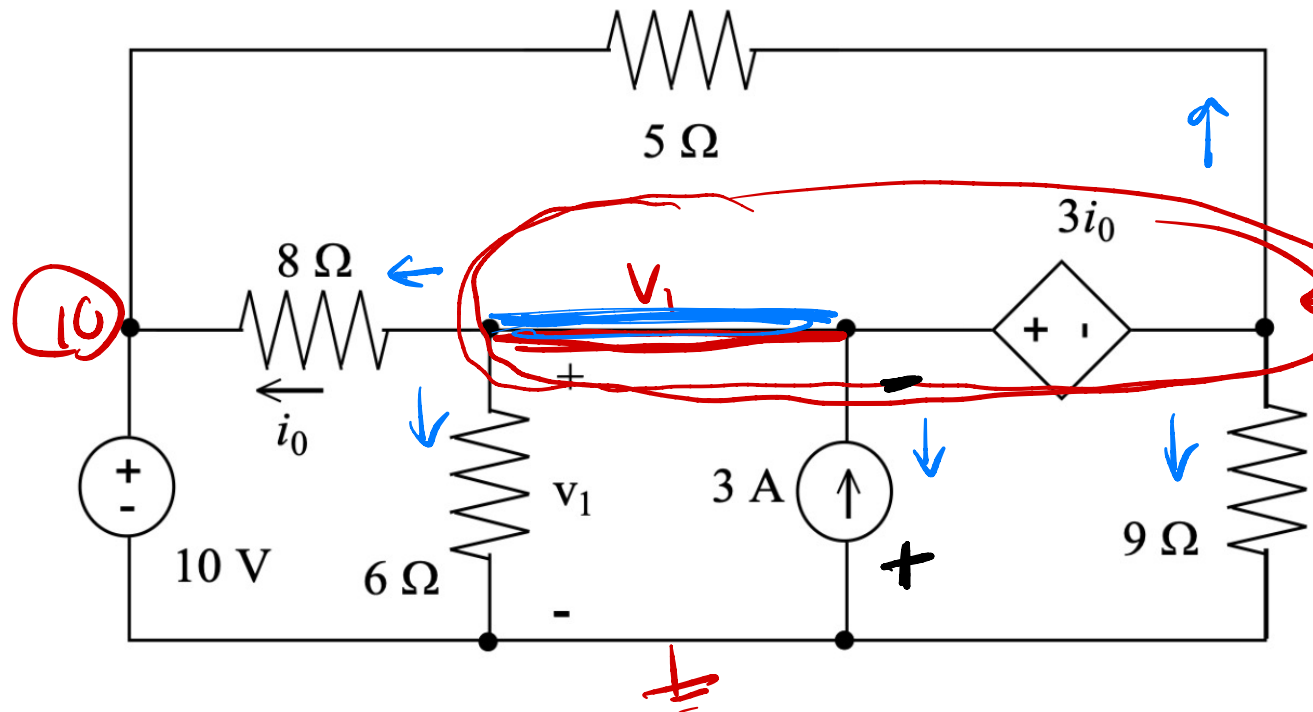

2-  $v_1 - 3i_0$

2- write KCL

$$\frac{v_1 - 10}{8} + \frac{v_1}{6} - 3$$


$$+ \frac{v_1 - 3i_0}{9} + \frac{v_1 - 3i_0 - 10}{5} = 0$$


$v_1 =$  \_\_\_\_\_

Power = \_\_\_\_\_


3- define  $i_0$

$$i_0 = \frac{v_1 - 10}{8}$$

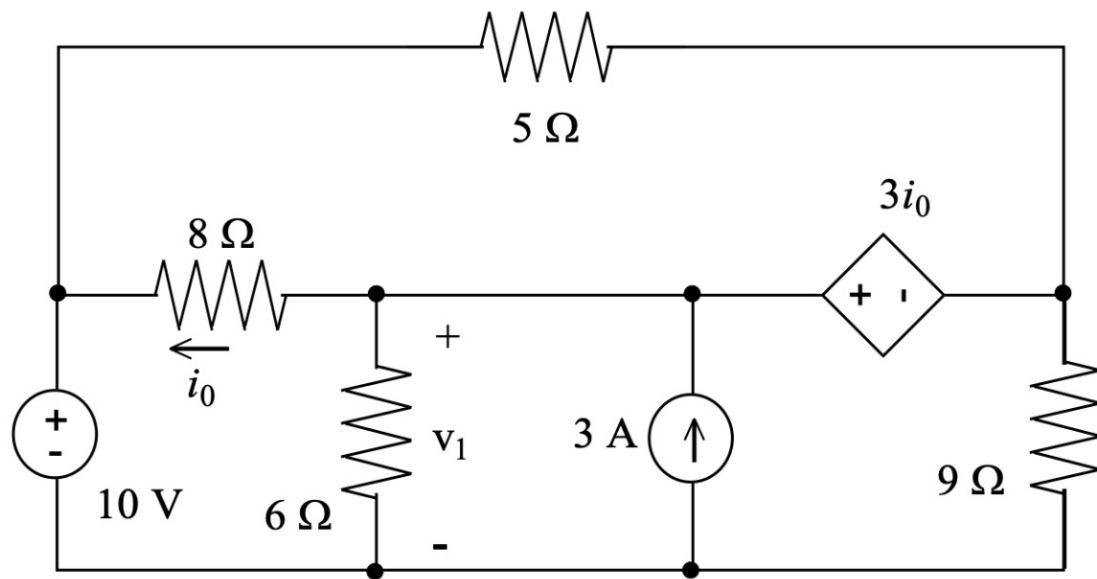

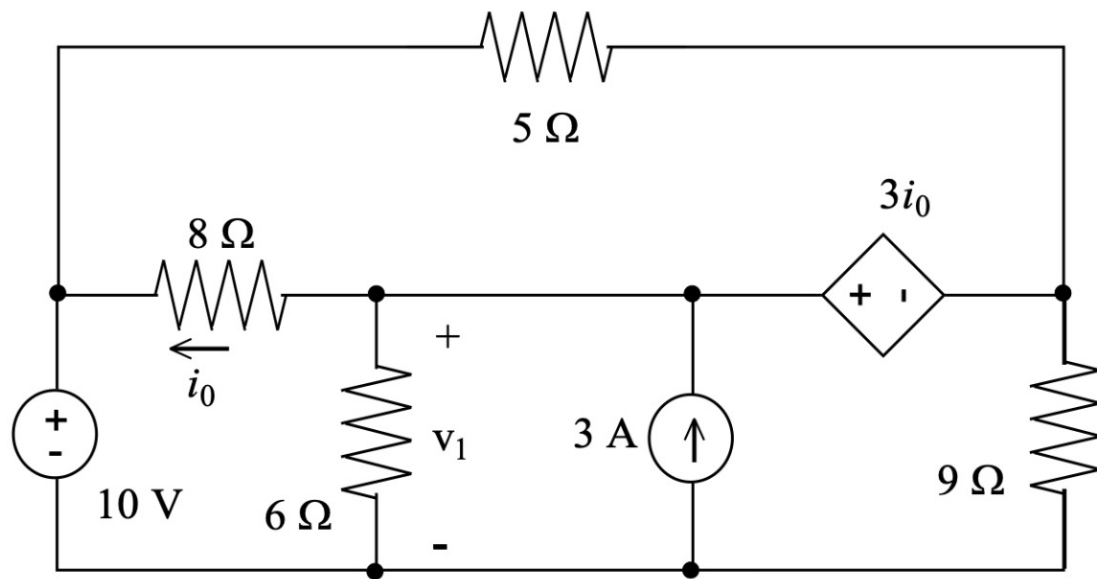


Example:

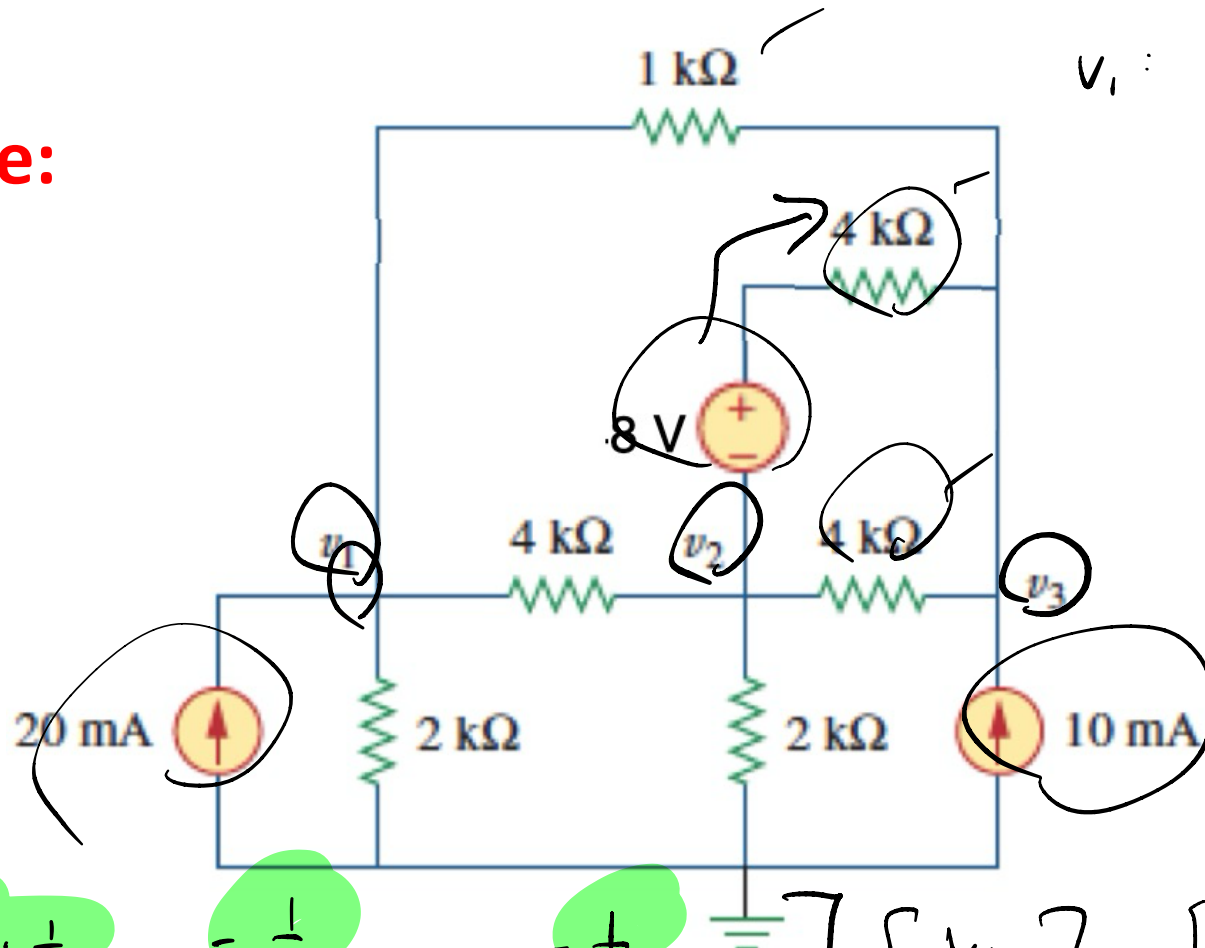

$$V_1: \frac{v_1}{2k} + \frac{v_1 - v_2}{4k} + \frac{v_1 - v_3}{1k} - .02 = 0$$

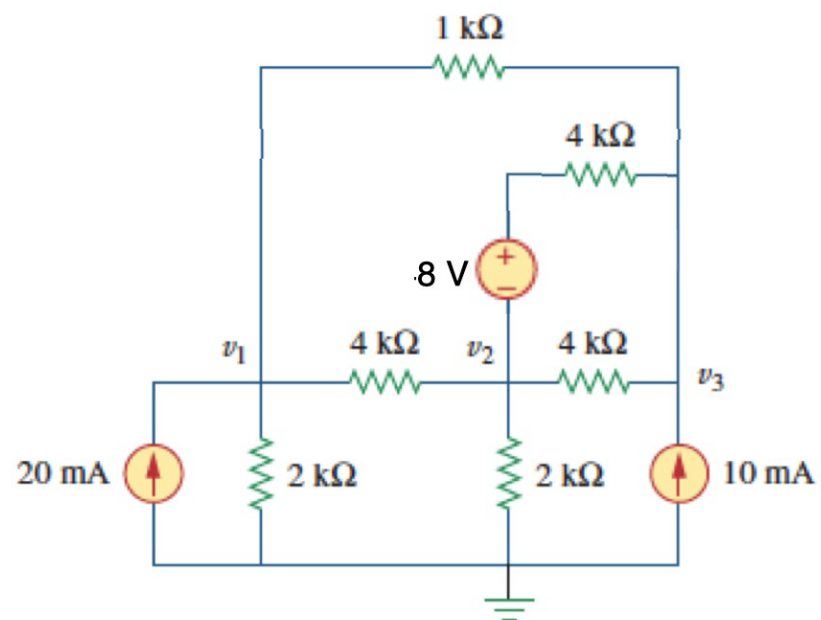
$$\begin{bmatrix} \frac{1}{2k} + \frac{1}{4k} + \frac{1}{1k} & -\frac{1}{4k} & -\frac{1}{1k} \\ -\frac{1}{4k} & \frac{3}{4k} + \frac{1}{2k} & -\frac{2}{4k} \\ -\frac{1}{1k} & -\frac{2}{4k} & \frac{1}{1k} + \frac{2}{4k} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} .02 \\ -.02 \\ .01 + .02 \end{bmatrix}$$



$$\begin{aligned} v_1 &= 37.8\text{ V} \\ v_2 &= 22.2\text{ V} \\ v_3 &= 40.6\text{ V} \end{aligned}$$


60 W

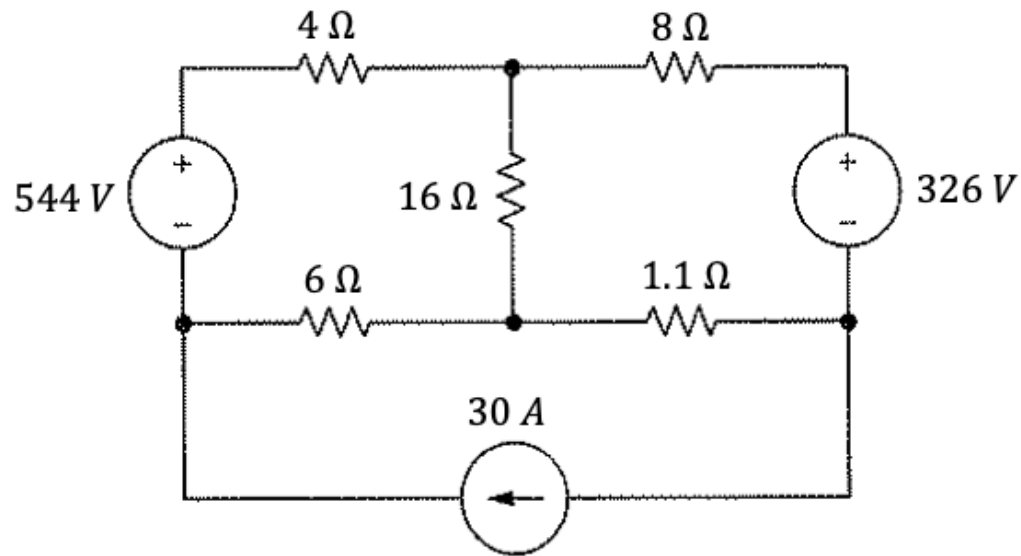**Practice problem:** find the power of the current source



**Practice problem:** find  $i_0$  and  $i_1$
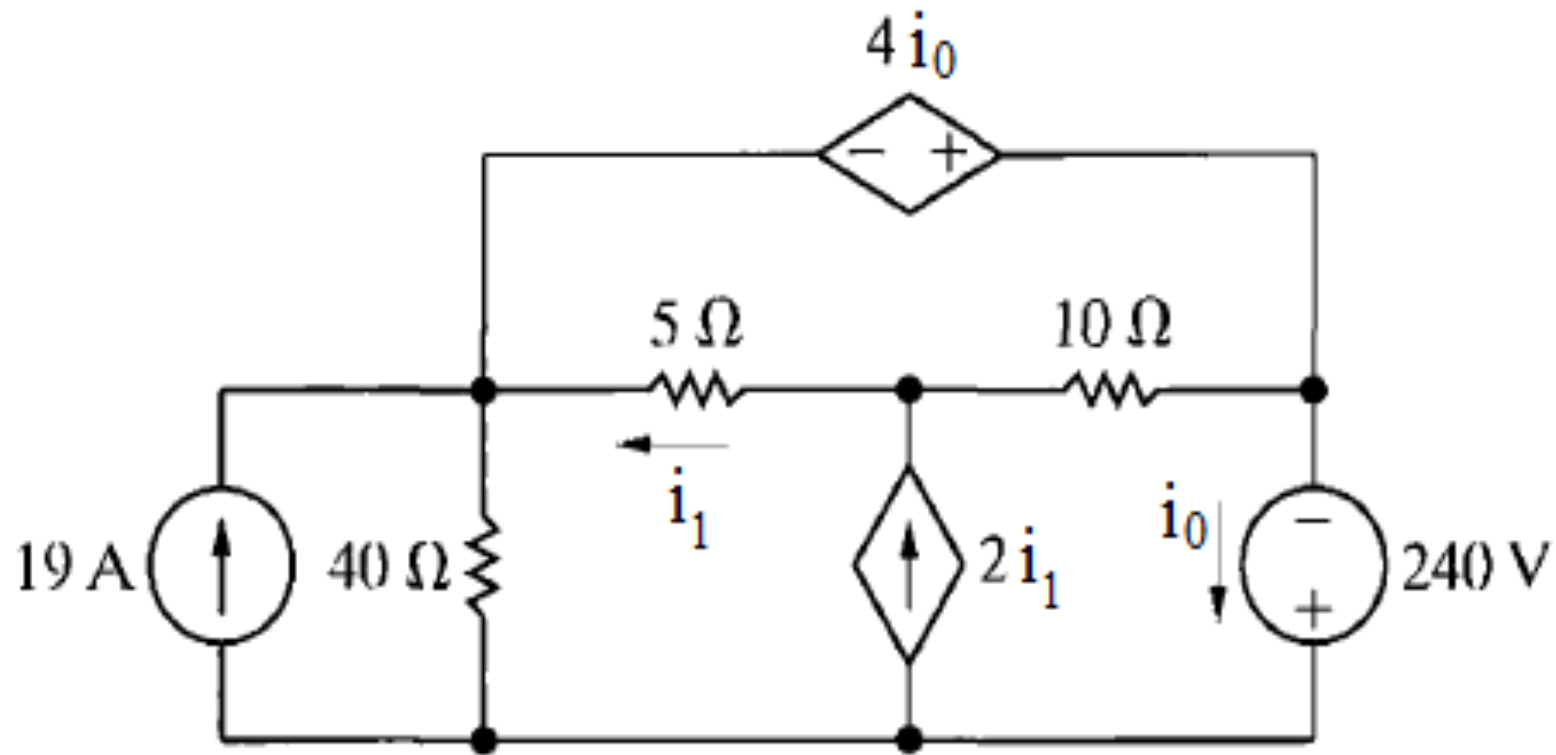
$$i_0 = 10 \text{ A}$$
$$i_1 = -8 \text{ A}$$



**Practice problem:** The variable voltage source shown in the circuit below (the source with the diagonal line through it) is adjusted so that the power absorbed by the  $5\ \Omega$  resistor is 5 watts. Find the value of  $v_{DC}$ .

