

# Lecture 6

## Basics – 6 of 7


circuit analysis; dependent sources

# Circuit Analysis

- Noted in the last class that sometimes we can do a full analysis using series/parallel combining, voltage/current division
- Let's do another example or two

0.2 A, 0.6 V

**Example:** find  $I$  and  $V_o$

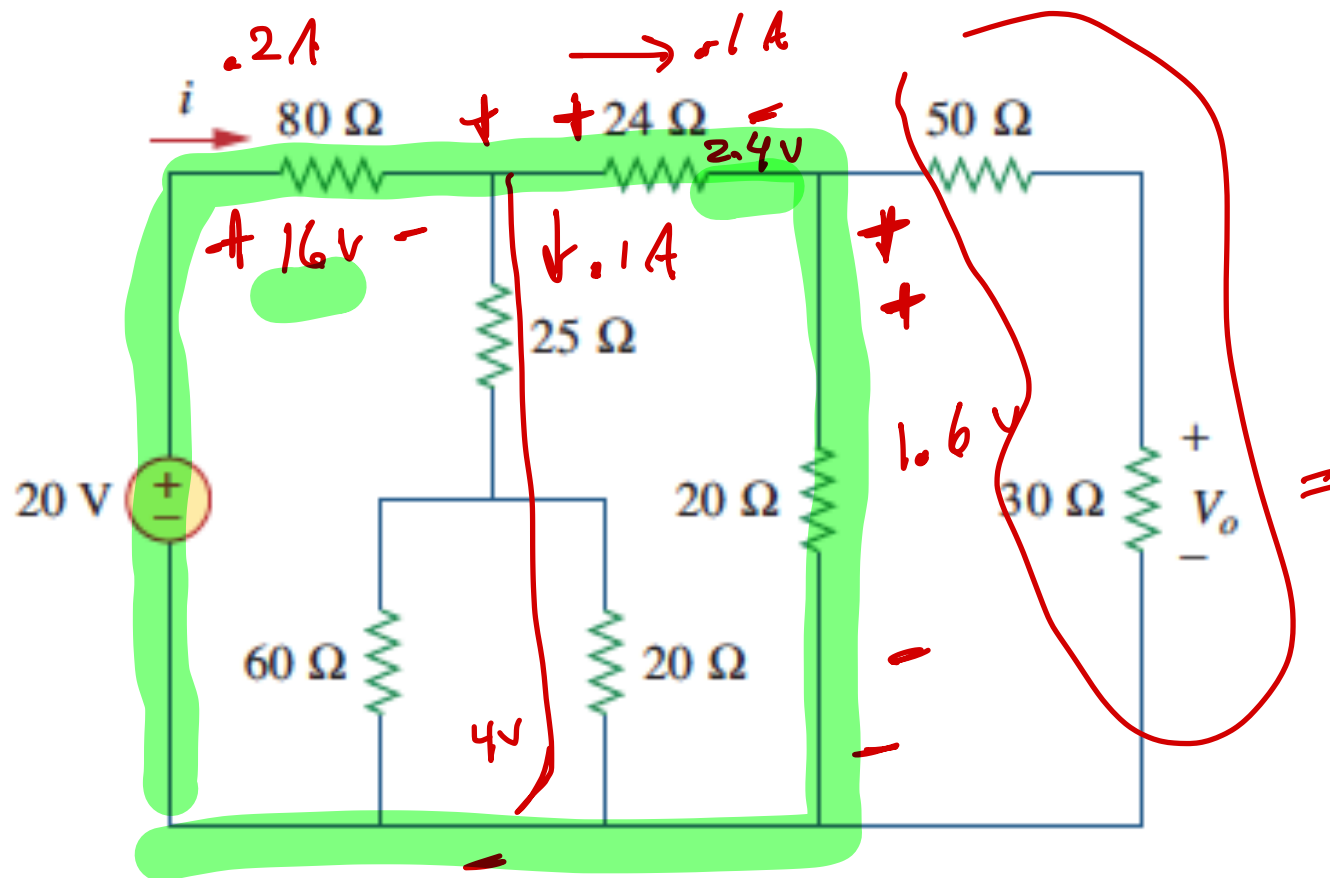

$$= \frac{30}{50+30} \cdot 16$$
$$= 0.6 \text{ V}$$




$$I_{20} = \frac{168}{70} \text{ A}$$

$$I_{20} = \frac{32}{20} \text{ A}$$

$$32 \text{ V}, 0.6 \text{ A}$$


**Example:** find  $V_o$  and  $I_o$

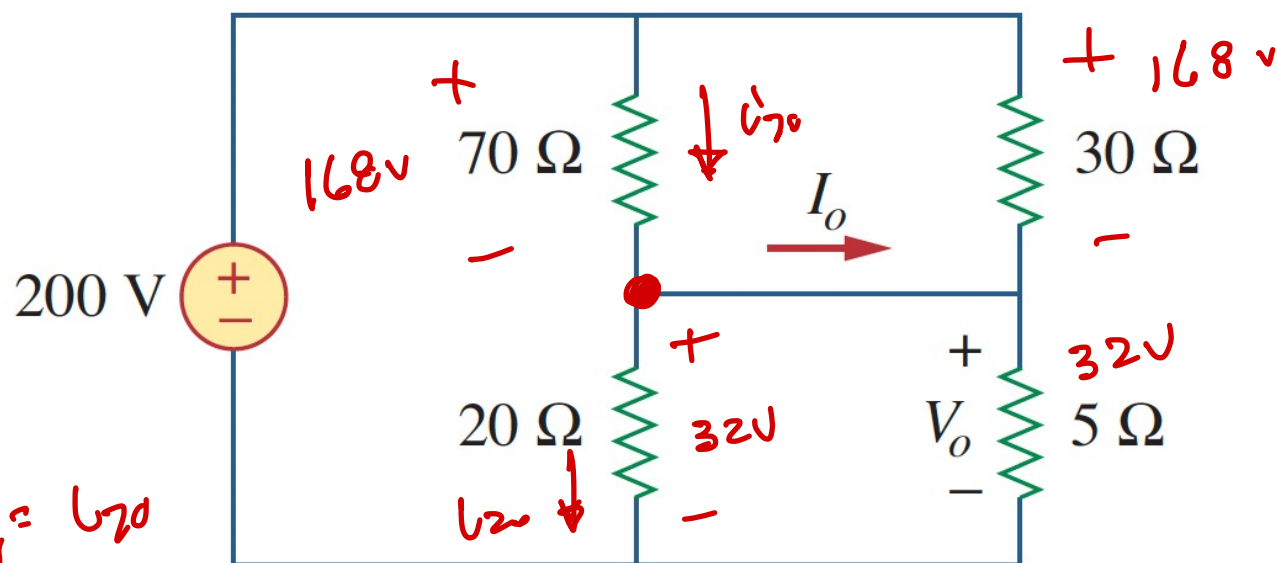

$$\frac{30 \cdot 70}{100} = 21 \Omega$$

$$\frac{20 \cdot 5}{25} = 4 \Omega$$



$$I_o = I_{20}$$

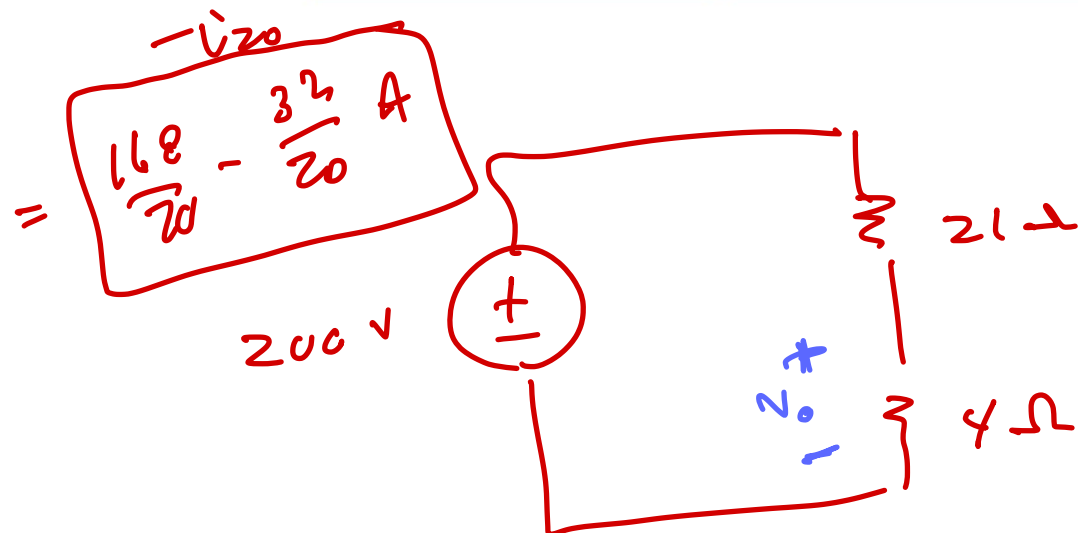

$$V_o = \frac{4}{21+4} \cdot 200 = 32 \text{ V}$$



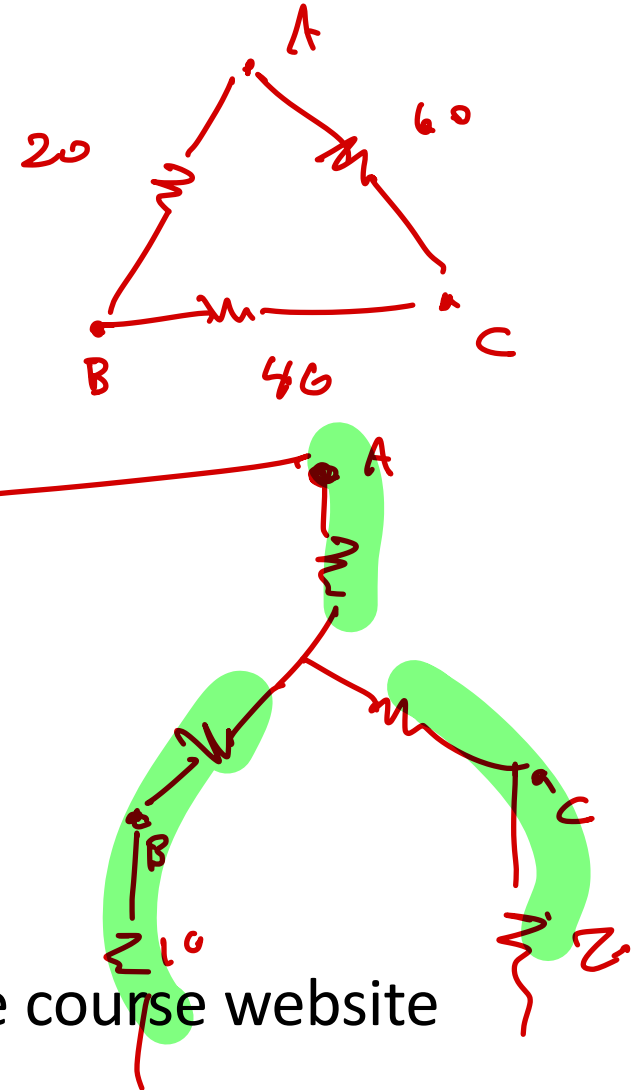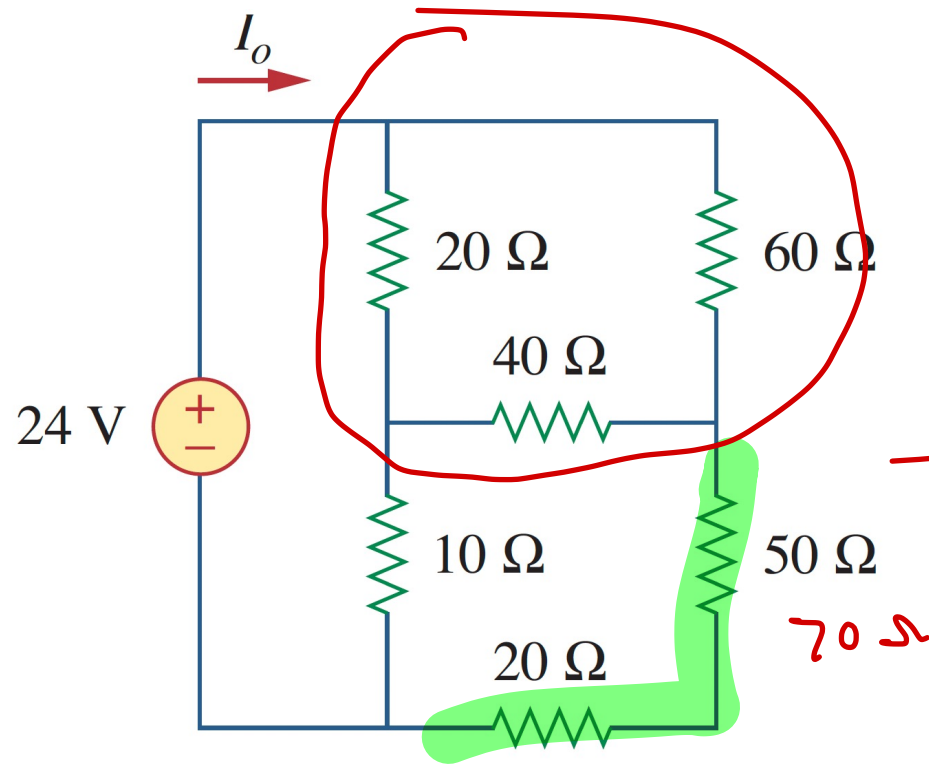
But sometimes you cannot: how do you find the current  $I_o$  now?



Watch/read materials on Delta-Wye on the course website

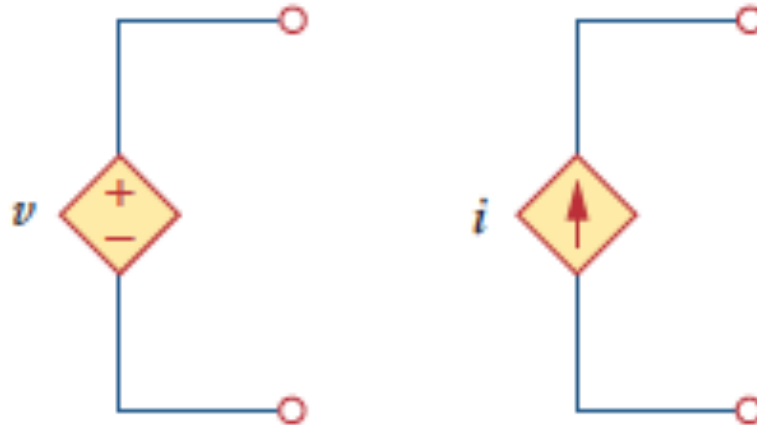
# Dependent Sources

- The voltage or current is dependent upon some other circuit variable
- Drawn as a diamond or rhombus







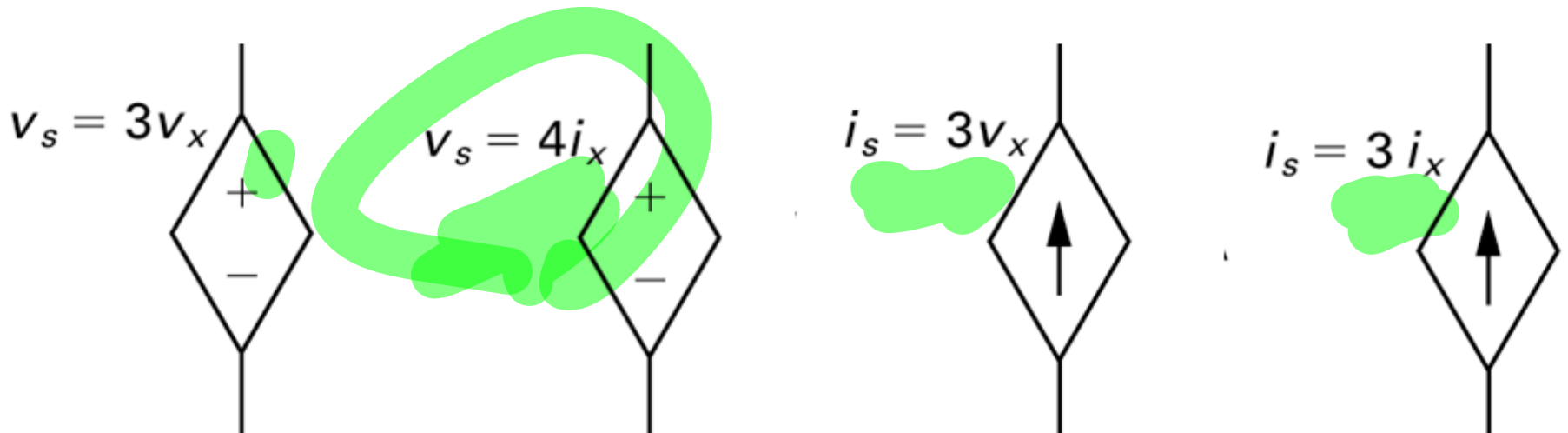
- A linear relationship to some other circuit variable is common
  - What units does the entire label have?
  - What units does the multiplier have?



Example:

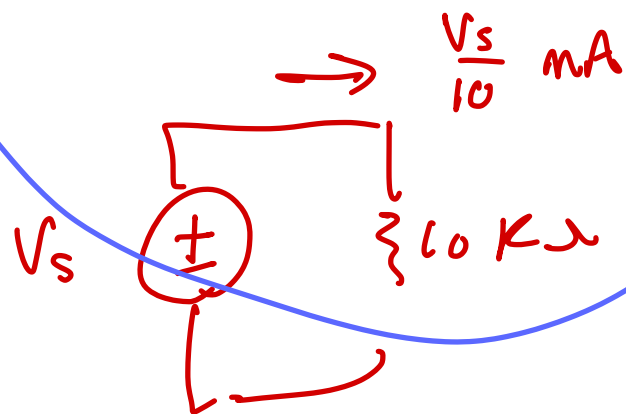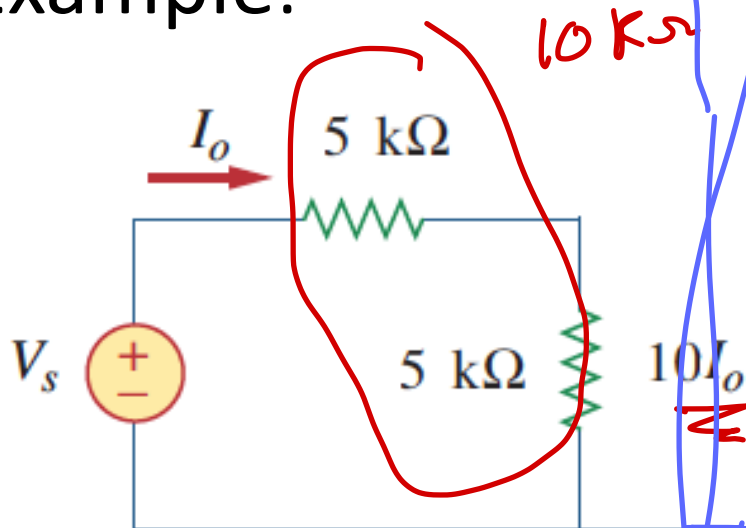

$$I_o = \frac{V_s}{10} \text{ mA}$$

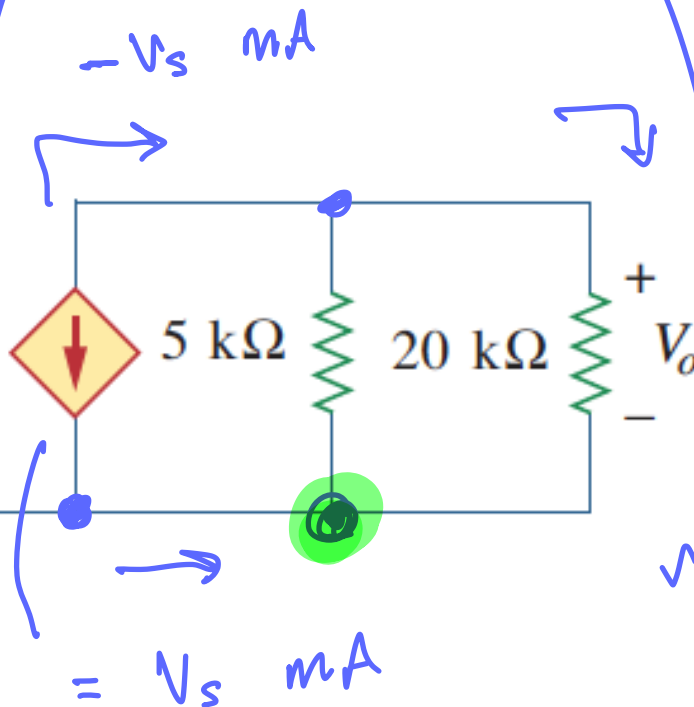

$$V_s \frac{5k}{5k + 20k} \text{ mA}$$

$$= -\frac{V_s}{5} \text{ mA}$$

$$V_o = \left( -\frac{V_s}{5} \text{ mA} \right) (20 \text{ k}\Omega)$$

$$\boxed{-4V_s \text{ Volts}}$$

# Example:

2.21 Find  $V_x$  in the circuit of Fig. 2.85.

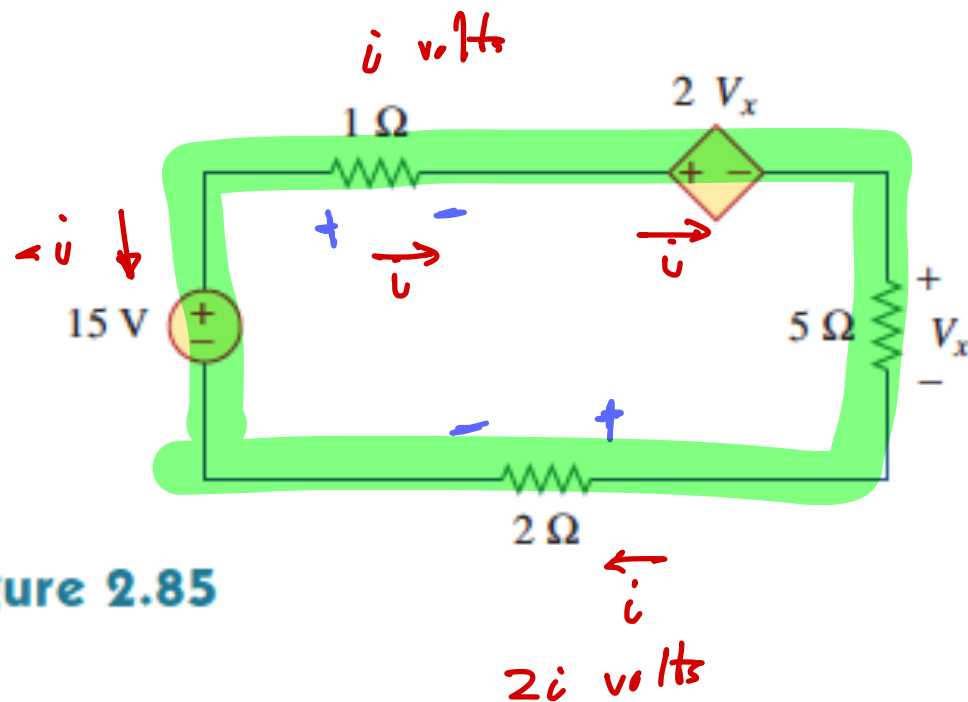


Figure 2.85

$$15 - i - 2V_x - 5i - 2i = 0$$

$$-10i$$

$$5i \text{ volts} = V_x$$


$$15 - i(1 + 10 + 5 + 2) = 0$$

$$i = \frac{15}{18}$$

$$V_x = 5 \cdot \frac{15}{18} = \underline{\hspace{2cm}}$$


- 2 A, - 60 W

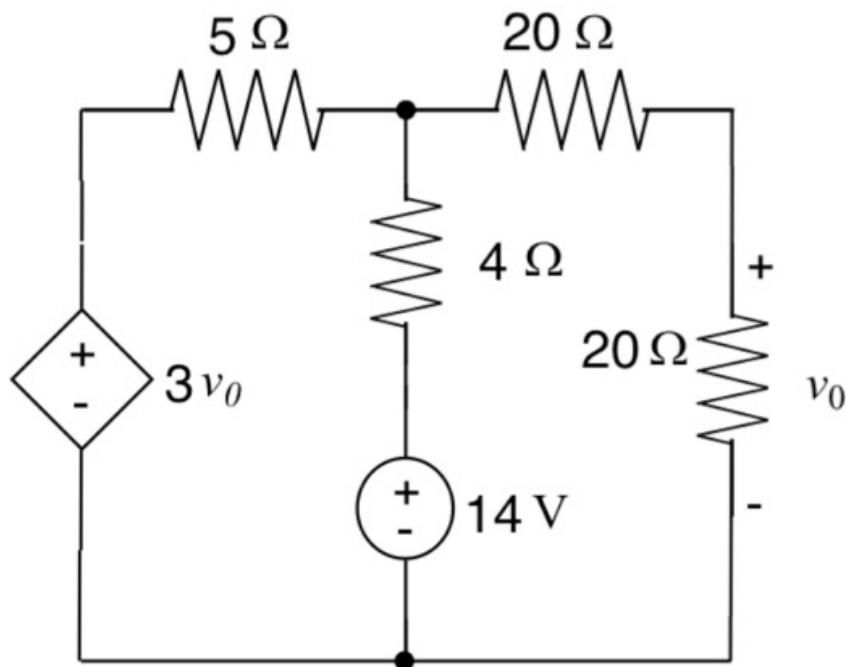**Example:** given that the current in the 4 ohm resistor is 1.5 A going down, find the current and power of the dependent source




2.5 A

**Practice problem:** find  $i_o$

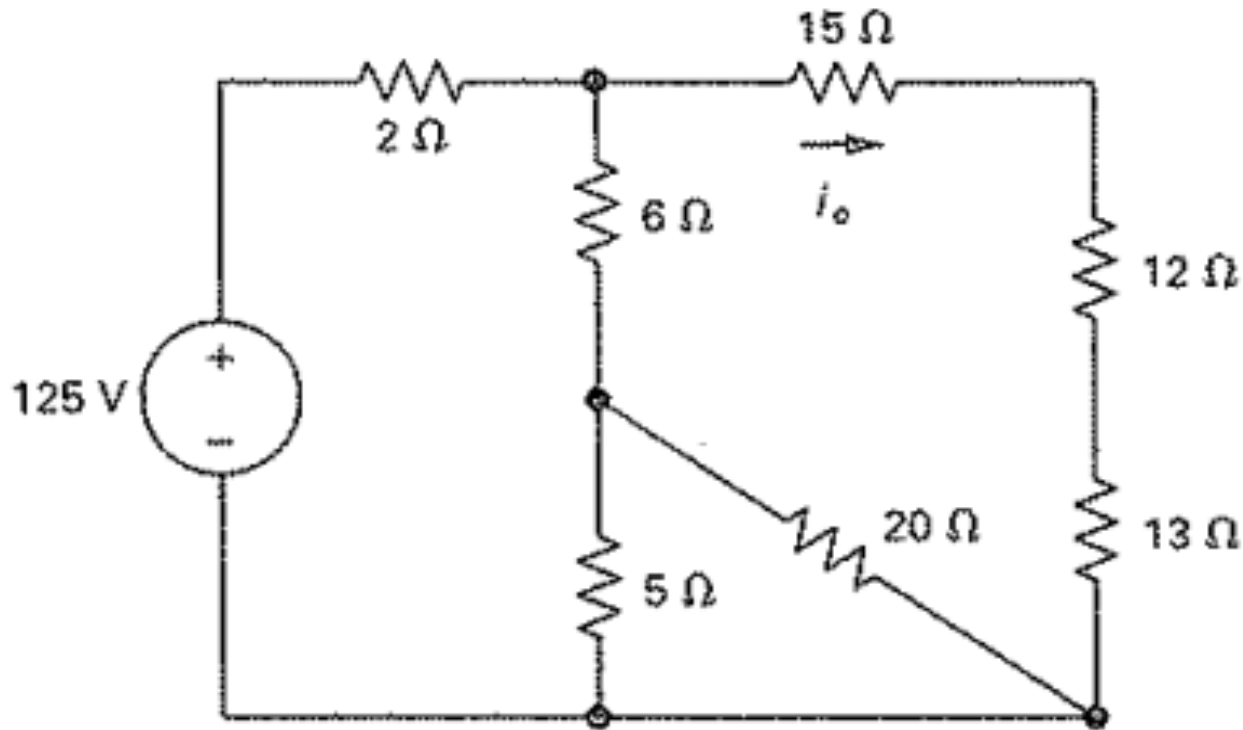

5 V, 5 W

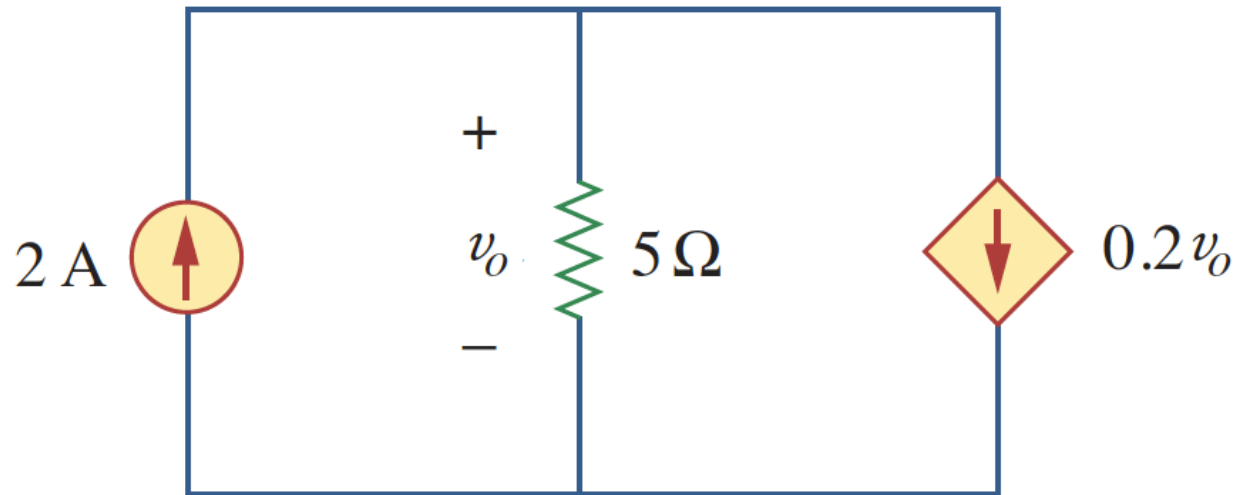**Practice problem:** Find  $v_o$  and the power of the dependent source



57 V

**Practice problem:** find  $v_o$

