

# Lecture 2

## Basics – 2 of 7


time variation; sources; resistors

# Circuit Variables

Current	$i(t)$	amperes	directional
Voltage	$v(t)$	volts	directional
Power	$p(t) = v(t)i(t)$	watts	
Energy	$E(t)$	joules	


- Typically, these are time varying

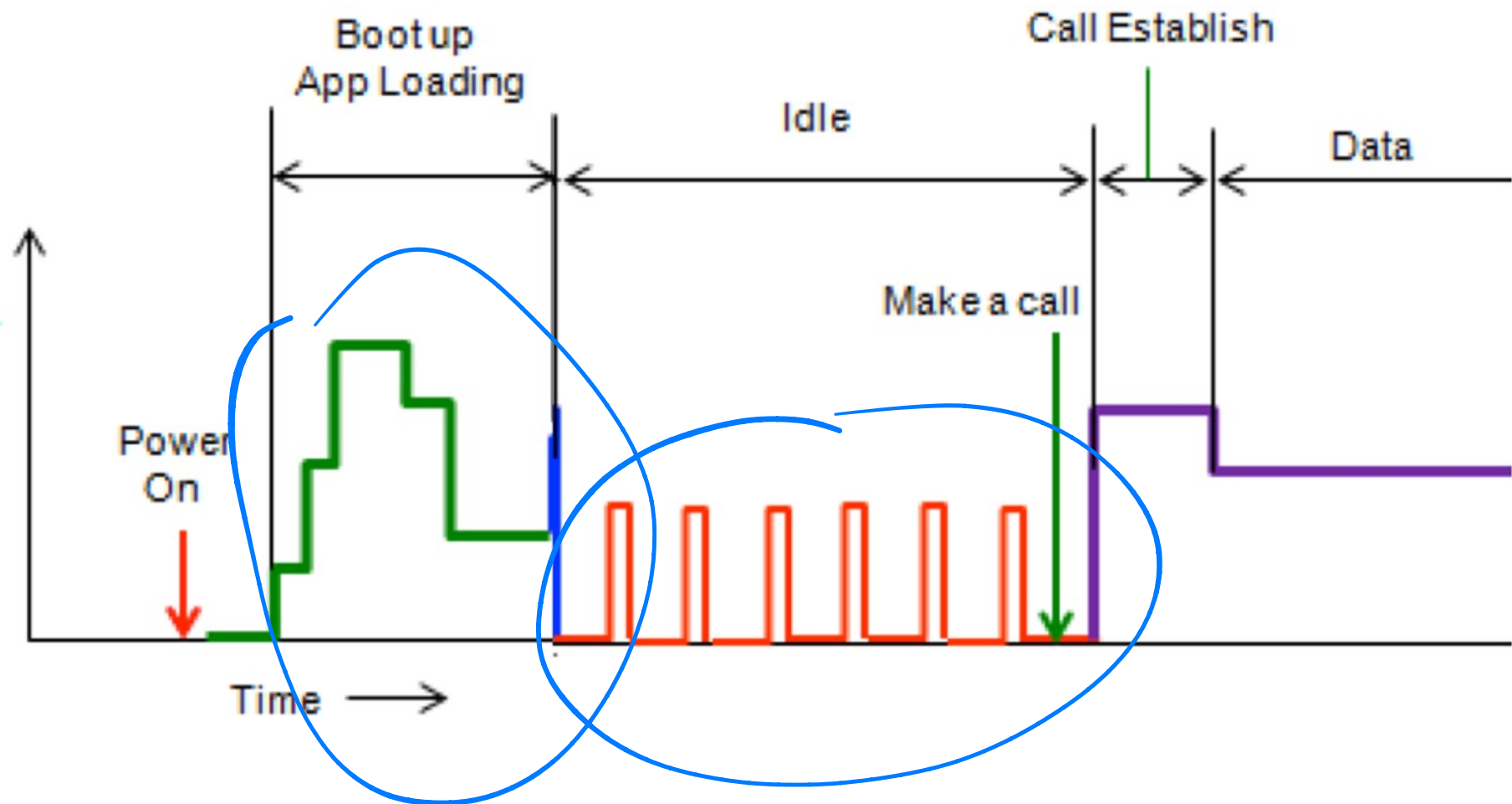- As an example – smart phone power usage




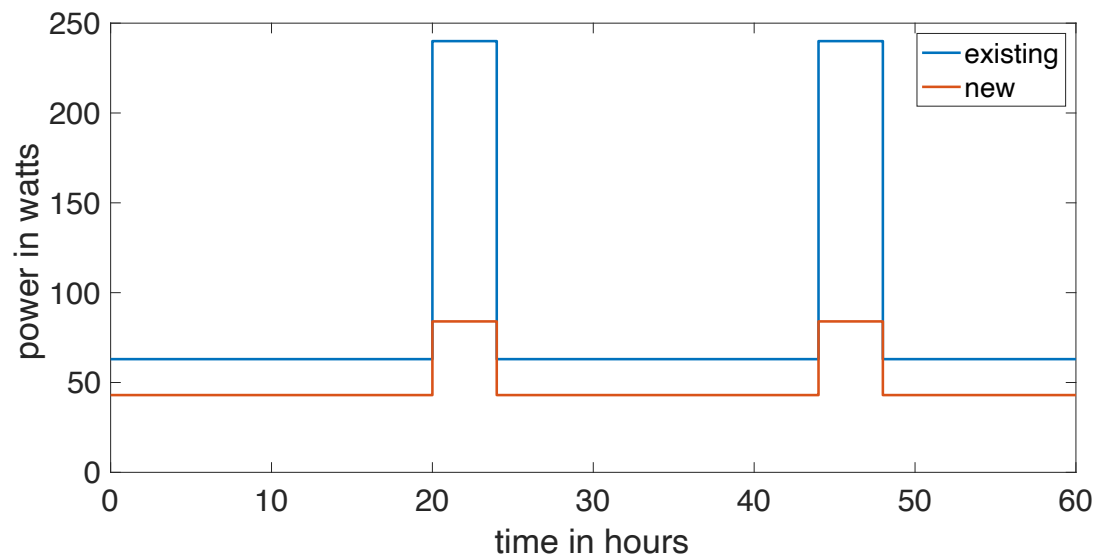**Example:** I currently have a 3-year-old iMac on my desk with power consumption of 63 watts (idle) to 240 watts (active computing). A new iMac is better vis-à-vis power with levels of 43-84 Watts, respectively. Can I argue the \$1,600 price tag based upon the obvious energy savings?

- Assumptions:
  - Low/high power usage for a typical day is 20/4
  - Electricity rate of 18 cents/kWh



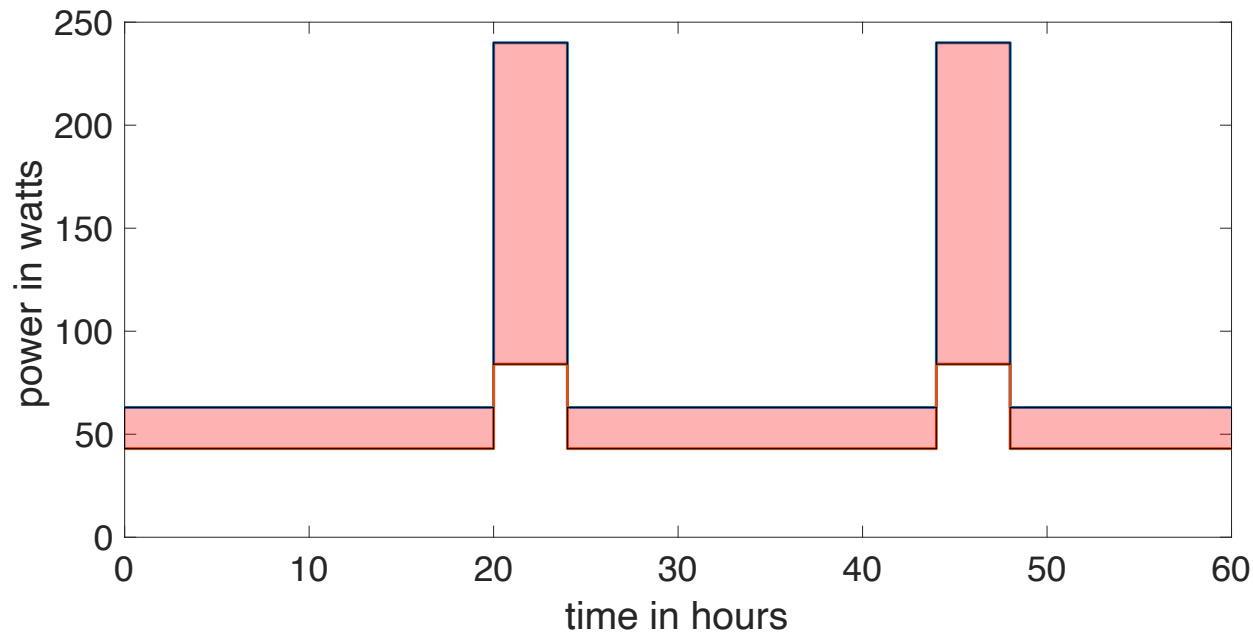- Answer: Consider the extra power over a year




- High power:  $365 * 4 * (240 - 84) = 228 \text{ kWh}$
- Low power:  $365 * 20 * (63 - 43) = 146 \text{ kWh}$
- Savings per year  $= (228 + 146) * 0.18 = \$67$

**Example:** The voltage and current at the terminals of a two-terminal circuit device for  $t > 0$  seconds are

$$v(t) = 20 (1 - e^{-5t}) \text{ V}$$


$$i(t) = 10 e^{-5t} \text{ mA}$$

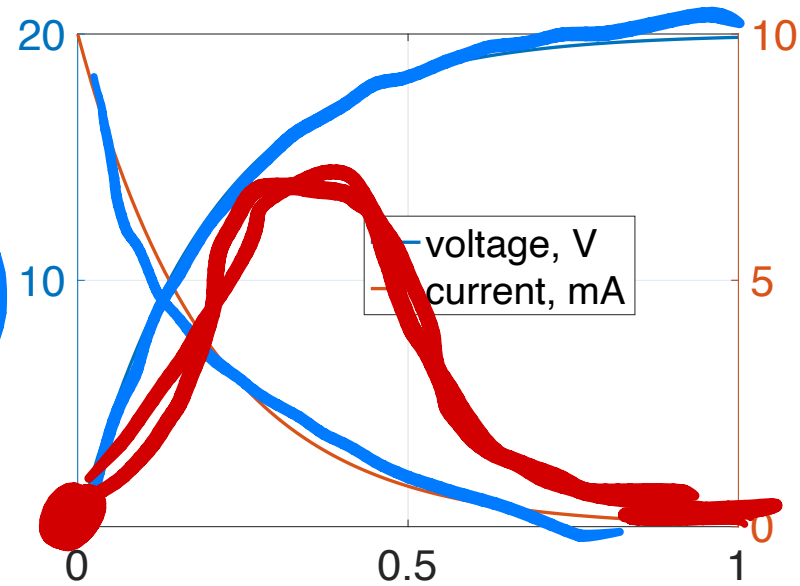

- At what time is the power being delivered to the device a maximum?
- What is that maximum?

- Answer:
  - First, use the fact that power is the product of voltage and current
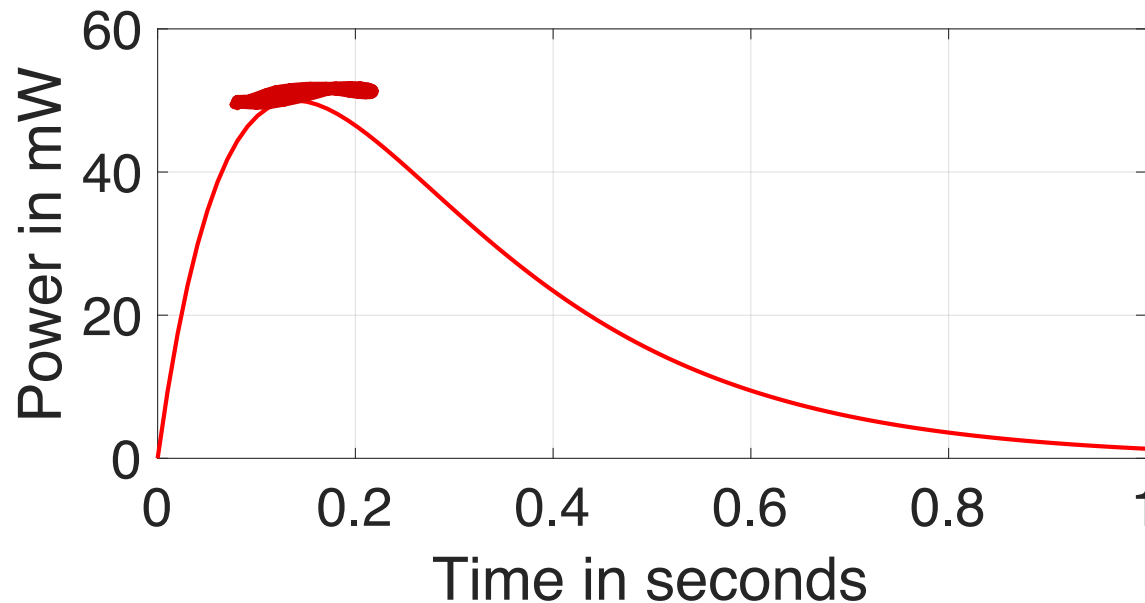
$$\begin{aligned} p(t) &= v(t) * i(t) \\ &= \underline{200 (e^{-5t} - e^{-10t}) \text{ mW}} \end{aligned}$$




- Calculus gets us the extreme point:

$$\frac{dp(t)}{dt} = 200 (-5e^{-5t} + 10e^{-10t})$$

- This derivative is zero when

$$t = \frac{\ln 2}{5} = \underline{0.139 \text{ sec.}}$$

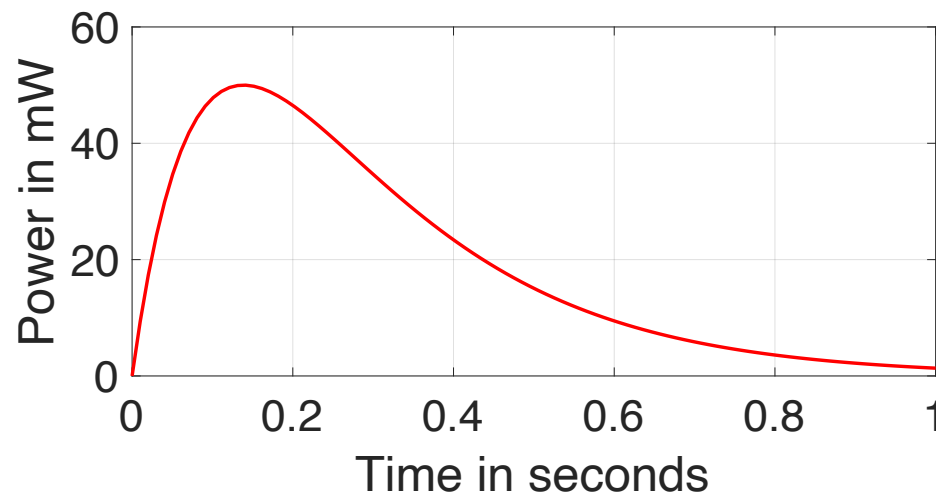
- The peak is  $p\left(\frac{\ln 2}{5}\right) = 50 \text{ mW}$






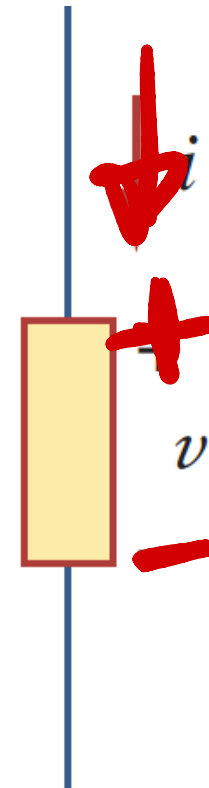
## 2 Terminal Devices

- Typical components for ELE 212/215:
  - Voltage and current sources
  - Resistors, inductors, capacitors
- Each has its own  $v, i$  characteristic
- Passive sign convention
  - Power  $p = v i$ 
    - $p > 0$  “absorbed”
    - $p < 0$  “delivered”


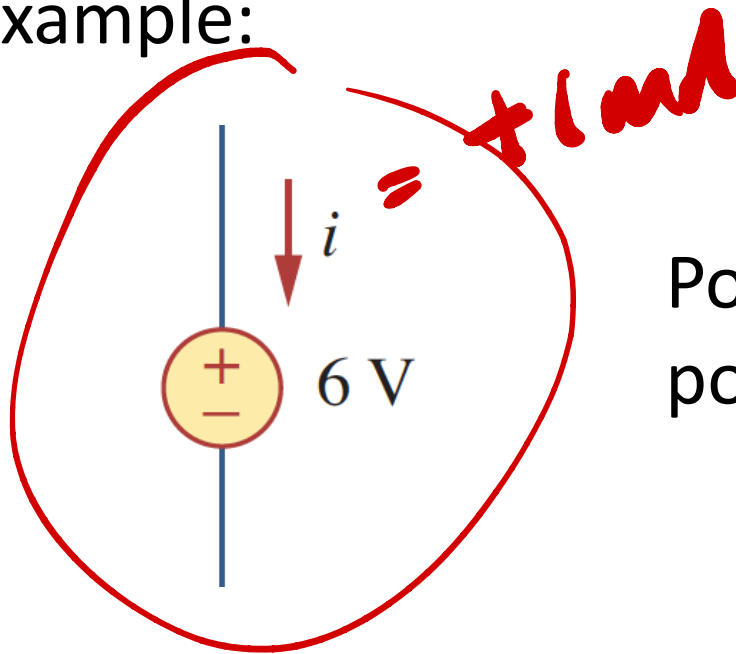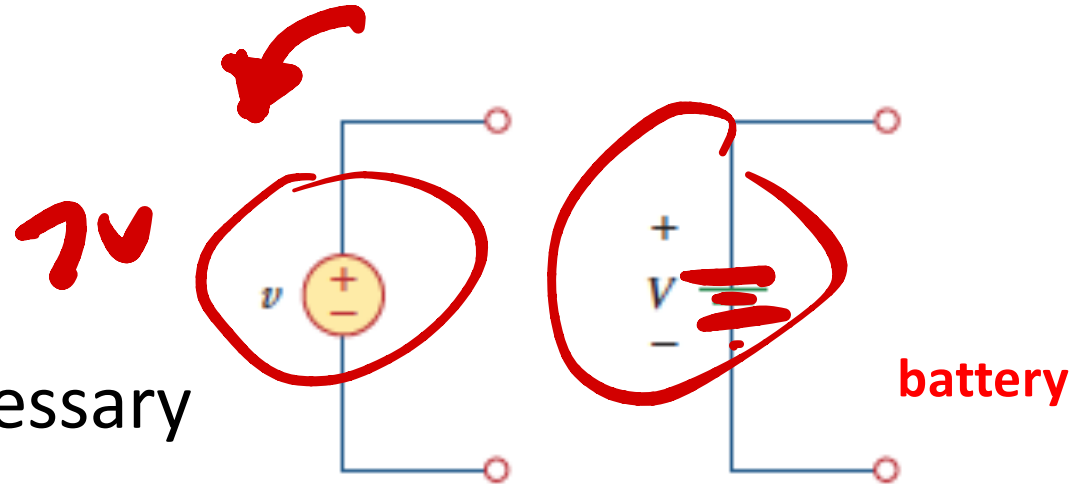
# Sources



- Voltage source:
  - Fixed voltage
  - Any current necessary
  - Example:



Power  $p = v i$  can be positive or negative



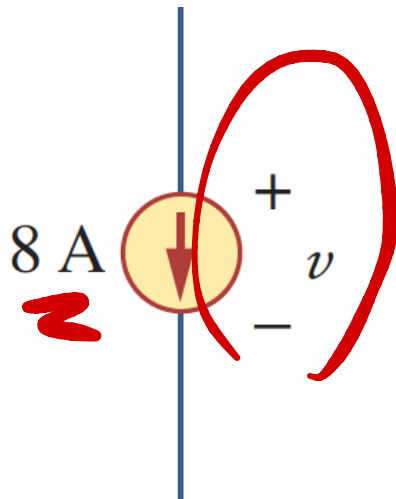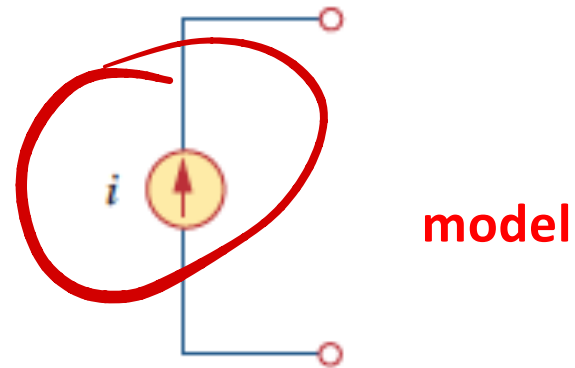- Current source:
  - Fixed current
  - Any voltage necessary
  - Example:





Power  $p = v i$  can be positive or negative



# Resistors

- Ohm's Law

$$v = R i$$

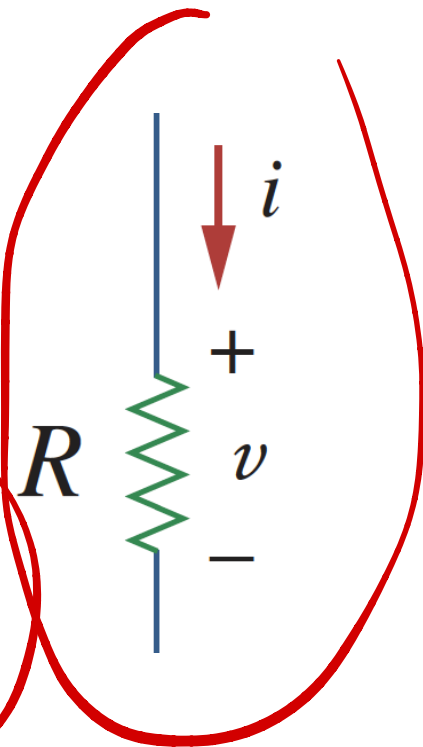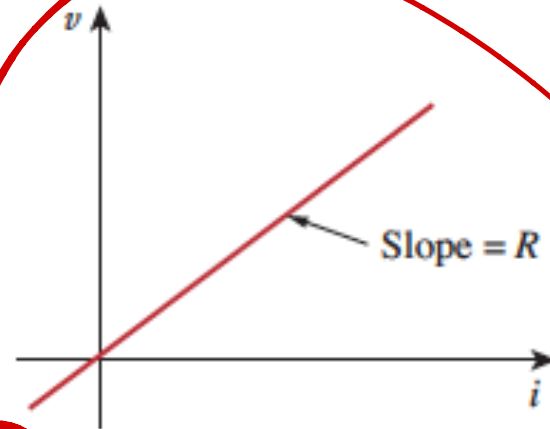

- Unit is ohms ( $\Omega$ ,  $k\Omega$ ,  $M\Omega$ )

– Also written as  $i = \frac{v}{R} = v G$

–  $G$  = conductance (mhos, Siemens,  $\mathcal{U}$ )

- Power is  $p = v i = R i^2 = \frac{v^2}{R} = v^2 G$

– Always positive; power is always absorbed

**Example:** If the current through a 60  $\Omega$  resistor is 0.3 A, what is the voltage across it? How much power is it absorbing?

$$V = RI = 60 (.3) = 18 \text{ V}$$

$$P = V \cdot I = 18 \cdot (.3) = 5.4 \text{ W}$$

$$= I^2 R \quad (.3)^2 \cdot 60 = 5.4 \text{ W}$$

$$= \frac{V^2}{R} = 5.4 \text{ W}$$

**Practice problem:** I'm thinking of buying an electric car. How much would I save by having a home charger versus using the publicly available charging stations?

– Assumptions:

- Average 330 miles from 82 kWh (Tesla model 3)
- Drive 15,000 miles per year
- Electricity rate of 18 cents/kWh at home vs 42 cents/kWh at the chargers

0.424 mA

**Practice problem:** If the voltage across a  $33\text{ k}\Omega$  resistor is 14 volts, what is the current through the resistor?

137 volts

**Practice problem:** If a  $150\text{ k}\Omega$  resistor has a power rating (i.e. maximum power allowed) of  $1/8$  watt, what is the maximum voltage that can be applied across the resistor?



3.57 mA

**Practice problem:** If the voltage across a  $56\ \Omega$  resistor is 200 mV, what is the current through the resistor?

34.6 mA

**Practice problem:** If a  $100\ \Omega$  resistor is absorbing 120 mW, what is the current through the resistor?