



Lecture 7

Basics – 7 of 7

odds and ends

Special Cases

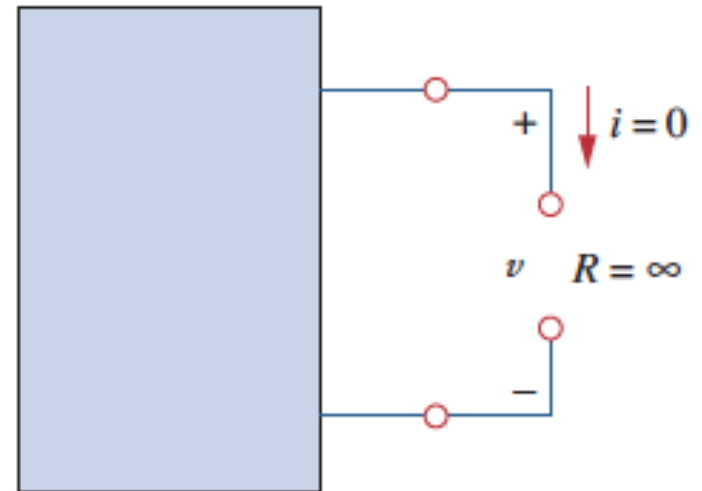
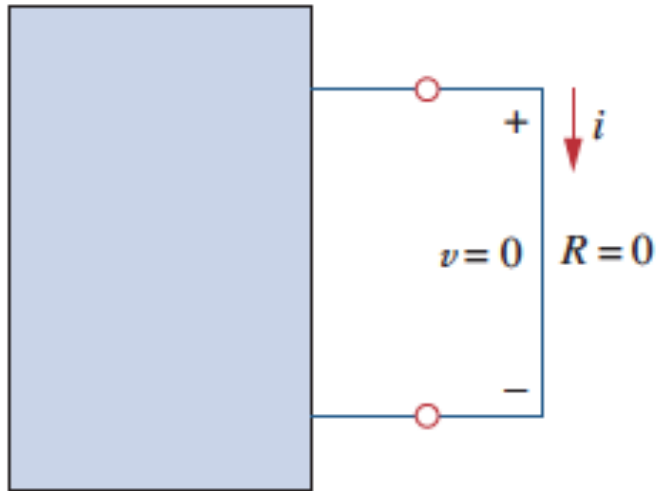
- Short circuit ($R = 0$)
- Open circuit ($R = \text{infinity}$)



- Voltage division

$$v_1 = \frac{R_1}{R_1 + R_2} v$$



$$v_2 = \frac{R_2}{R_1 + R_2} v$$

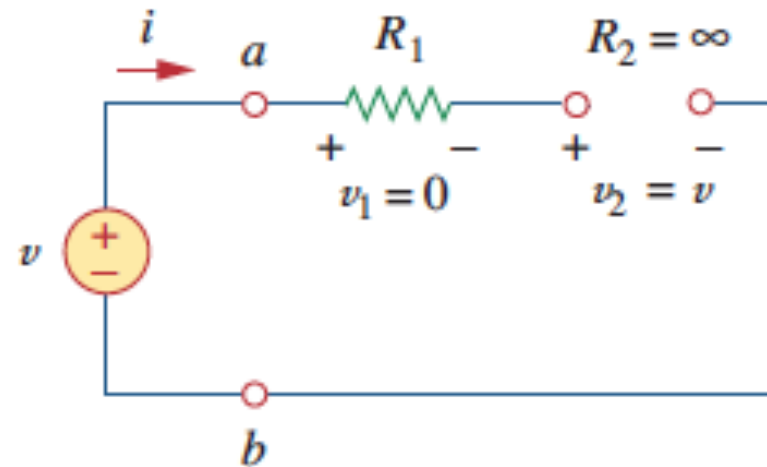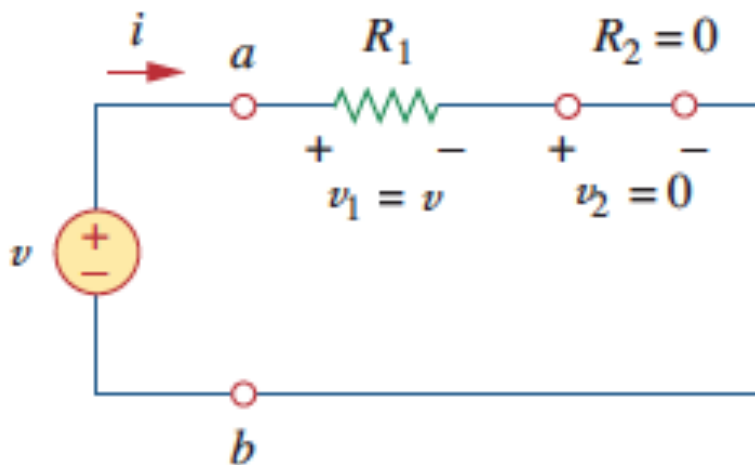


- Current division

$$i_1 = \frac{R_2}{R_1 + R_2} i$$


$$i_2 = \frac{R_1}{R_1 + R_2} i$$

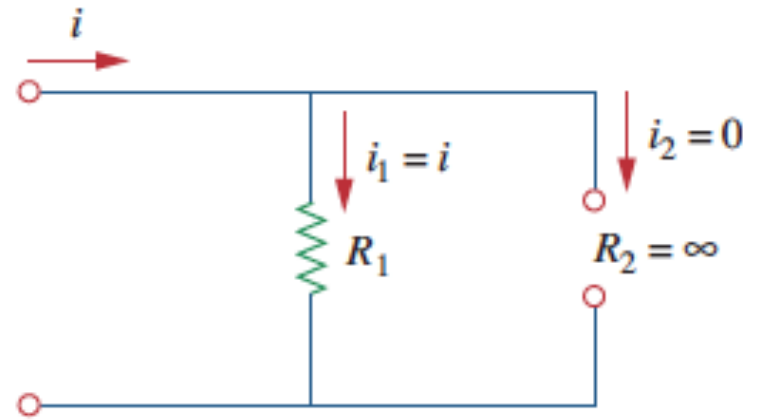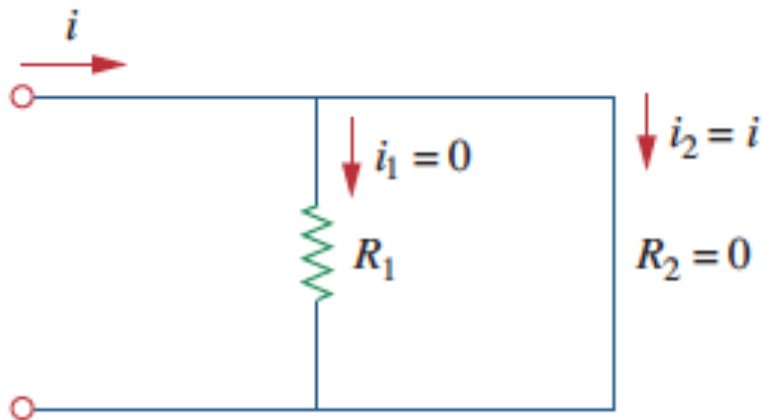


Example:

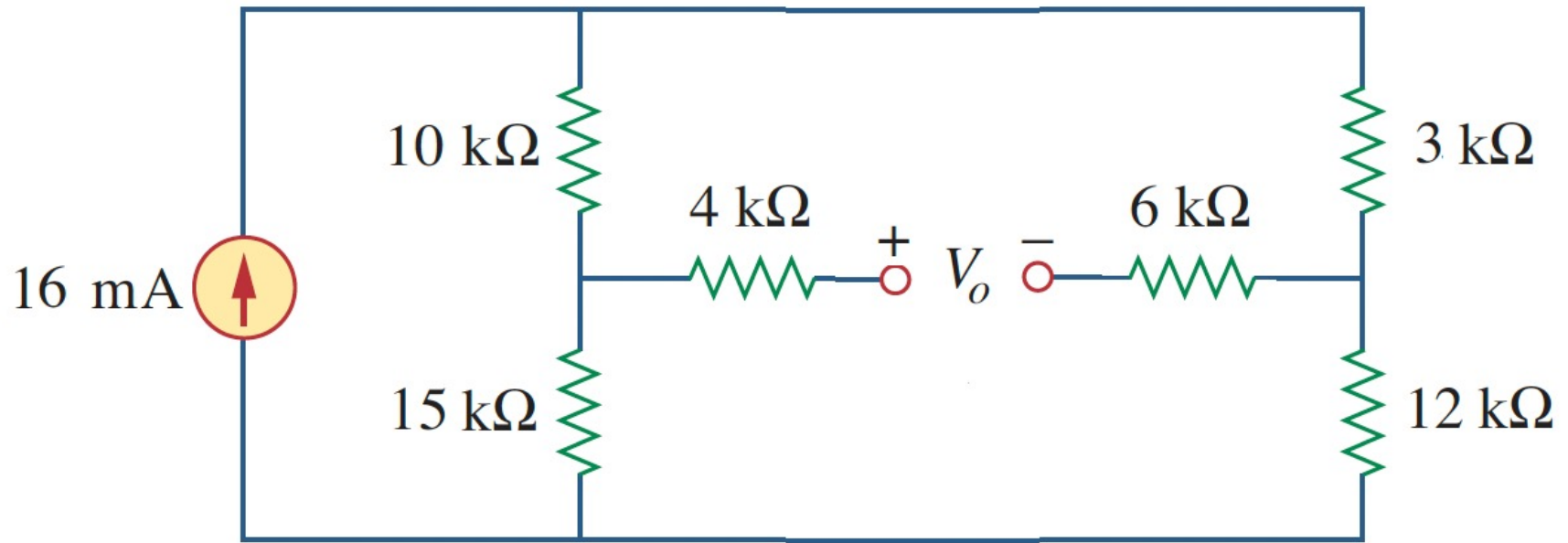


Example: find i and v

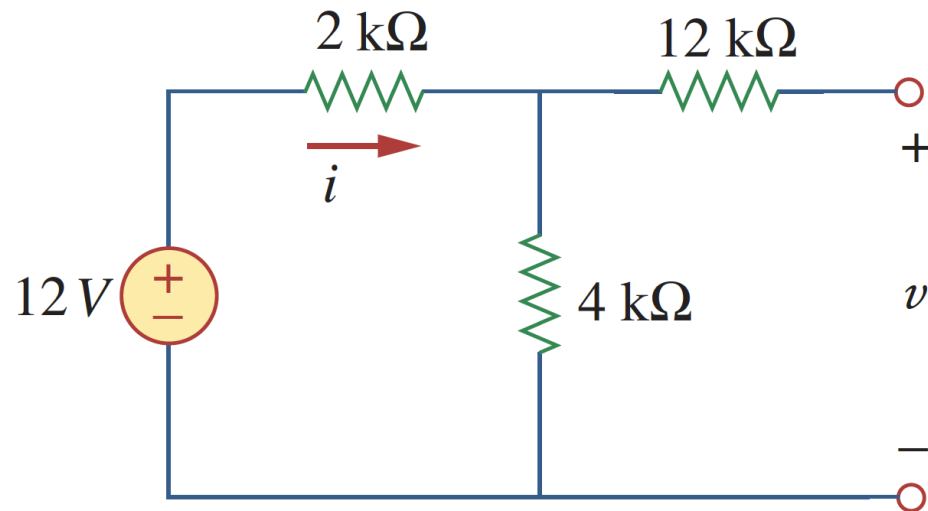


Example: find i and v

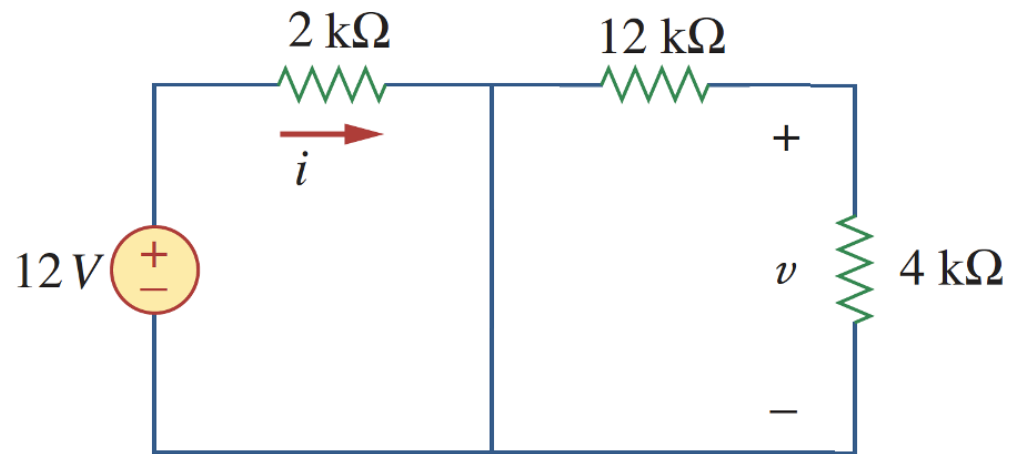



Do We Allow Series Sources?


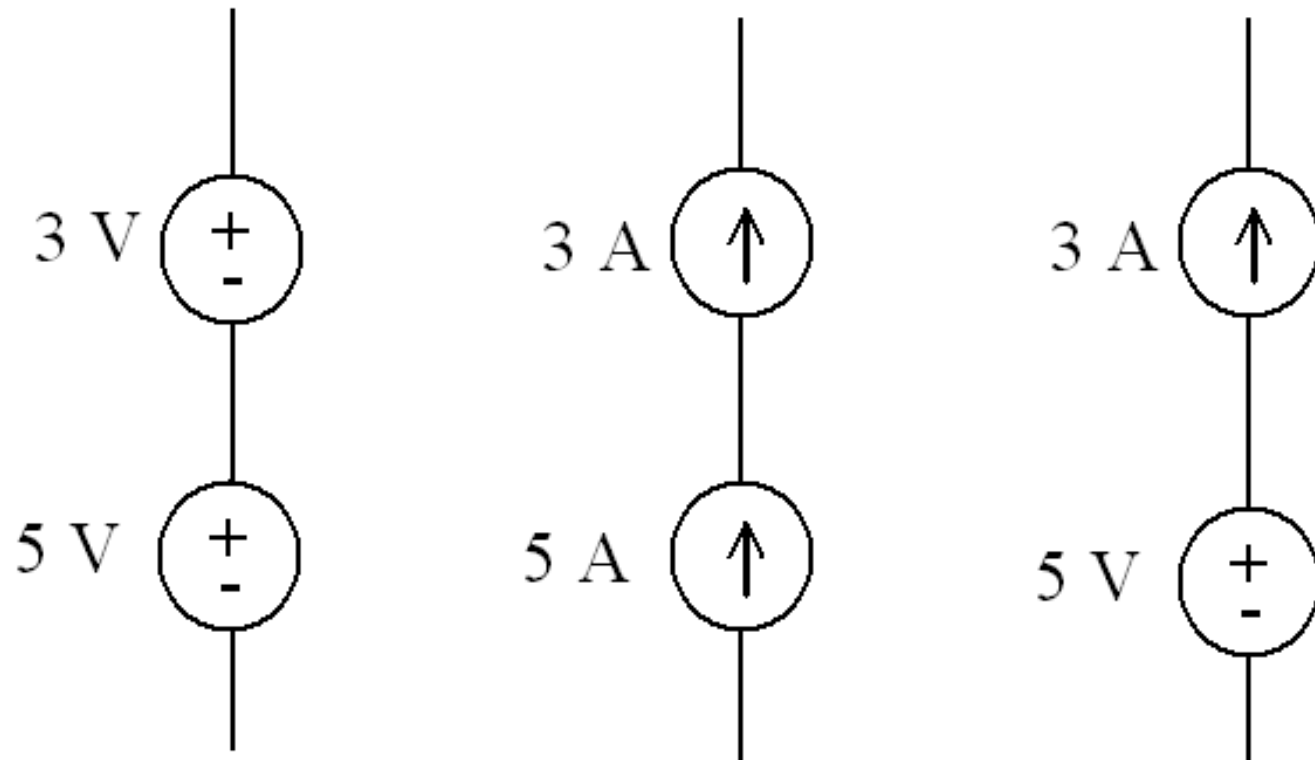


How about parallel sources?

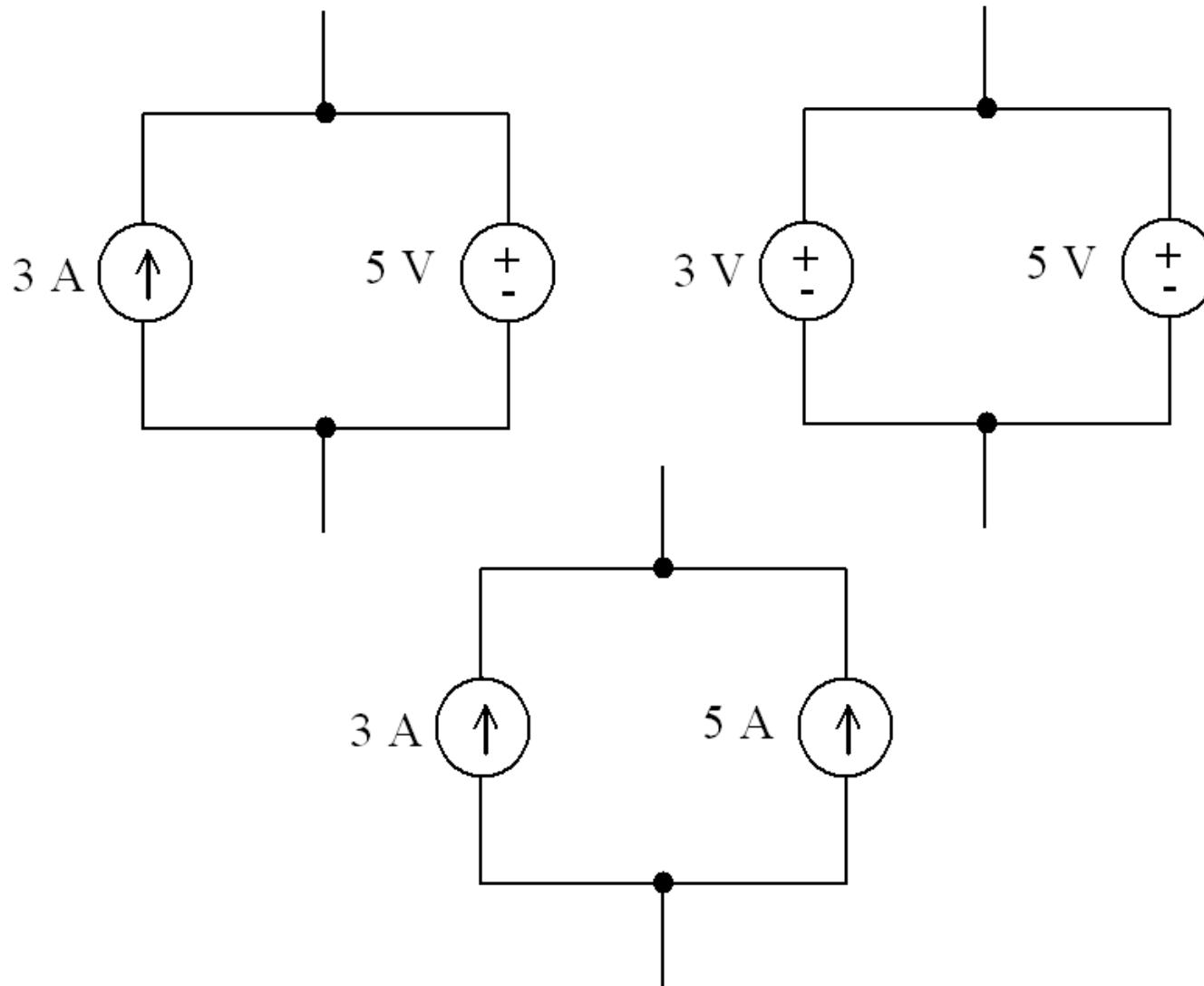


How about resistors and sources?

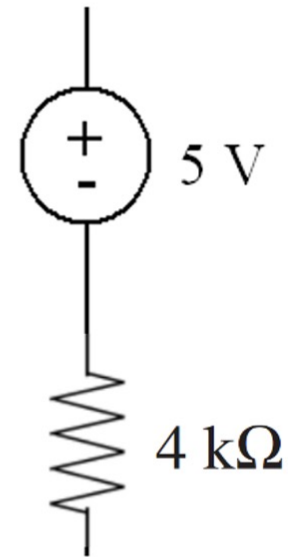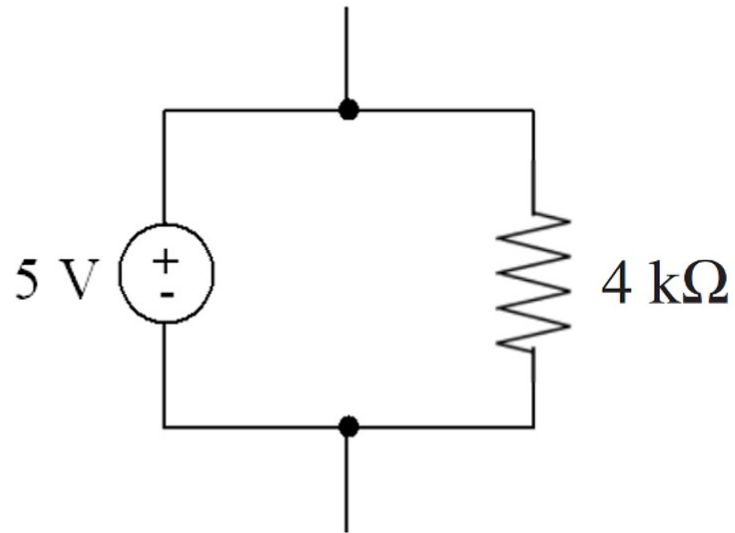


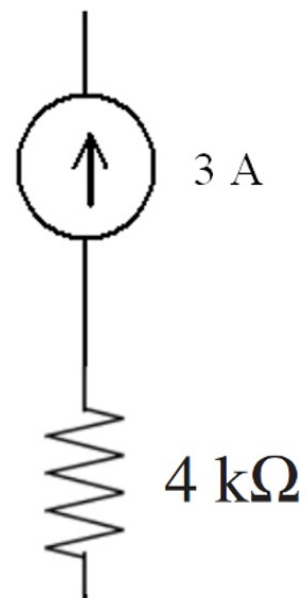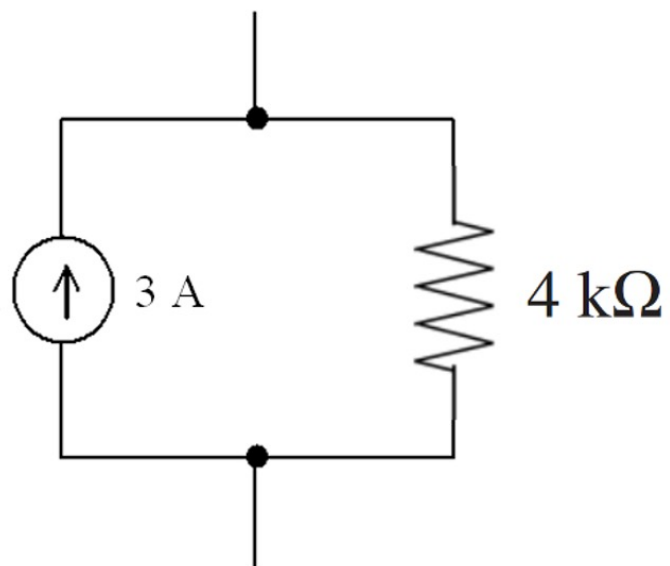

Example: find I

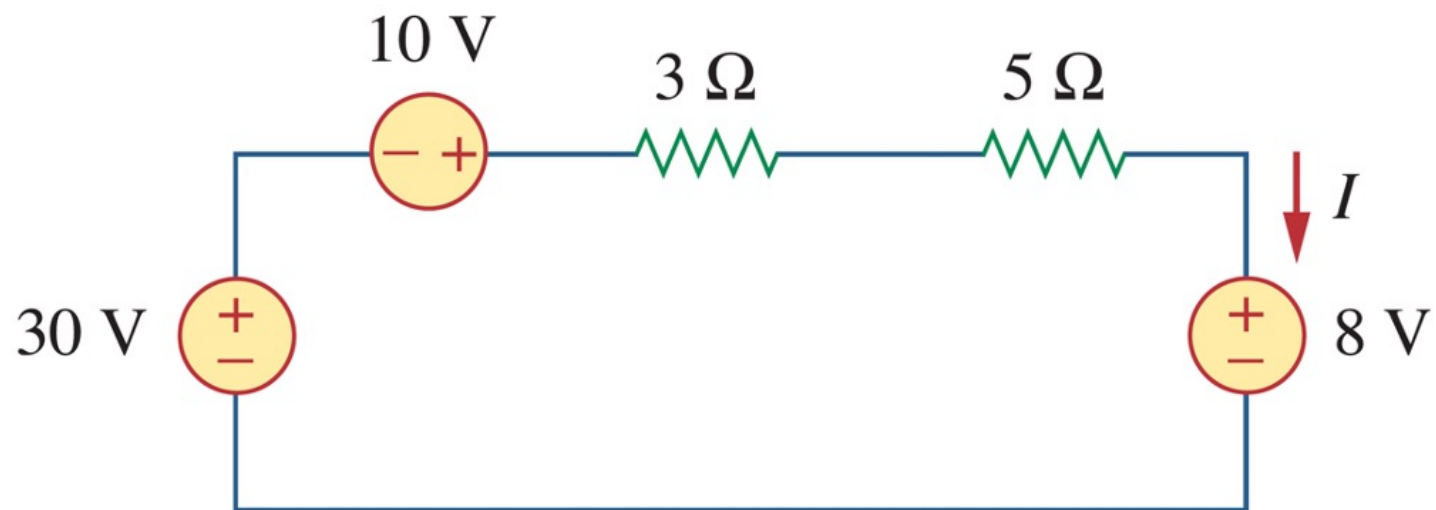


And now?

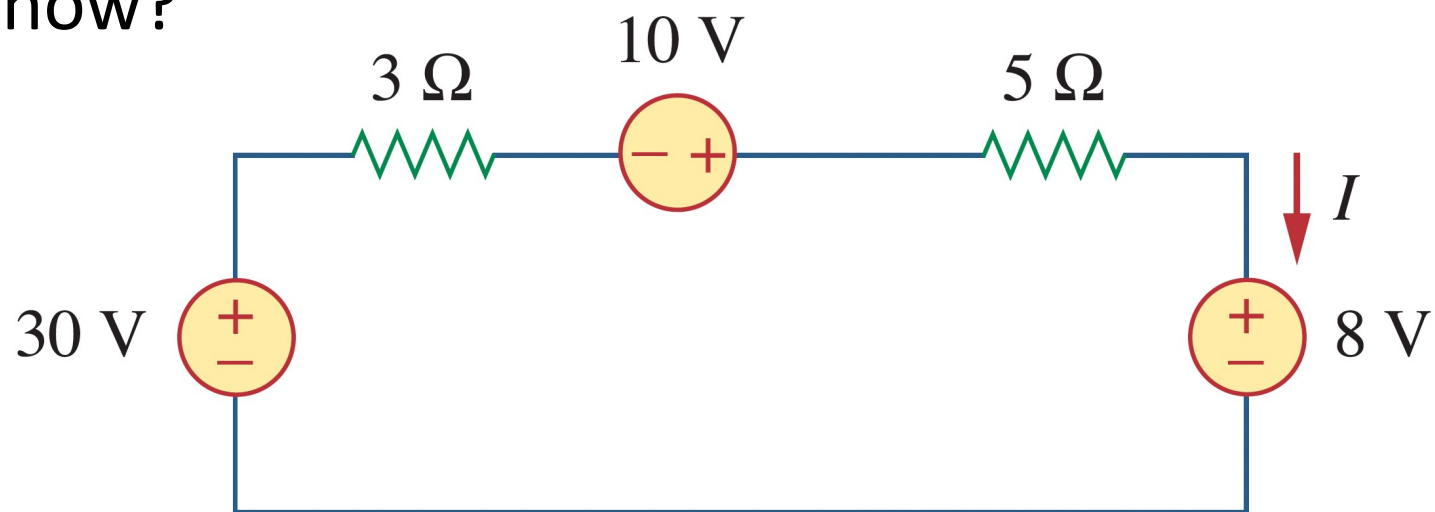

Time Varying Example

Consider this voltage division

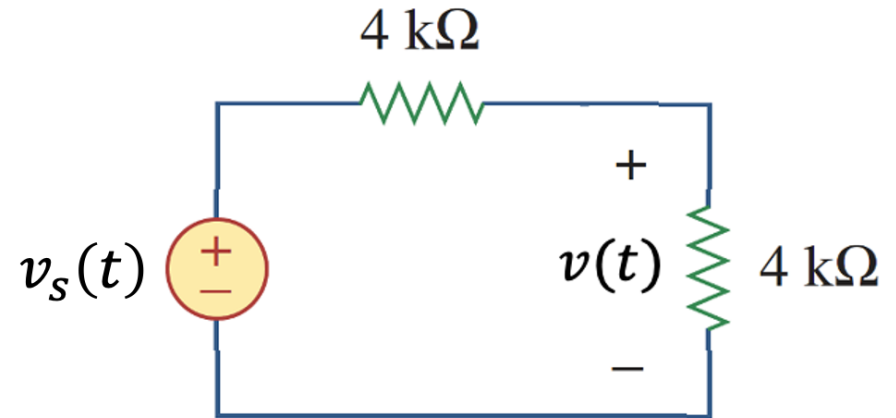

- $v_s(t) = 12\text{ V}$, then $v(t) = 6\text{ V}$
- If $v_s(t)$, then ???

