


# Lecture 20

## Phasors – 6 of 9

more examples
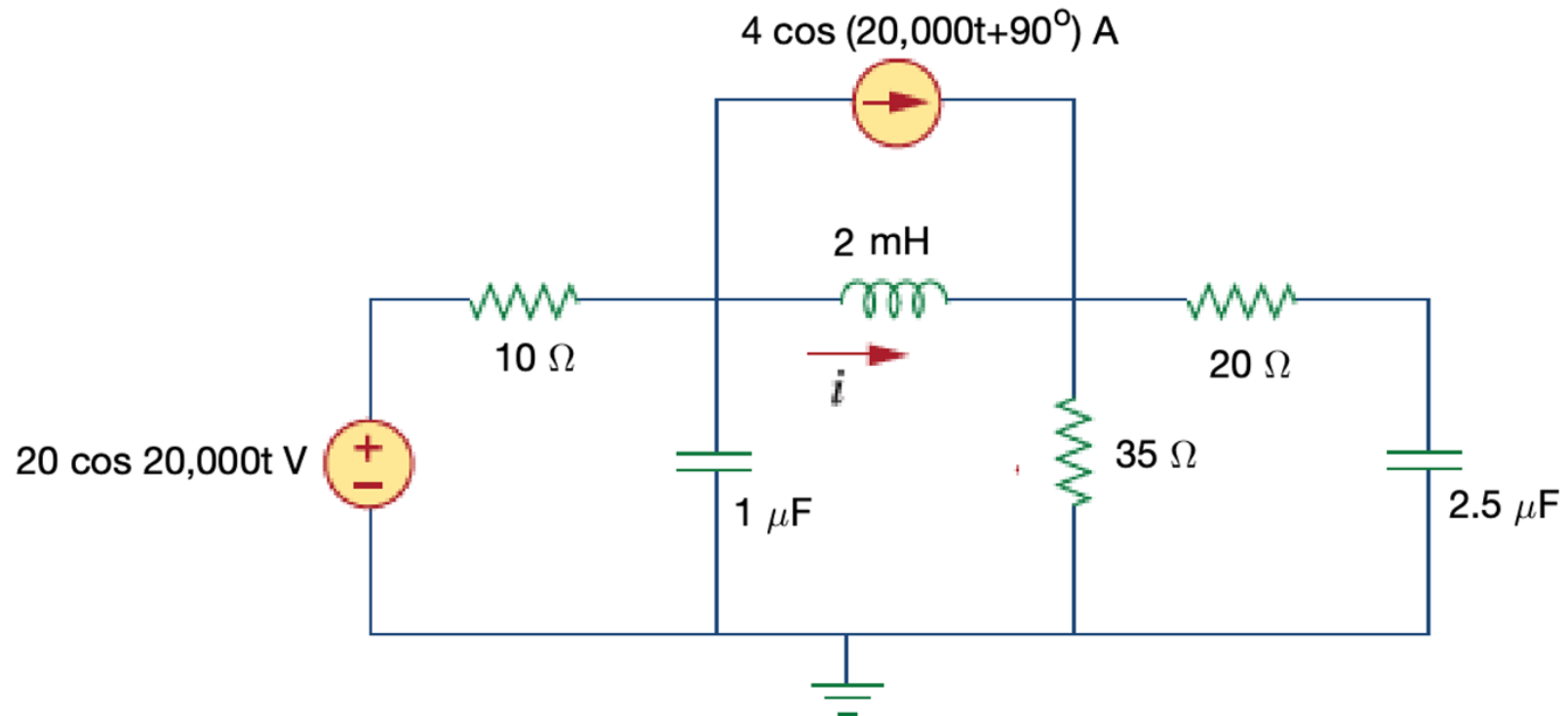
# Where Are We?


- What we know how to solve: find  $i(t)$ :




$$1.91 \cos(20,000t - 123^\circ) \text{ A}$$
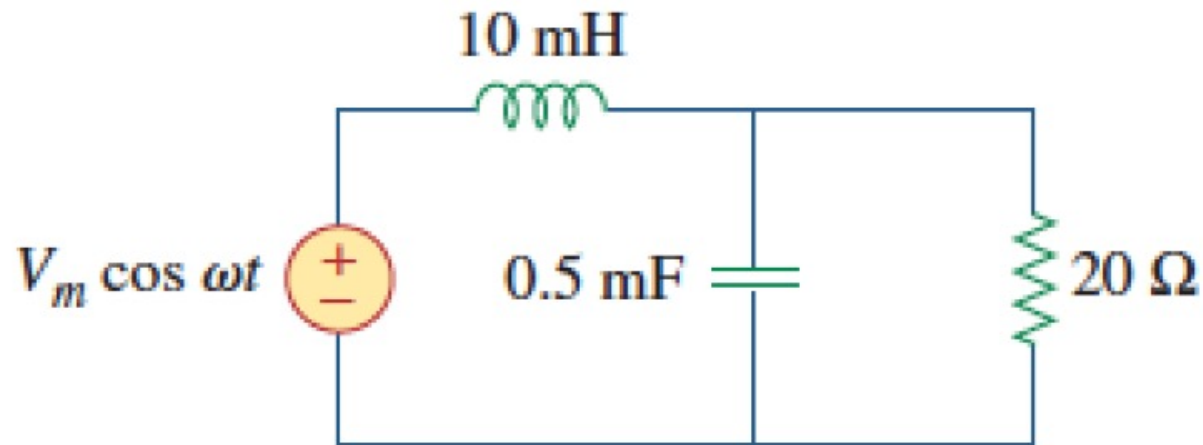
# Other Question Types

Sample: for what frequency is the source current the largest?





- Method?
  - Numerical calculation
  - Analysis (paper and symbolic)

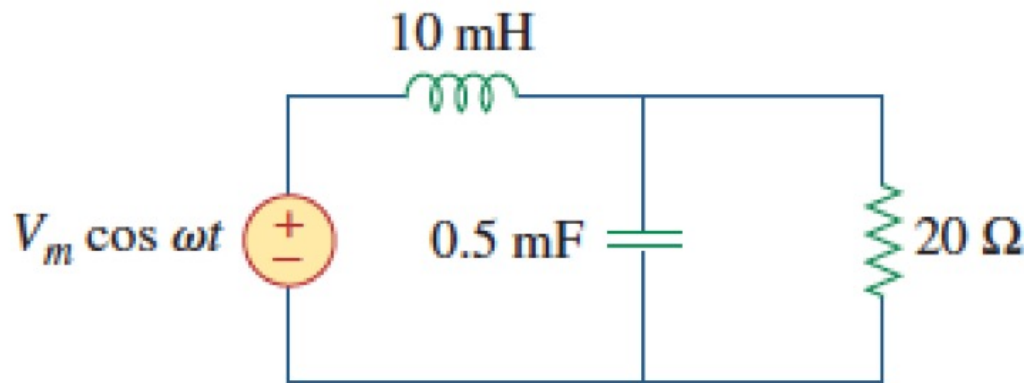

Idea 1 – compute it

```
om = logspace(0,6,500);
ZC = 1./(1j*om*0.5e-3);
ZP = 20*ZC./(20+ZC);
I0 = 1./(1j*om*10e-3+ZP);
semilogx(om,(abs(I0)), 'linewidth', 3)
```

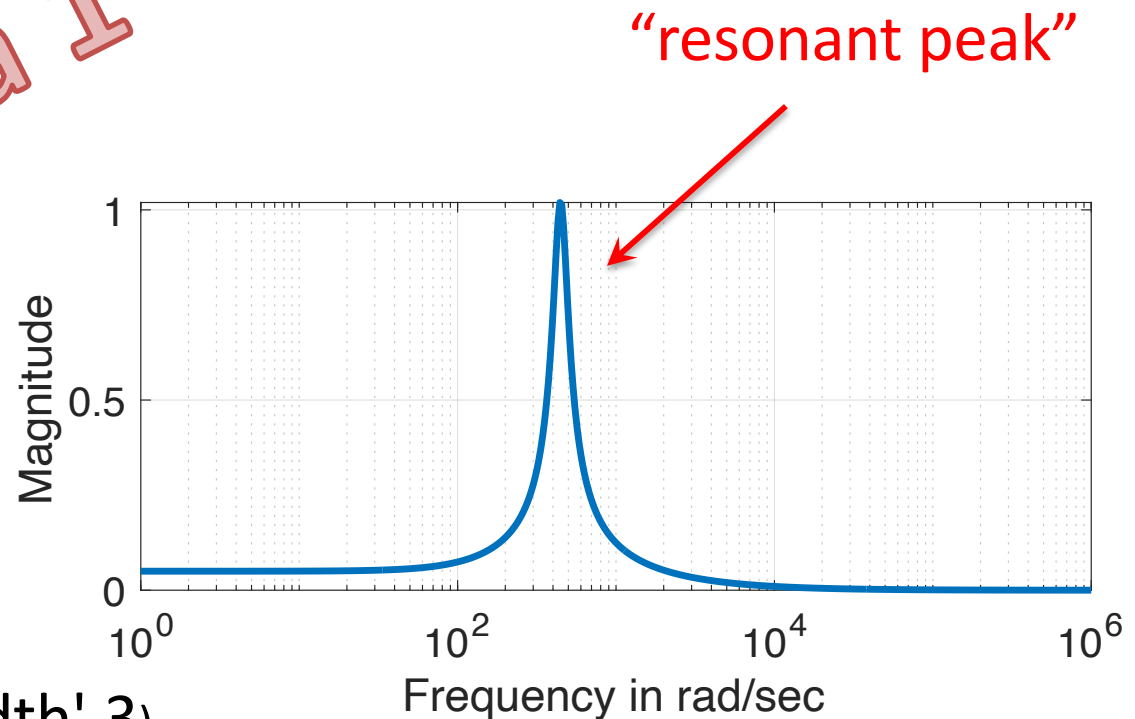

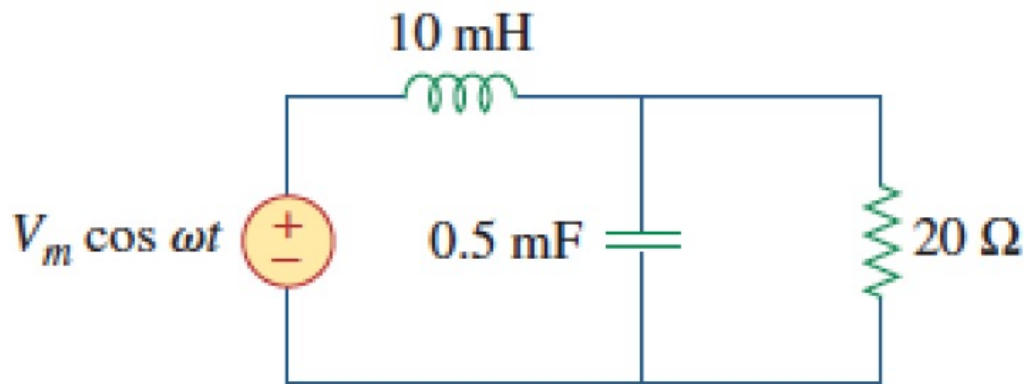


Idea 2 – analyze it

- Equivalent impedance  $Z = Z_L + R || Z_C$
- Source current  $I_S = -\frac{V_m}{Z}$
- By “largest” we mean largest in magnitude

$$|I_S| = \left| \frac{V_m}{Z} \right| = \frac{|V_m|}{|Z|} = \frac{V_m}{|Z|}$$

- So largest is the same as finding minimum  $|Z|$

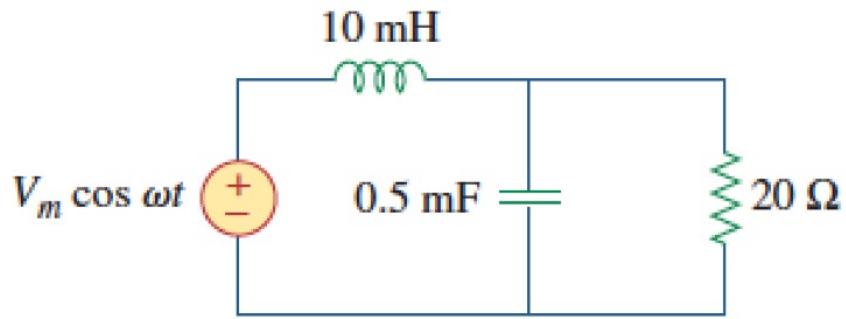

$$Z = Z_L + R || Z_C = \frac{j\omega}{100} + \frac{(20) \left( -j \frac{200}{\omega} \right)}{20 - j \frac{200}{\omega}} = \dots$$

and

$$|Z| = \sqrt{\frac{\omega^4 - 390,000\omega^2 + 40 \times 10^9}{10,000(\omega^2 + 10,000)}}$$

To minimize  $|Z|$ , we set its  $\omega$  derivative to zero; for math simplicity, let's work with the square of  $|Z|$

$$|Z|^2 = \frac{\omega^4 - 390,000\omega^2 + 40 \times 10^9}{10,000(\omega^2 + 10,000)} = \frac{N(\omega)}{D(\omega)}$$

And we want

$$\frac{\partial |Z|^2}{\partial \omega} = \frac{\omega(\omega^4 + 20,000 \omega^2 - 439 \times 10^8)}{5,000(\omega^2 + 10,000)^2} = 0$$

or

$$\omega^4 + 20,000 \omega^2 - 439 \times 10^8 = 0 \rightarrow \omega = 447$$

```
>> syms w real
>> zc = 1/(1j*w*5e-4)
```

```
zc =
```

```
-2000i/w
```

```
>> zp = 20*zc/(20+zc)
```


```
zp =
```

```
40000i/(w*(2000i/w - 20))
```

```
>> z = 1j*w*1e-2 + zp
```

```
z =
```
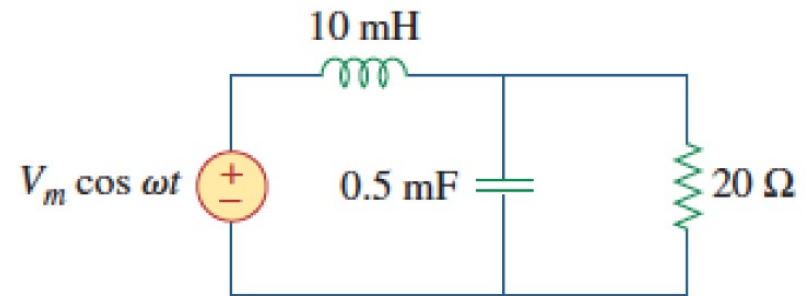
```
(w*1i)/100 + 40000i/(w*(2000i/w - 20))
```




Or use a tool



```
>> H = 1/z;
>> aH = sqrt( real(H)^2 + imag(H)^2 );
>> pretty(aH)
```
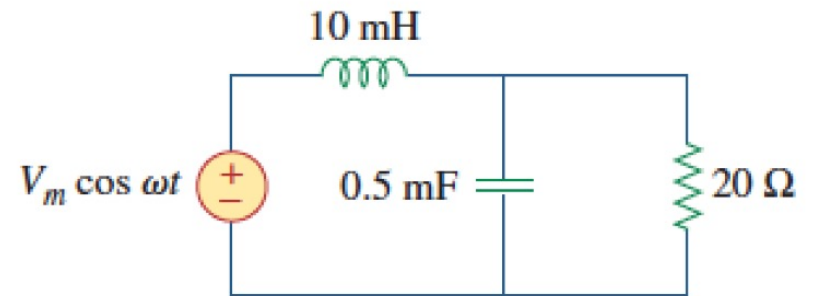
$$\sqrt{\frac{\frac{800000}{100} - \frac{\frac{4000000}{w^2} + 400}{w}}{\sqrt{\frac{640000000000000000}{4w\sqrt{\frac{4000000}{w^2} + 400}} + \frac{800000}{100} - \frac{\frac{4000000}{w^2} + 400}{w}}}}$$



where

$$\#1 == \sqrt{\frac{640000000000000000}{4w\sqrt{\frac{4000000}{w^2} + 400}}} + \sqrt{\frac{800000}{100} - \frac{\frac{4000000}{w^2} + 400}{w}}$$

```
>> daH = diff(aH,w);
>> solve(daH,w)
```



ans =

$$\begin{aligned} & (20000*110^{(1/2)} - 10000)^{(1/2)} \\ & -(20000*110^{(1/2)} - 10000)^{(1/2)} \end{aligned}$$


```
>> eval(ans(1))
```

ans =

446.9472

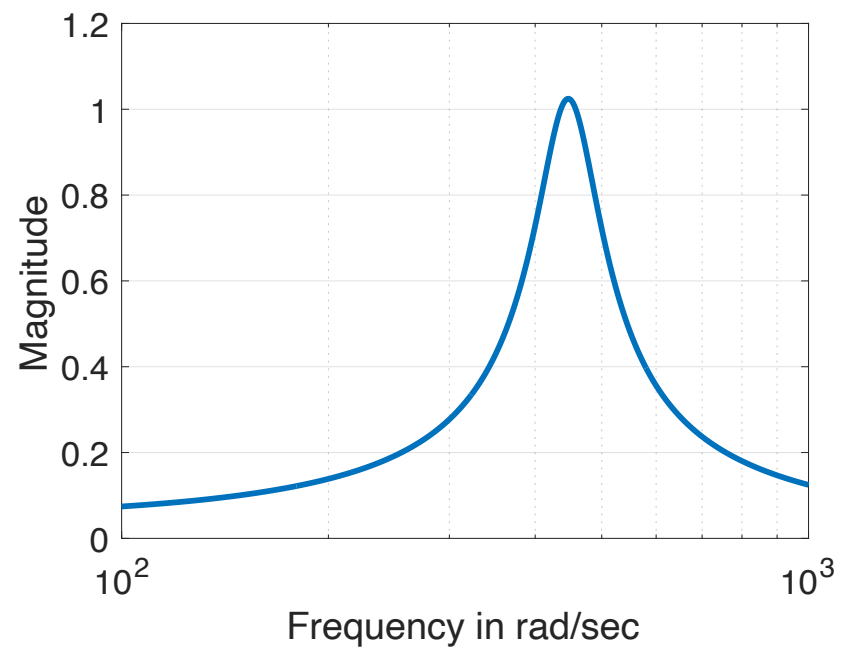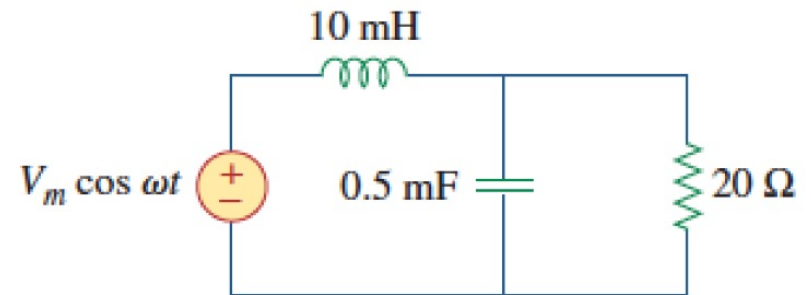

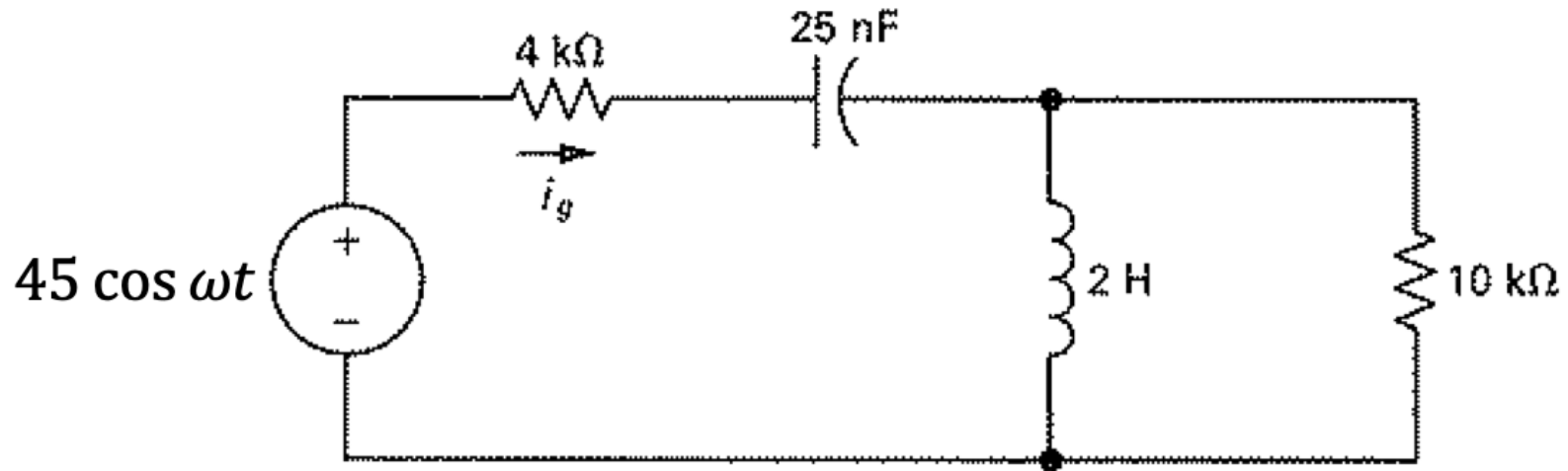
**Example:** At what frequency  $\omega$  is  $i_g$  in phase with the voltage source?



$10^4 \text{ rad/sec}$


$10^4$  rad/sec

**Example:** We model a real inductor as shown with a series parasitic resistance  $R_L$ . To measure its parameters,  $R_L$  and  $L$ , we build the circuit shown (with a 60 Hz source) and use an AC voltmeter to measure the amplitudes of the component voltages. Given  $|V_S| = 120\text{ V}$ ,  $|V_R| = 100\text{ V}$ ,  $|V_L| = 30$ , find  $R_L$  and  $L$ .

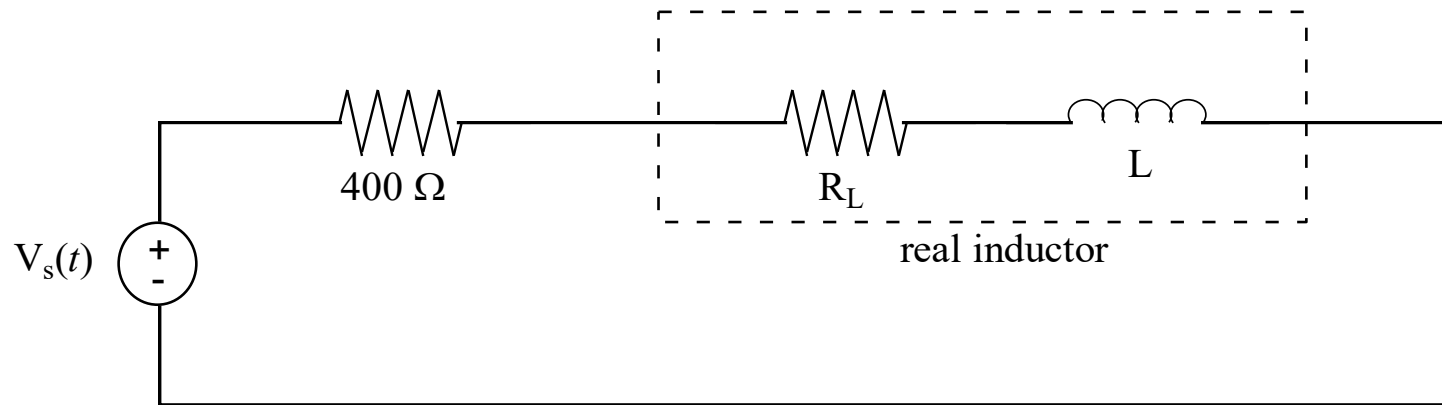

$70\ \Omega, 259\ mH$

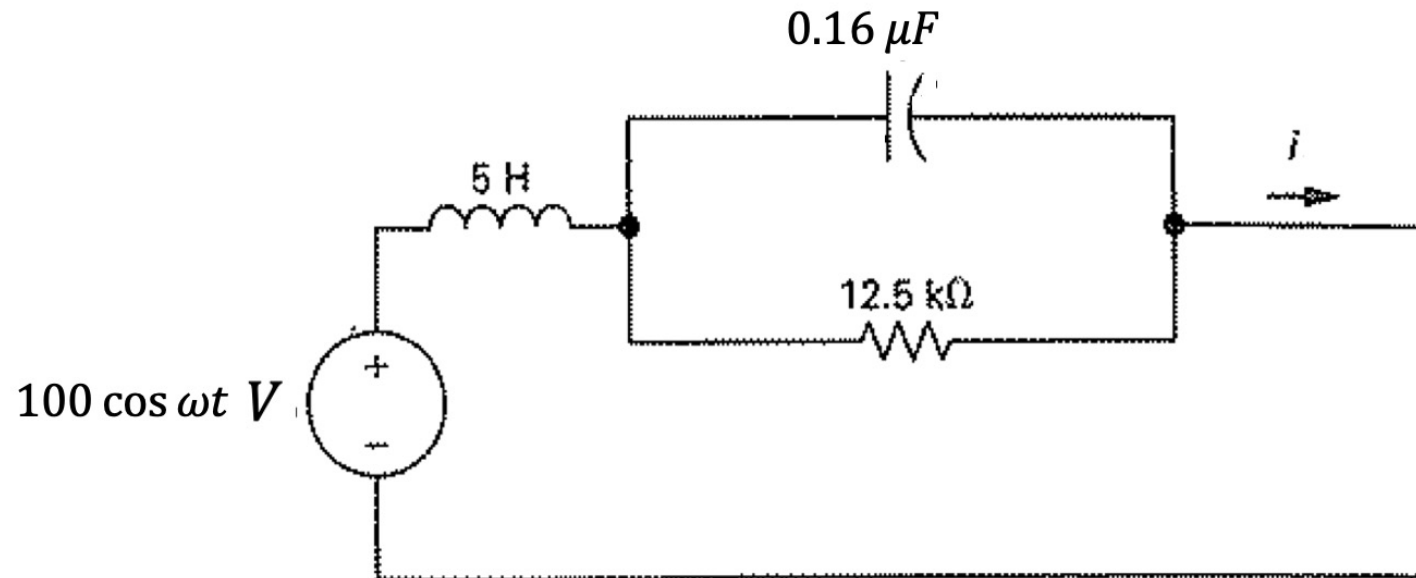**Practice problem:** At what frequency does the current  $i$  have the largest magnitude? What is that magnitude?



$$1120 \frac{\text{rad}}{\text{sec}}; 43.8 \text{ mA}$$