

Lecture 22


Phasors – 8 of 9

op amps; start design

Op Amps and Phasors


- Recall the inverting amplifier

$$\text{gain} = -\frac{R_f}{R_i}$$

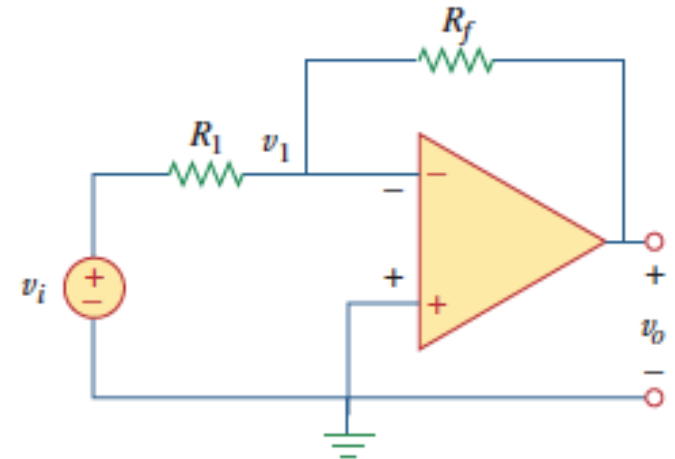


- Now, an “active” filter

$$H(\omega) = -\frac{Z_f}{Z_i}$$

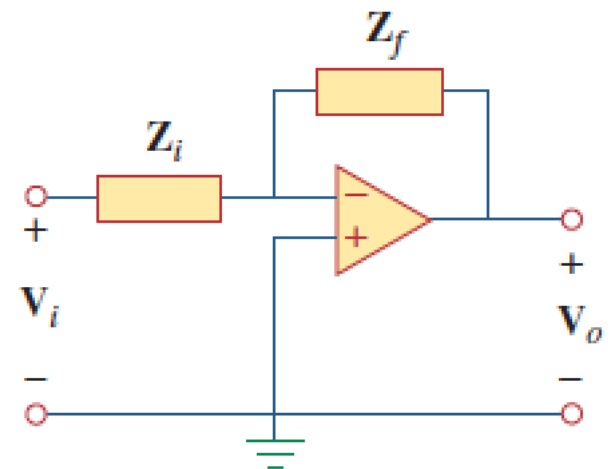


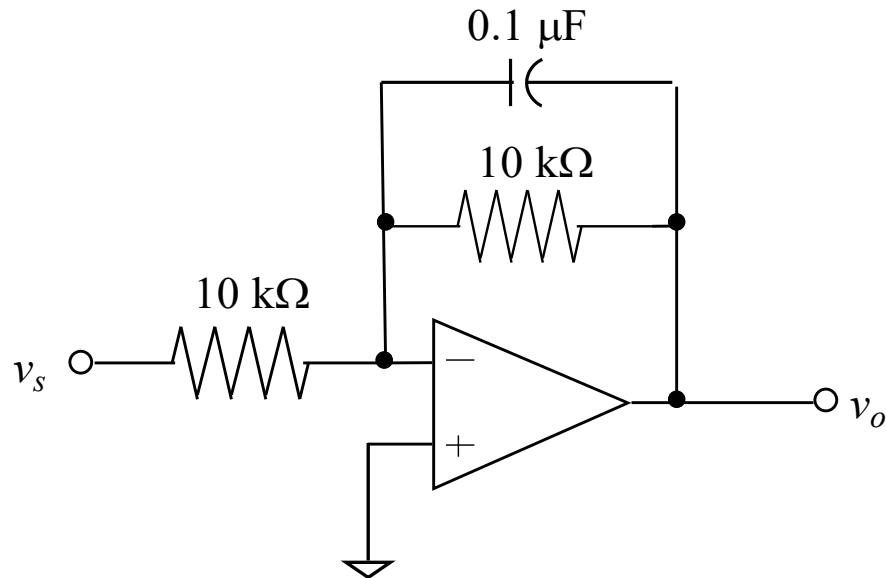Example: find v_o if $v_s(t) = 2 \cos 1000t$ V



$$v_o(t) = \sqrt{2} \cos(\omega t + 135^\circ) \text{ V}$$

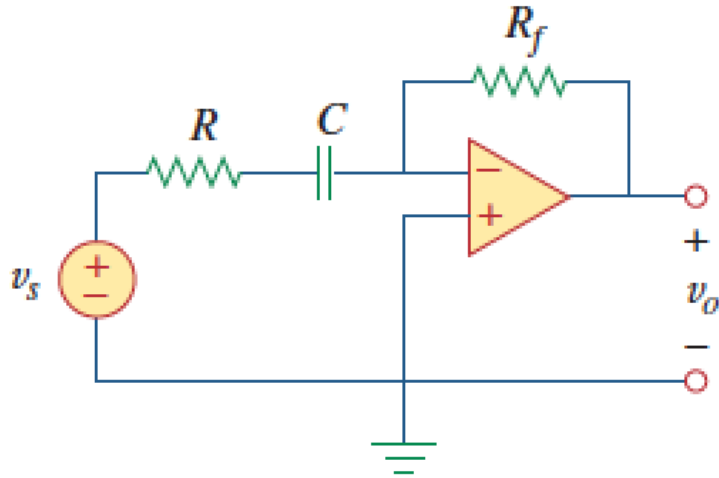
Example: find v_o if $v_i(t) = A \cos \omega t$ V Is the result low pass, bandpass, or highpass?



$$v_o(t) = \frac{A\omega R_f C}{\sqrt{1 + \omega^2 R_i^2 C^2}} \cos(\omega t + 180^\circ - \tan^{-1}(\omega R_i C)) \text{ V}$$


Analysis vs Design

- Voltage division **analysis** yields

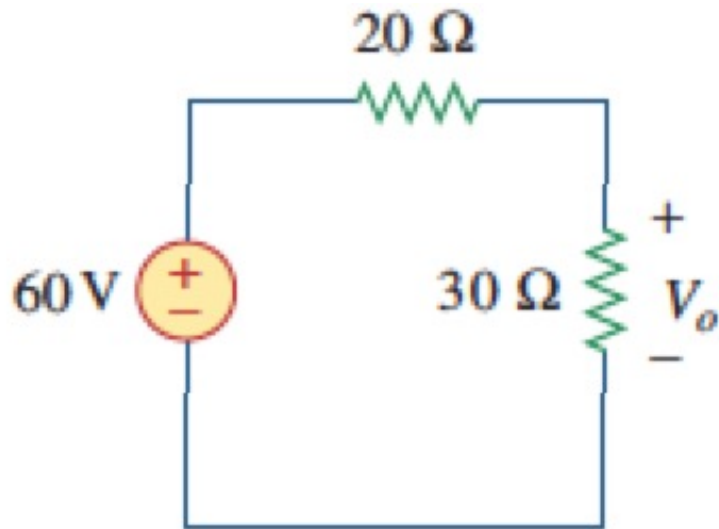

$$V_o = \frac{30}{20+30} 60 = 36 \text{ volts}$$

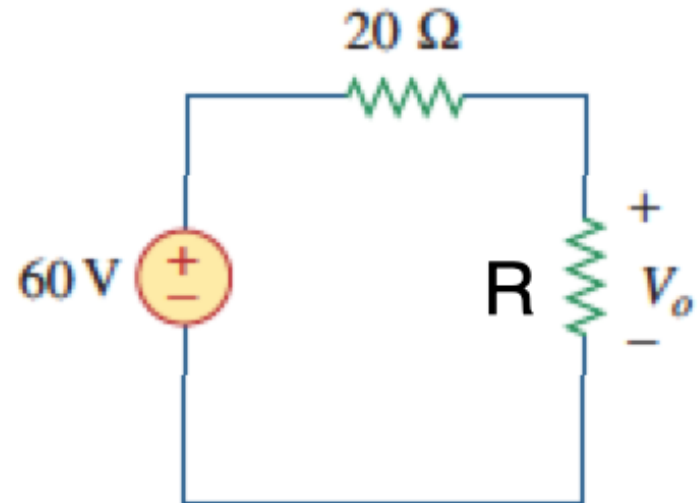
- **Design**: How do we choose R for $V_o = 10$ volts? And is this even possible?



- Solving :


$$V_o = \frac{R}{20 + R} 60 \quad \Rightarrow \quad R = \frac{20V_o}{60 - V_o}$$

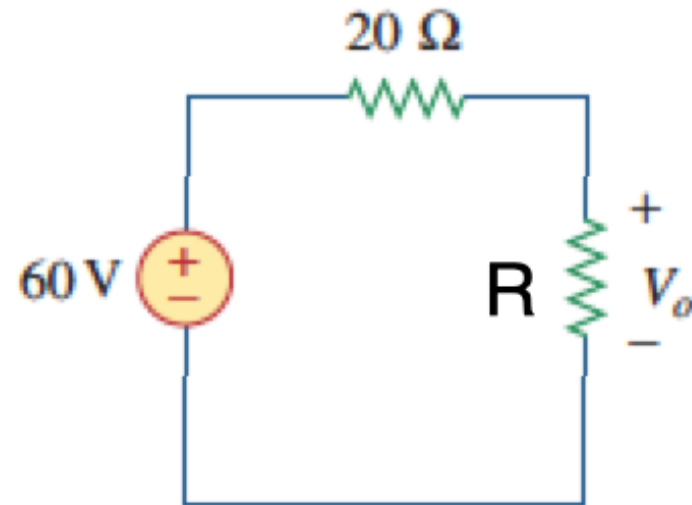- One solution if $0 < V_o < 60$
- None otherwise




Phasor Circuit **Design**

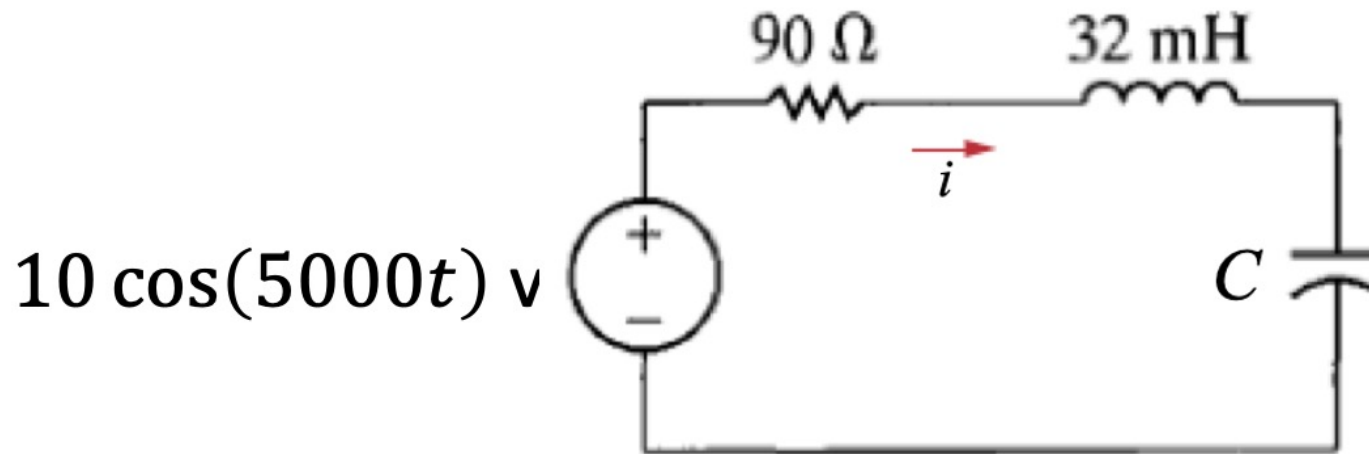- Choose components to achieve a certain goal.
- Example:



- Can you choose a capacitor C so that the steady state current i has a phase angle of -45° relative to the source ? If so, what is the current's amplitude?

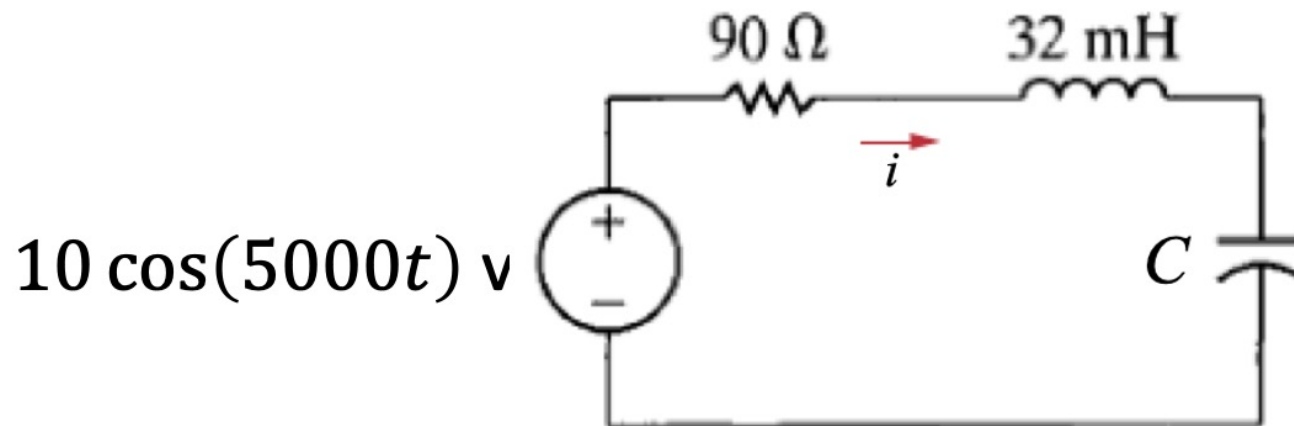
- Considerations:
 - Is the request even possible? How many degrees of freedom do you have versus the number of quantitative goals? Is more than one solution possible?
 - For our example, what range of angles is even possible?




```

om = 5000;
R = 90;
L = 32e-3;
ZL = 1j*om*L;
C = logspace(-9,-1,1000);
ZC = 1./(1j*om*C);
I = 10./(R+ZL+ZC);



```

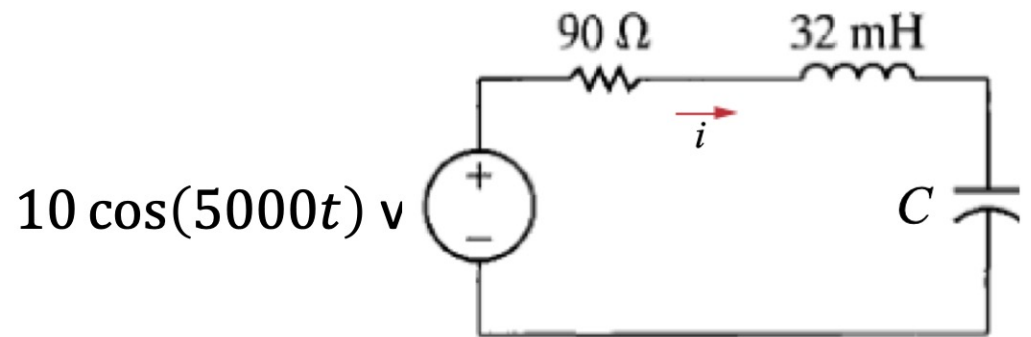


```

subplot(211)
semilogx(C,20*log10(abs(I)), 'linewidth',3)
xlabel('Capitance in Farads')
ylabel('Magnitude in dB')
set(gca,'fontsize',16)
grid on
subplot(212)
semilogx(C,180/pi*angle(I), 'linewidth',3)
xlabel('Capitance in Farads')
ylabel('Phase in degrees')
set(gca,'fontsize',16)
grid on

```

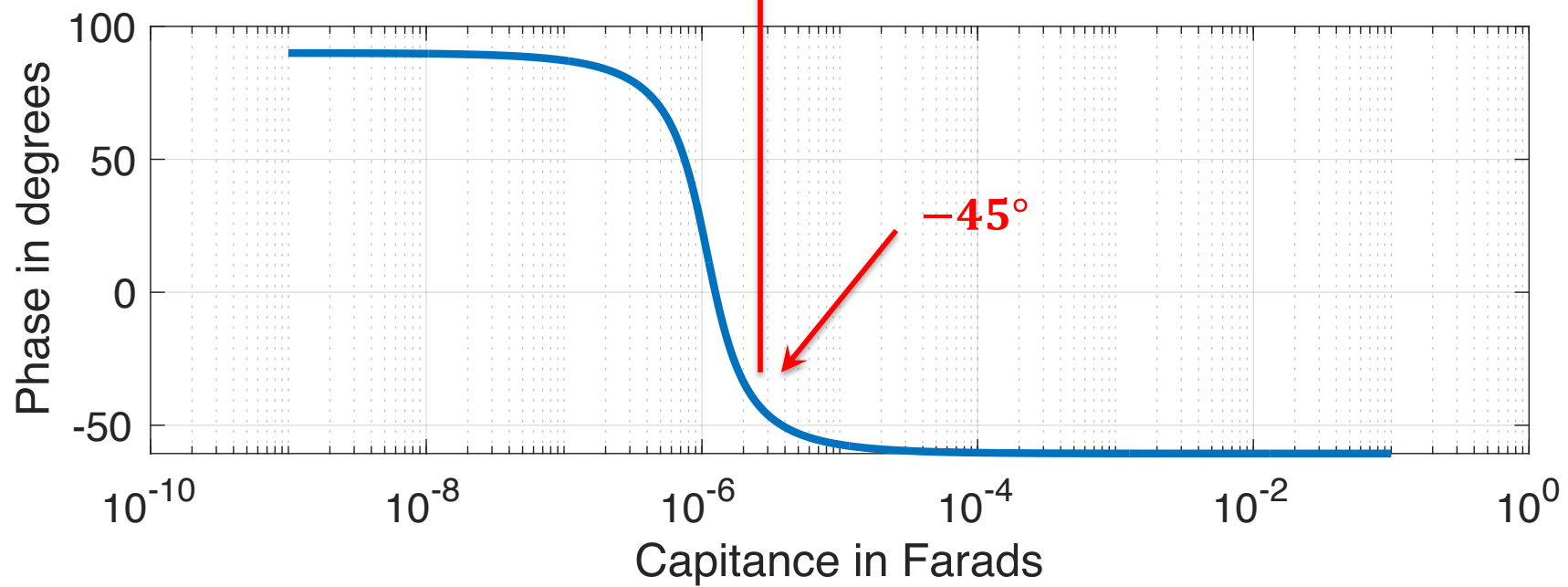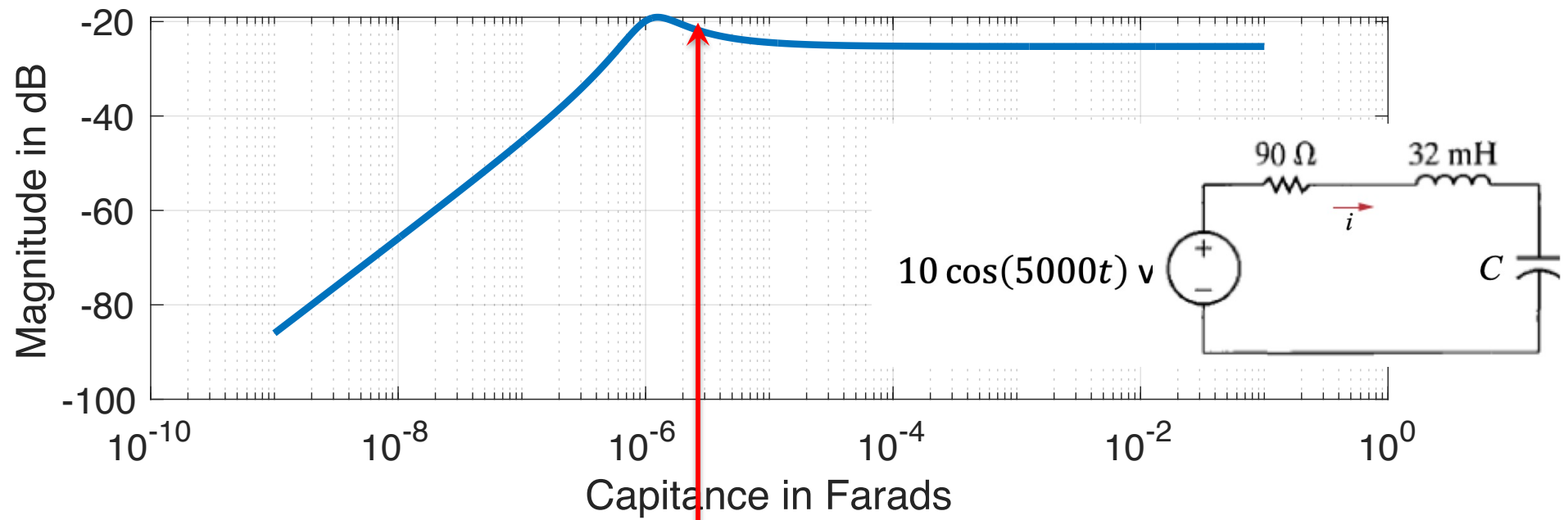


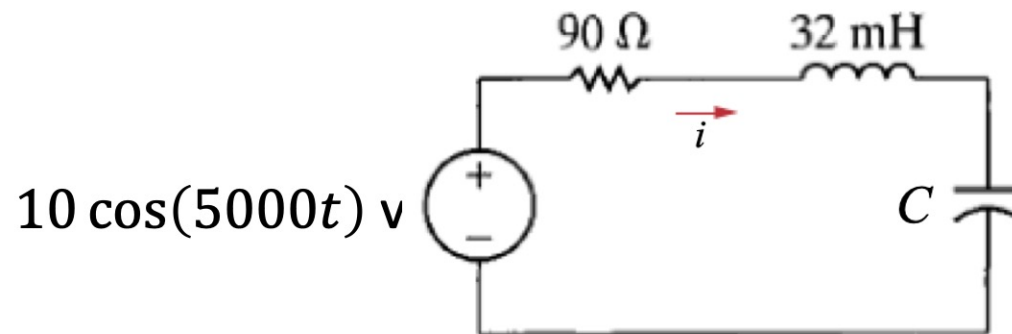Let's actually solve for C and the current's amplitude




$2.86 \mu F; 78.6 \text{ mA}$

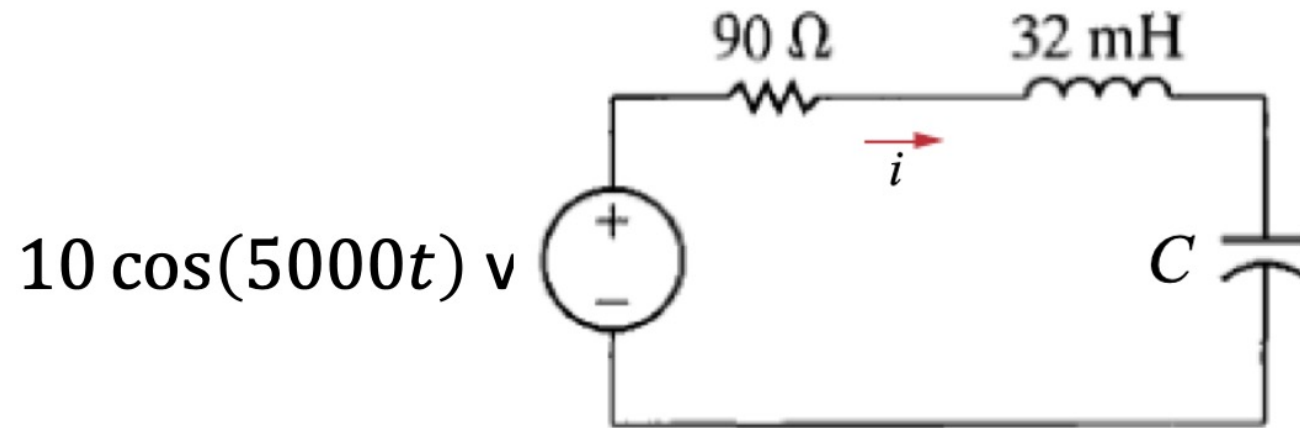Example: For the same circuit, can you choose a capacitor C so that the steady state current i has a magnitude of 0.1 A ?




$0.172\ \mu\text{F}$

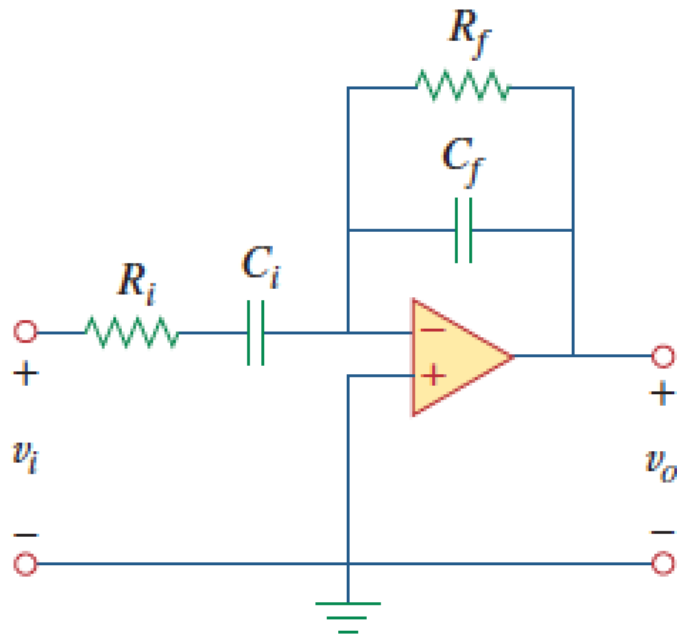Practice problem: find v_o if $v_i(t) = A \cos \omega t$ V



$$v_o(t) = \frac{A\omega R_f C_i}{\sqrt{1+\omega^2 R_i^2 C_i^2} \sqrt{1+\omega^2 R_f^2 C_f^2}} \cos(\omega t + 270^\circ - \tan^{-1}(\omega R_i C_i) - \tan^{-1}(\omega R_f C_f)) \text{ V}$$

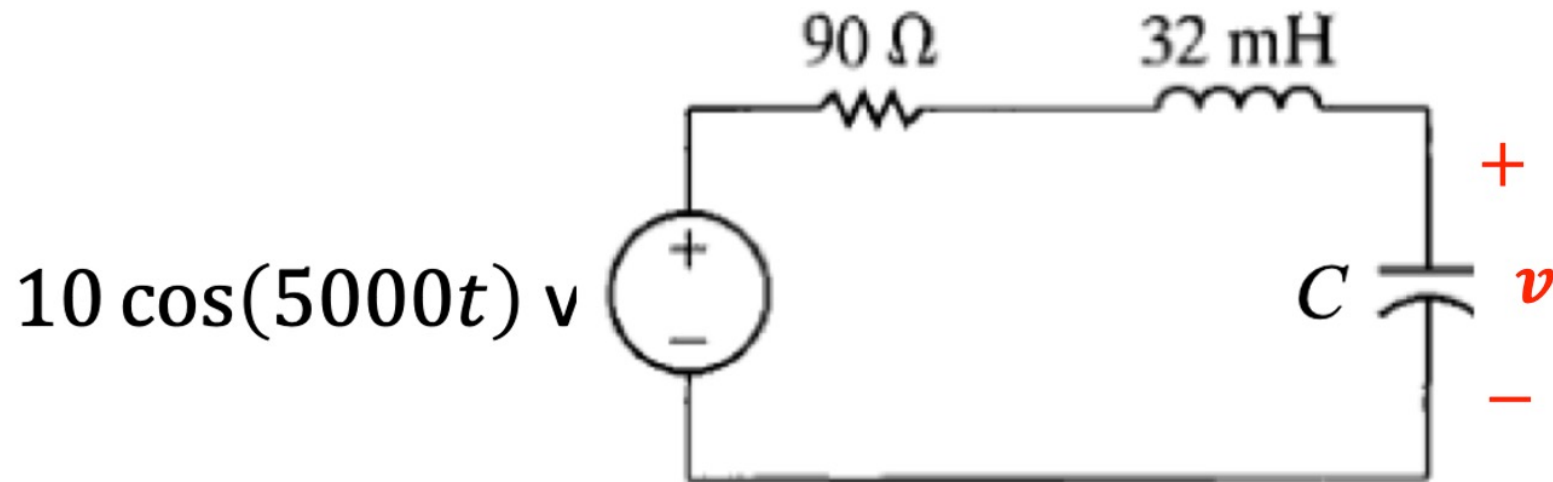Practice problem: For the same circuit, can you choose a capacitor C so that its steady state voltage v has a phase angle of -45° relative to the source ?



0.118 nF