


Lecture 11

Node Analysis – 4 of 7

dependent sources


Extension #3 – dependent sources

- Consider:

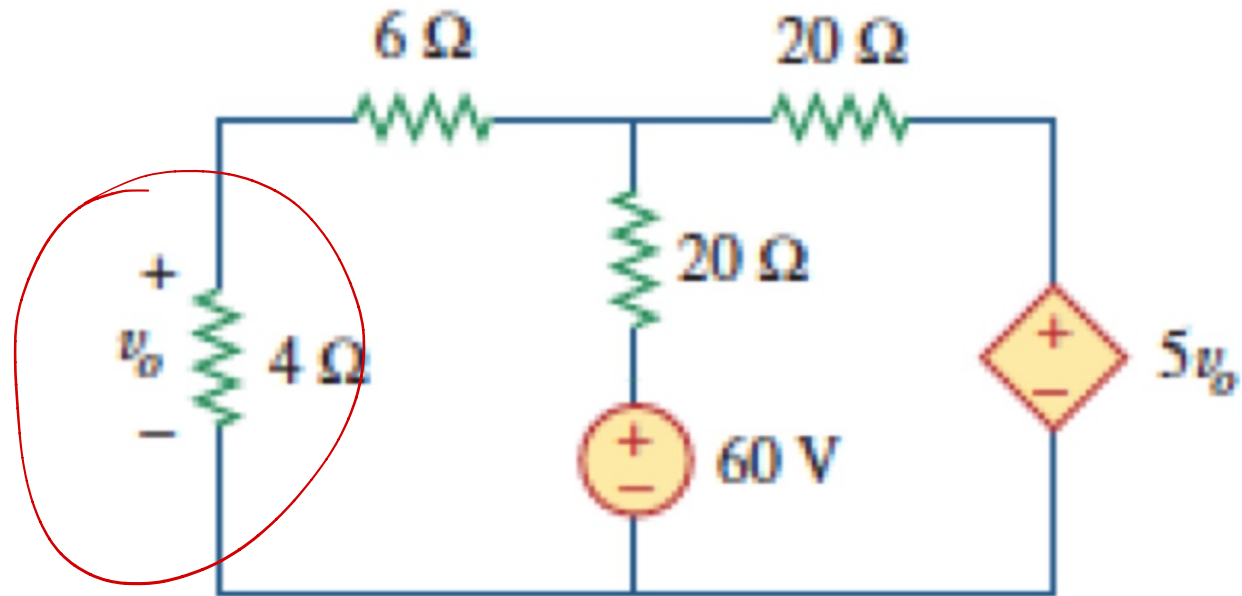

- Write node equations as usual,
- Add an equation “defining” the controlling variable in terms of the node voltages

Example (solved on next slide)

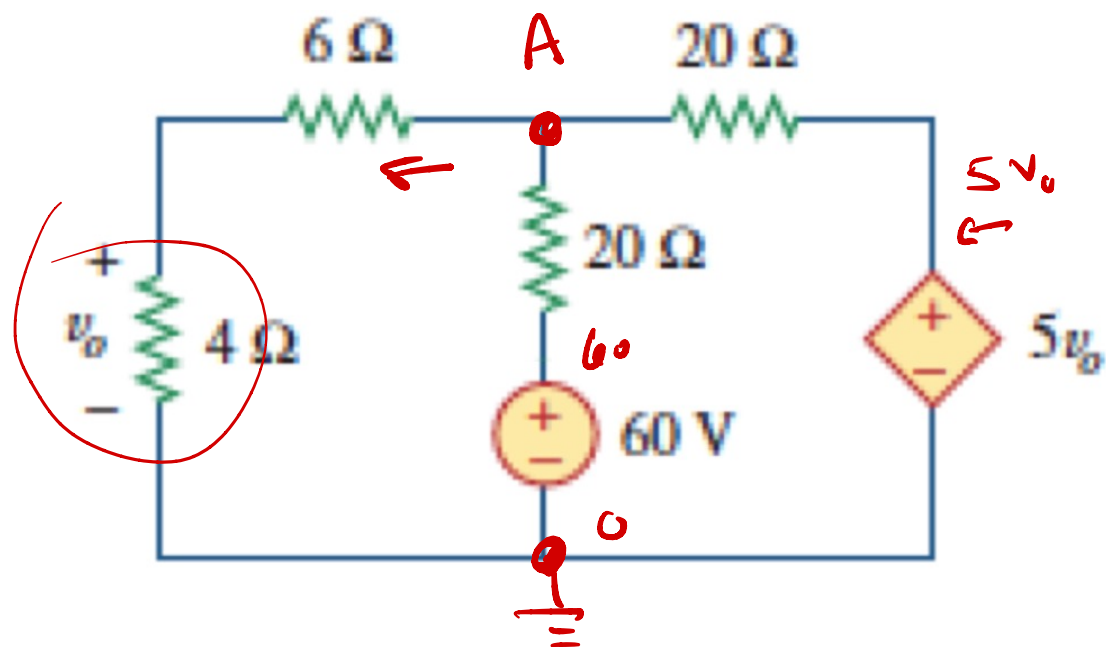

1- label under + ground

2- KCL at A

$$\frac{A}{10} + \frac{A-60}{20} + \frac{A-5v_o}{20} = 0$$


3- write voltage div. eq

$$v_o = A \cdot \frac{4}{10}$$

4 solve - substitute

$$\frac{A}{10} + \frac{A-60}{20} + \frac{A-2A}{20} = 0$$
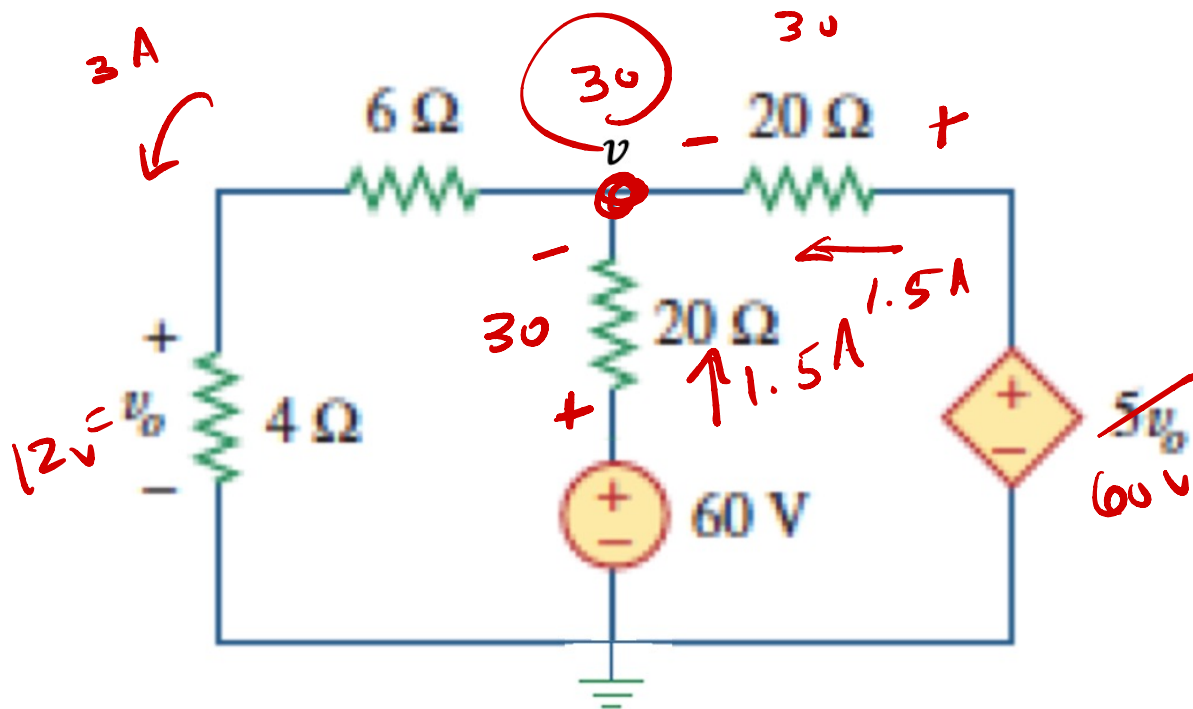
$$A \left(\frac{1}{10} + \frac{1}{20} - \frac{1}{20} \right) = \frac{60}{20}$$



Node equation:

$$\frac{v}{10} + \frac{v - 60}{20} + \frac{v - 5v_0}{20} = 0$$

Relate v_0 to the node:

$$v_0 = \frac{4}{10}v$$

$$4v - 5v_0 = 60$$

$$4v - 5 \frac{4}{10}v = 60$$


$$v = 30 \text{ volts}$$

1 - KCL

$$V_o = 10V$$

Example: find V_o

2 - KCL

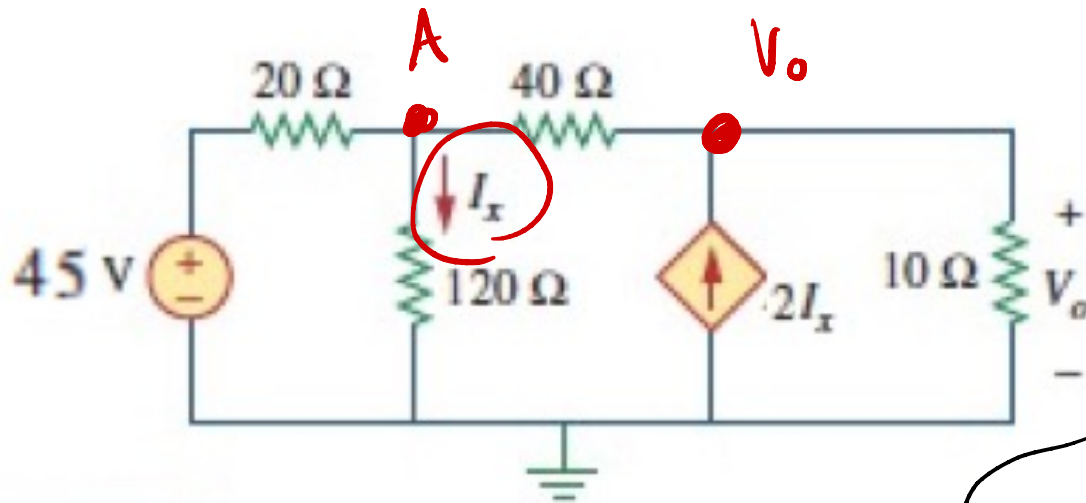

A:

$$\frac{A - 45}{20} + \frac{A}{120} + \frac{A - V_o}{40} = 0$$

V_o :

$$\frac{V_o - A}{40} + \frac{V_o}{10} - 2I_x = 0$$

$I_x = \frac{A}{120}$

$$A \left(\frac{1}{20} + \frac{1}{120} + \frac{1}{40} \right) - V_o \left(\frac{1}{40} \right) = \frac{45}{20}$$


$$-A \left(\frac{1}{40} + \frac{1}{60} \right) + V_o \left(\frac{1}{40} + \frac{1}{10} \right) = 0$$

3 - define I_x - direction

$$I_x = \frac{A}{120}$$

Example:

1 - label

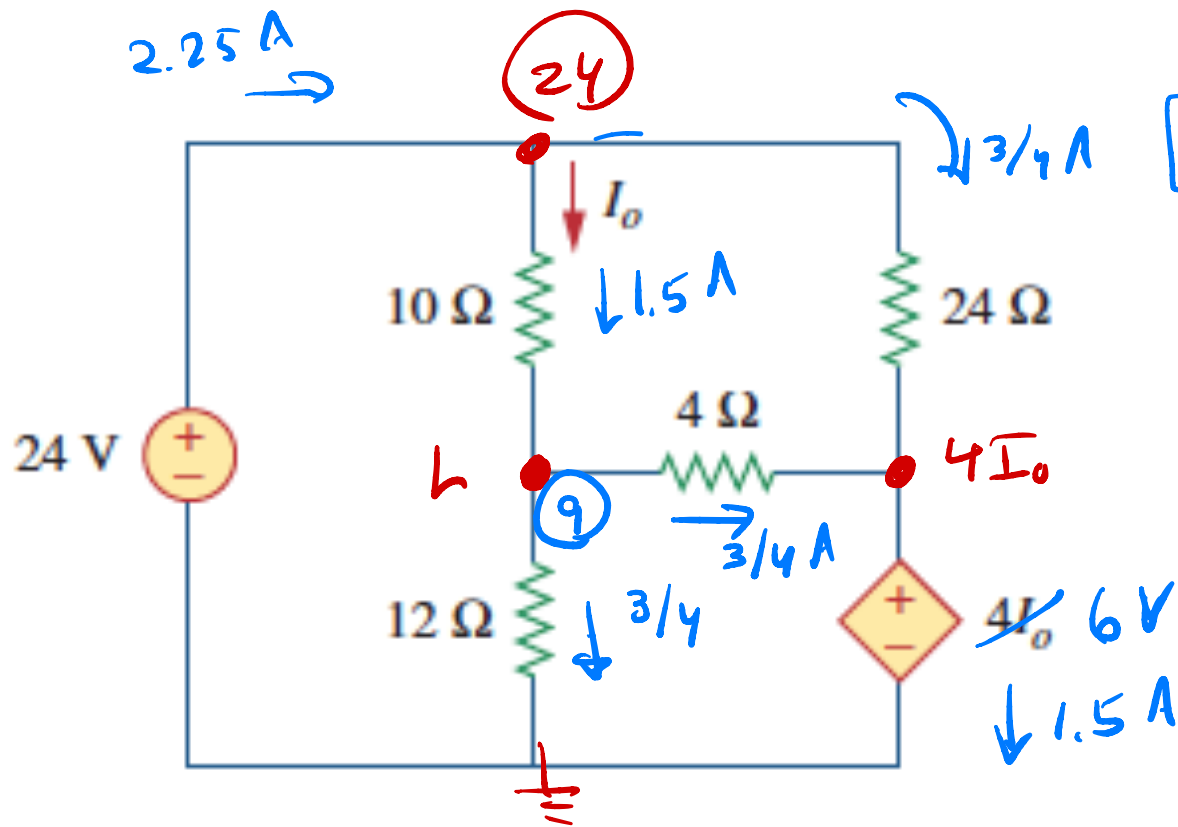

$$\boxed{v_L = 9V, \\ I_o = 1.5A \\ v_R = 6V}$$

2 - write KCL @ L

$$\frac{L}{12} + \frac{L - 24}{10} + \frac{L - 4I_o}{4} = 0$$

3 - extra eq. Ohm's Law

$$I_o = \frac{24 - L}{10}$$

$$4I_o = \frac{48 - 2L}{5}$$

$$L = 9 \text{ volts}$$

$$P = -36 \text{ W}$$

Example: find the power of the dependent source

1- label and choose ground

2- nod. eqs:

$$\frac{A-25}{2} + \frac{A-10}{5} + \frac{A-B}{3} = 0$$

$$\frac{B}{1} + \frac{B-A}{3} + \frac{B-25+3V_0}{14} = 0$$

3- define V_0

$$V_0 = A - B$$


$$A = 10 \quad B = 20$$

$$V_0 = -10$$

$$V_s = 30 \text{ V}$$

$$i_s = -\frac{35}{14}$$
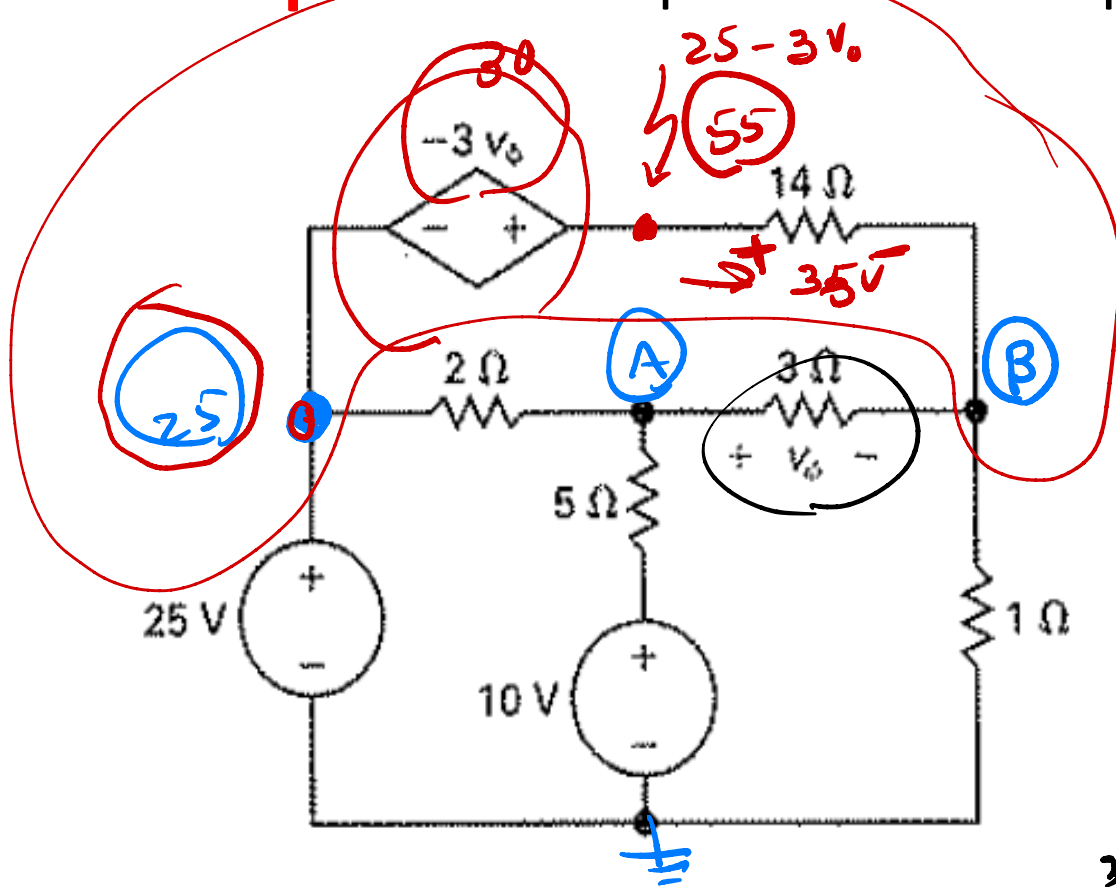
$$P = 30 \cdot \left(-\frac{35}{14}\right)$$



$$30 \left[\frac{A-25}{2} + \frac{A-10}{5} + \frac{A-B}{3} = 0 \right]$$

$$42 \left[\frac{B}{1} + \frac{B-A}{3} + \frac{B-25+3(A-B)}{14} = 0 \right]$$

$$\underline{15A} - 375 + \underline{6A} - 60 + \underline{10A} - 10B$$


$$\underline{42B} + \underline{14B} - \underline{14A} + \underline{3B} - 75 + \underline{9A} - \underline{9B}$$

$$31A - 10B = 435$$

$$-5A + 50B = 75$$


$$i_0 = 11.25 \text{ A}$$

Practice problem: find i_0

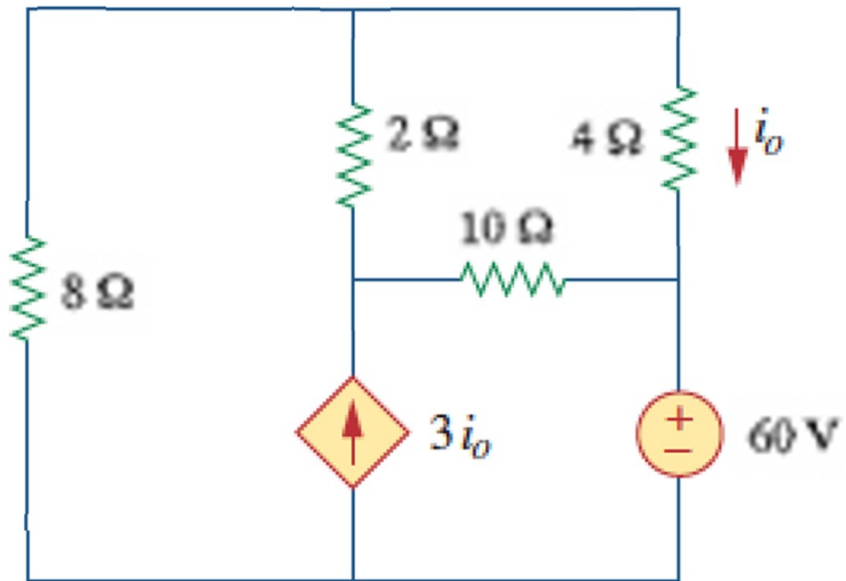


$$v_o = -50 \text{ V}$$

Practice problem: find v_o

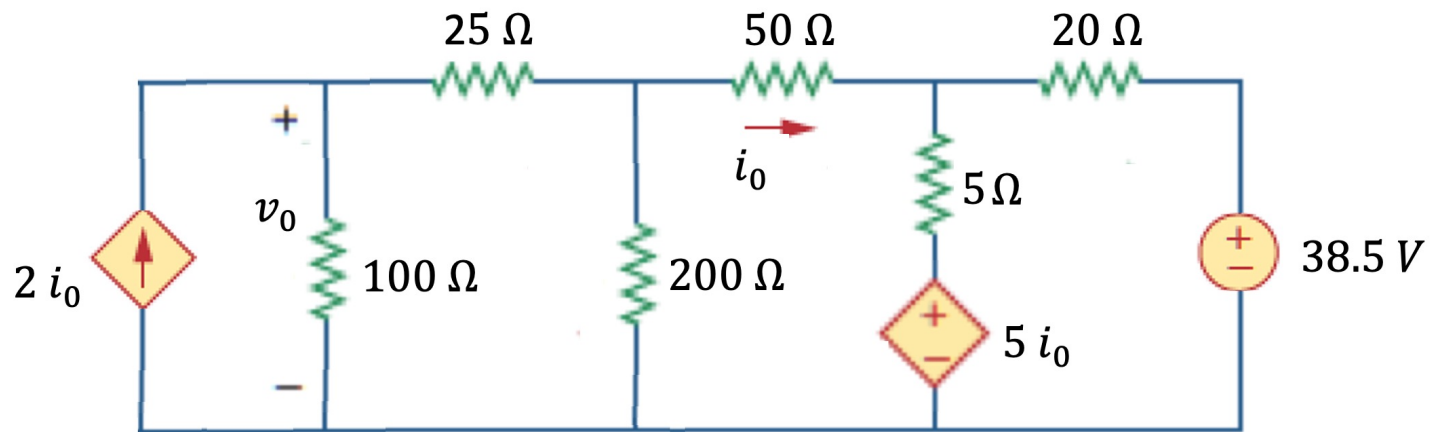

Practice Problem:

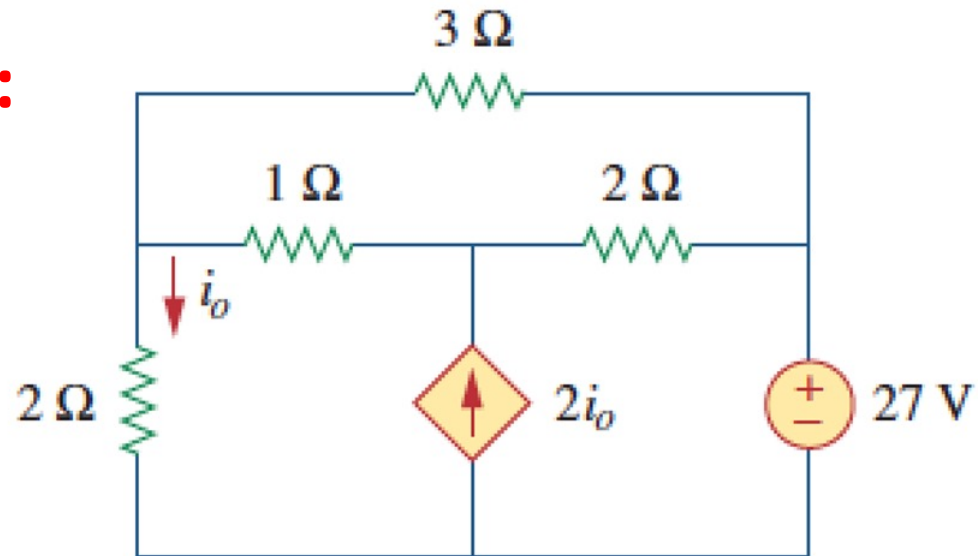

$$v_L = 36\text{ V}$$
$$v_R = 57\text{ V}$$

$$I_0 = 7.5 \text{ A}$$

Practice problem: find I_0

