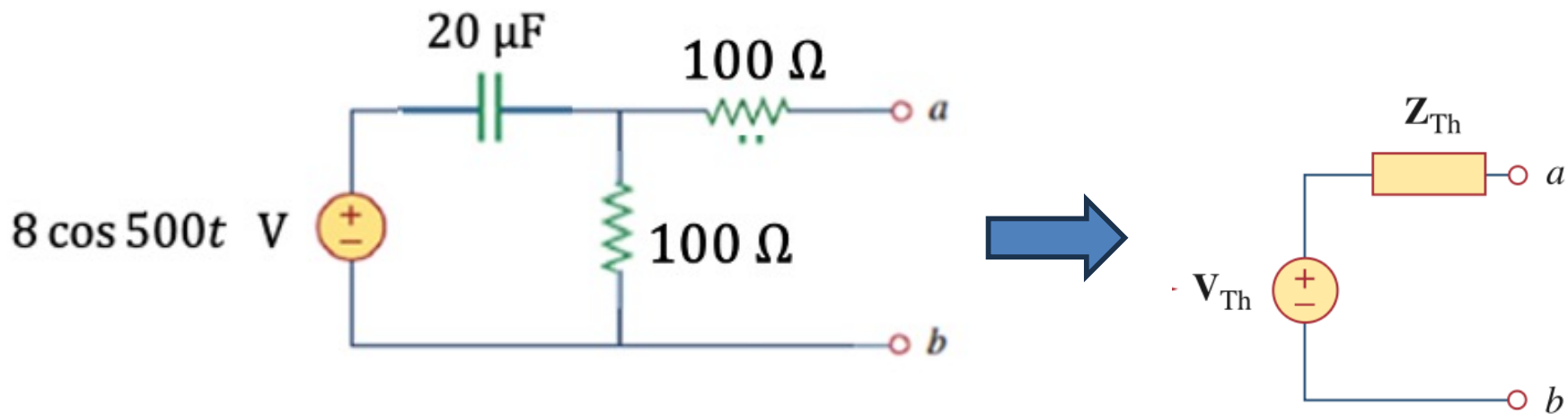


Lecture 28

Theorems – 5 of 6

Thevenin with phasors


Thévenin and Phasors




With

$$V_{TH} = A \cos(500 t + \phi) \text{ volts}$$
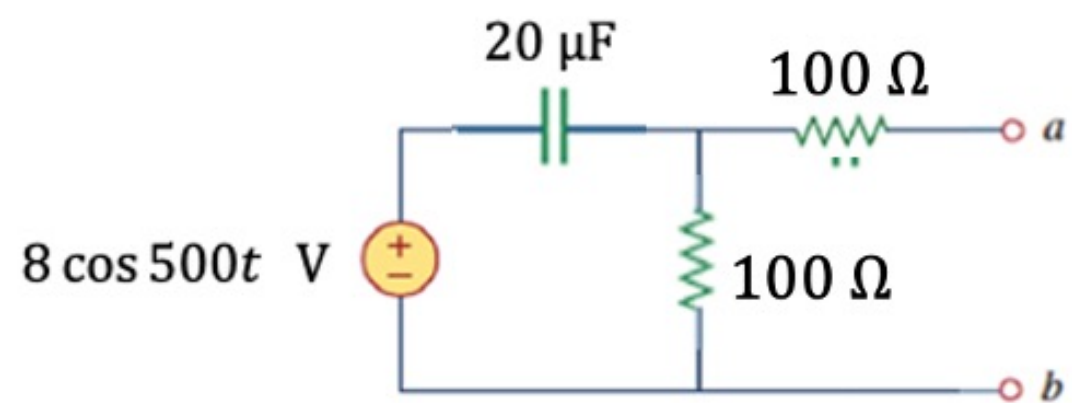
$$Z_{TH} = \begin{cases} \text{series resistor and inductor} & \text{imag} > 0 \\ \text{series resistor and capacitor} & \text{imag} < 0 \end{cases}$$




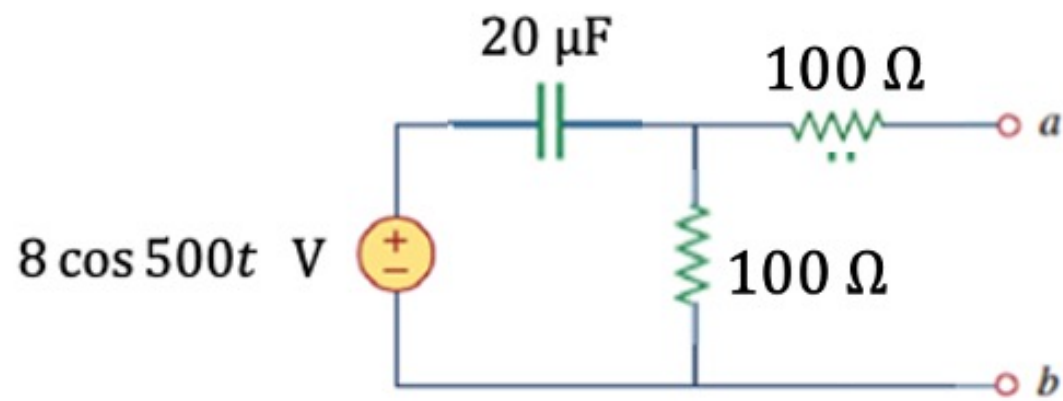



$$4\sqrt{2} \cos(500t + 45^\circ) \text{ V},$$

$$150 \Omega, 40 \mu\text{F}$$

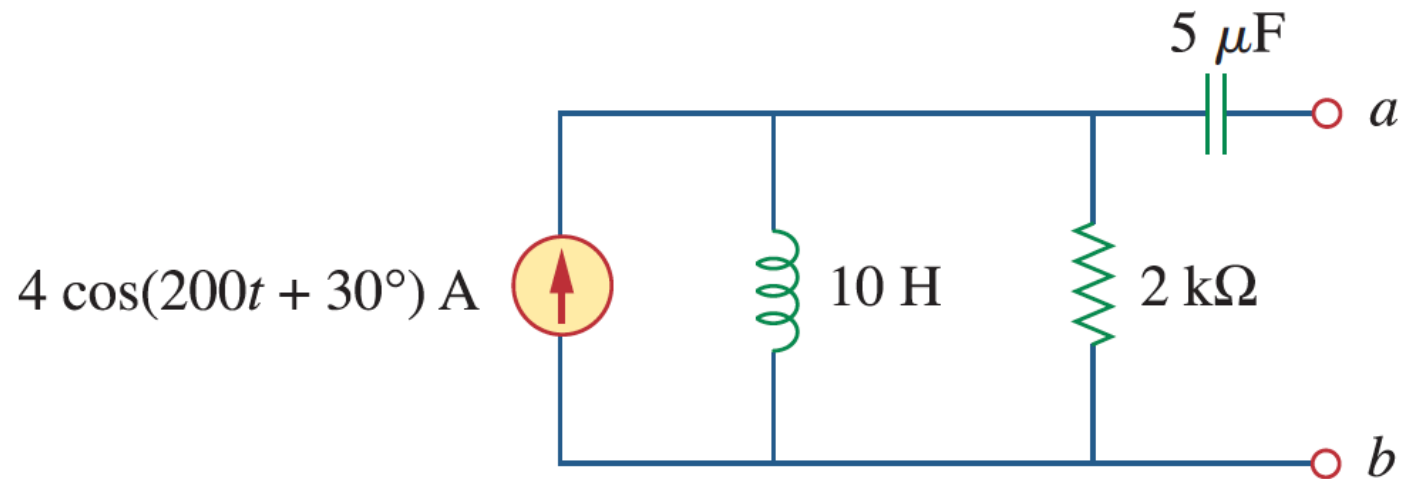Example: find the Thevenin and Norton models




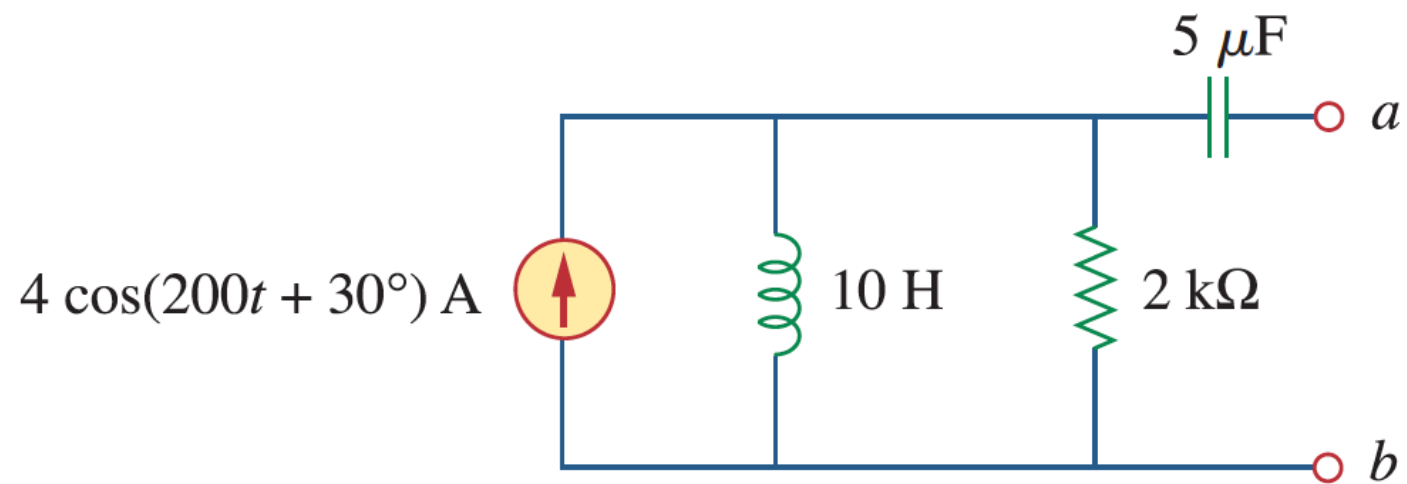


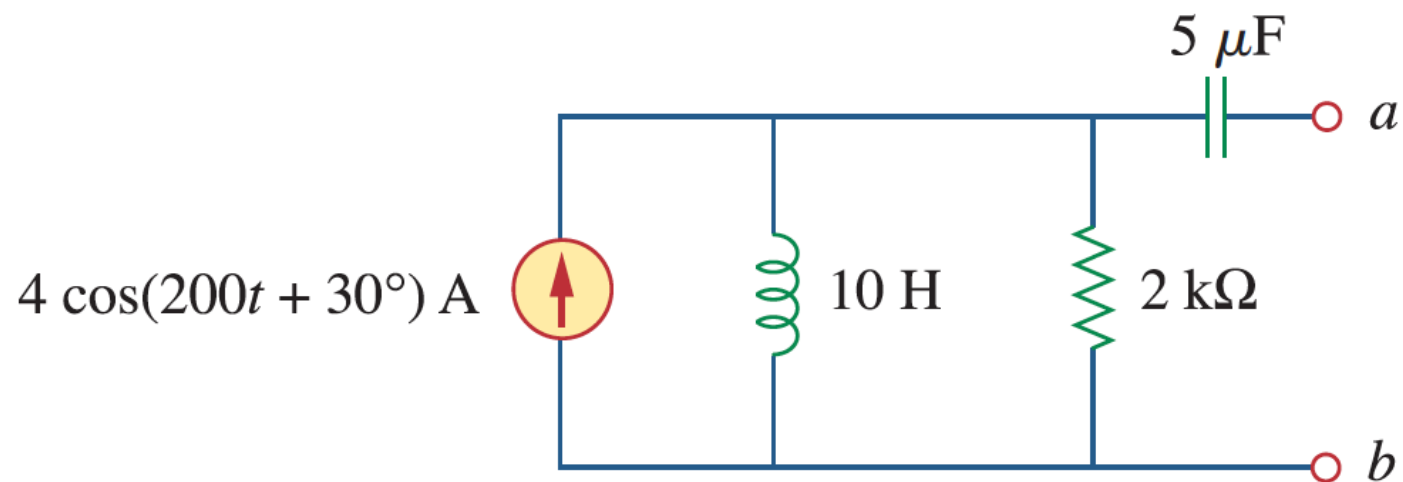


$$\begin{aligned}
 &4000\sqrt{2} \cos(200t + 75^\circ) \text{ V}, \\
 &1000 \Omega, \\
 &4\sqrt{2} \cos(200t + 75^\circ) \text{ A}
 \end{aligned}$$

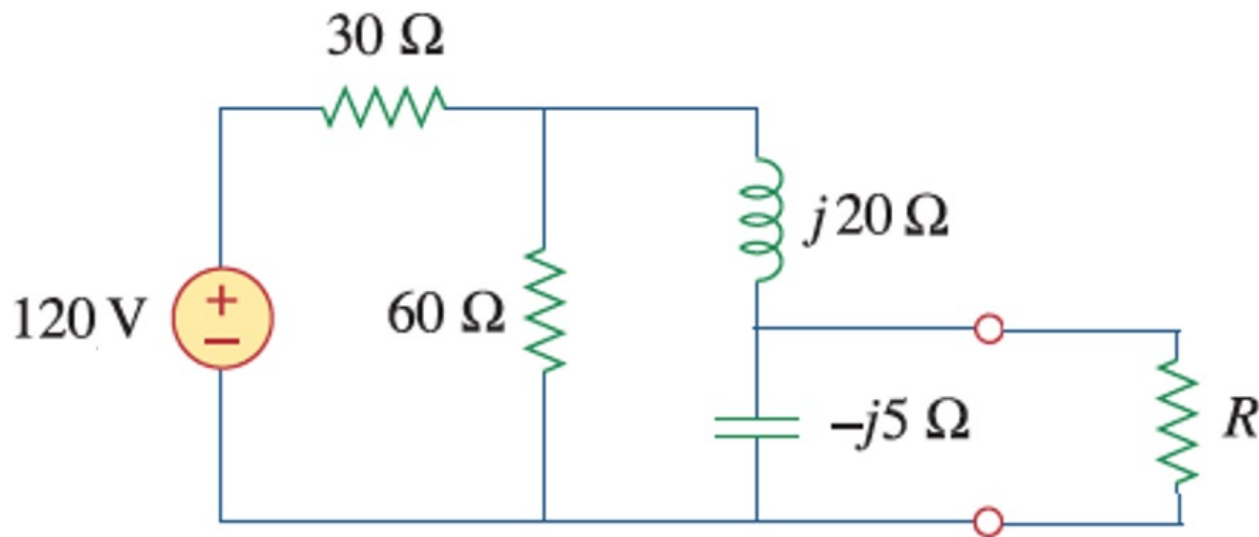Example: find the magnitude of the current through R as a function of R – hint: first find the Thevenin equivalent




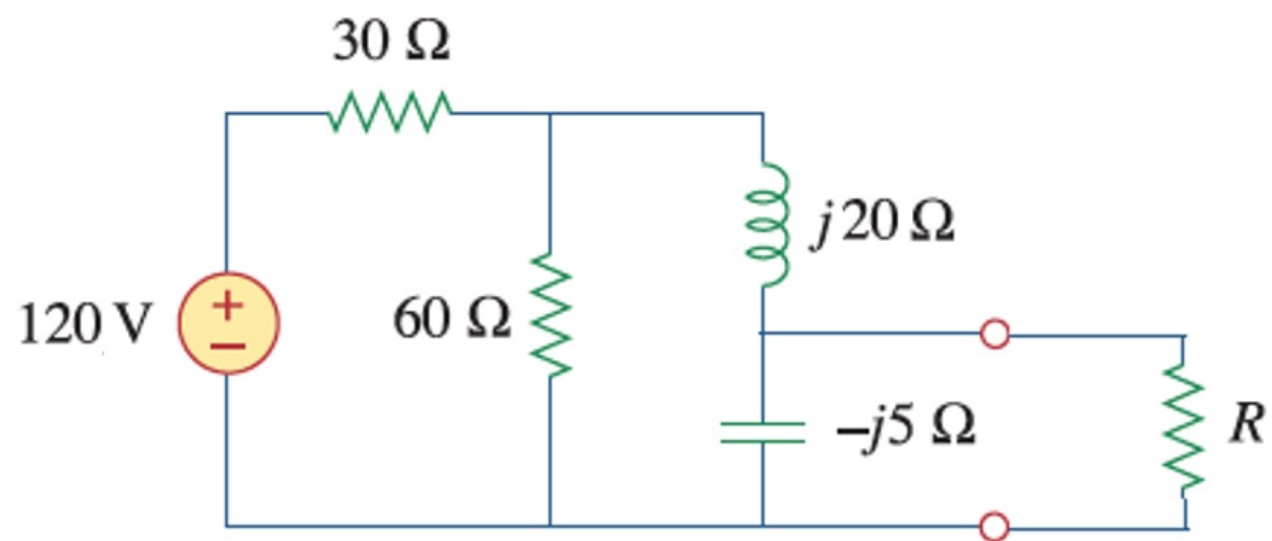

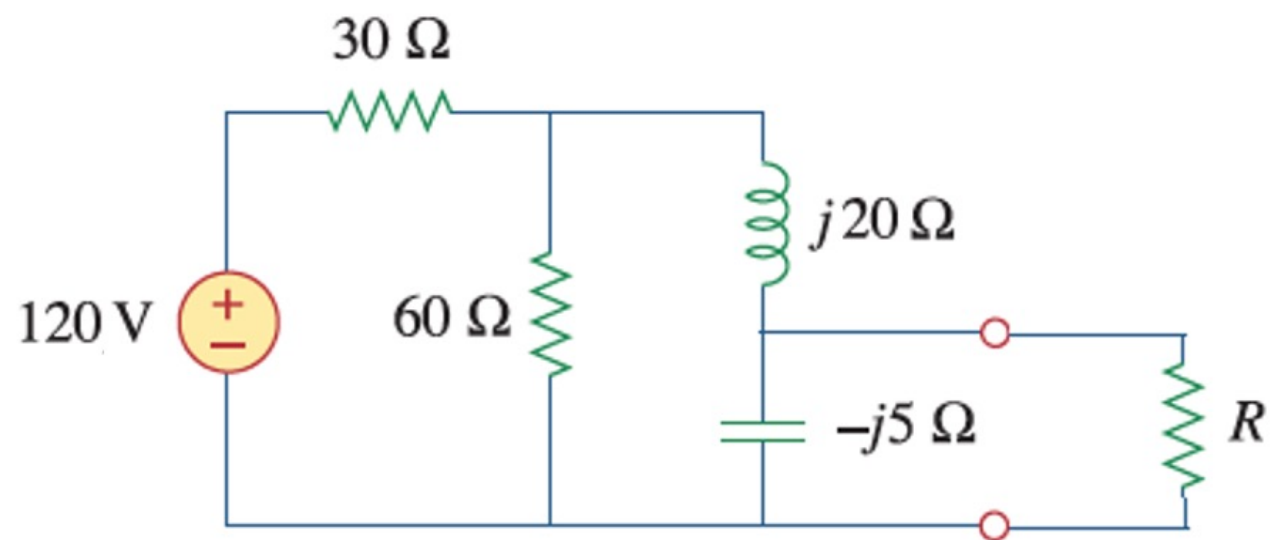


$$\frac{16}{\sqrt{(R + 0.8)^2 + 5.6^2}}$$

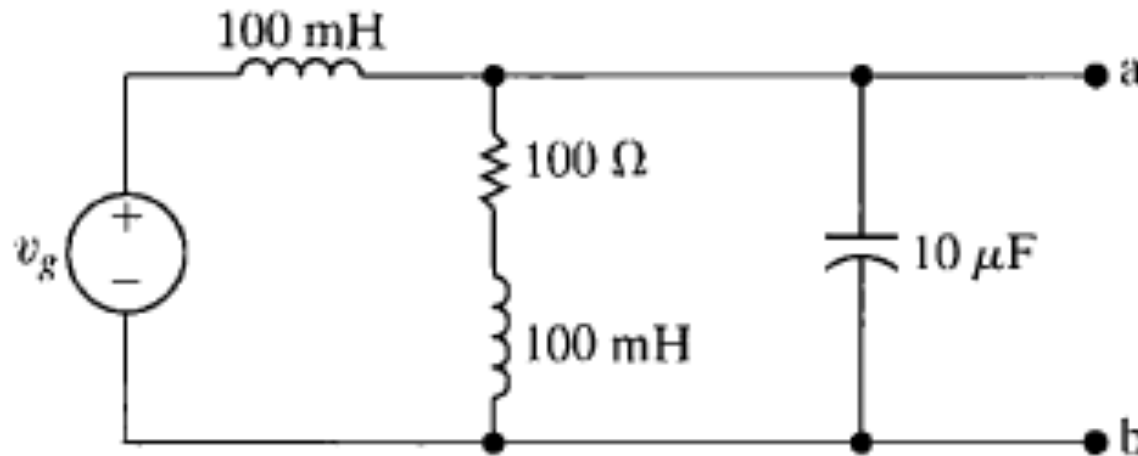Practice problem: find the Thevenin and Norton models if $v_g(t) = 247.49 \cos(1000t + 45^\circ) \text{ V}$



$350 \cos 1000t \text{ V},$
 $100 \Omega, 100 \text{ mH},$
 $2.475 \cos(1000t - 45^\circ) \text{ A}$

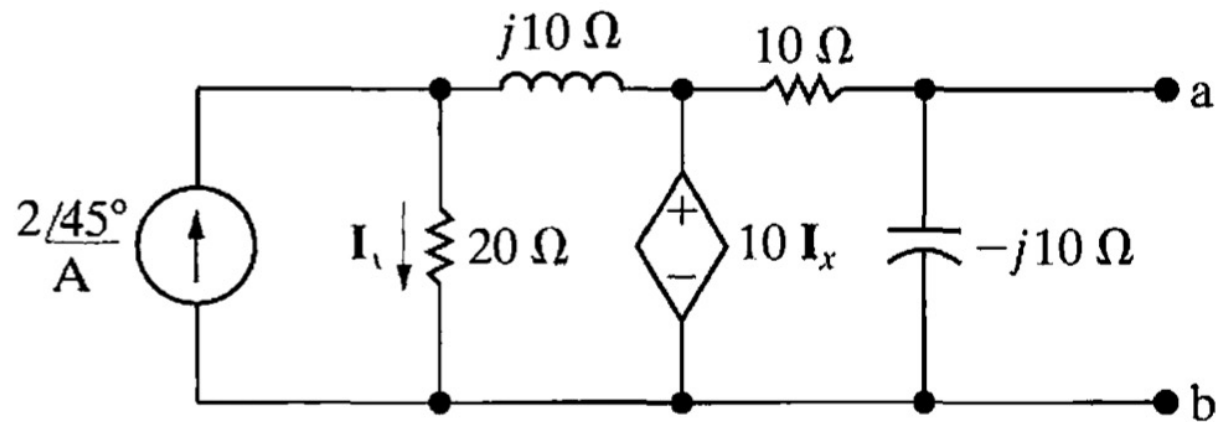Practice problem: Find V_{Th} and Z_{Th} in phasor form



$10 \angle 45^\circ \text{ V}, 5 - 5j \Omega$