

Lecture 19


Phasors – 5 of 9

examples


What Now?

- Have used seen that voltage division, series and parallel impedance, and simple analysis all work with phasors
- Let's practice analysis methods
 - Node analysis
 - Dependent sources
 - Super nodes
 - ...

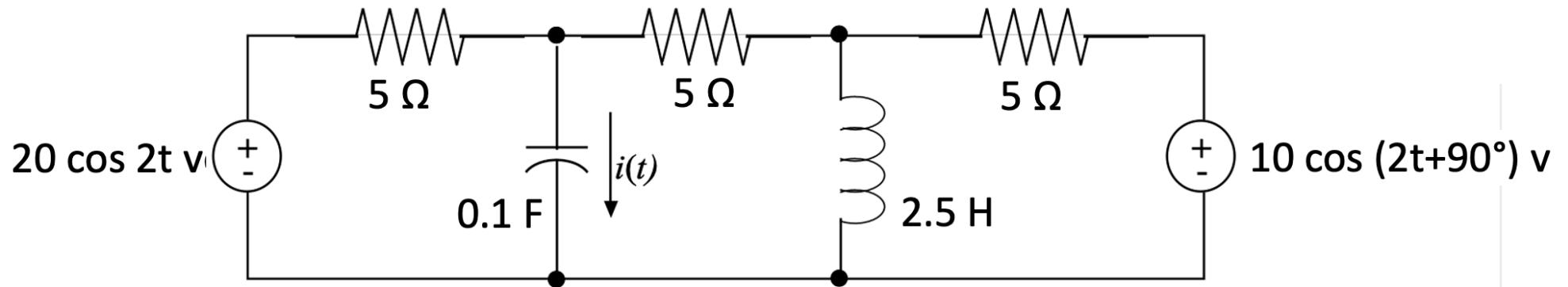Example: Find the current $i(t)$ (solved on next slides)




1 - Convert to phasors

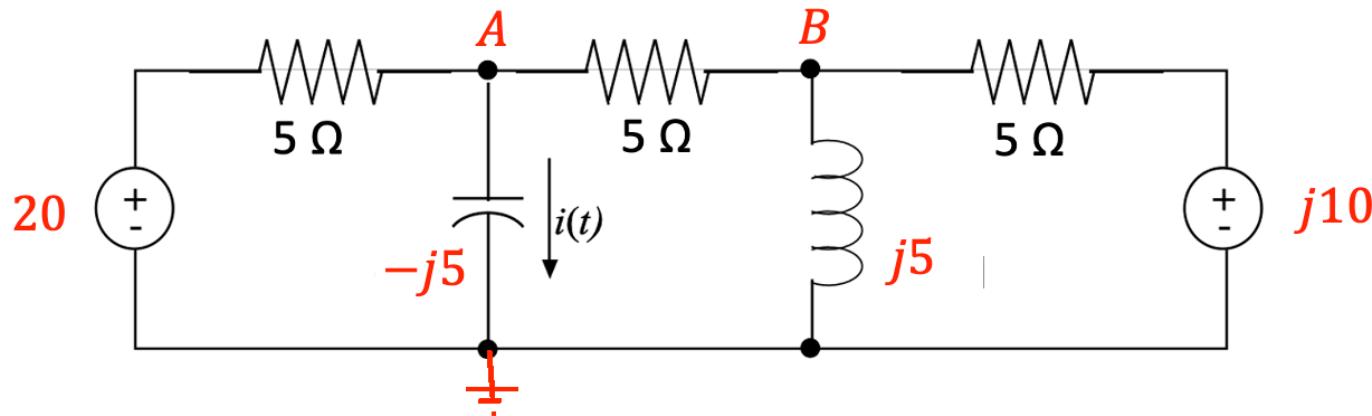

2 – Write node equations

$$\begin{bmatrix} \frac{1}{5} + \frac{1}{5} + \frac{1}{-j5} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{1}{5} + \frac{1}{5} + \frac{1}{j5} \end{bmatrix} \begin{bmatrix} A \\ B \end{bmatrix} = \begin{bmatrix} \frac{20}{5} \\ \frac{j10}{5} \end{bmatrix}$$

2 – Solve for A

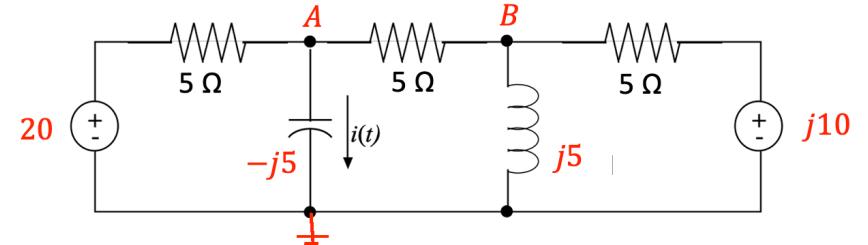

$$A = \frac{\begin{vmatrix} 4 & -\frac{1}{5} \\ j2 & \frac{2-j}{5} \end{vmatrix}}{\begin{vmatrix} \frac{2+j}{5} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{2-j}{5} \end{vmatrix}} = \frac{\frac{8}{5} - j\frac{4}{5} + \frac{j2}{5}}{\frac{1}{5} - \frac{1}{25}} = \frac{\frac{8}{5} - j\frac{2}{5}}{\frac{4}{25}} = 10 - j\frac{5}{2}$$


3 – Solve for I

$$I = \frac{A}{-j5} = \frac{10 - j\frac{5}{2}}{-j5} = \frac{1}{2} + j2 = 2.06 \angle 76^\circ$$

3 – Convert to time function


$$i(t) = 2.06 \cos(2t + 76^\circ) \text{ A}$$

Example: Find V

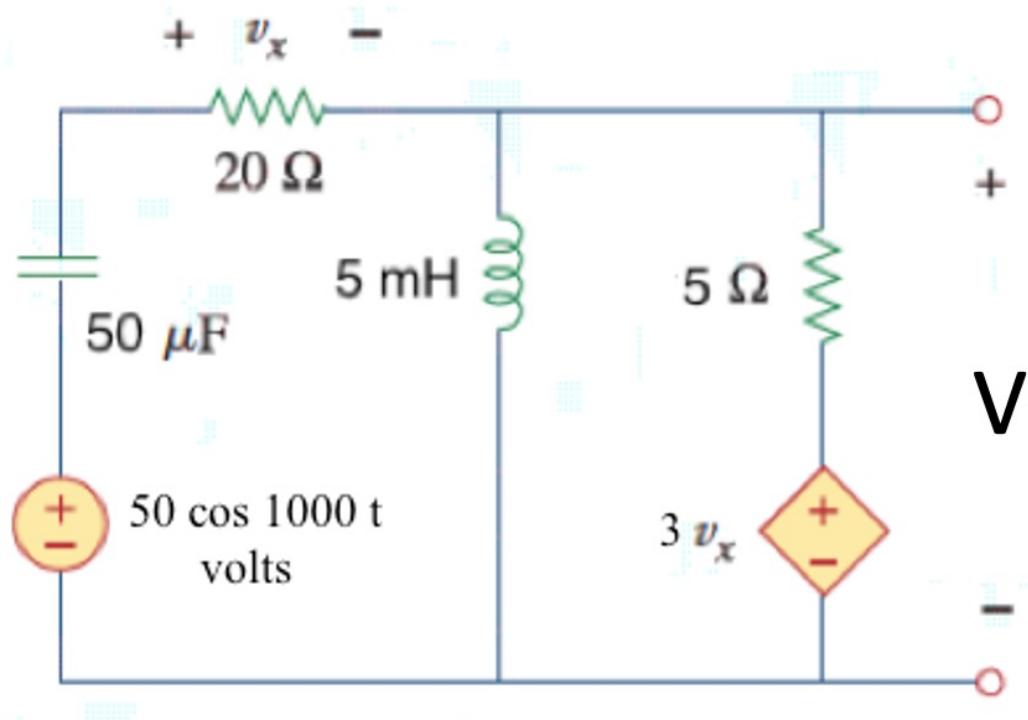


$$5.24 \cos(1000t + 31.6^\circ) V$$

Example: Find i_o

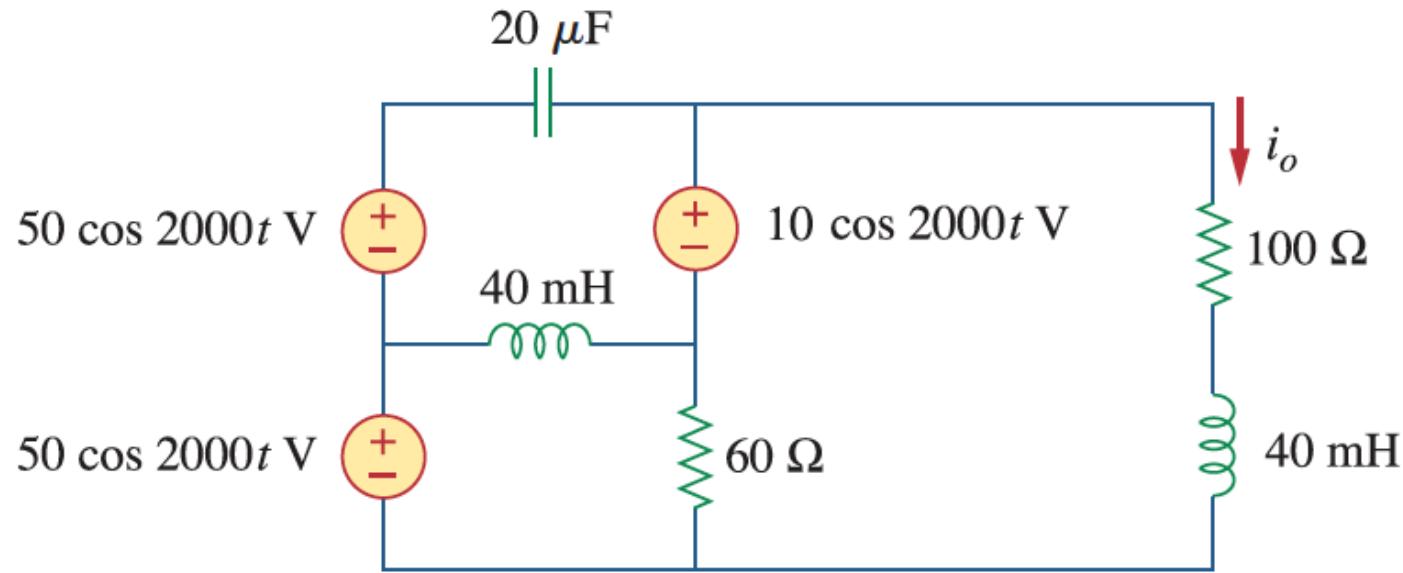


$$822 \cos(2000t + 3.69^\circ) \text{ mA}$$

Example: Find $v(t)$

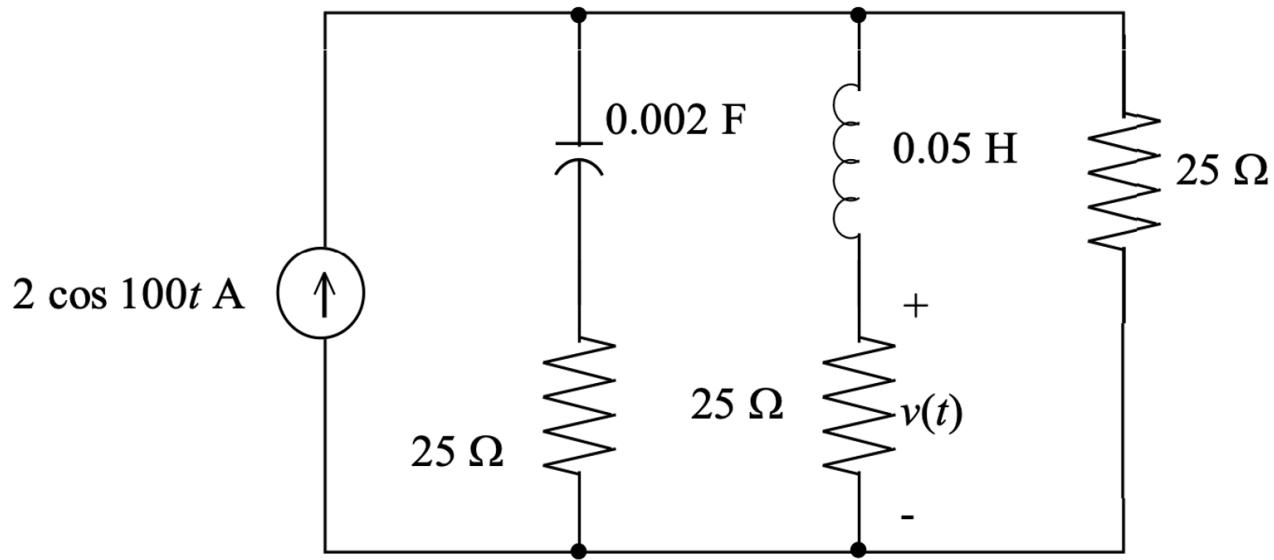


$$16.8 \cos(100t - 11.3^\circ) V$$

Example: find $v(t)$ – try node analysis

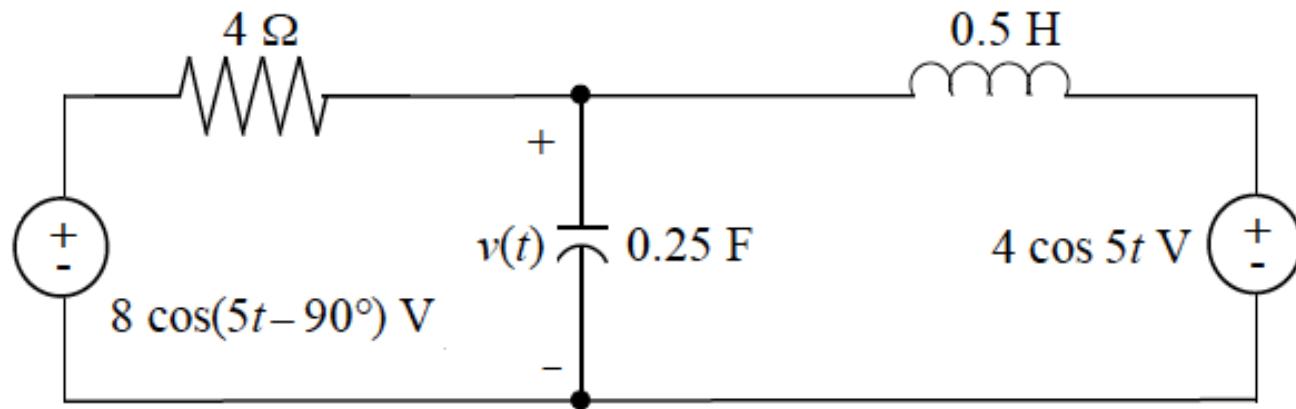


$$4.06 \cos(5t - 164^\circ)~V$$

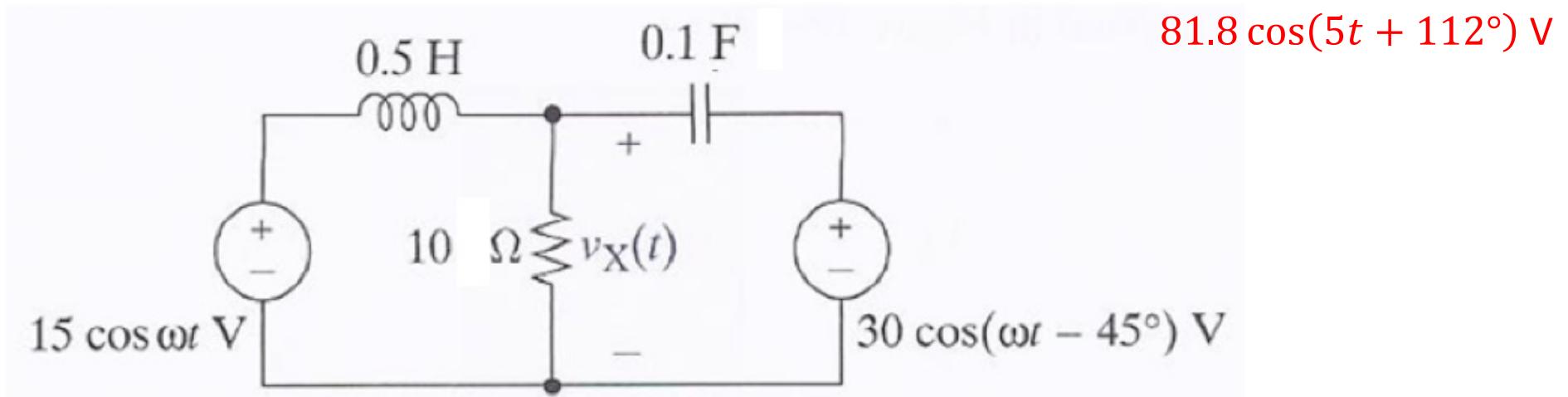Practice problem: find $v(t)$ with $\omega = 5 \text{ rad/sec}$




Practice problem: find $v_X(t)$

$$6.67 \cos(2000t - 90^\circ) V$$

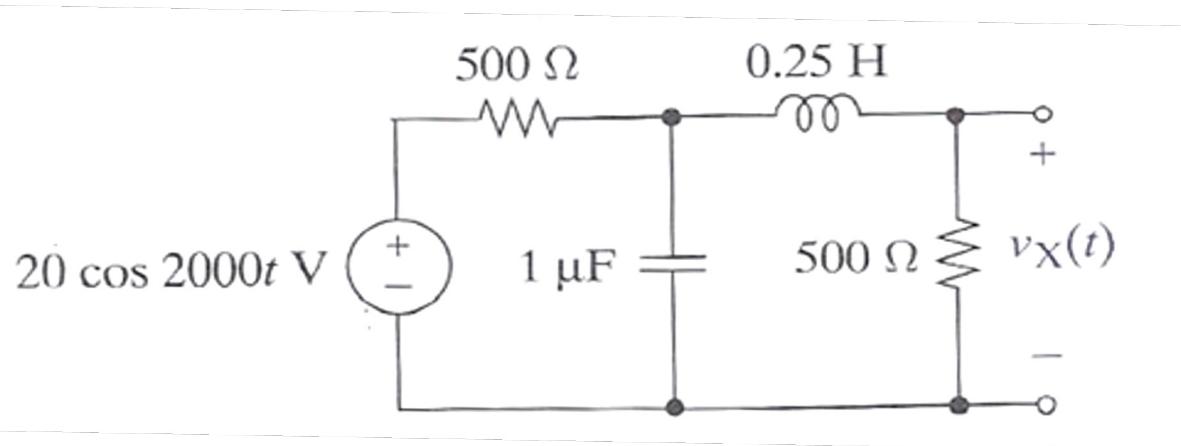


Practice problem: find $v(t)$
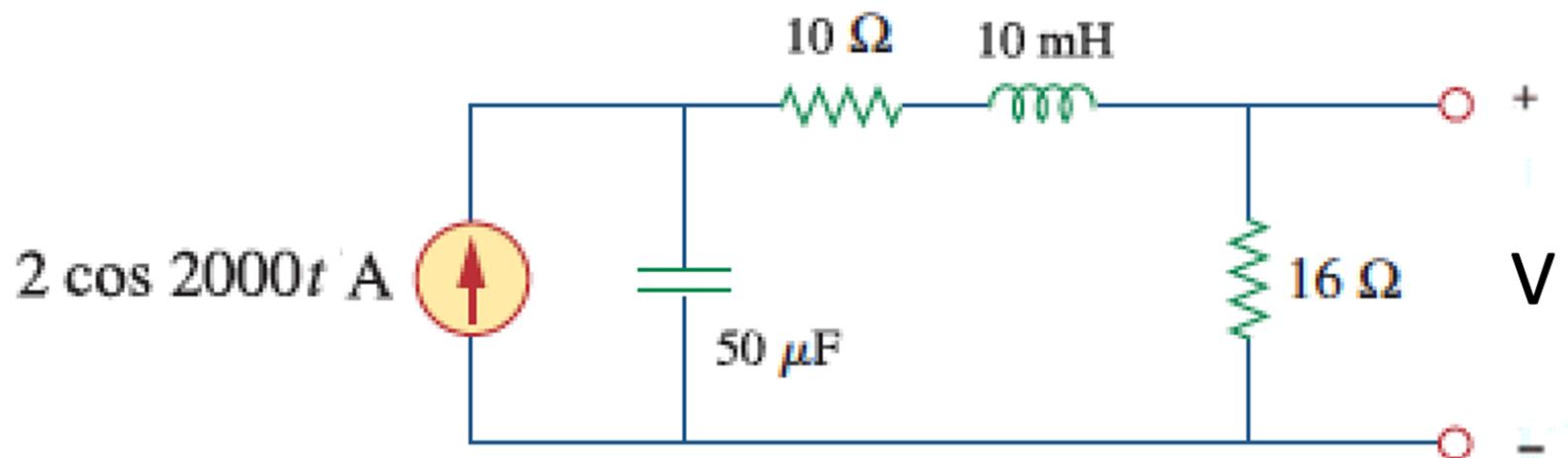
$$13.8 \cos(2000t - 115^\circ) \text{ V}$$



Practice problem: find $v(t)$

$$3.71 \cos(1000t + 21.8^\circ) V$$

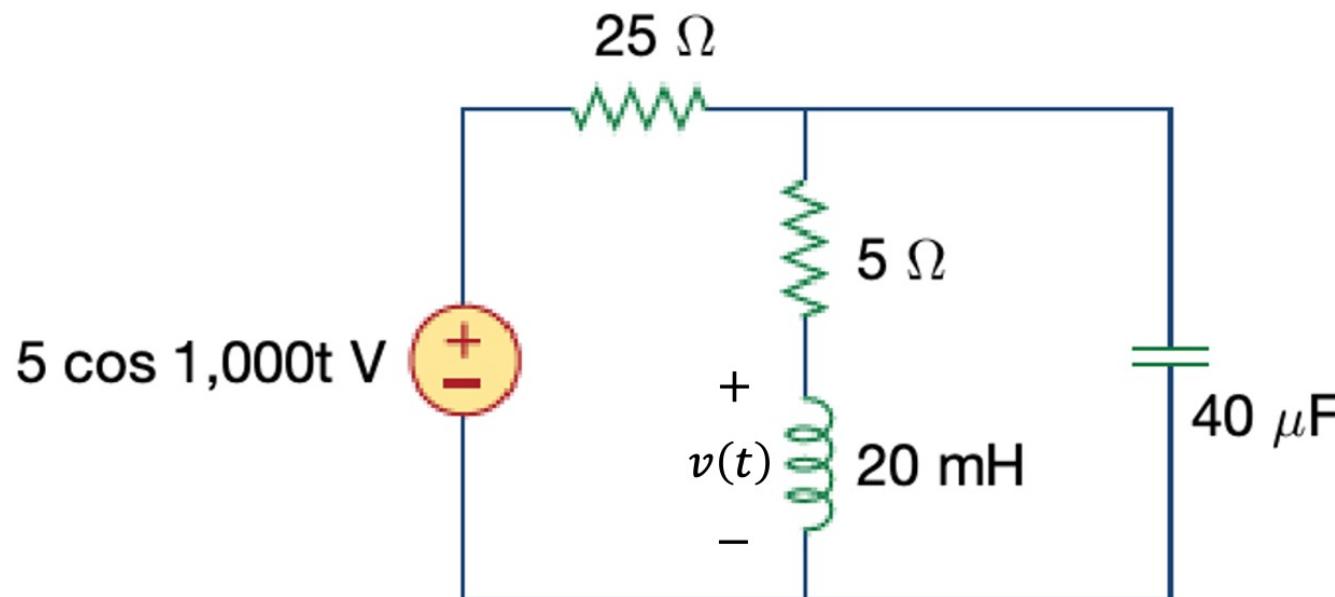

Example: find $v(t)$ if $v_g(t) = 130 \cos 10,000 t$ V,

f

