

# Lecture 24

## Theorems – 1 of 6


linearity & superposition;  
transformations

# Linearity & Superposition


- Linearity: we have already seen that for a single “input” (voltage or current), the “output” (voltage or current) is proportional to that input

$$v_o = k v_s$$

- e.g.

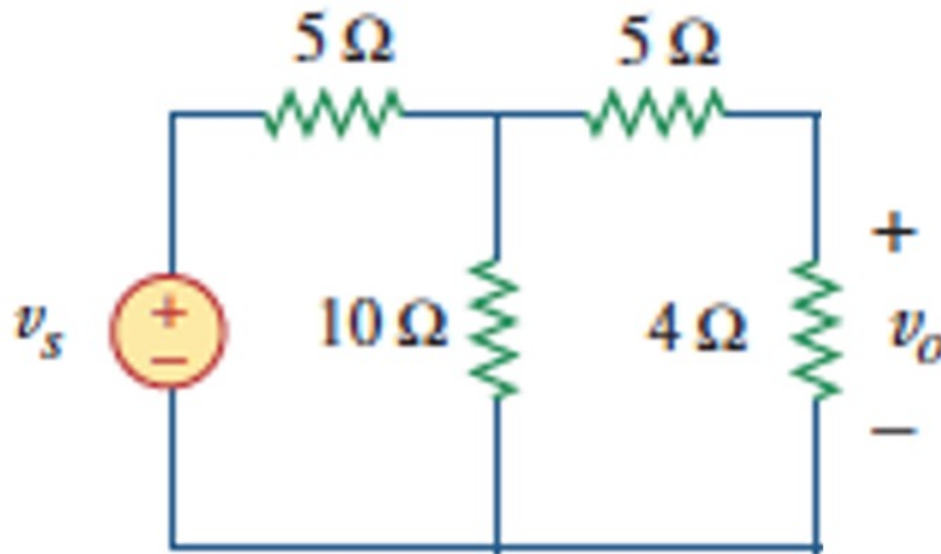

- What about multiple “input” sources?

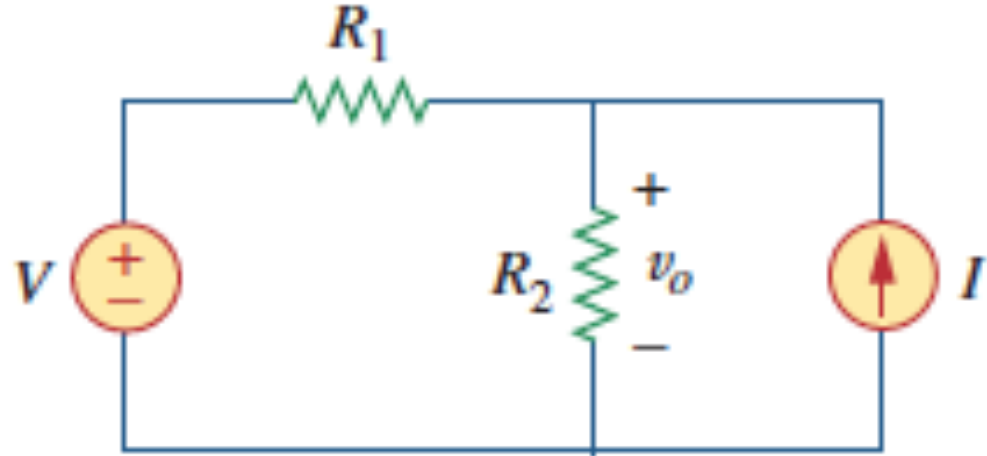

- Analyzing

$$\frac{v_o - V}{R_1} + \frac{v_o}{R_2} - I = 0$$

or

$$v_o = \frac{R_1 R_2}{R_1 + R_2} I + \frac{R_2}{R_1 + R_2} V$$

- Linearity extends to multiple “input” sources

$$v_o = k_1 v_{s1} + k_2 v_{s2} + k_3 i_{s3} + \dots$$



**“Superposition”**

- We can exploit this idea to decompose problems



$$\begin{aligned} v_o(I, V) &= \frac{R_1 R_2}{R_1 + R_2} I + \frac{R_2}{R_1 + R_2} V \\ &= v_o(I, 0) + v_o(0, V) \end{aligned}$$

- Example:

$$v_o(I, V) = v_o(I, 0) + v_o(0, V)$$

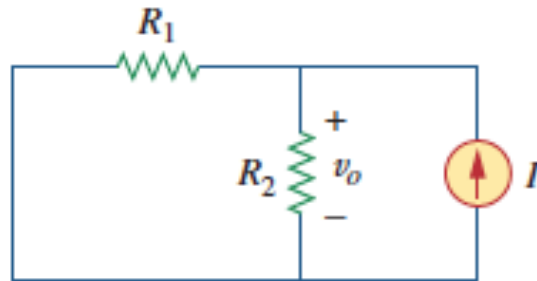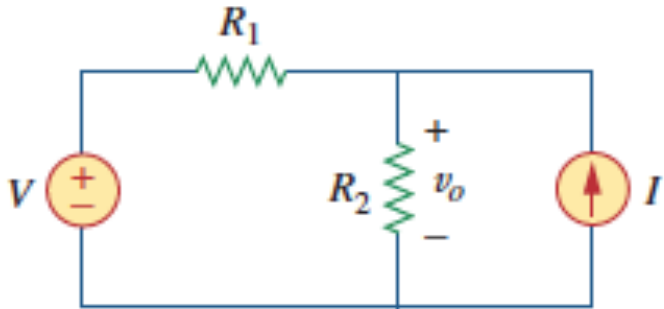

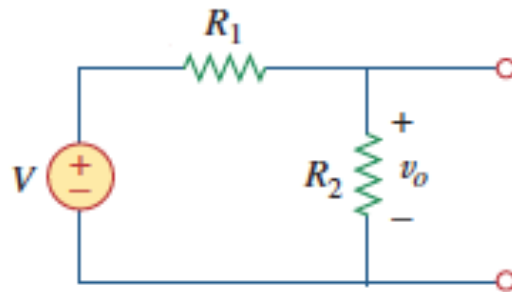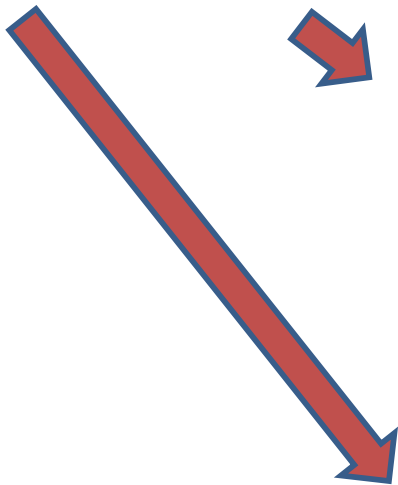
$$v_o(I, 0) = \frac{R_1 R_2}{R_1 + R_2} I$$




$$v_o(0, V) = \frac{R_2}{R_1 + R_2} V$$

**Example:** find  $i$

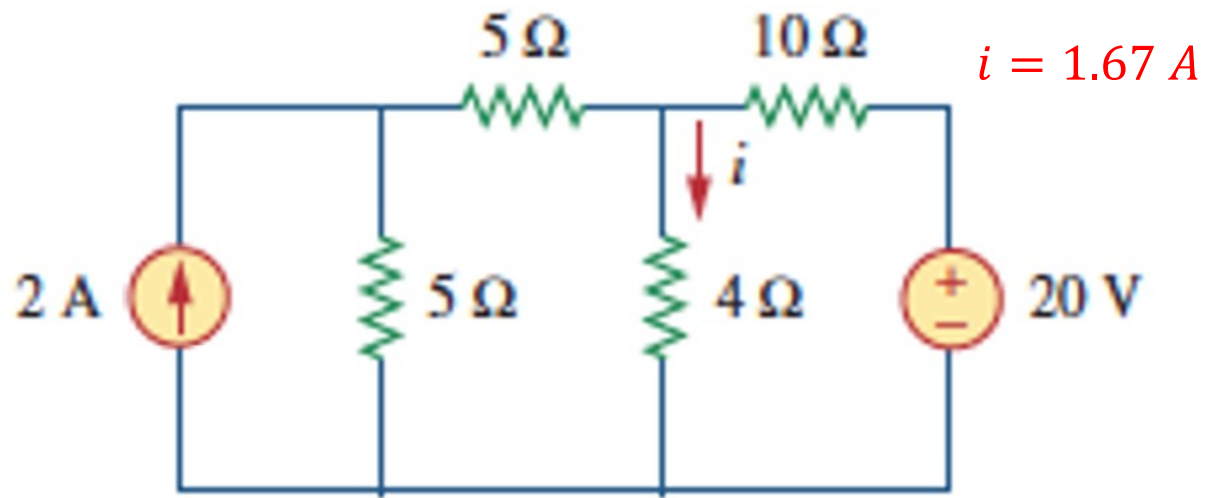

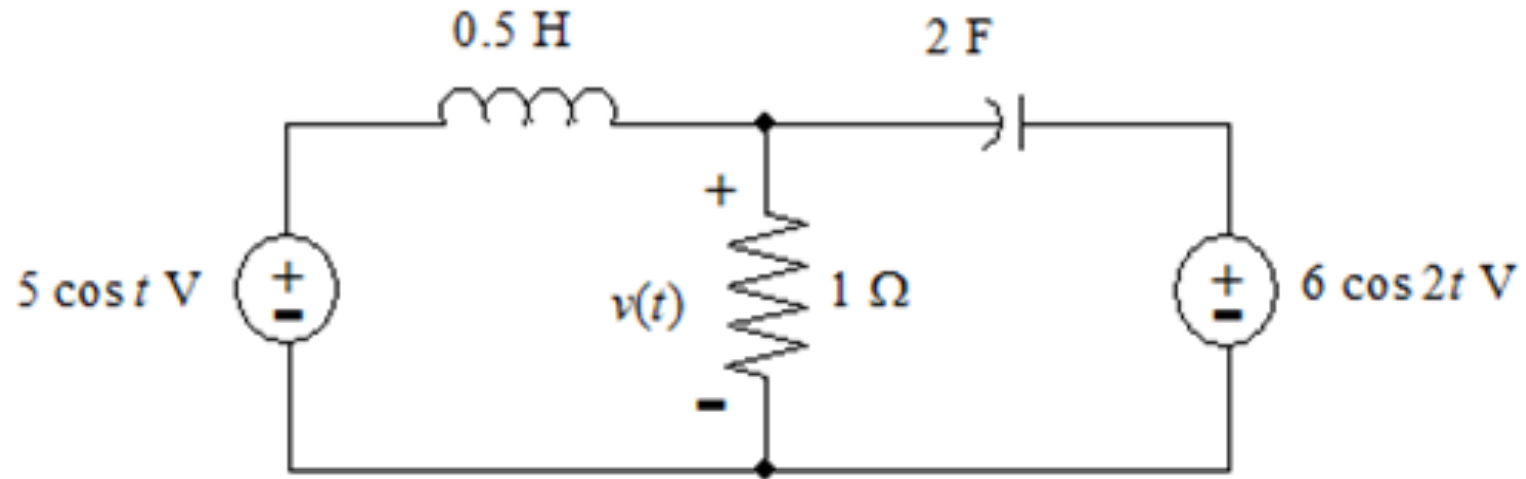
**Phasor example:** note different frequencies



$$v(t) = 10 \cos(t - 90^\circ) + 17.59 \cos(2t + 18.4^\circ) \text{ V}$$



# Source Transformations


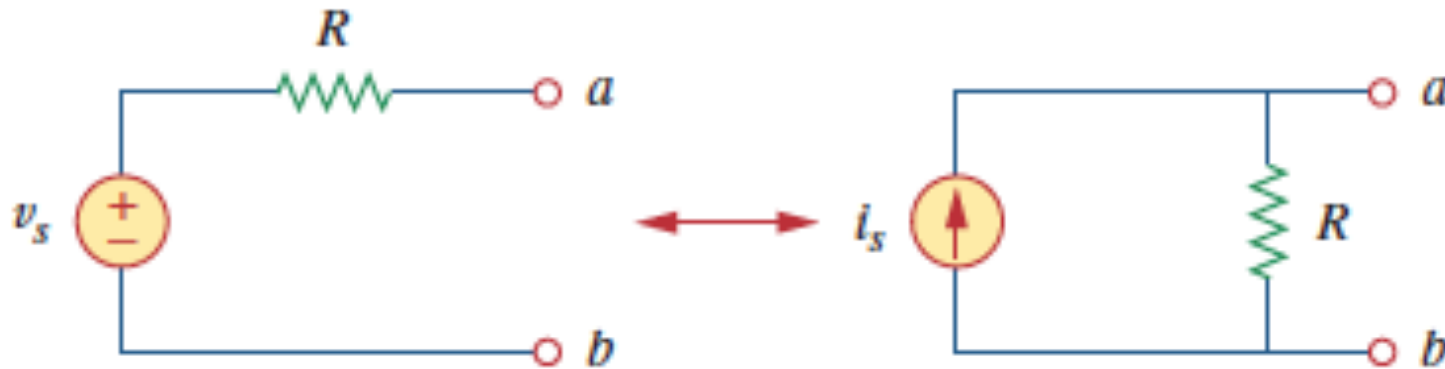


- These two sub-circuits are equivalent *at the terminals  $a, b$*

$$\text{iff } v_s = R I_s$$

- Utility: simplify circuit for quick analysis


- Example:

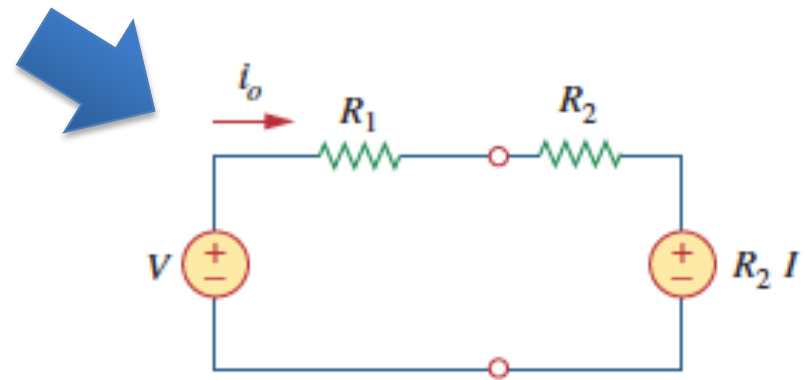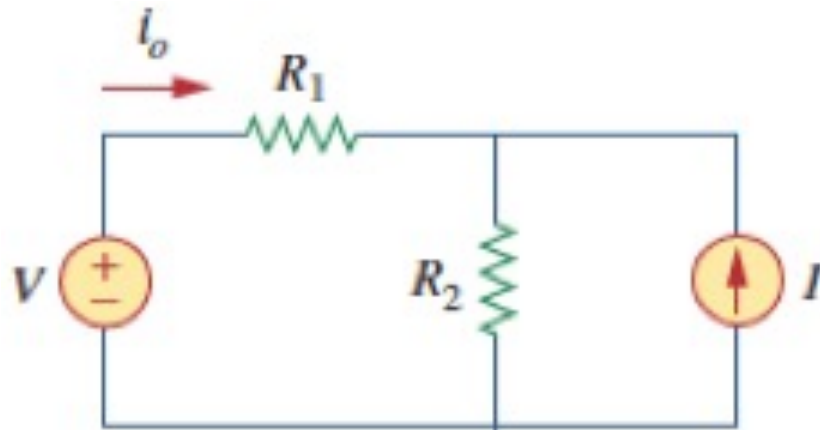


$$i_o = \frac{V - R_2 I}{R_1 + R_2}$$

1.67 A

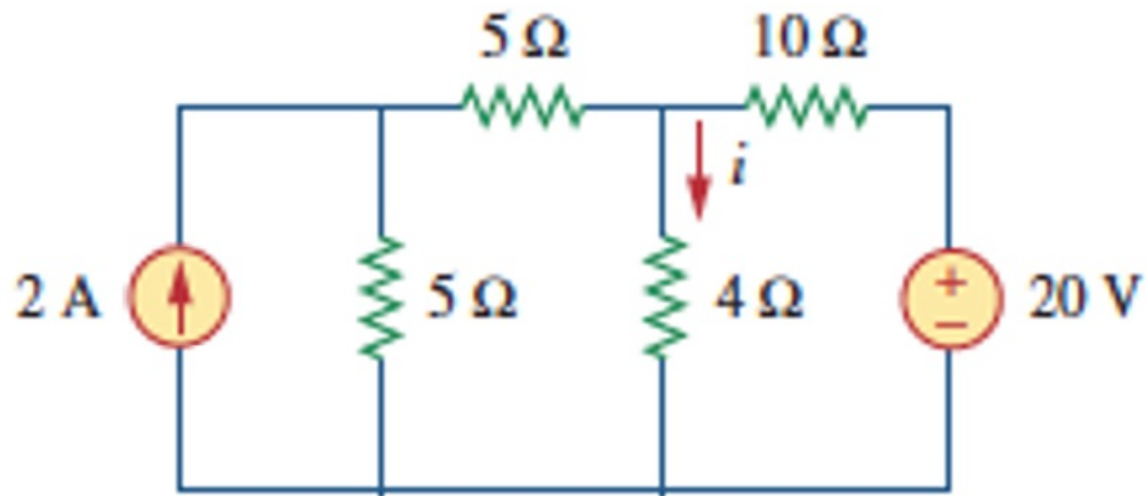**Example:** find  $i$  (convert to just one node)




**Example:** find  $i_x(t)$

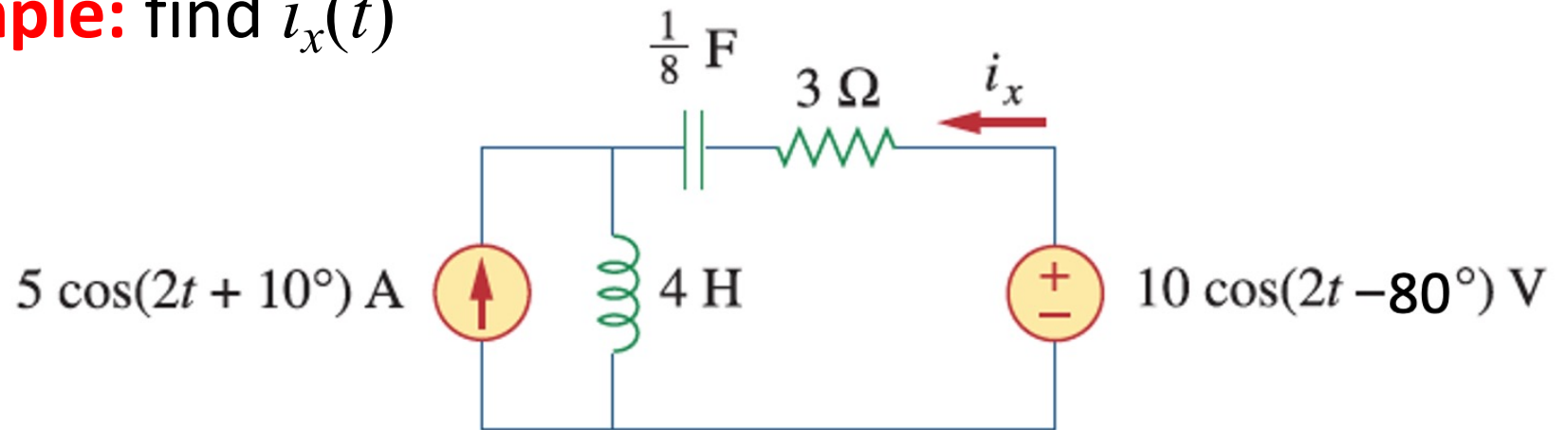





$$i_x(t) = 10 \cos(2t + 174^\circ) \text{ V}$$

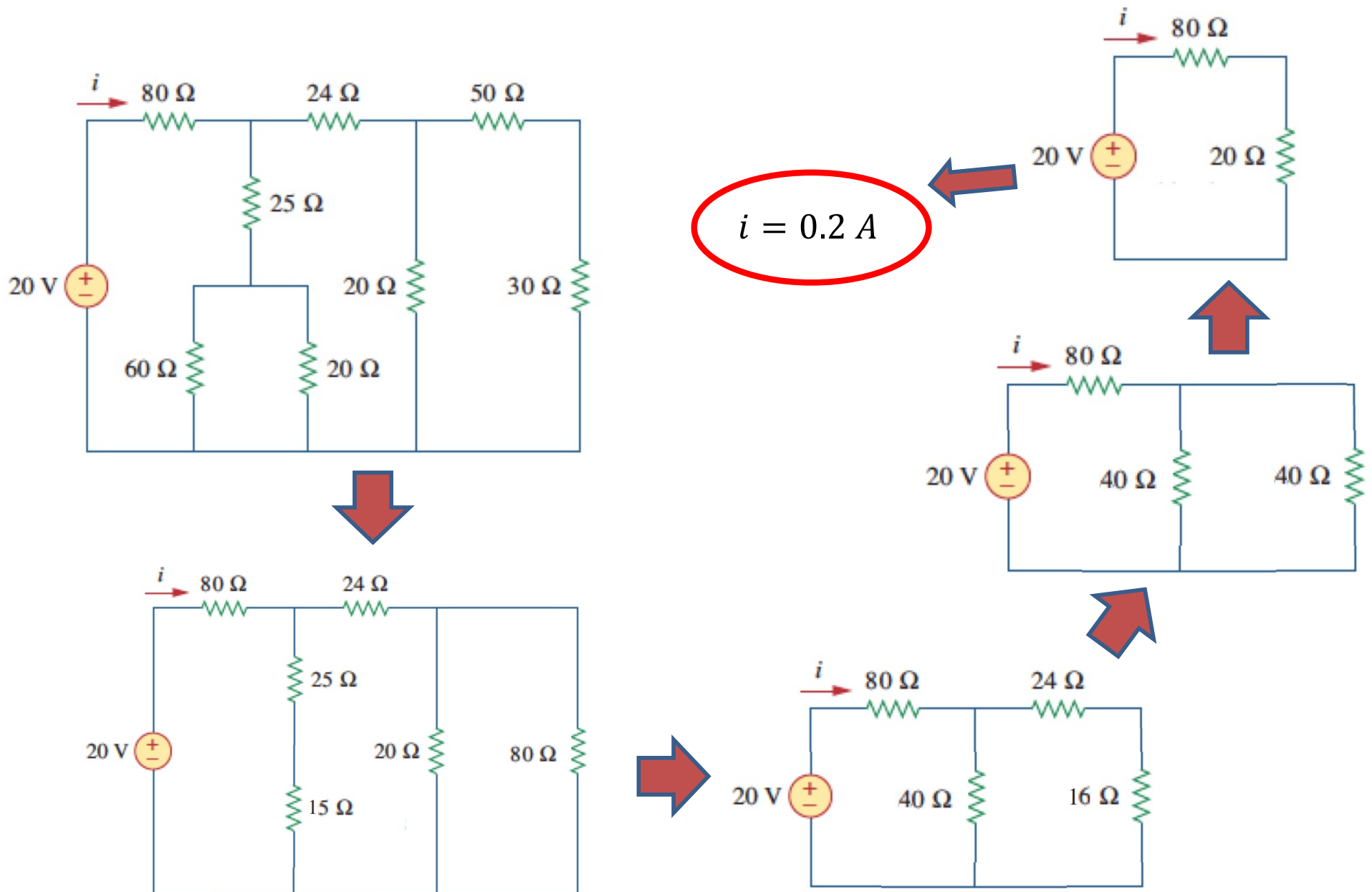- Application: recall repetitive use of series/parallel R:








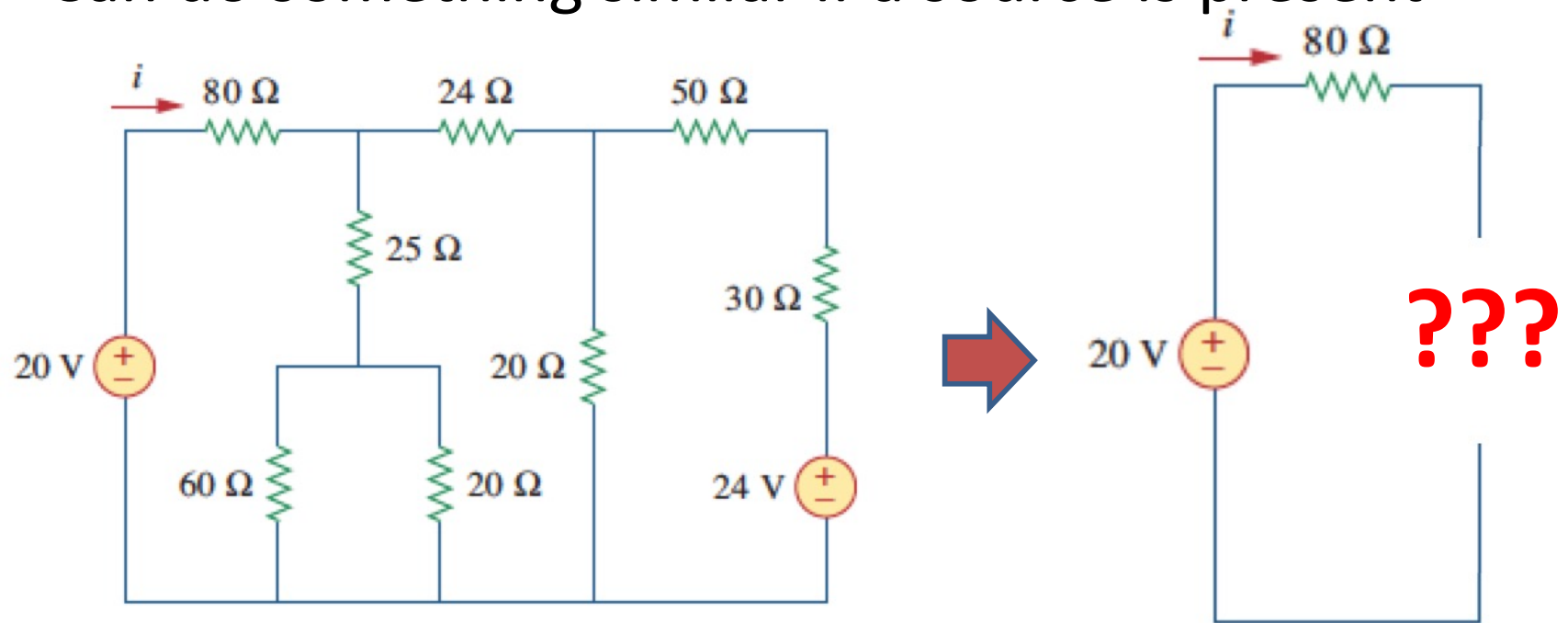
- Can do something similar if a source is present






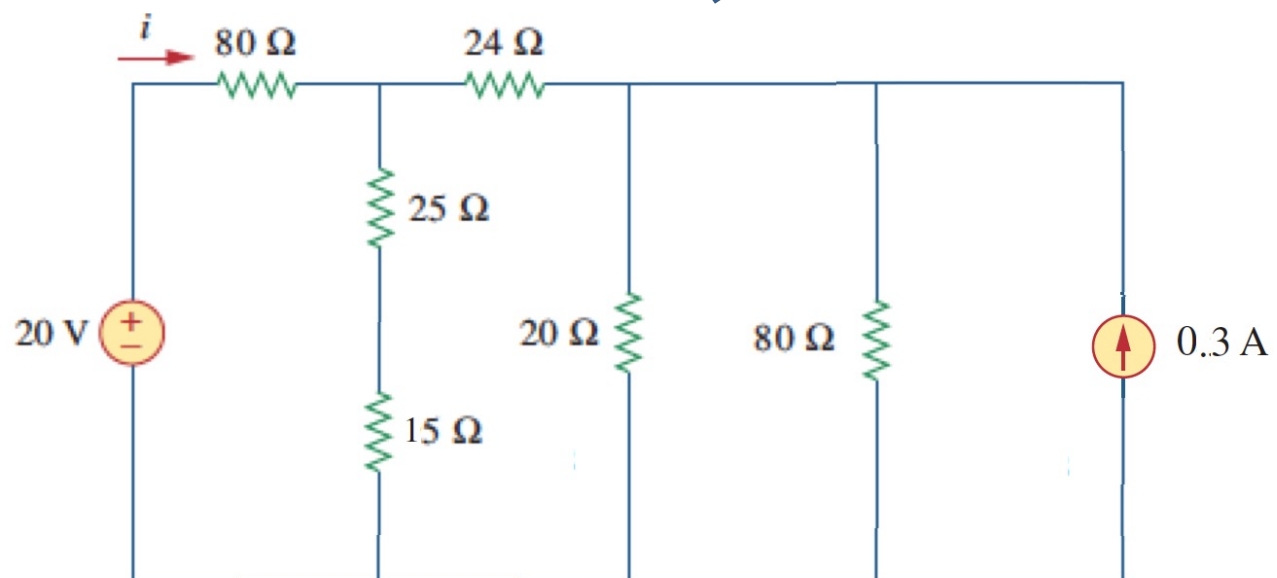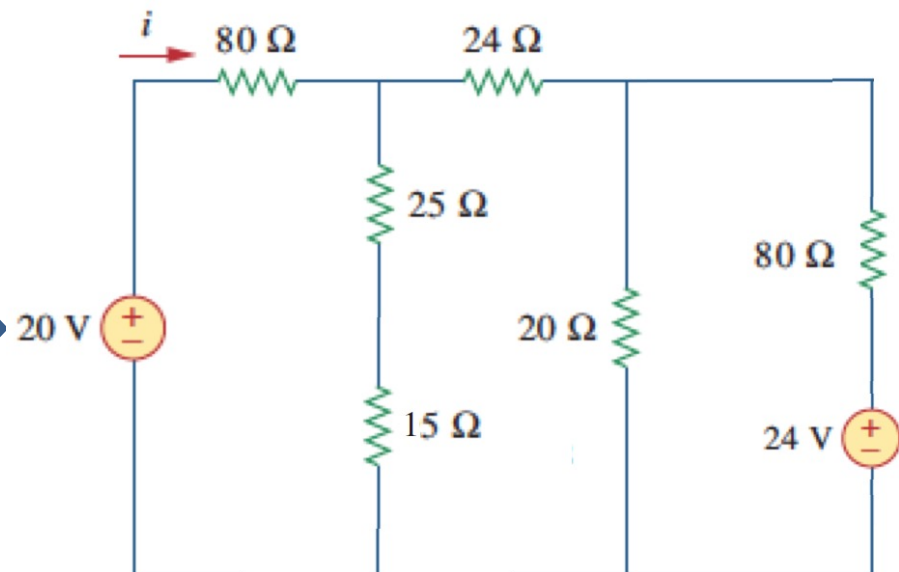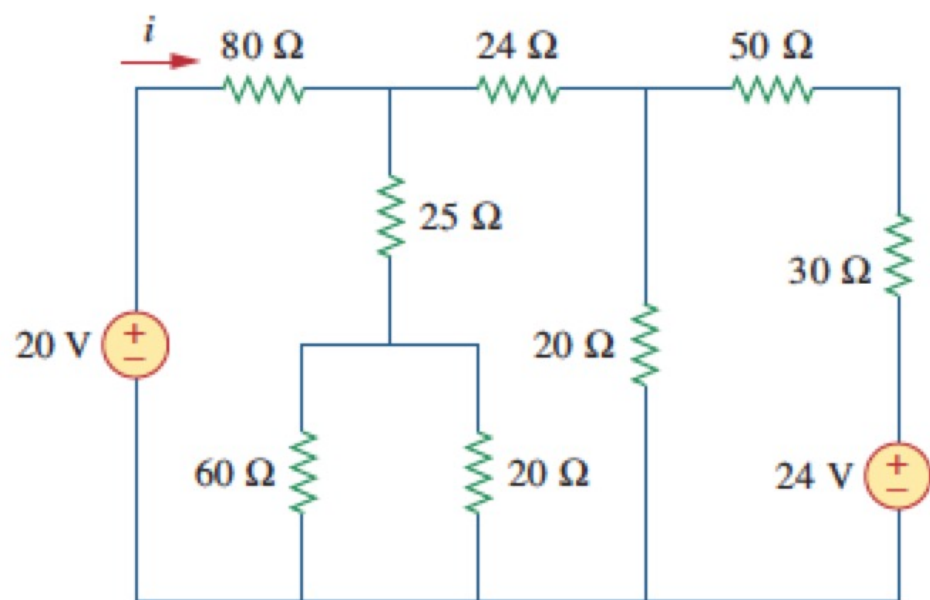



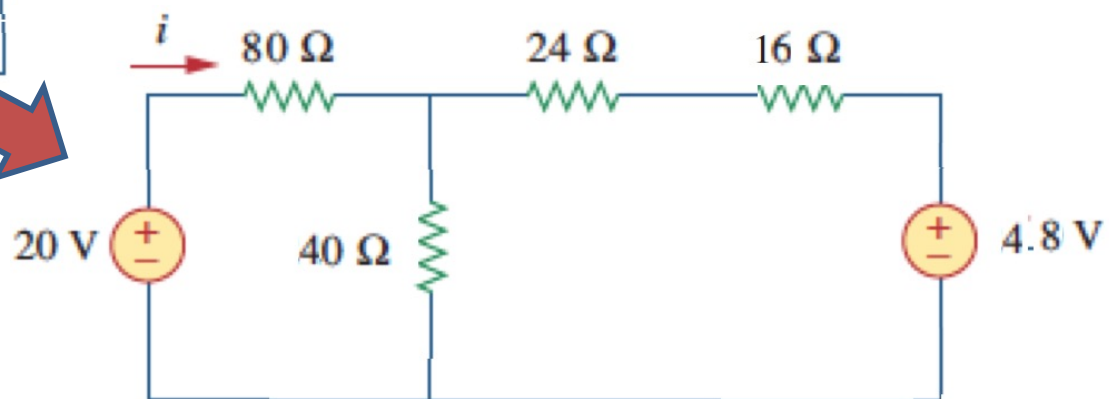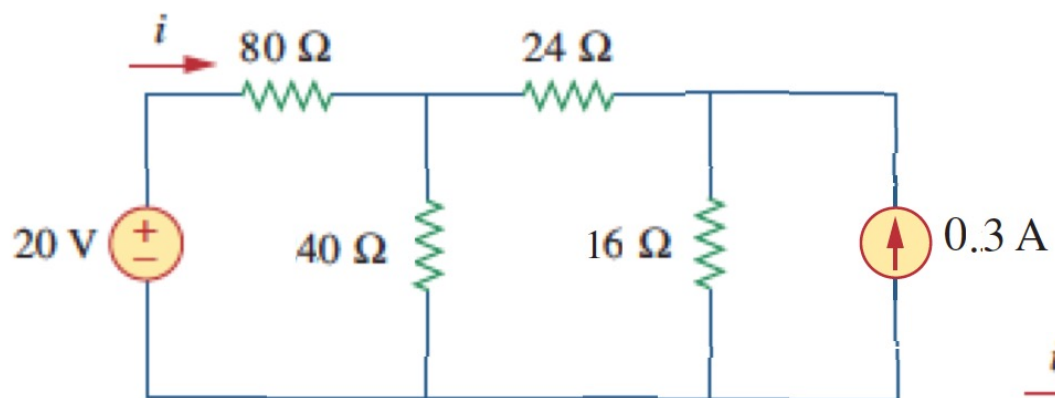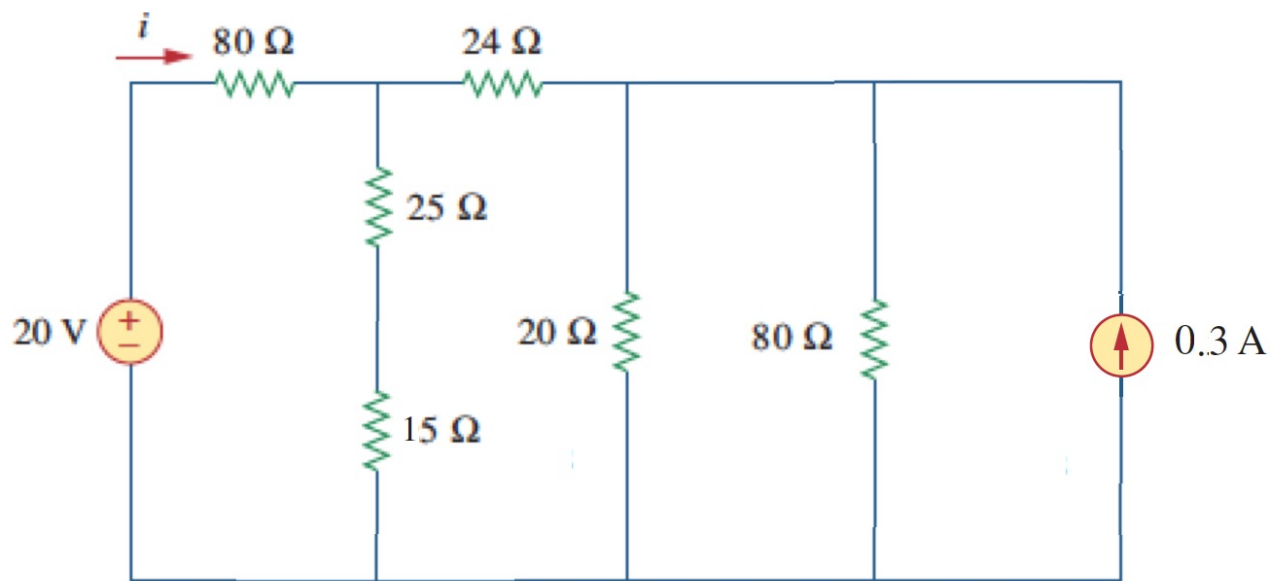


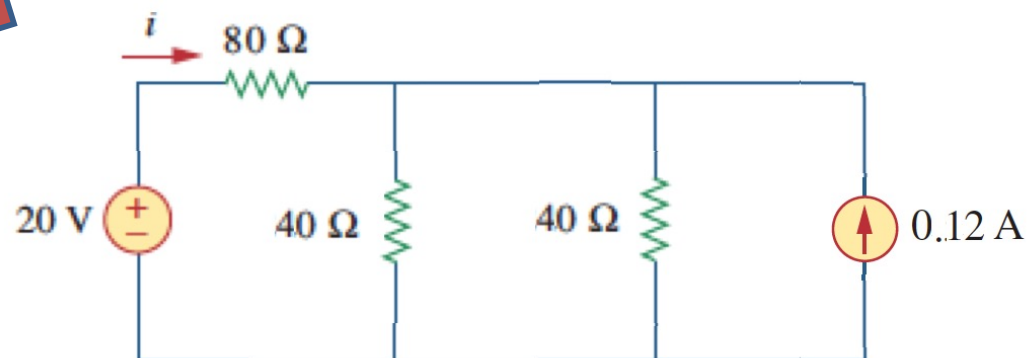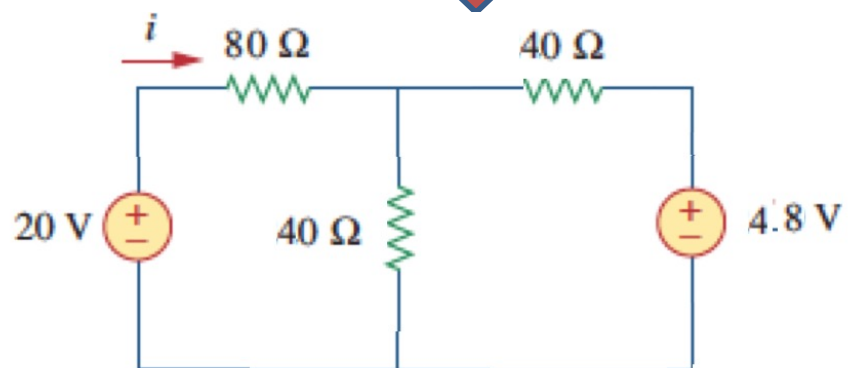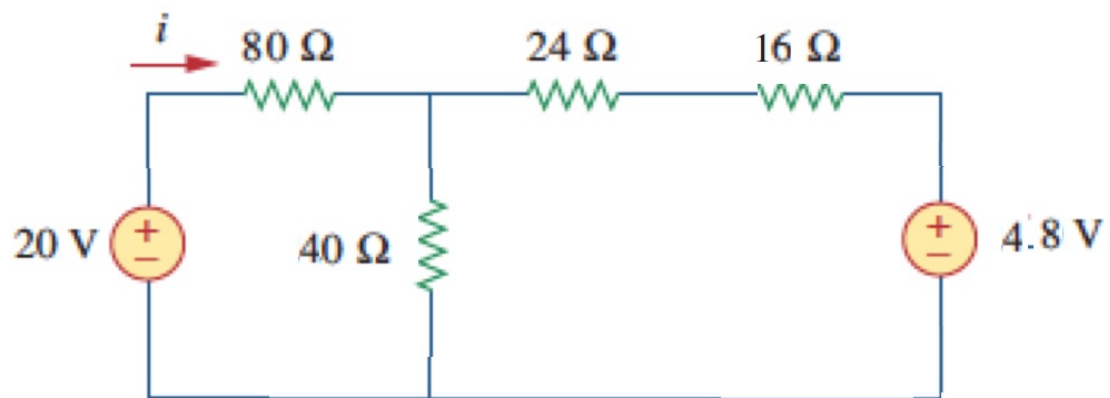

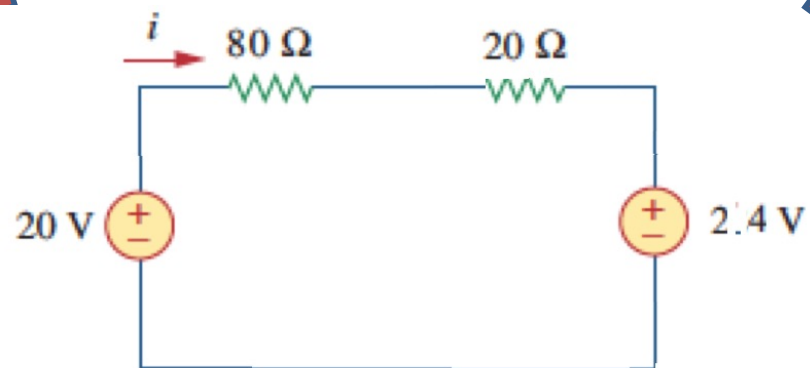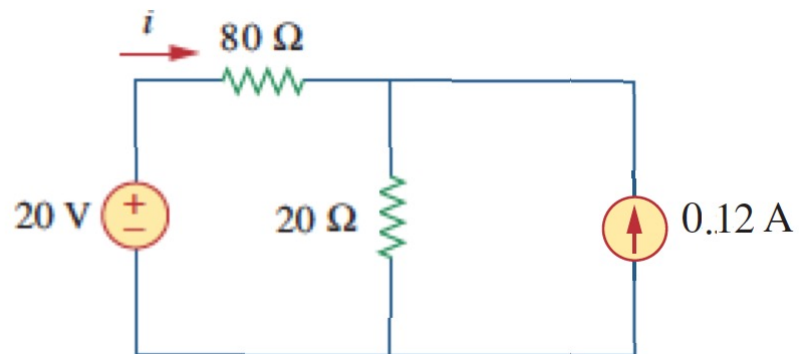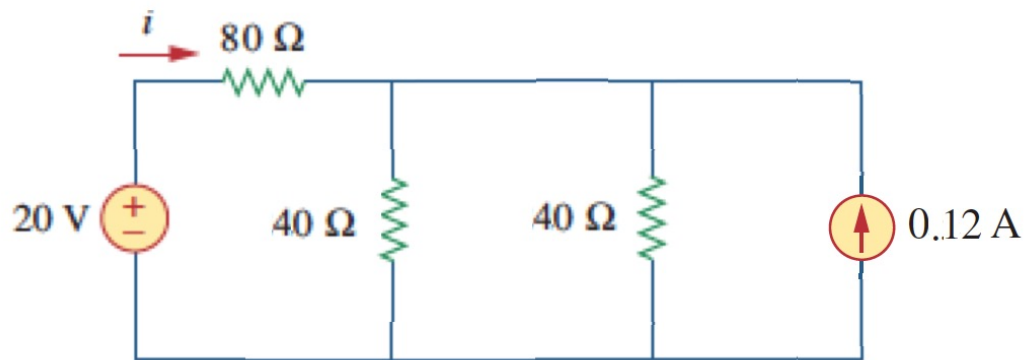

$i = 0.176\text{ A}$

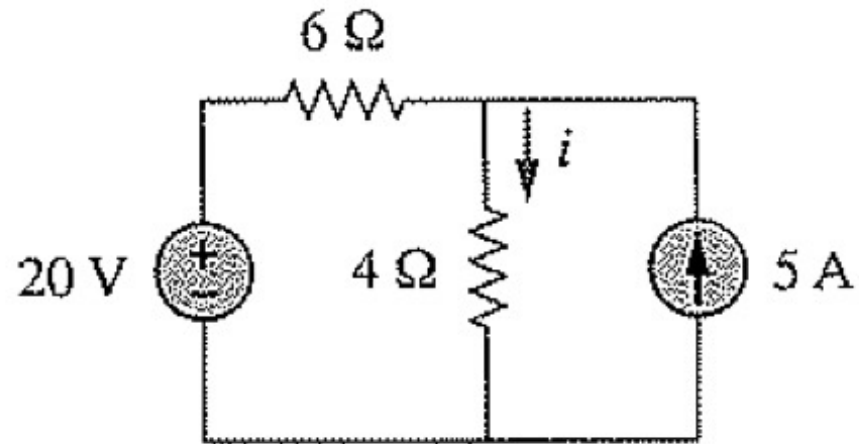
**Example:** find  $i$  (convert to parallel current sources and then current division)



$$i = 5 A$$

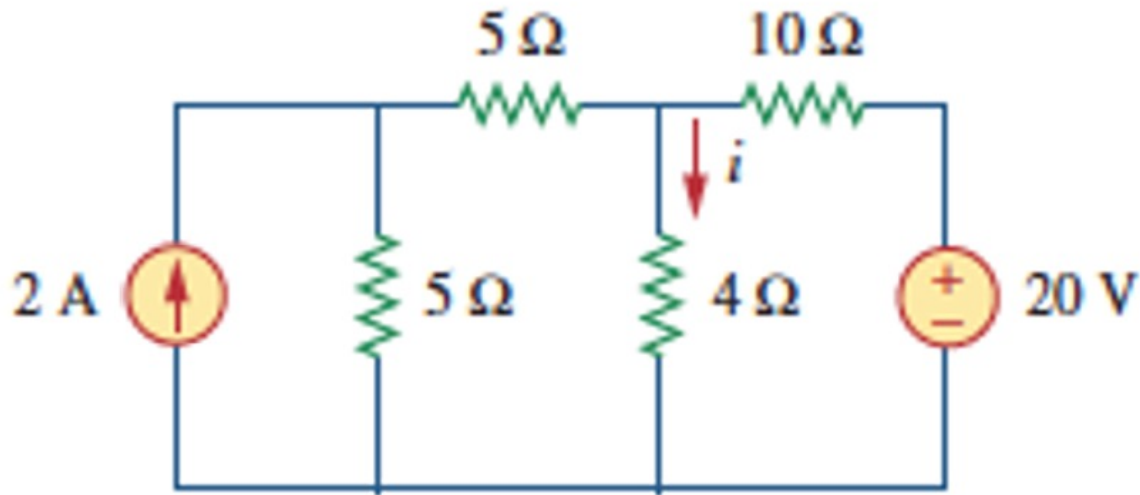
**Alternative for superposition example from above:**

find  $i$  (use transformations, then current division)






**Example:** find  $i_{\Delta}$

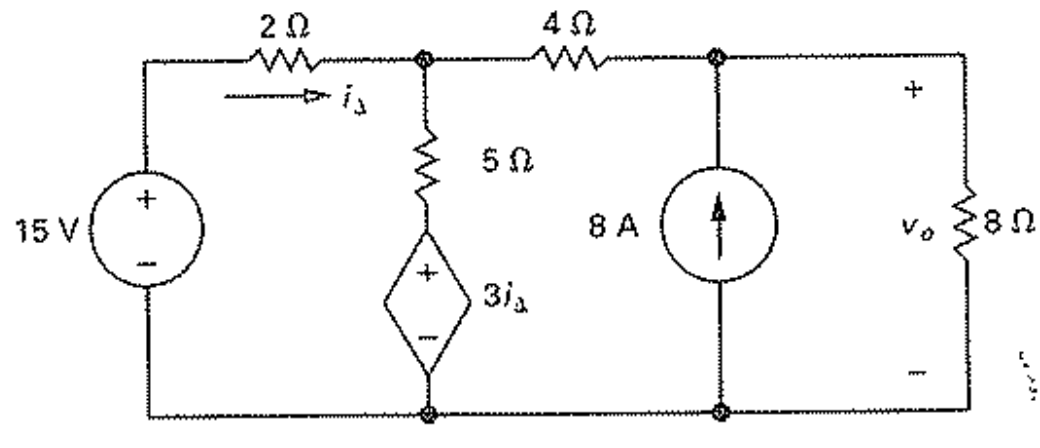

$$i_{\Delta} = \frac{223}{130} A$$




**Example:** find  $i$

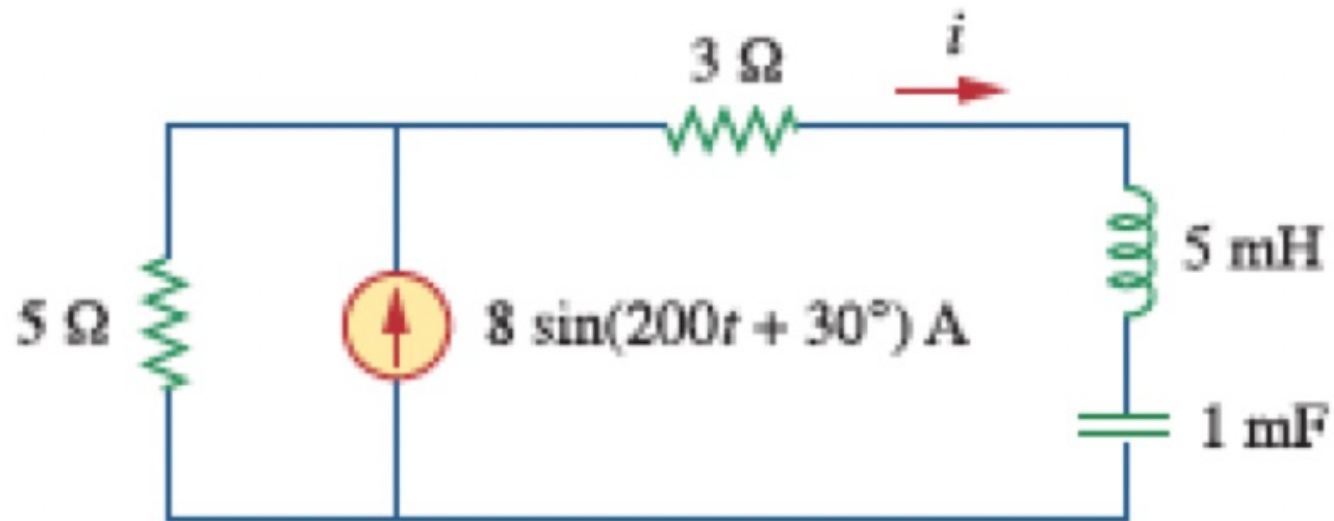

$$i(t) = 8.94 \cos(200t + 56.6^\circ) \text{ A}$$


**Practice problem:** find  $v_o$  and  $i_o$
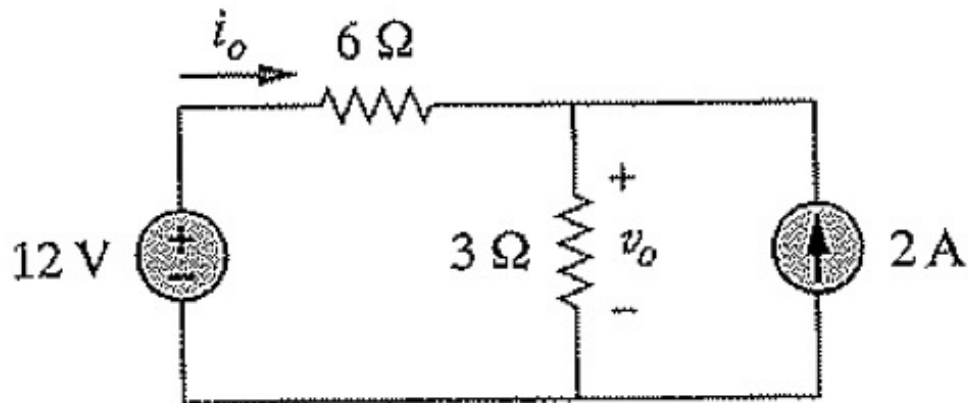
$$v_o = 8\text{ V}, \quad i_o = \frac{2}{3}\text{ A}$$




**Practice problem:** find  $i_o$

$$i_o = \frac{14}{3} \text{ A}$$

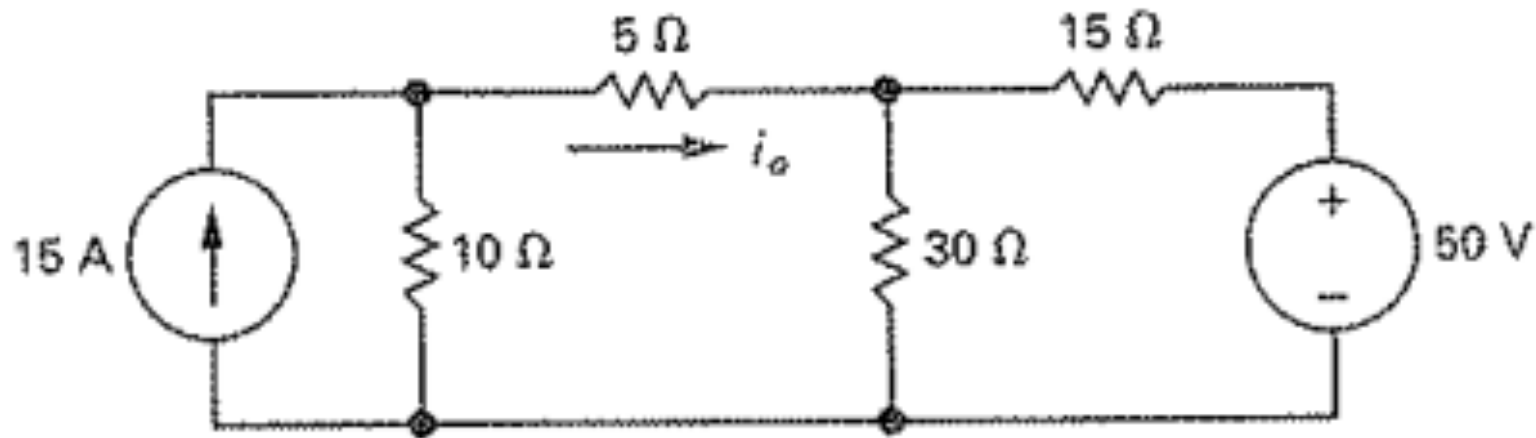


**Practice problem:** find  $i_o$

$$i_o = 1.79 \text{ A}$$

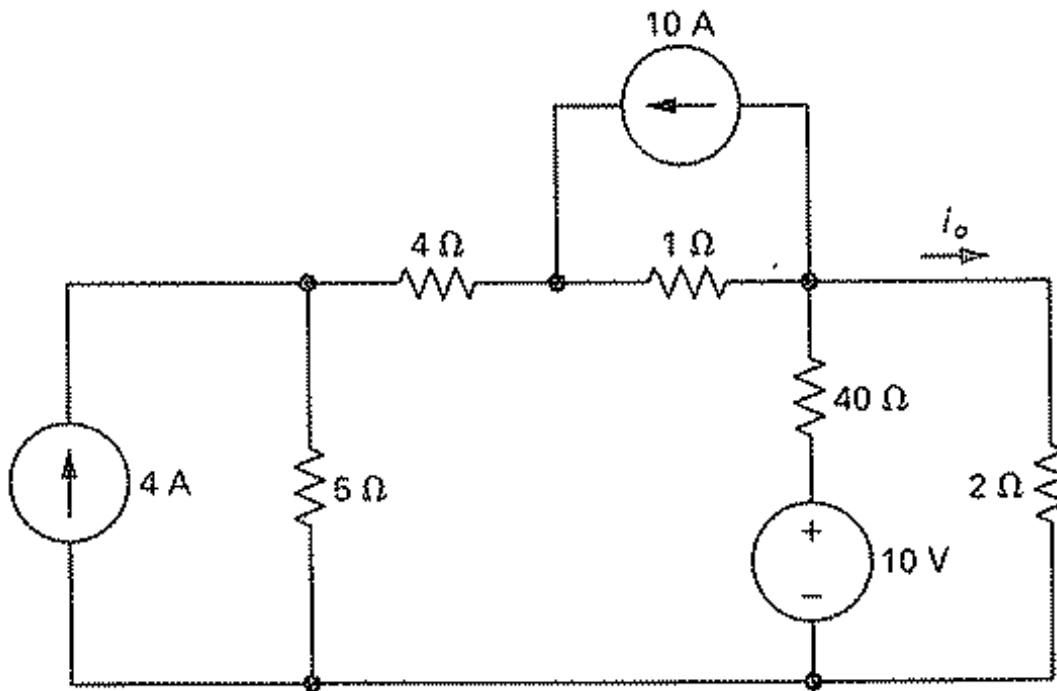

**Practice problem:** find  $v_o$

$$v_o = -11 \text{ V}$$

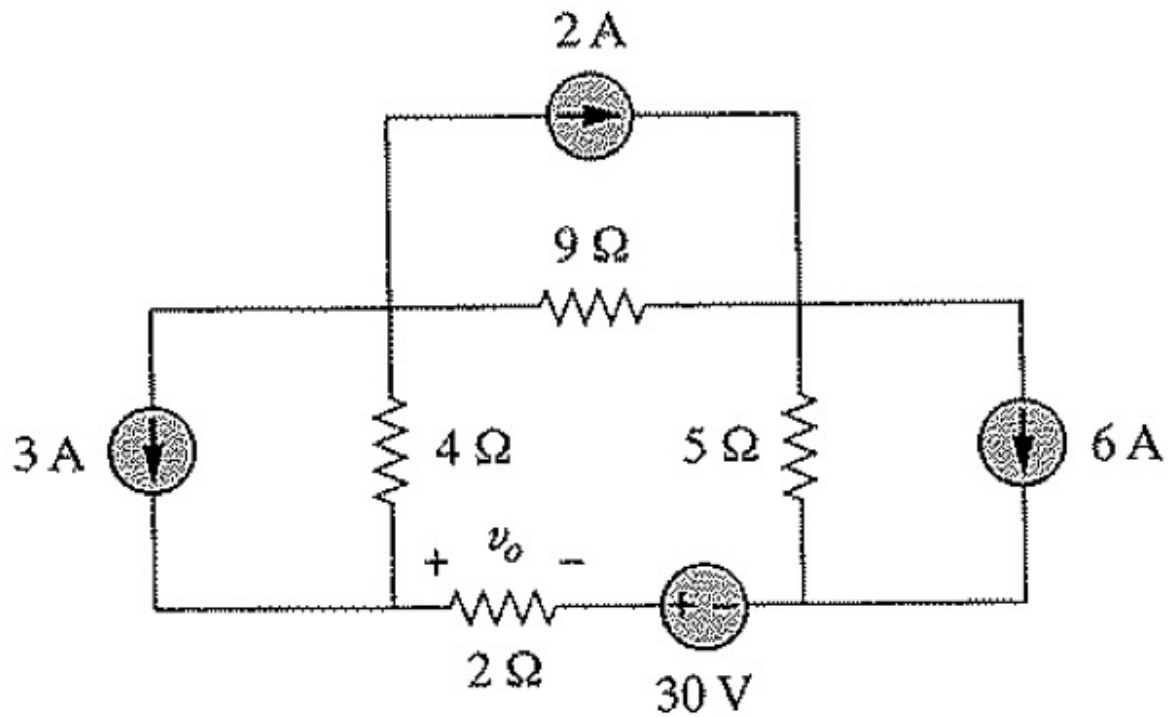

**Practice problem:** find  $v_x$  if  
 $= v_s(t) = 50 \cos(2t + 90^\circ) \text{ V}$   
and  $i_s(t) = 12 \cos(2t + 10^\circ) \text{ A}$

$$v_x(t) = 129 \cos(2t + 28.76^\circ) \text{ V}$$

