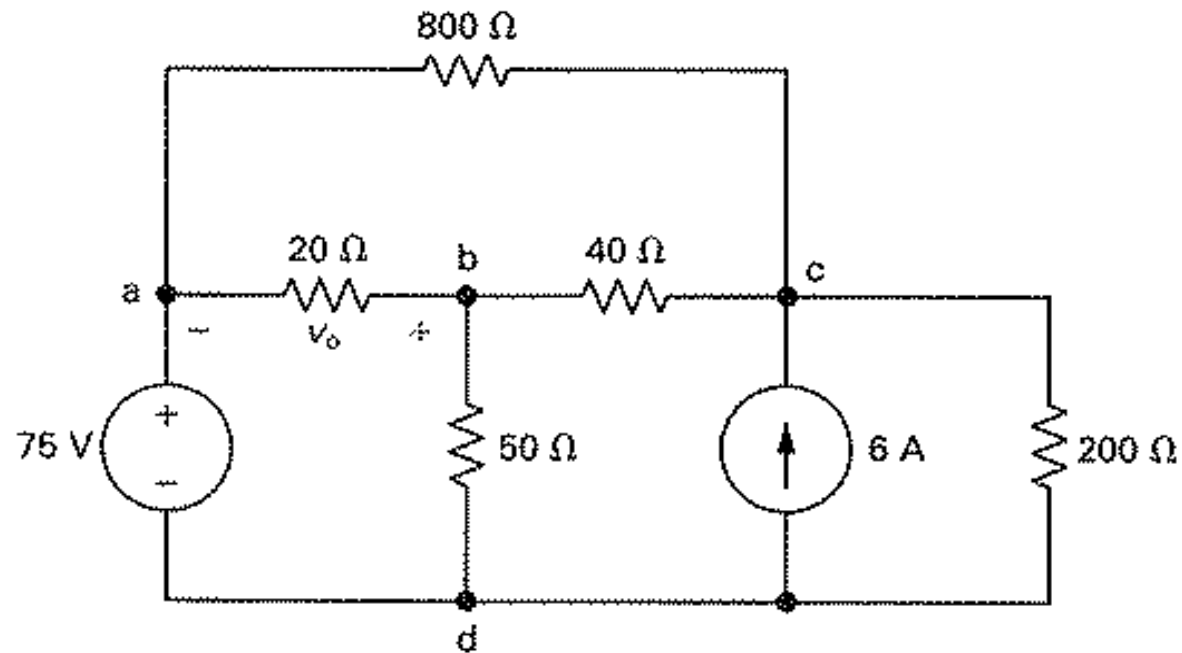



Lecture 13

Node Analysis – 6 of 7

examples


Example: find v_o




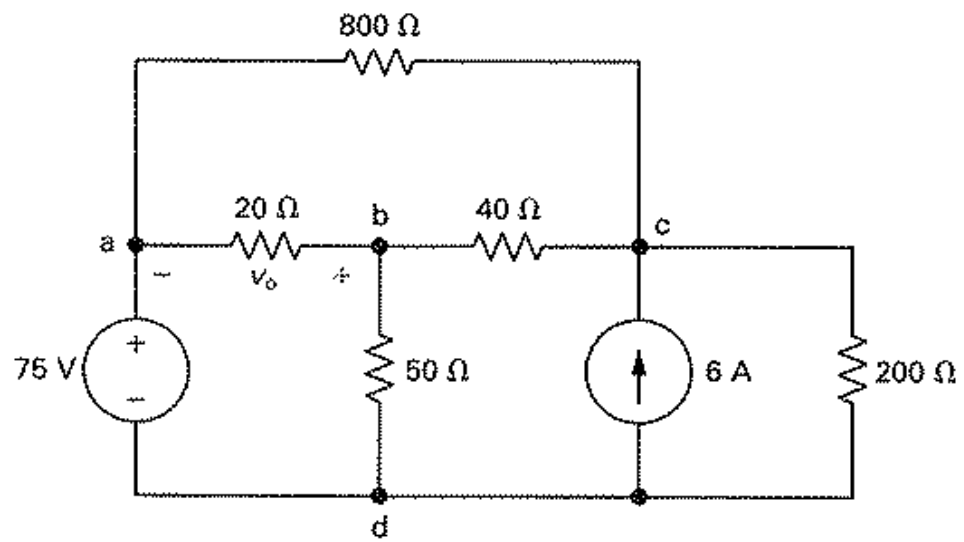

$$v_o = 40 \text{ V}$$


Example: find i_0

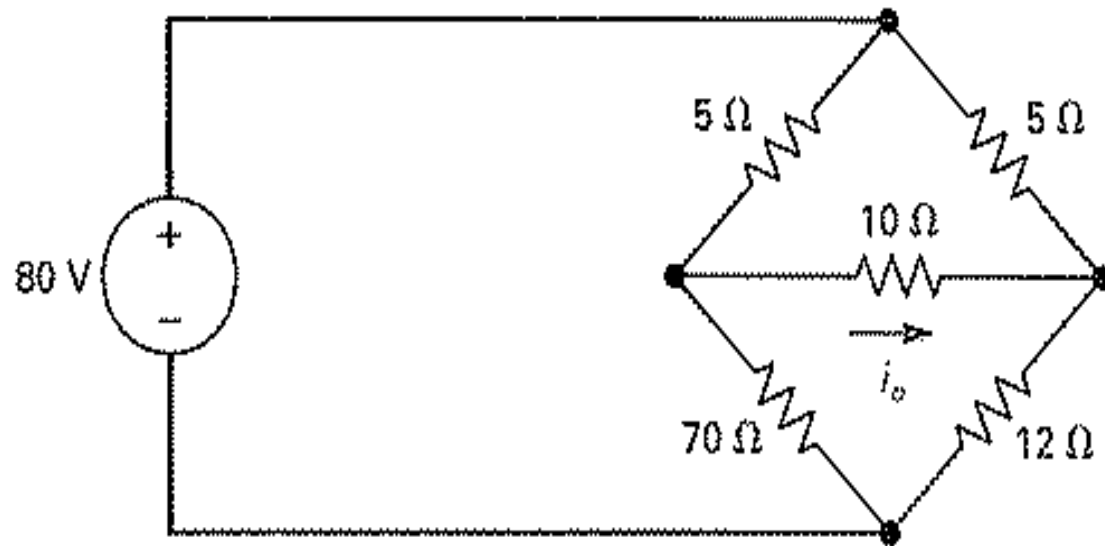


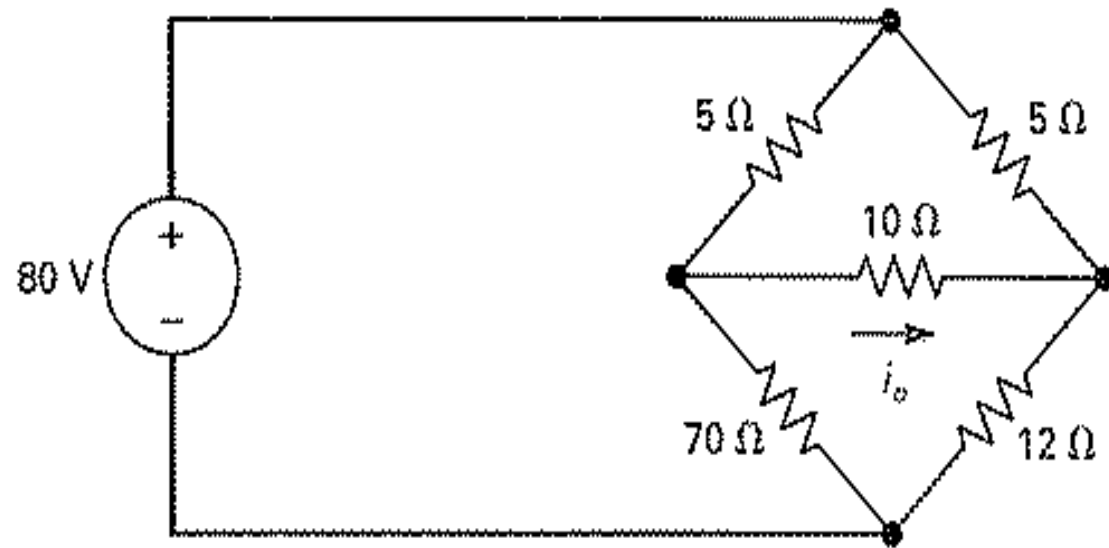

$$i_o = 1 \text{ A}$$

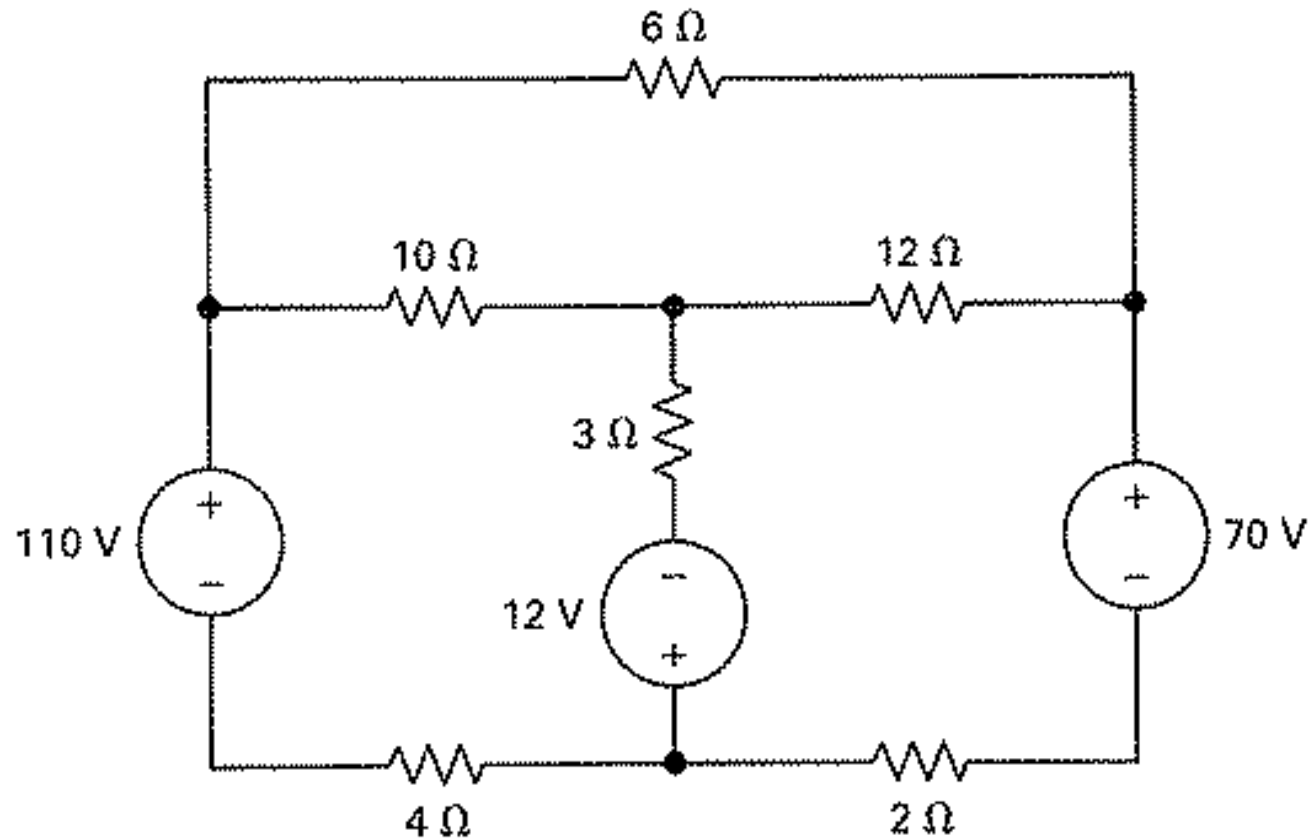Example: find the power of the $10\ \Omega$ resistor




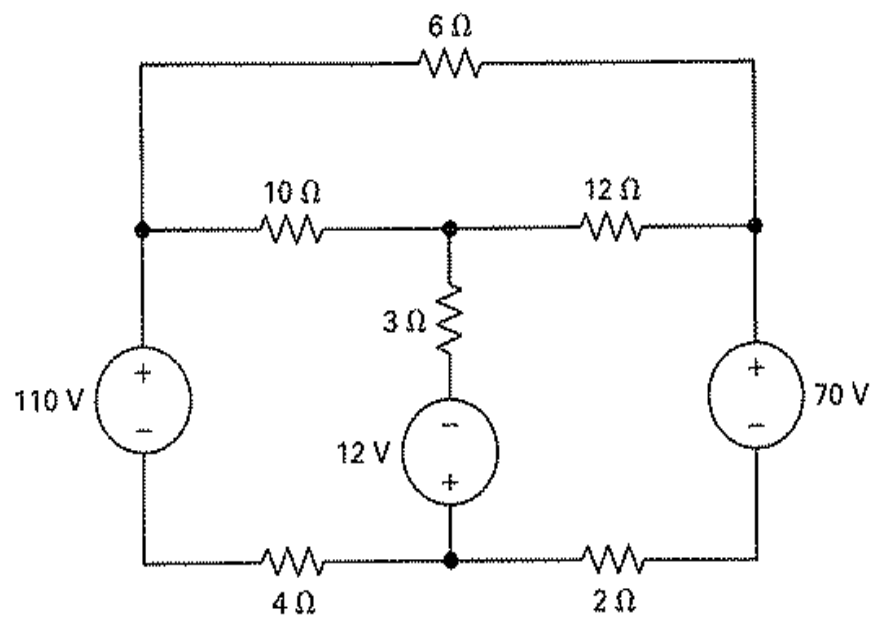

$$P = 360 \text{ W}$$


$$v = 30 \text{ V}$$

Example: find v

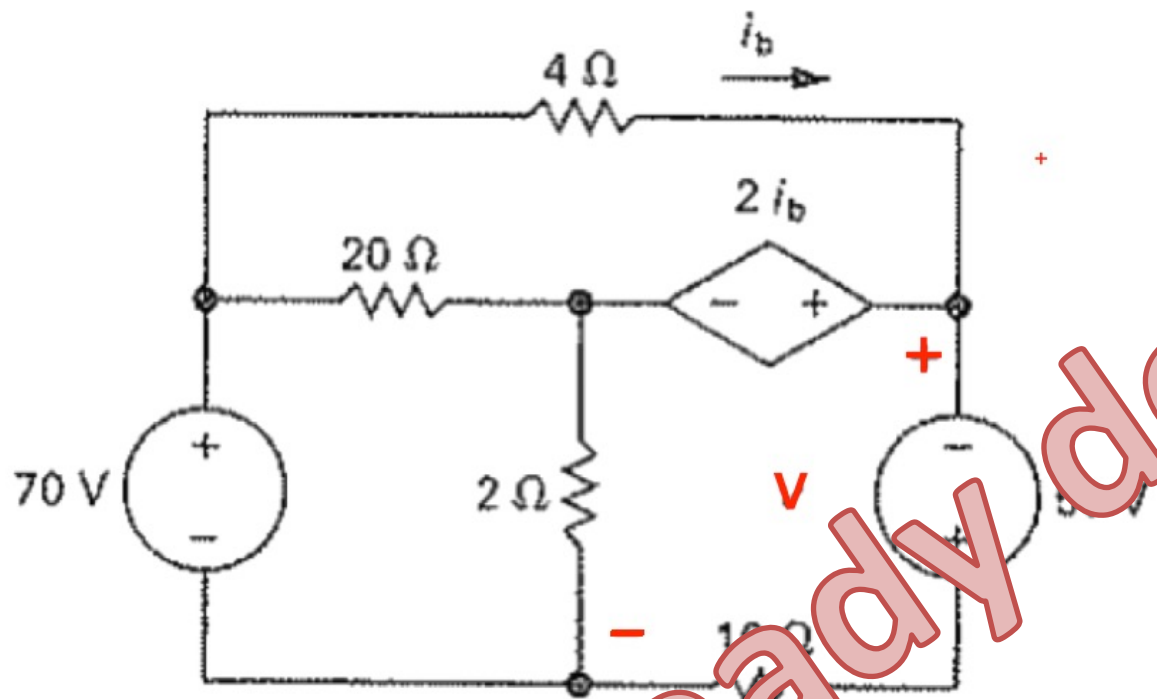



Already done

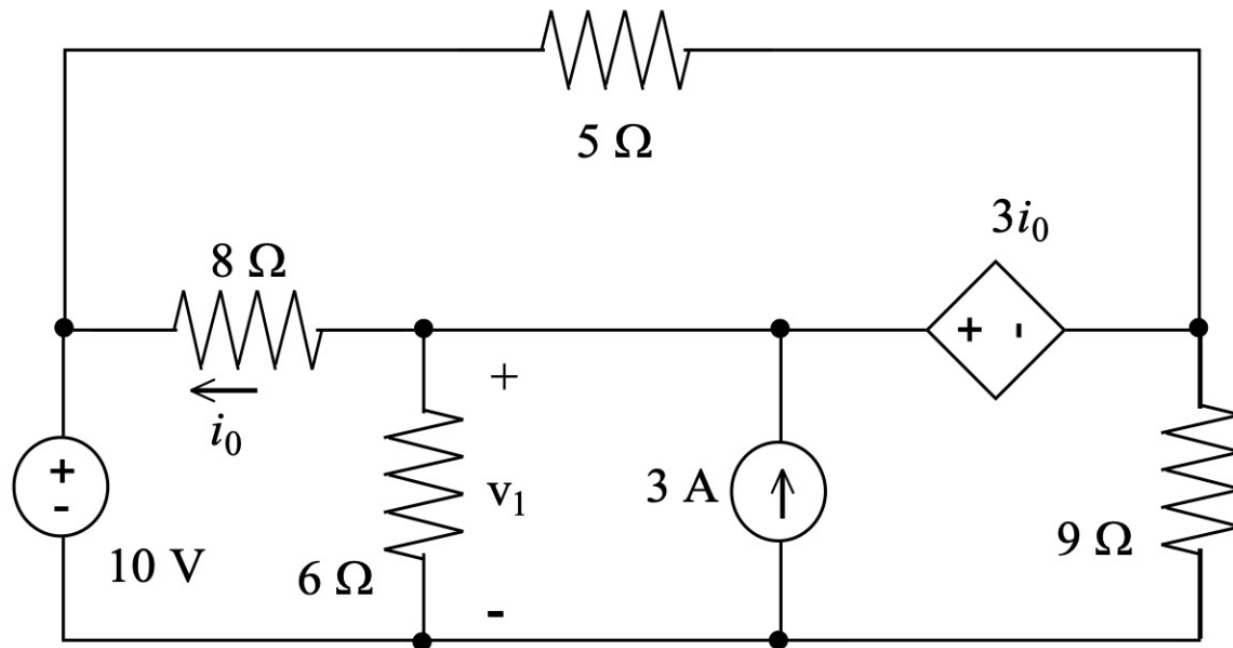2. For the circuit shown below, find v_1 . How much power is supplied by the current source?





$v_1 =$ _____ Power = _____

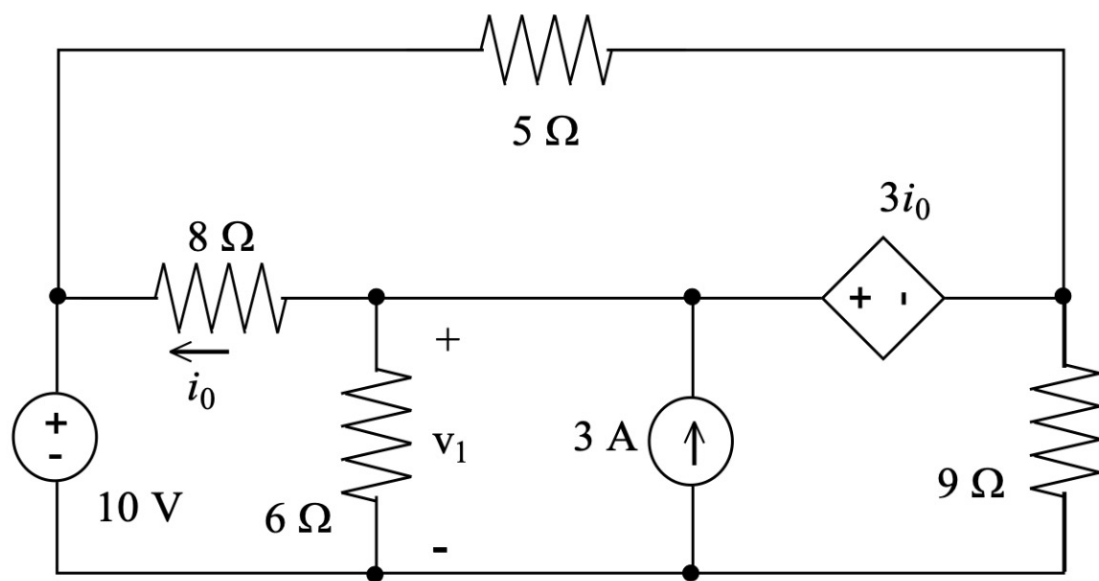

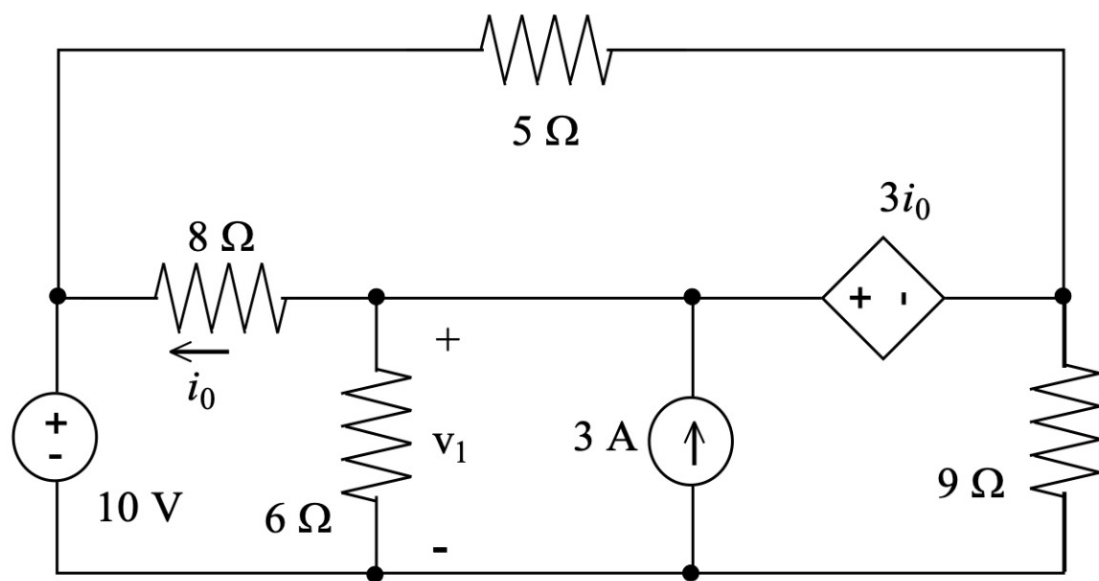

Example:

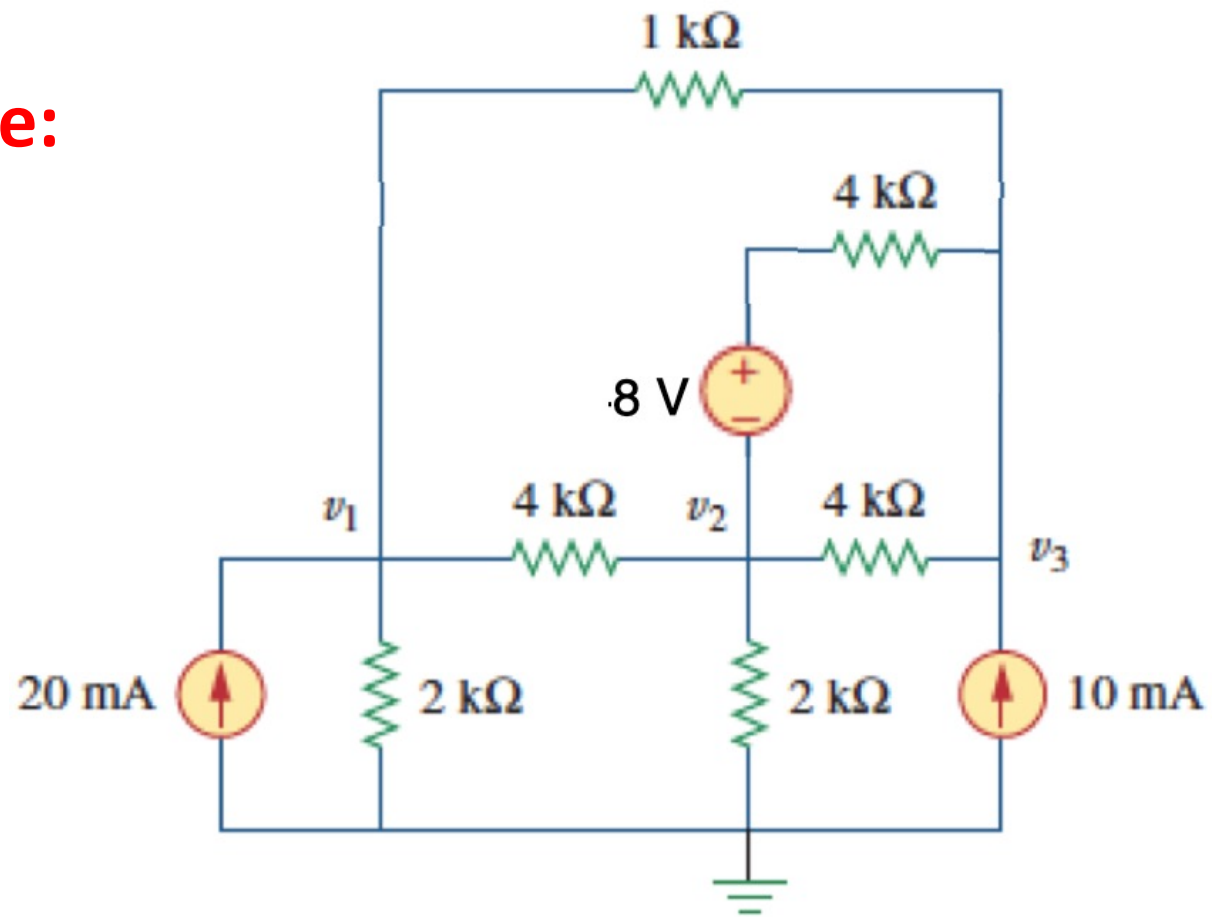


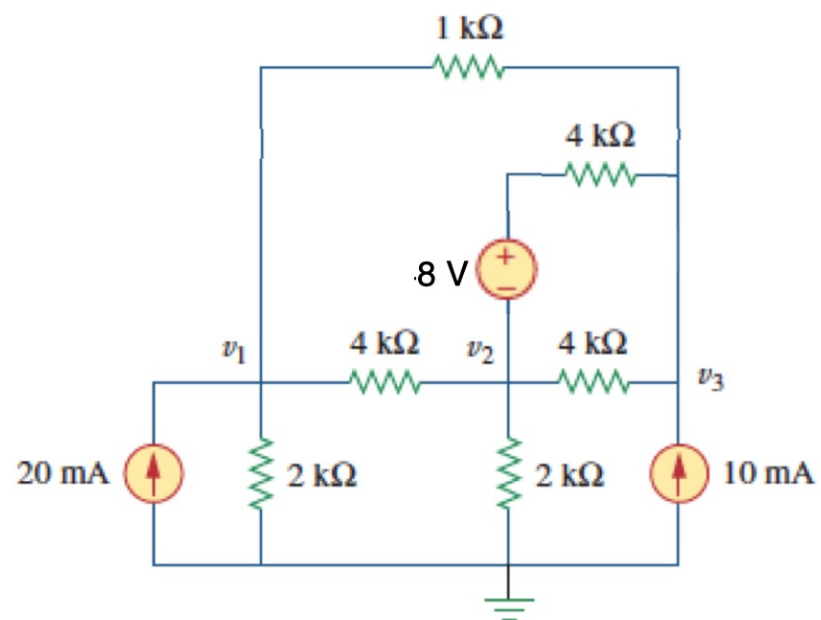

$$\begin{aligned} v_1 &= 37.8\text{ V} \\ v_2 &= 22.2\text{ V} \\ v_3 &= 40.6\text{ V} \end{aligned}$$


60 W

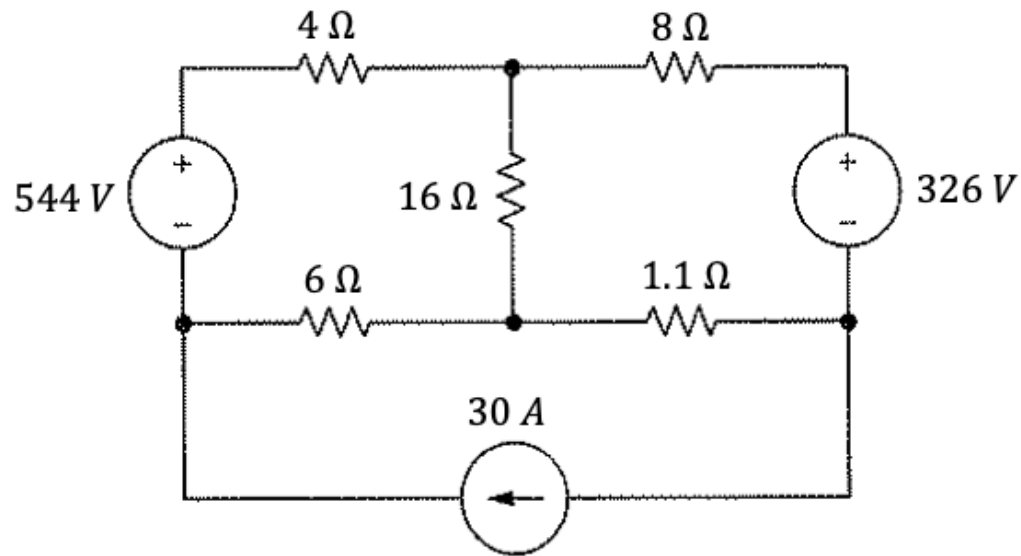Practice problem: find the power of the current source



Practice problem: find i_0 and i_1
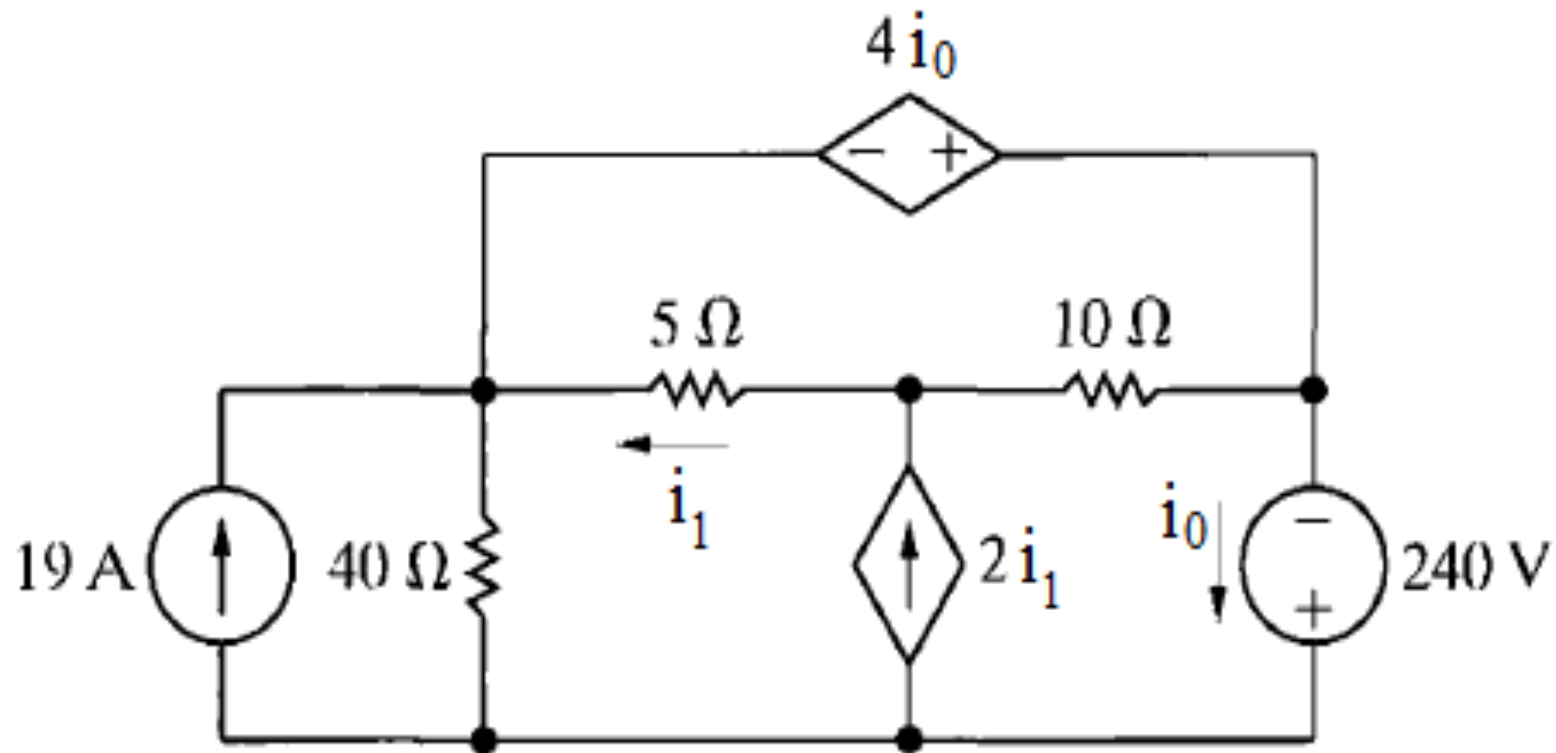
$$i_0 = 10 \text{ A}$$
$$i_1 = -8 \text{ A}$$



Practice problem: The variable voltage source shown in the circuit below (the source with the diagonal line through it) is adjusted so that the power absorbed by the $5\ \Omega$ resistor is 5 watts. Find the value of v_{DC} .

