

# Lecture 36


## 2<sup>nd</sup> Order Transients – 2 of 4

Form; more resistances;  
initial and final conditions

# So far, for “simple” RLC circuits


- Step 1 – identify type and form characteristic polynomial

Parallel

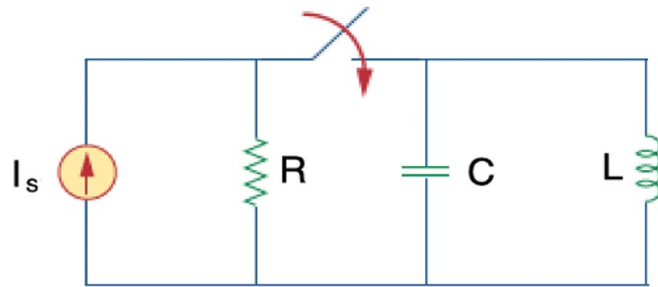

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

Series

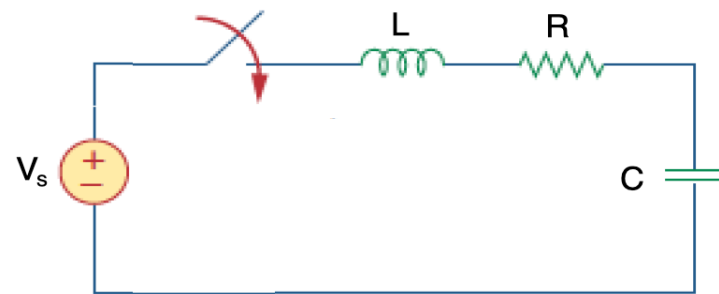

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

- Step 2 – based on real vs complex roots, identify form of solution

Real roots:



$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + x_\infty$$

Complex roots:


$$x(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t + x_\infty$$

- Step 3 – use final value to evaluate  $x_\infty$
- Step 4 – the other constants?

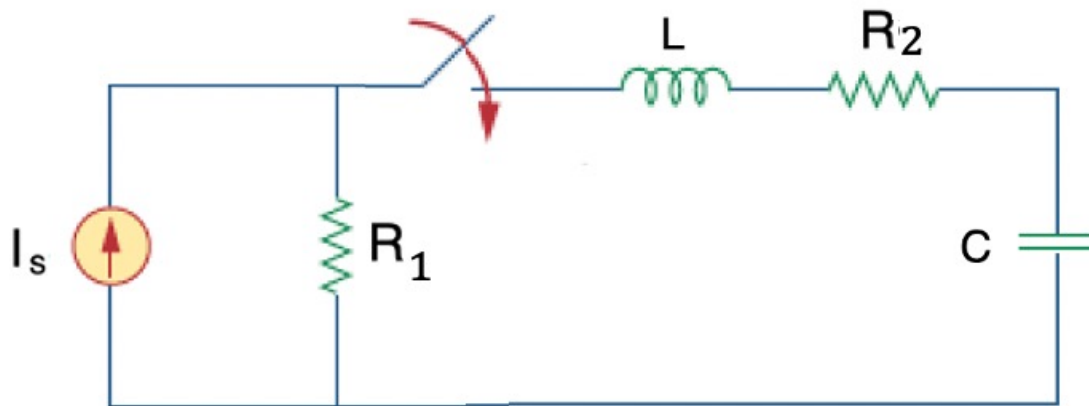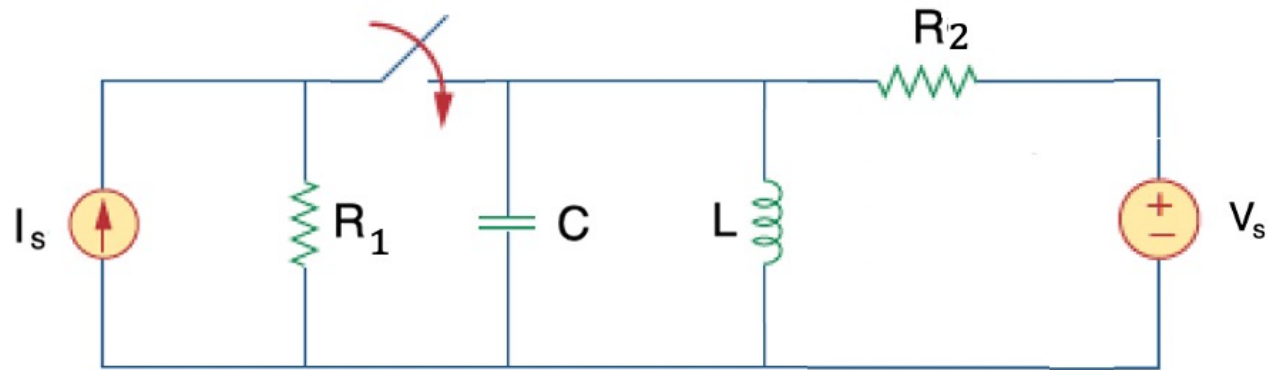
- Aside – what if we add an extra resistor?



- Or several?

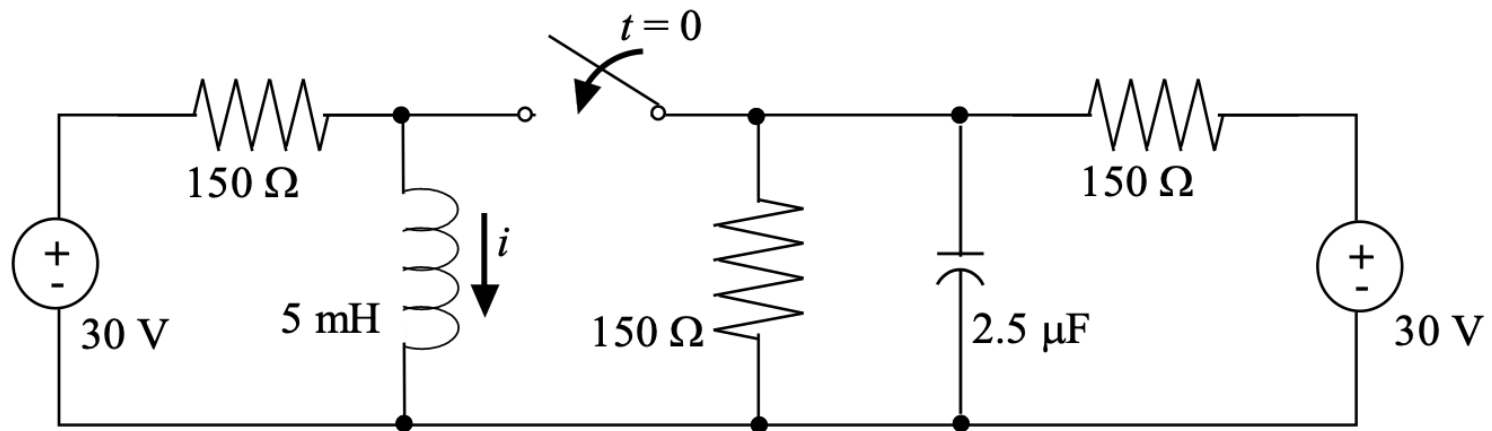

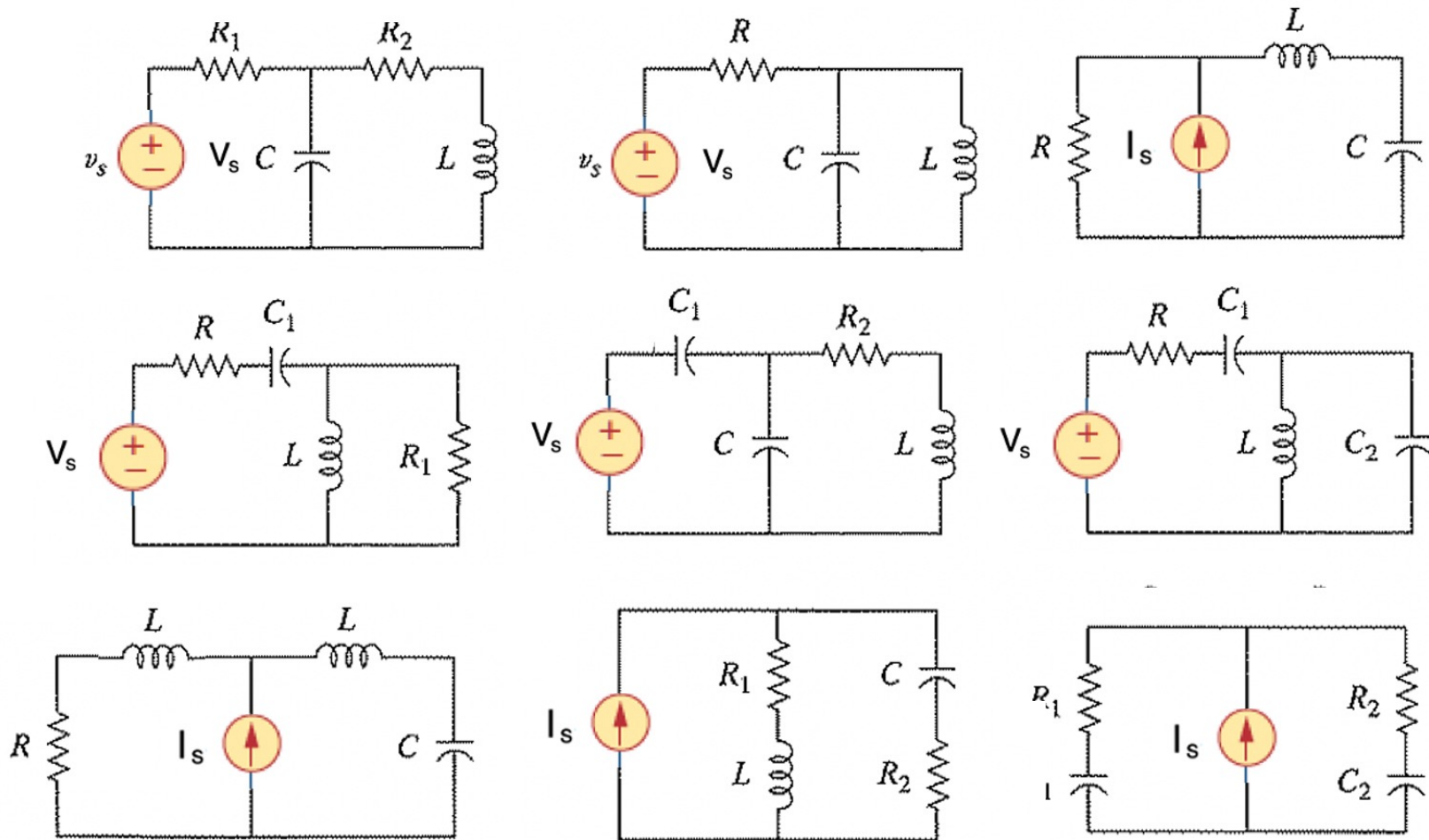
**Question:** Which of these circuits match our assumed 2<sup>nd</sup> order RLC circuit form? If yes, which form, series or parallel?



# Initial and Final Conditions

- Just like the 1<sup>st</sup> order case:
  - From a DC analysis based on “open” or “short” models for C and L both before and after the switch event
    - Before switching event yields initial values
    - After switching event yields final values

**Example:**

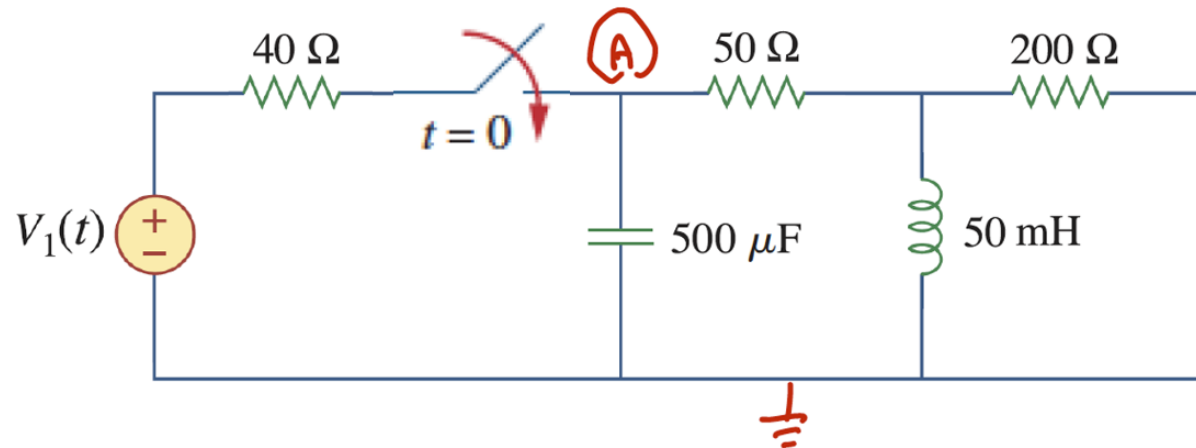

$$A(t) = a_0 + a_1 e^{-94.3t} + a_2 e^{-764t}$$


- $A(0) = 0$
- $A(\infty) = \frac{5}{9} V_1$

$$a_0 = \frac{5}{9} V_1$$


$$a_0 + a_1 + a_2 = 0$$



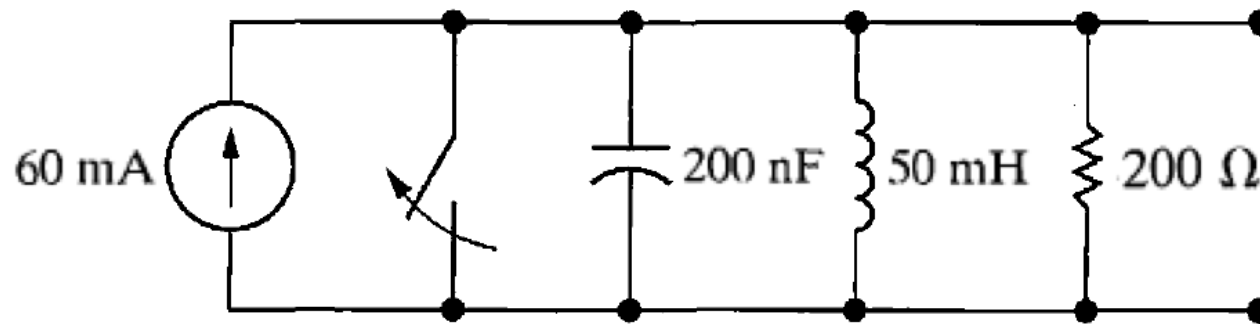
**Example:** Find the initial/final conditions



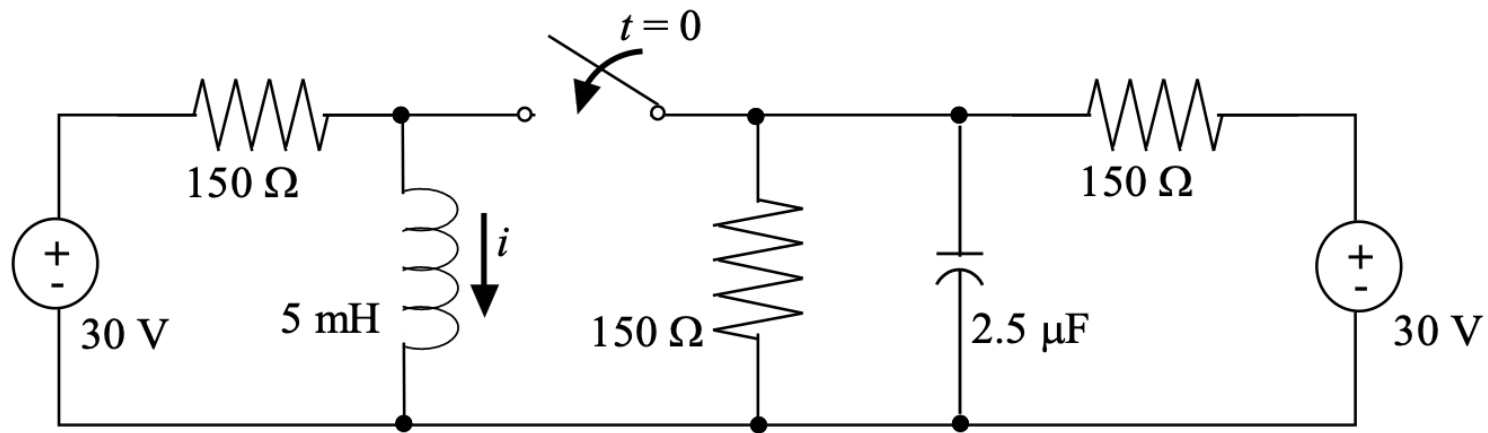
**Example:** Find the initial/final conditions




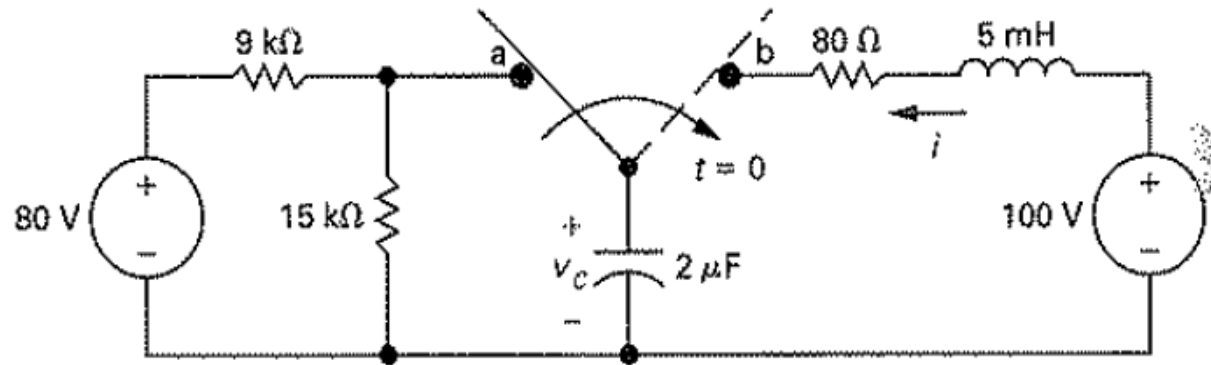**Example:** Find the initial/final conditions



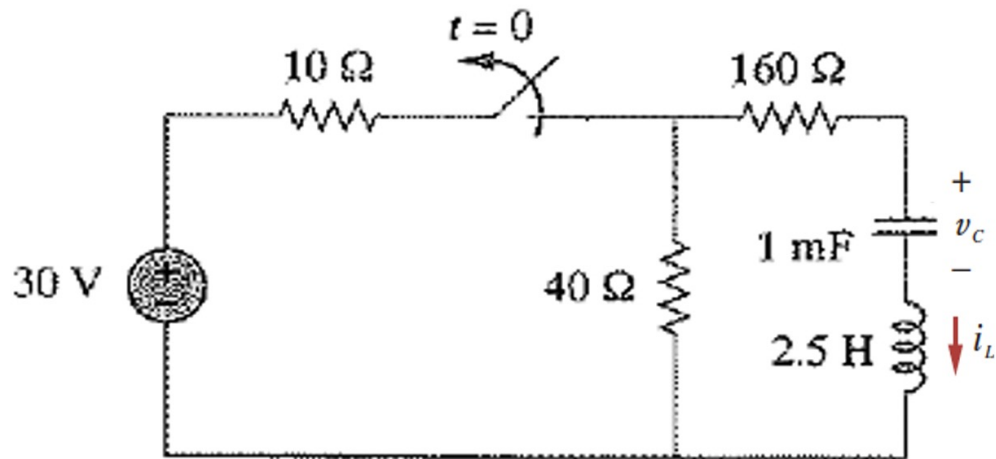**Practice problem:** Find the form of solution and the initial/final conditions



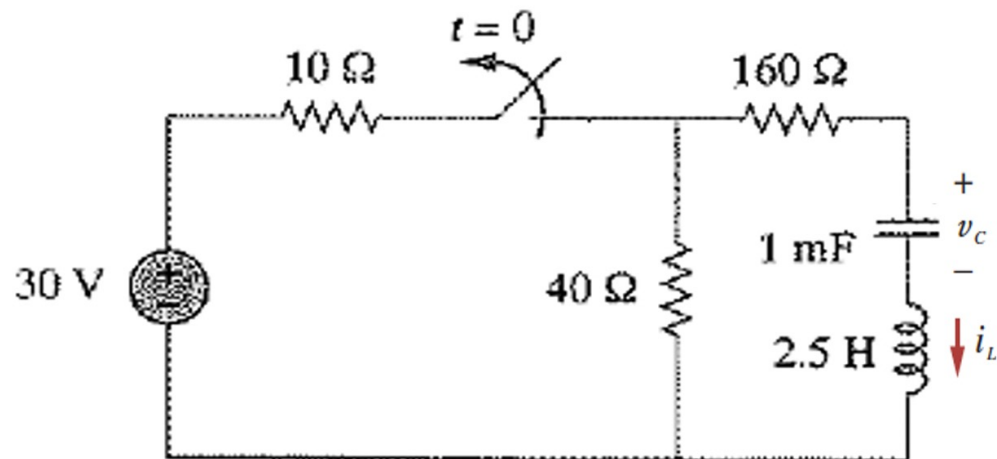

$$x(t) = A_1 e^{-5.36t} + A_2 e^{-74.6t} + x_\infty$$


$$i_L(0) = 0 \text{ A}$$


$$i_L(\infty) = 0 \text{ A}$$

$$v_C(0) = 24 \text{ V}$$

$$v_C(\infty) = 0 \text{ V}$$

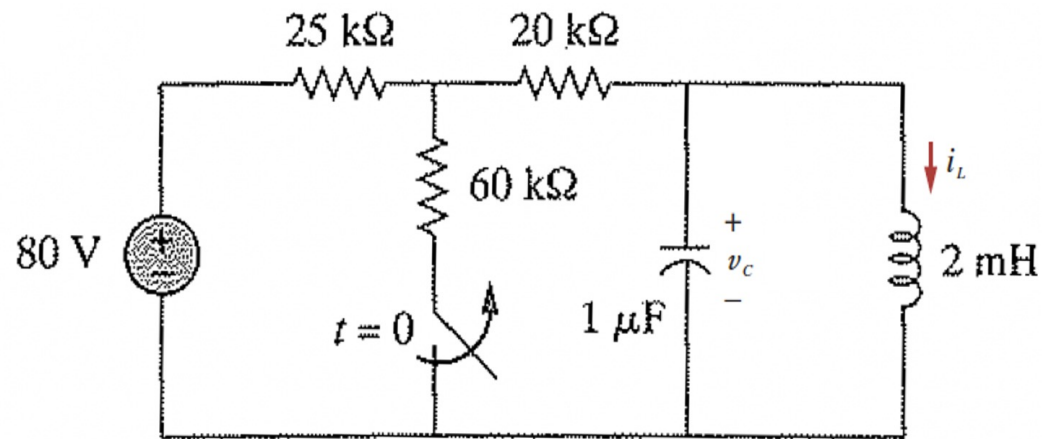**Practice problem:** Find the form of solution and the initial/final conditions



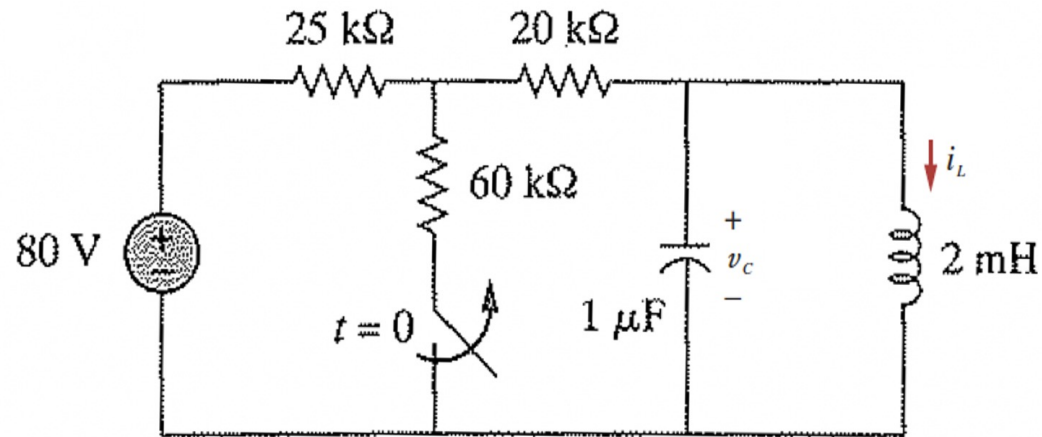

$$x(t) = B_1 e^{-11.1t} \cos 22361t + B_2 e^{-11.1t} \sin 22361t + x_\infty$$


$$i_L(0) = 1.5 \text{ A}$$

$$i_L(\infty) = \frac{16}{9} \text{ A}$$


$$v_C(0) = 0 \text{ V}$$

$$v_C(\infty) = 0 \text{ V}$$

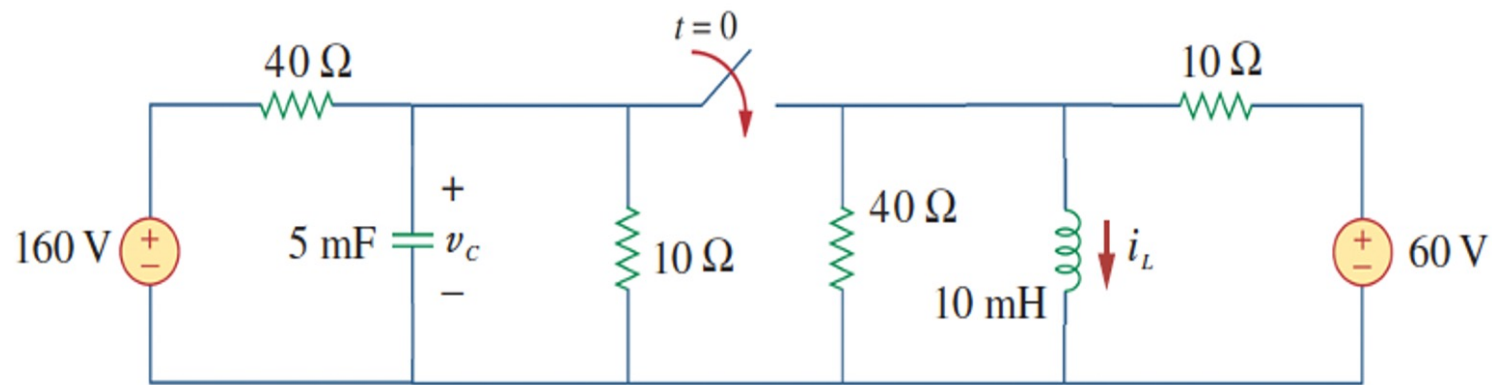**Practice problem:** Find the form of solution and the initial/final conditions





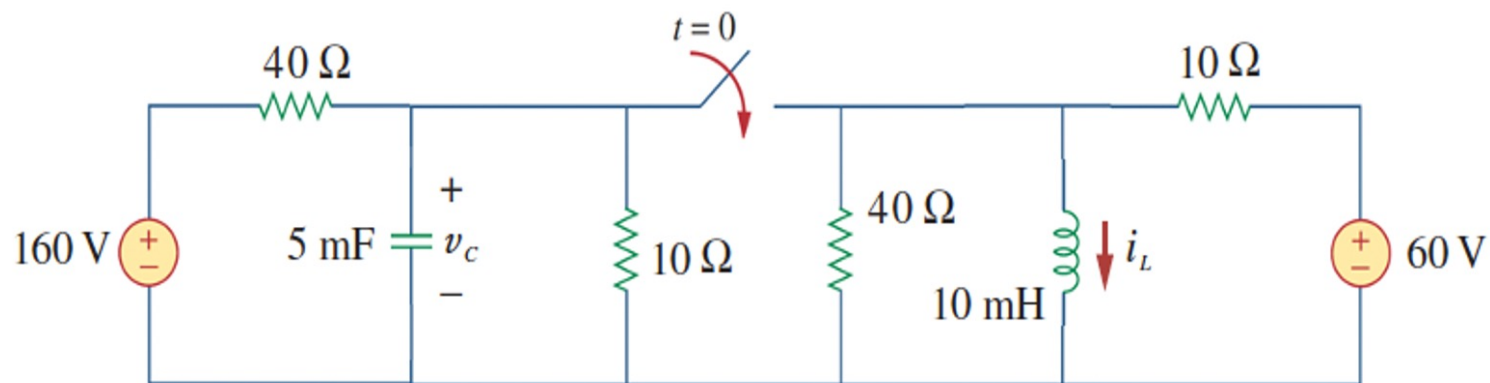

$$x(t) = B_1 e^{-25t} \cos 139t + B_2 e^{-25t} \sin 139t + x_\infty$$

$$i_L(0) = 6\text{ A}$$

$$i_L(\infty) = 10\text{ A}$$

$$v_c(0) = 32\text{ V}$$

$$v_c(\infty) = 0\text{ V}$$