


Lecture 14

Node Analysis – 7 of 7

op amp circuit analysis
(an example of circuit approximation)


Op Amps

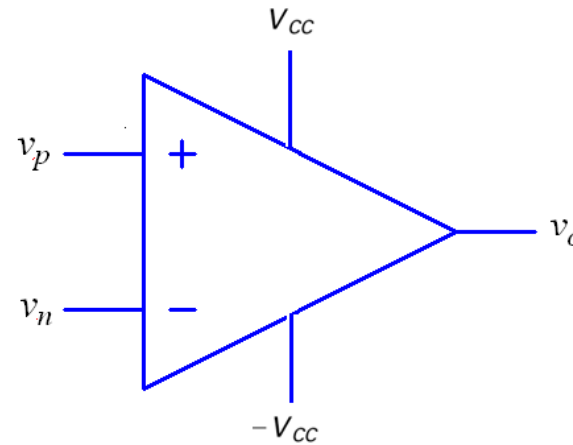- A 3-terminal device
 - Inverting input v_n
 - Non-inverting input v_p
 - Output v_o




- Is a powered device, not unlike gates in ELE 201/202

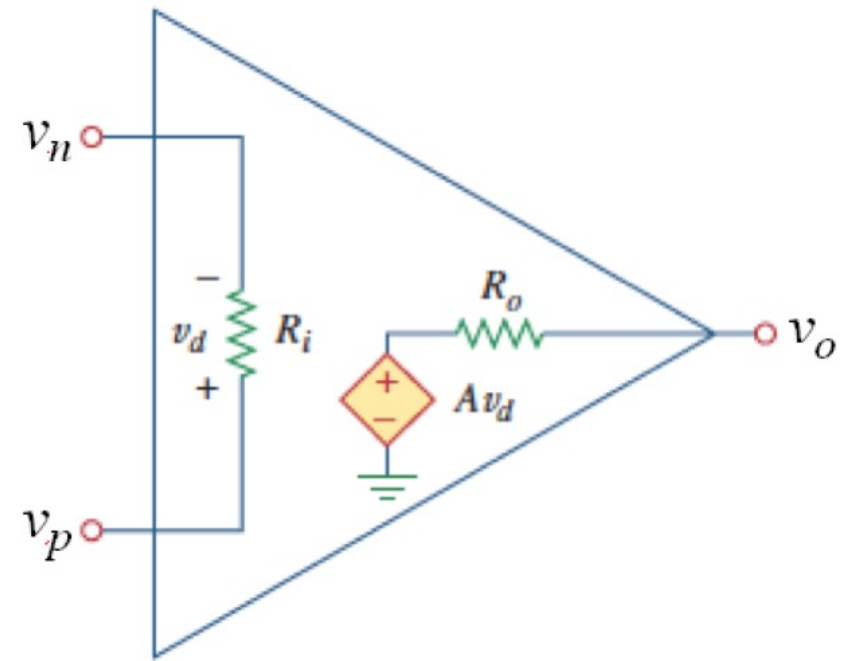- Nominally behaves like a voltage dependent voltage source:




- Control voltage is $v_d = v_p - v_n$
- “Open loop” gain A is large
- Two resistors:
 - “Input resistance” R_i is large
 - “Output resistance” R_o is small


- Experiences open loop “saturation”

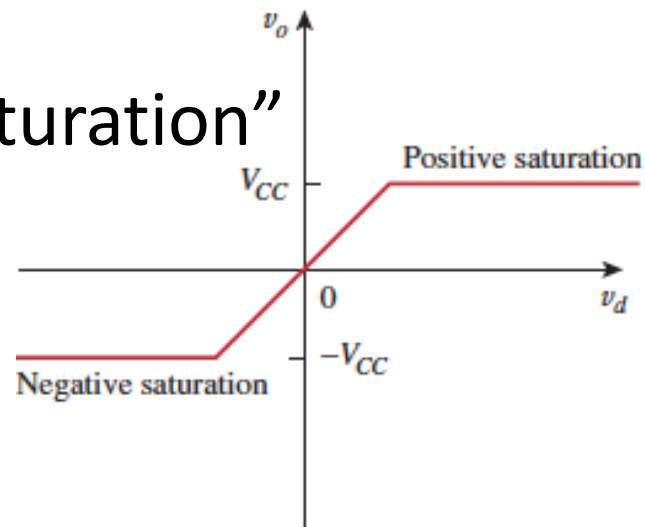

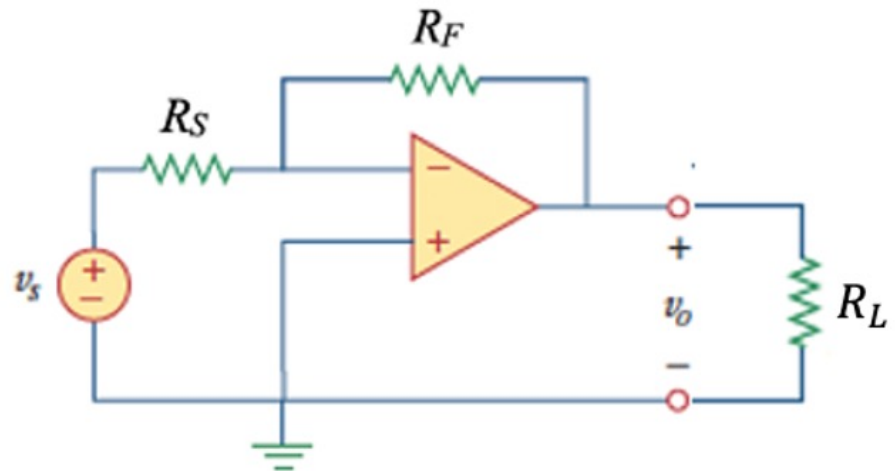
- Usually configured with “negative feedback”




Sample Analysis

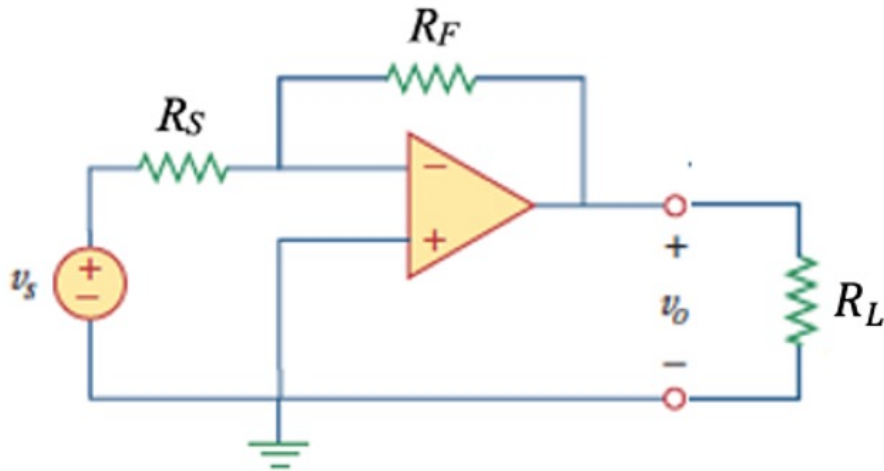

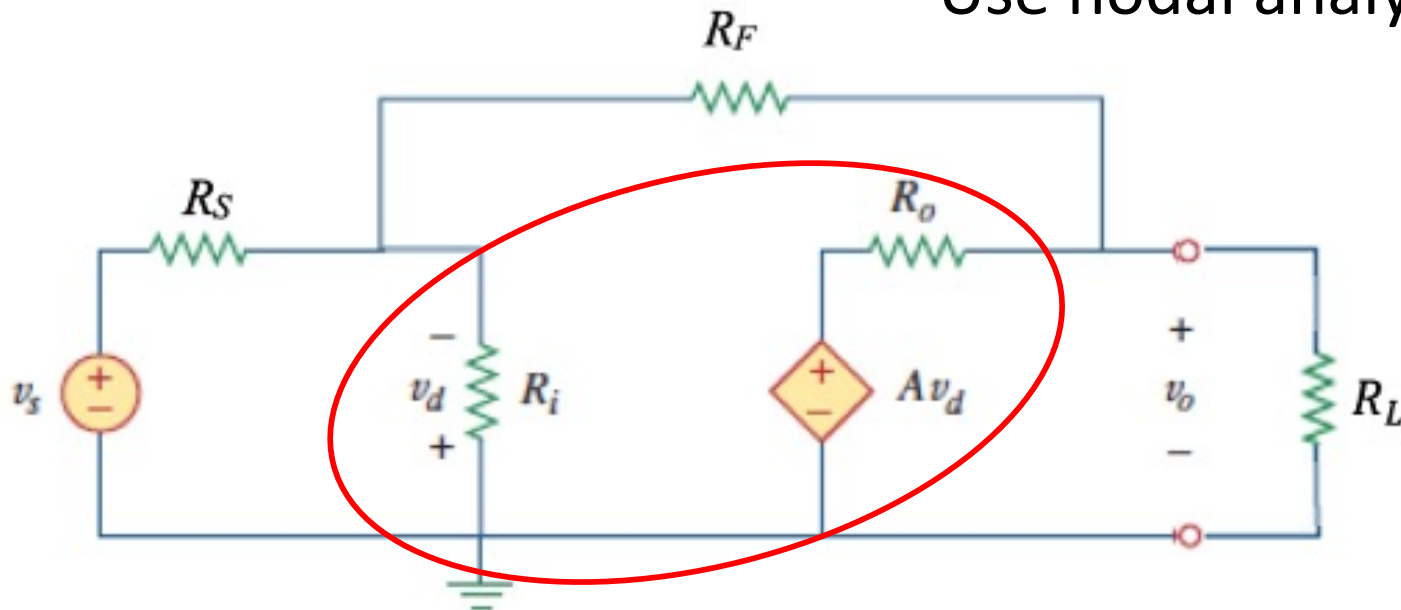- Circuit with “source”, “feedback”, and “load” resistors
- Substitute the simple model for the op amp
- Use nodal analysis




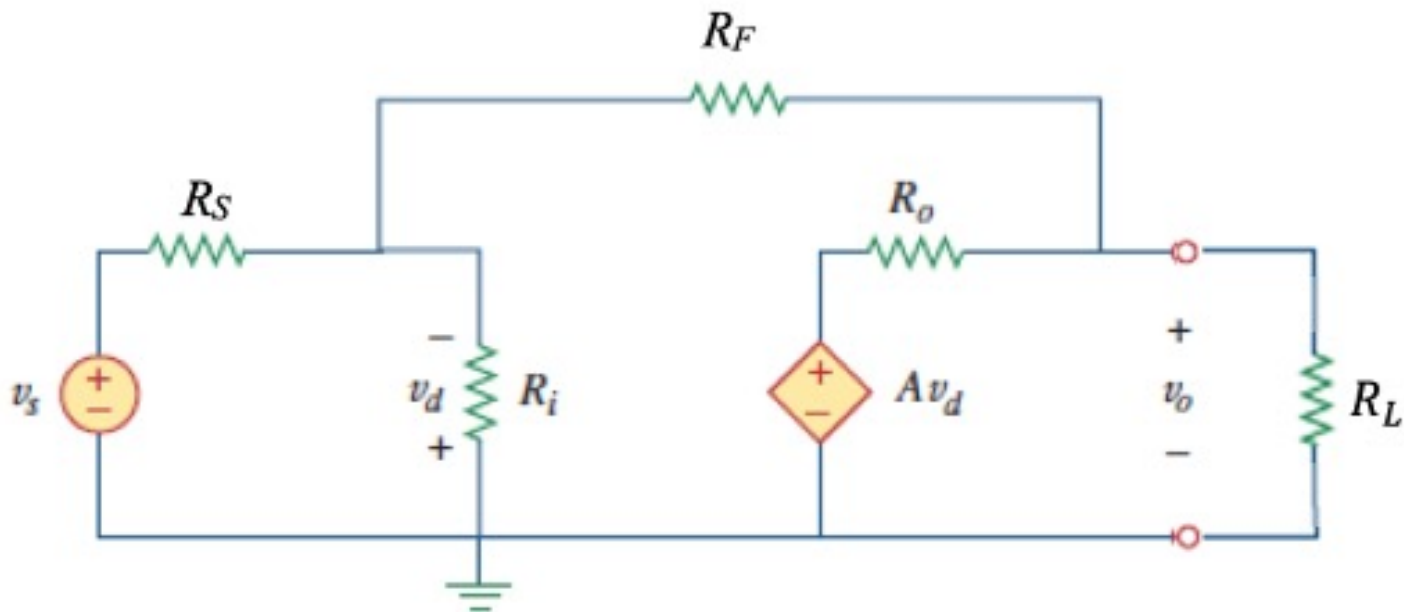

- **Nodes:** ground, v_o , and $v_1 = -v_d$

$$\frac{v_1}{R_i} + \frac{v_1 - v_s}{R_s} + \frac{v_1 - v_o}{R_F} = 0$$

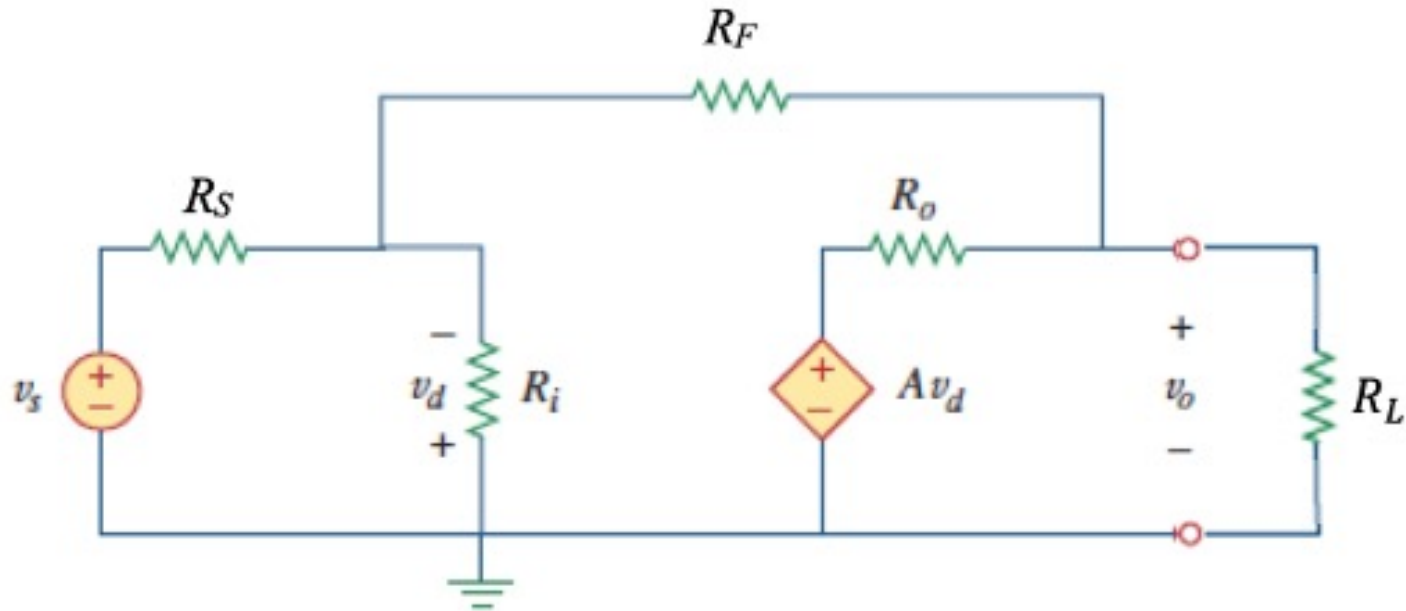
$$\frac{v_o + Av_1}{R_o} + \frac{v_o - v_1}{R_F} + \frac{v_o}{R_L} = 0$$



- After some tedious, symbolic algebra:

$$v_o = - \frac{R_i R_L (R_F A - R_o)}{R_L (R_S + R_i) (R_F + R_o) + (A + 1) R_S R_i R_L + R_o (R_S R_i + R_F R_i + R_S R_F)} v_s$$

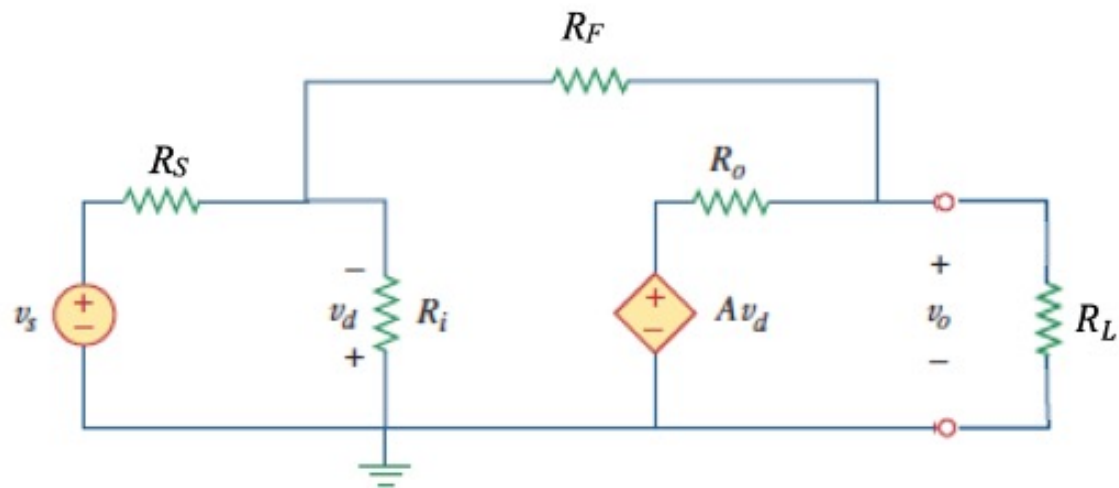- Note linearity, gain term is negative (“inverting amplifier”)




- External components:
 - $R_S = 10 \text{ k}\Omega$
 - $R_F = 20 \text{ k}\Omega$
 - $R_L = 40 \text{ k}\Omega$
- Nominal model parameters:
 - $R_i = 2 \text{ M}\Omega$
 - $R_o = 50 \Omega$
 - $A = 200,000$

$$v_o = -1.99997 v_s = -2.00 v_s$$

Sensitivity Analysis

For $R_S = 10\text{ k}\Omega$,
 $R_F = 20\text{ k}\Omega$, and
 $R_L = 40\text{ k}\Omega$

we have $\mathbf{v_o = -2.00 v_s}$

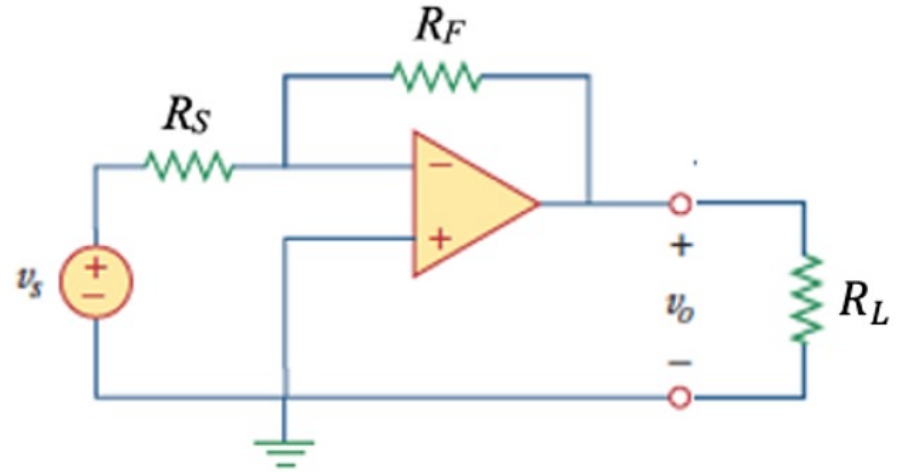

- How do the op amp's internal parameters (R_i , R_o , and A) impact this result?
- What happens when we change the circuit's components (R_S , R_F , and R_L)?

Sensitivity to internal values:

R_S	R_F	R_L	R_i	R_o	A	gain
10 k Ω	20 k Ω	40 k Ω	2 M Ω	50 Ω	200,000	-1.99997
10 k Ω	20 k Ω	40 k Ω	1 MΩ	50 Ω	200,000	-1.99997
10 k Ω	20 k Ω	40 k Ω	4 MΩ	50 Ω	200,000	-1.99997
10 k Ω	20 k Ω	40 k Ω	2 M Ω	25 Ω	200,000	-1.99997
10 k Ω	20 k Ω	40 k Ω	2 M Ω	100 Ω	200,000	-1.99997
10 k Ω	20 k Ω	40 k Ω	2 M Ω	50 Ω	100,000	-1.99994
10 k Ω	20 k Ω	40 k Ω	2 M Ω	50 Ω	400,000	-1.99998
10 k Ω	20 k Ω	40 k Ω	2 M Ω	50 Ω	50,000	-1.99988
10 k Ω	20 k Ω	40 k Ω	2 M Ω	50 Ω	20,000	-1.99970


Seems insensitive!

Sensitivity to circuit component values:

R_S	R_F	R_L	R_i	R_o	A	gain
10 k Ω	20 k Ω	40 k Ω	2 M Ω	50 Ω	200,000	-1.99997
10 k Ω	20 k Ω	20 kΩ	2 M Ω	50 Ω	200,000	-1.99997
10 k Ω	20 k Ω	80 kΩ	2 M Ω	50 Ω	200,000	-1.99997
10 k Ω	10 kΩ	40 k Ω	2 M Ω	50 Ω	200,000	-0.99999
10 k Ω	40 kΩ	40 k Ω	2 M Ω	50 Ω	200,000	-3.99990
10 k Ω	100 kΩ	40 k Ω	2 M Ω	50 Ω	200,000	-9.99945
5 kΩ	20 k Ω	40 k Ω	2 M Ω	50 Ω	200,000	-3.99990
20 kΩ	20 k Ω	40 k Ω	2 M Ω	50 Ω	200,000	-0.99999
40 kΩ	20 k Ω	40 k Ω	2 M Ω	50 Ω	200,000	-0.499996

Only depends upon source and feedback resistors!

Asymptotics

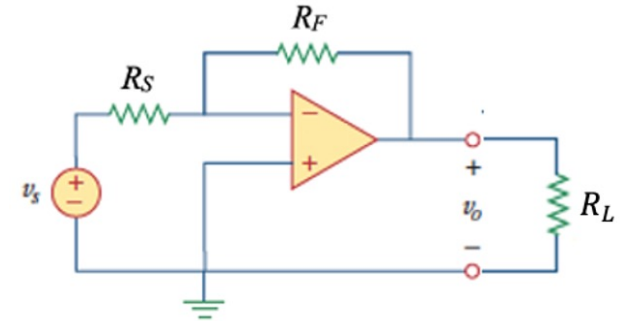


- Consider the gain term when A is large, R_i is large, and R_o is small

$$\frac{v_o}{v_s}$$

$$= - \frac{R_i R_L (R_F A - R_o)}{R_L (R_S + R_i) (R_F + R_o) + (A + 1) R_S R_i R_L + R_o (R_S R_i + R_F R_i + R_S R_F)}$$

$$\approx - \frac{R_i R_L R_F A}{R_L R_i R_F + A R_S R_i R_L + R_o R_S R_i + R_o R_F R_i}$$
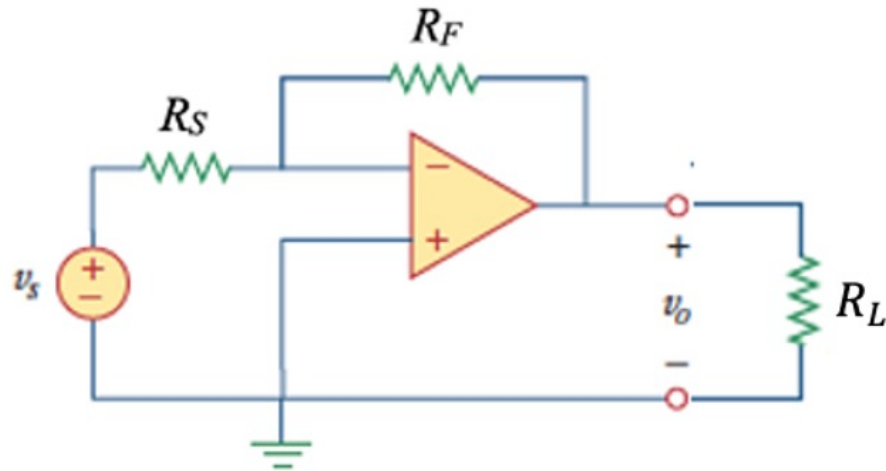
$$\approx - \frac{R_L R_F A}{R_L R_F + A R_S R_L + R_o R_S + R_o R_F} \approx - \frac{R_F}{R_S}$$



- So:

$$\frac{v_o}{v_s} \approx -\frac{R_F}{R_S}$$

- Similarly :

$$\frac{v_d}{v_s} \approx 0 \qquad \frac{i_d}{v_s} \approx 0$$

More general model:


- $v_d \approx 0$
 - we have a “virtual short” across the inputs

$$v_p = v_n$$


- $i_d \approx 0$
 - the inputs are open circuits

$$i_p = i_n = 0$$

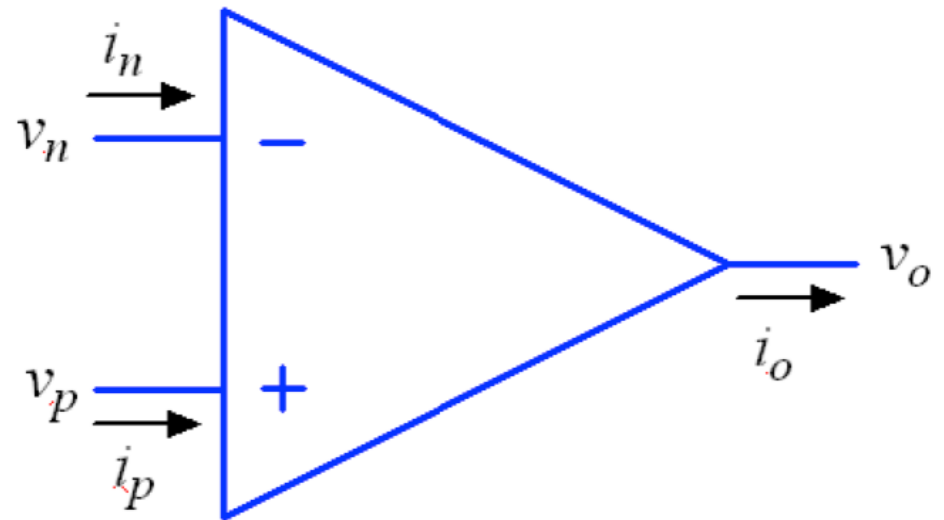- And $i_o = ?$
 - The device generates whatever current is needed




Using the Simple Model

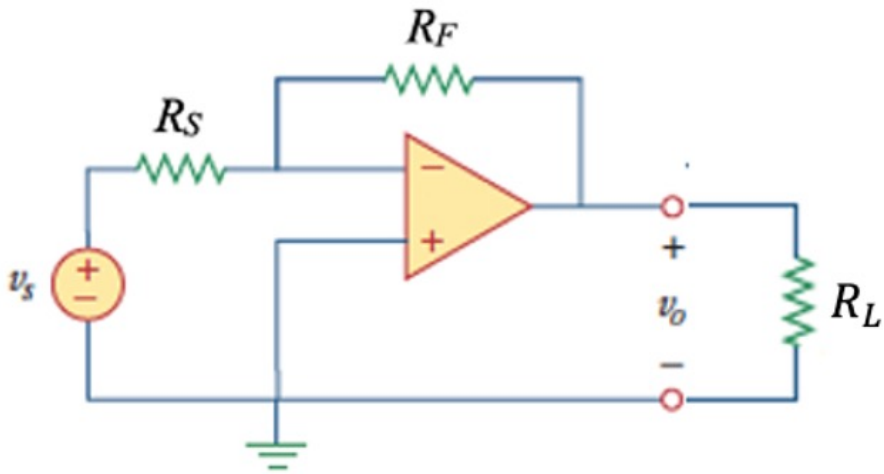

Input voltages equal
Input currents zero

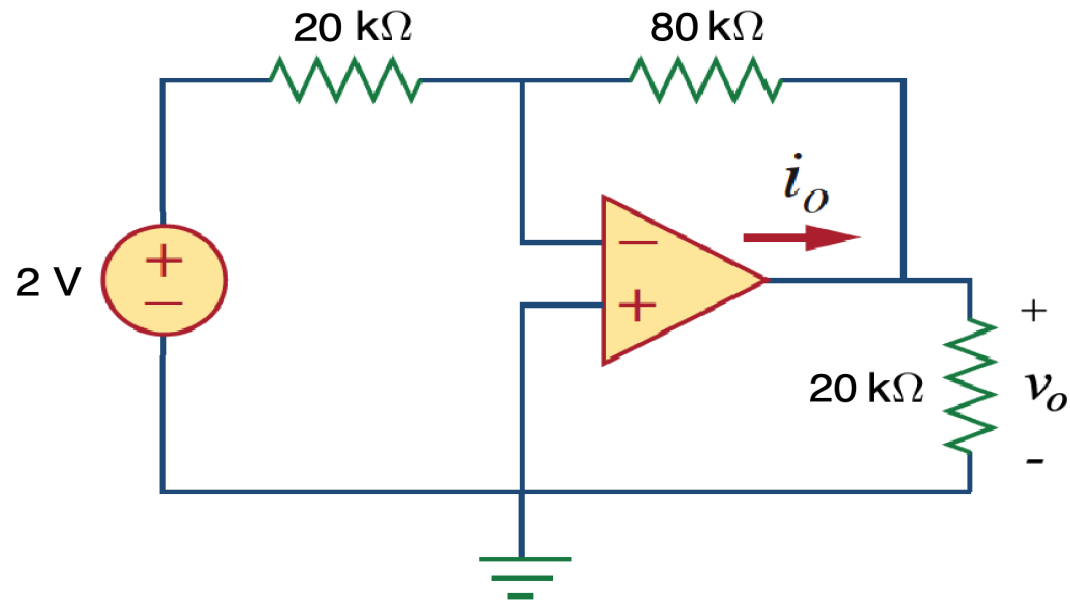Example: find v_o and i_o


$$v_o = -8\text{ V}, i_o = -0.5\text{ mA}$$



Input voltages equal
Input currents zero


Example: find v_o

$$v_o = -14\text{ V}$$

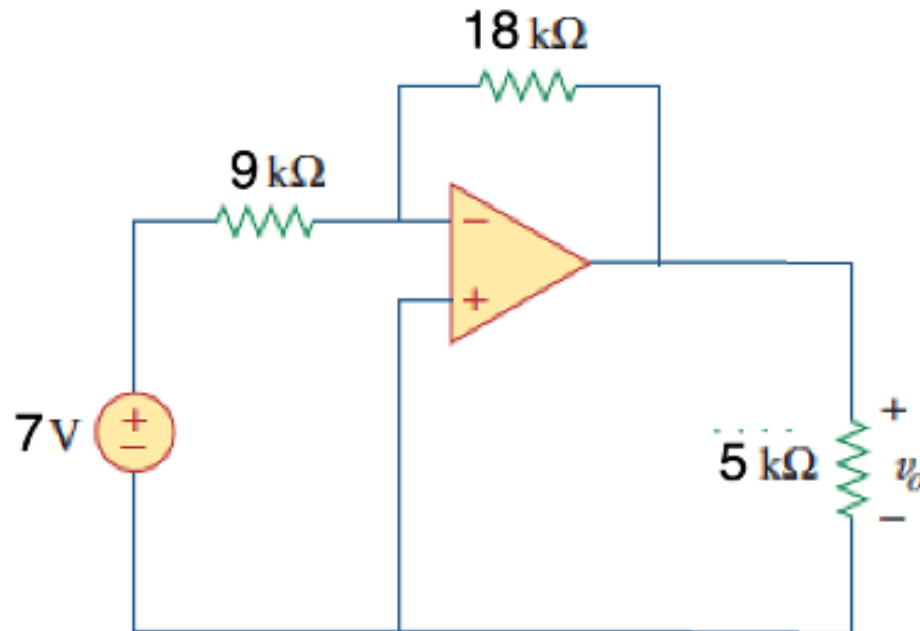


Other Op Amp Uses

- Inverting amplifier

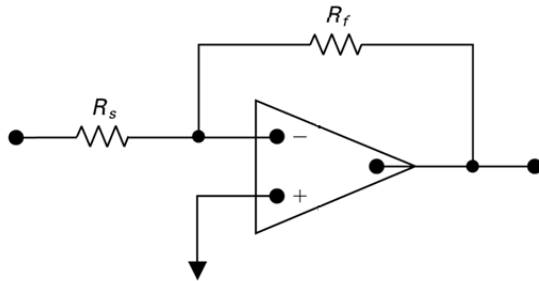


$$v_o = -\frac{R_F}{R_S} v_s$$

- Non-inverting amplifier

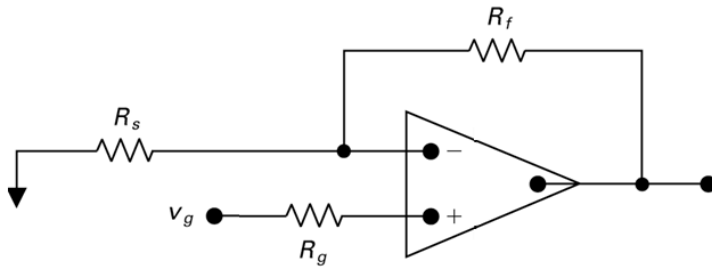


$$v_o = \left(1 + \frac{R_F}{R_1}\right) v_s$$

- Difference amplifier

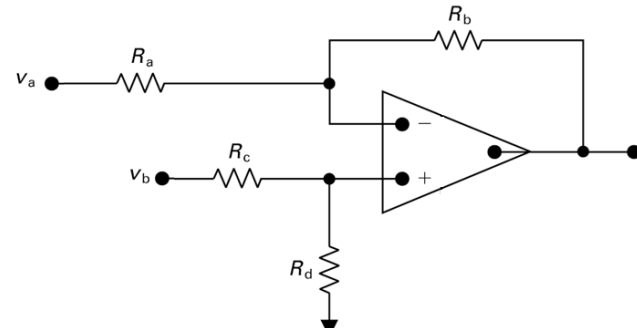

$$v_o = \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) v_2 - \frac{R_2}{R_1} v_1$$

- Summing amplifier

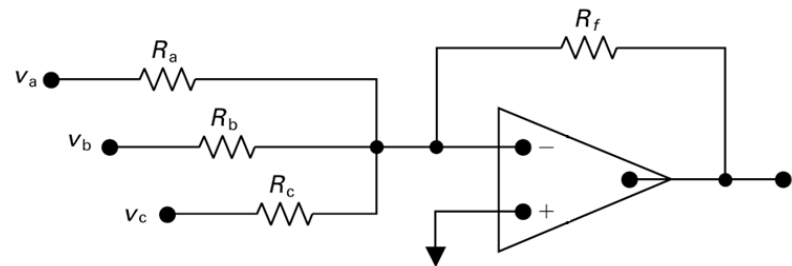

$$v_o = -\left(\frac{R_F}{R_1} v_1 + \frac{R_F}{R_2} v_2 + \frac{R_F}{R_3} v_3\right)$$

$$i = -0.51 \text{ mA}$$

Practice problem: find i

