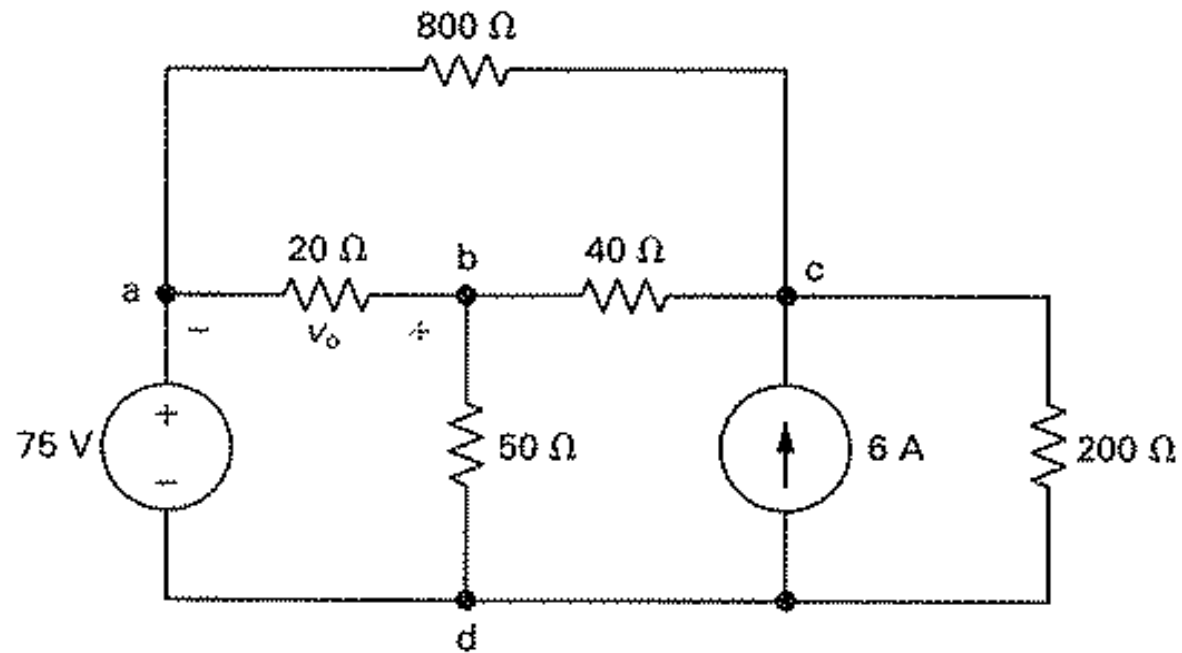



Lecture 13

Node Analysis – 6 of 7

examples


Example: find v_o




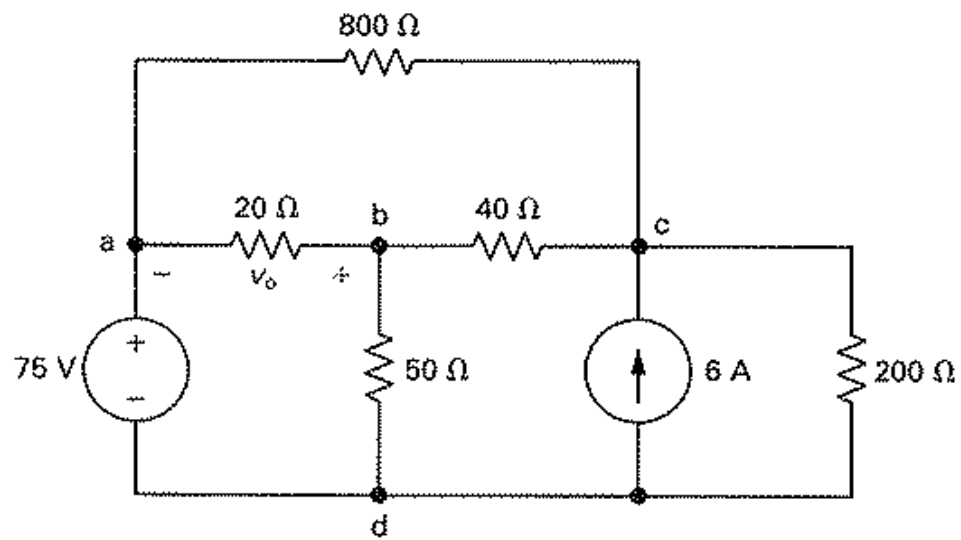

$$v_o = 40\text{ V}$$


Example: find i_0

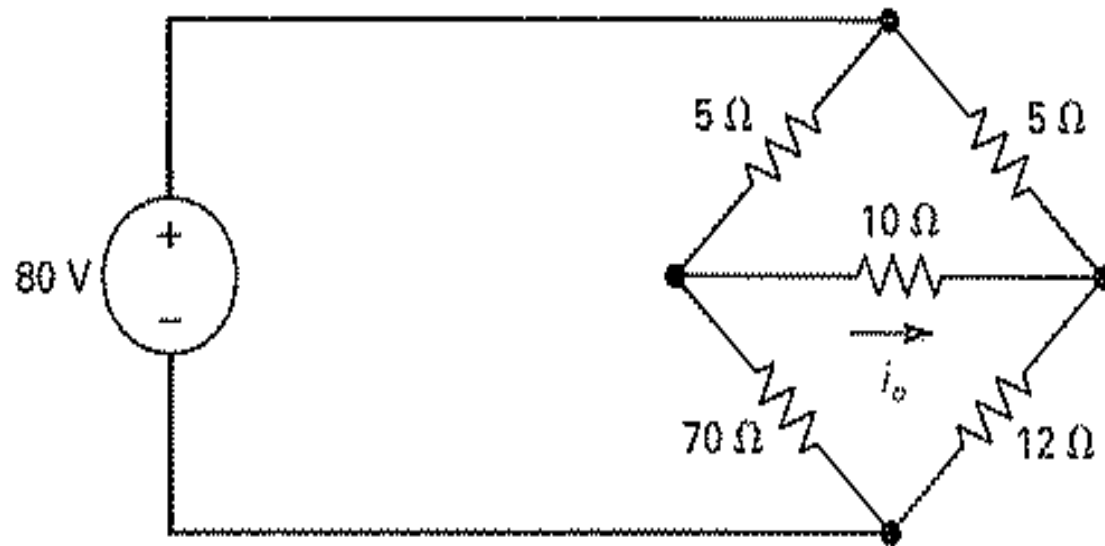


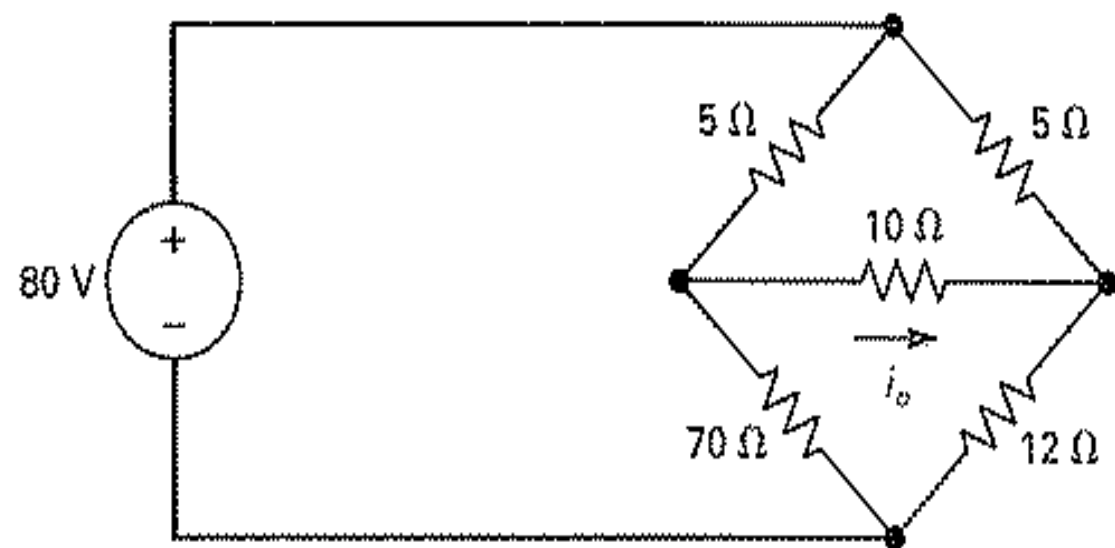

$$i_o = 1 \text{ A}$$

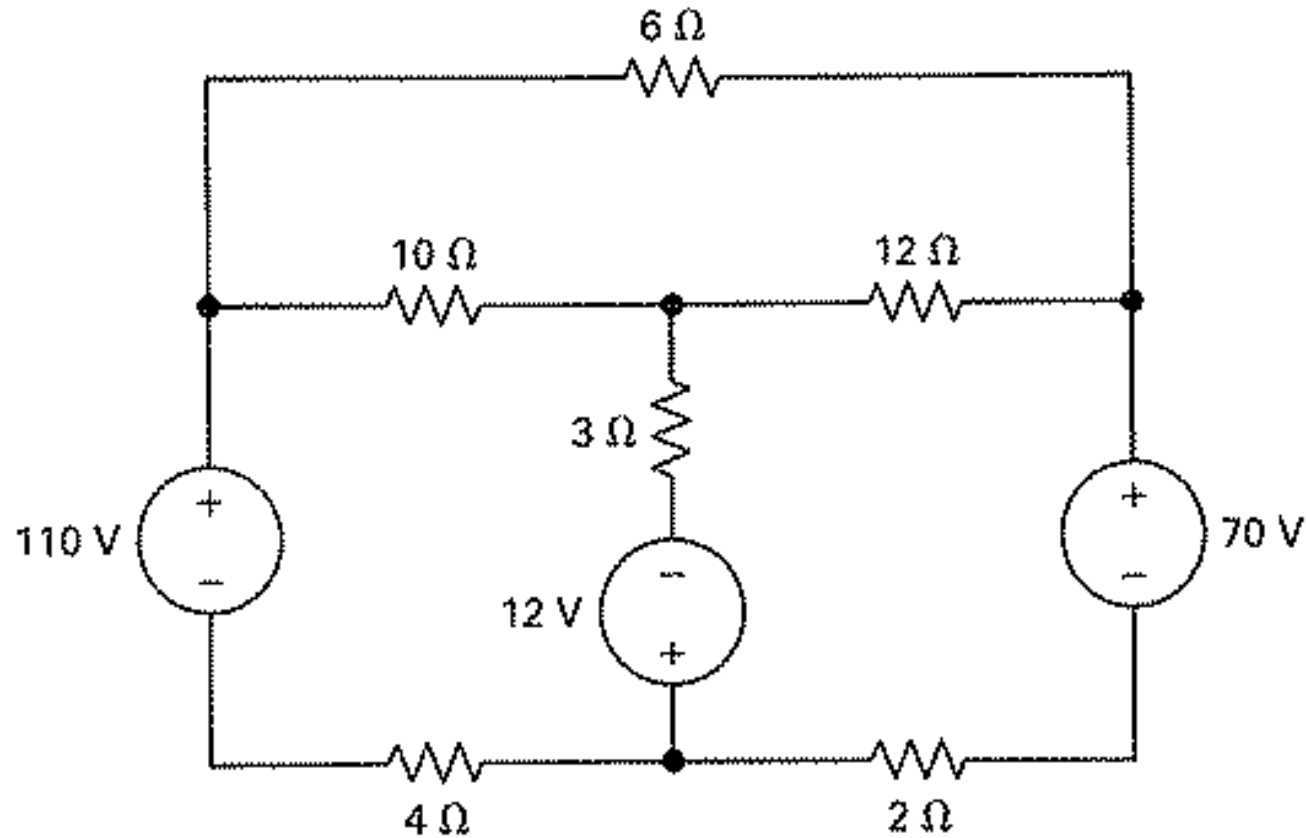
Example: find the power of the $10\ \Omega$ resistor




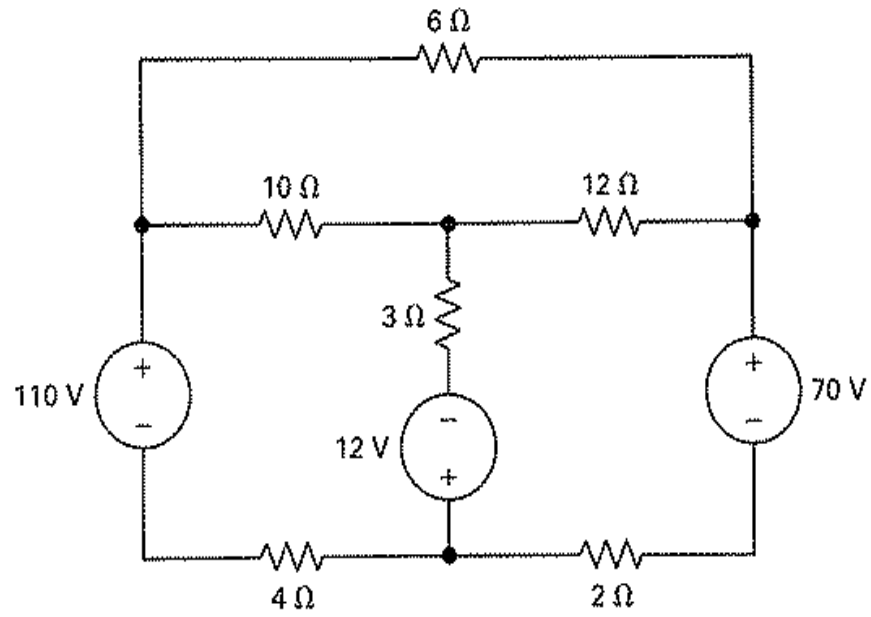

$$P = 360 \text{ W}$$


Example: find v

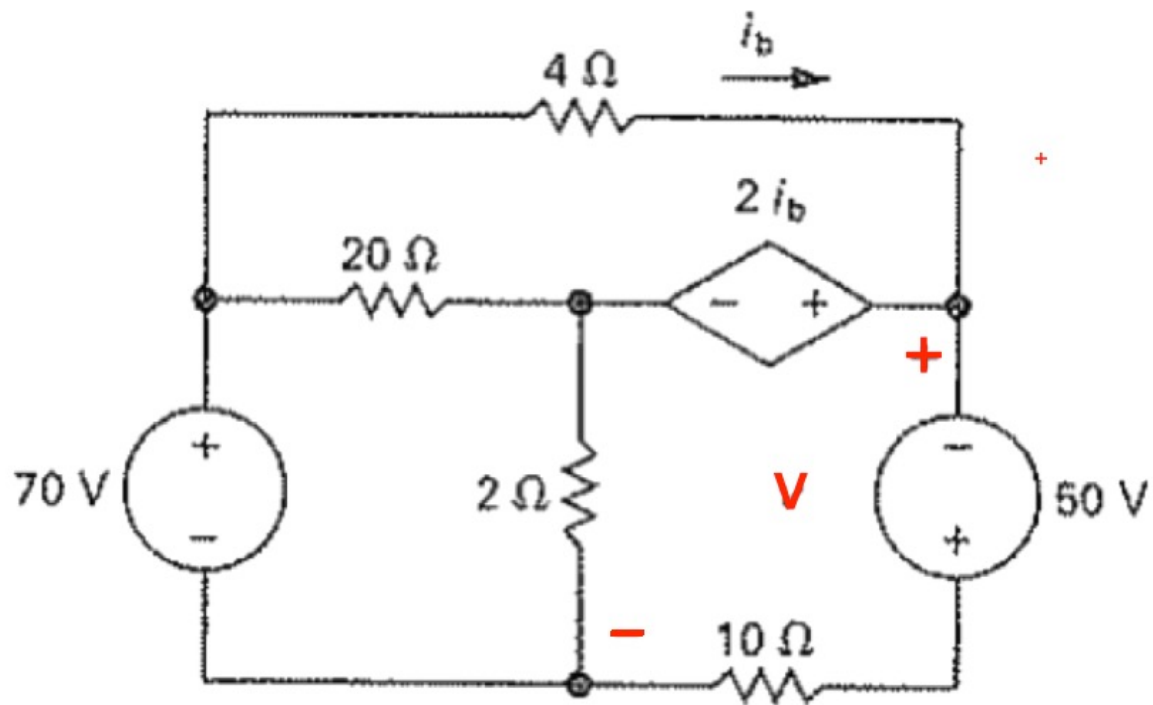


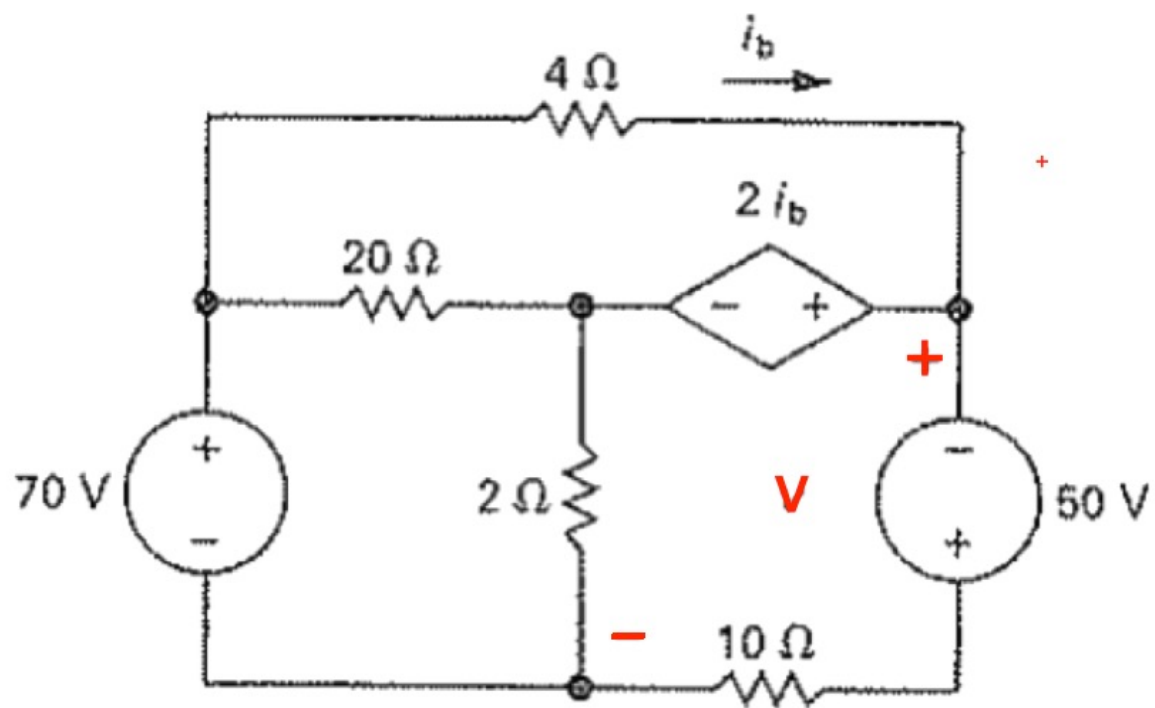

$$v = 30\text{ V}$$

Example:

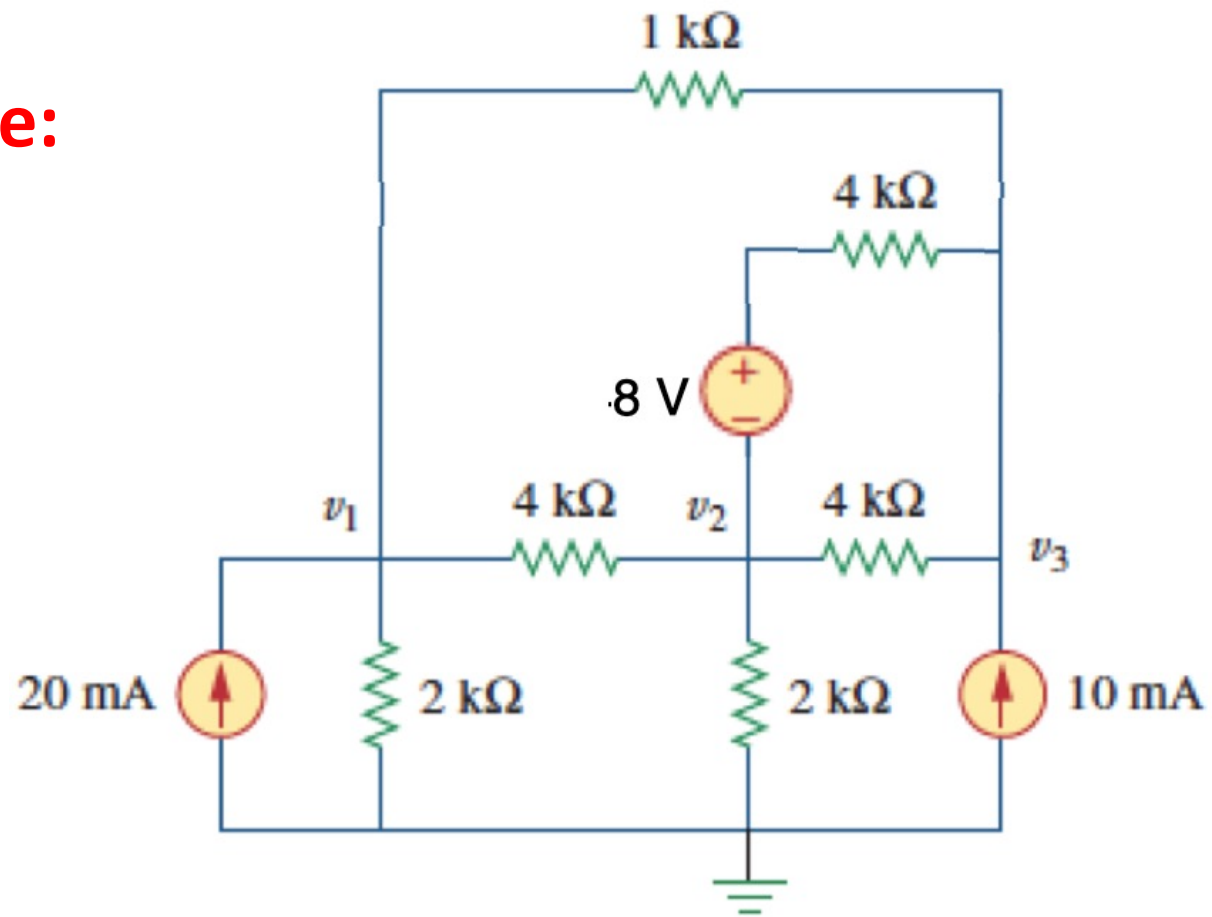

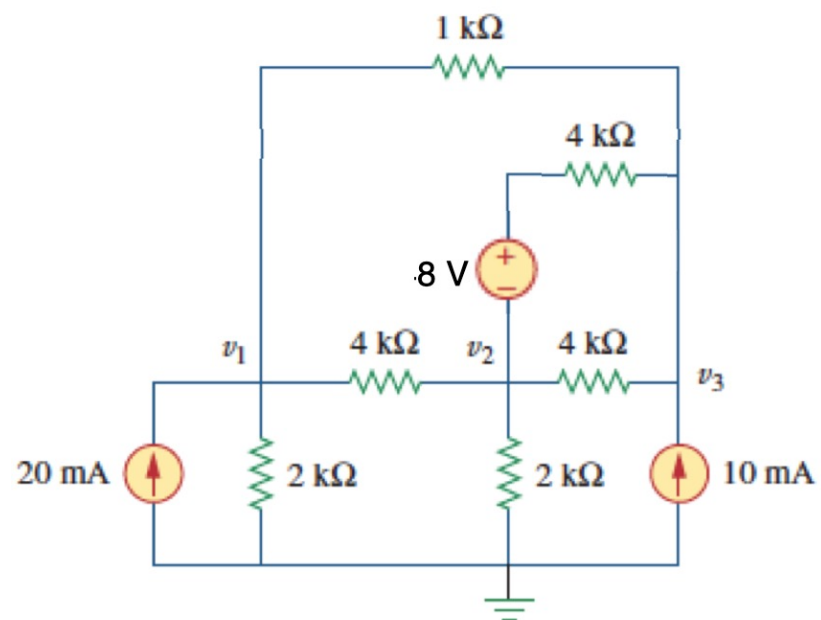


$$v_1 = 37.8\text{ V}$$

$$v_2 = 22.2\text{ V}$$

$$v_3 = 40.6\text{ V}$$


60 W

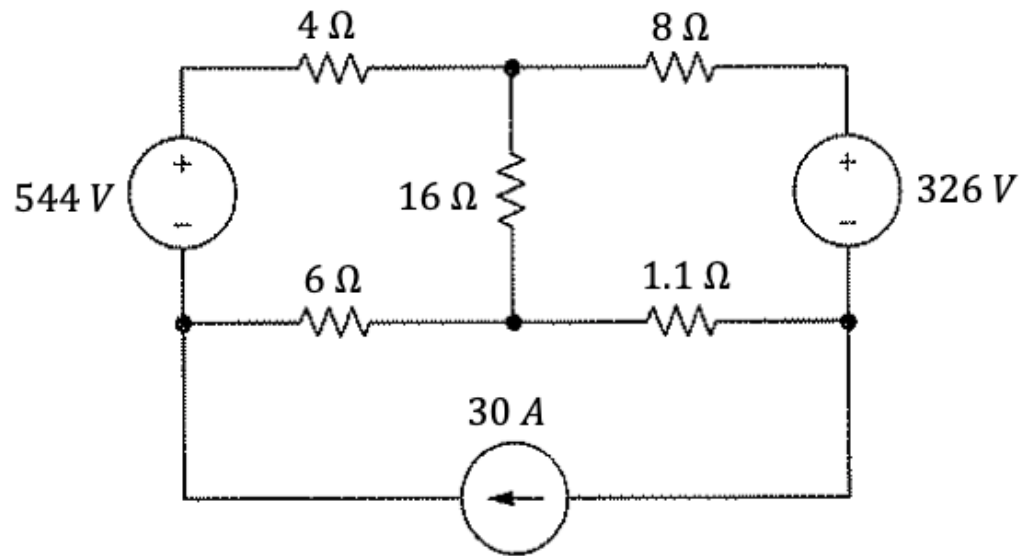Practice problem: find the power of the current source



Practice problem: find i_0 and i_1
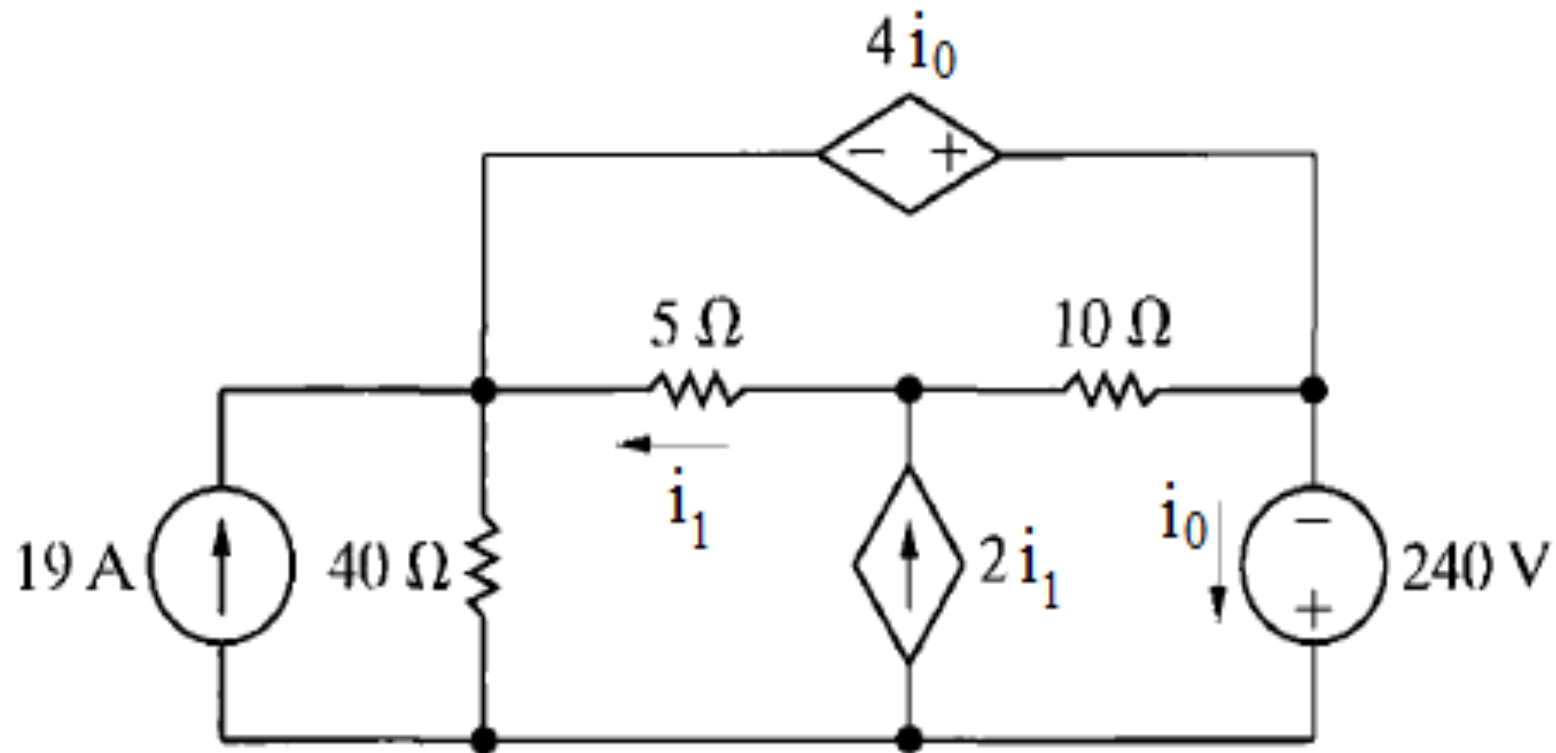
$$i_0 = 10 \text{ A}$$
$$i_1 = -8 \text{ A}$$



Practice problem: The variable voltage source shown in the circuit below (the source with the diagonal line through it) is adjusted so that the power absorbed by the $5\ \Omega$ resistor is 5 watts. Find the value of v_{DC} .

