


Lecture 9

Node Analysis – 2 of 7

more complex branches


Extension #2 – V + R branches


- Consider:

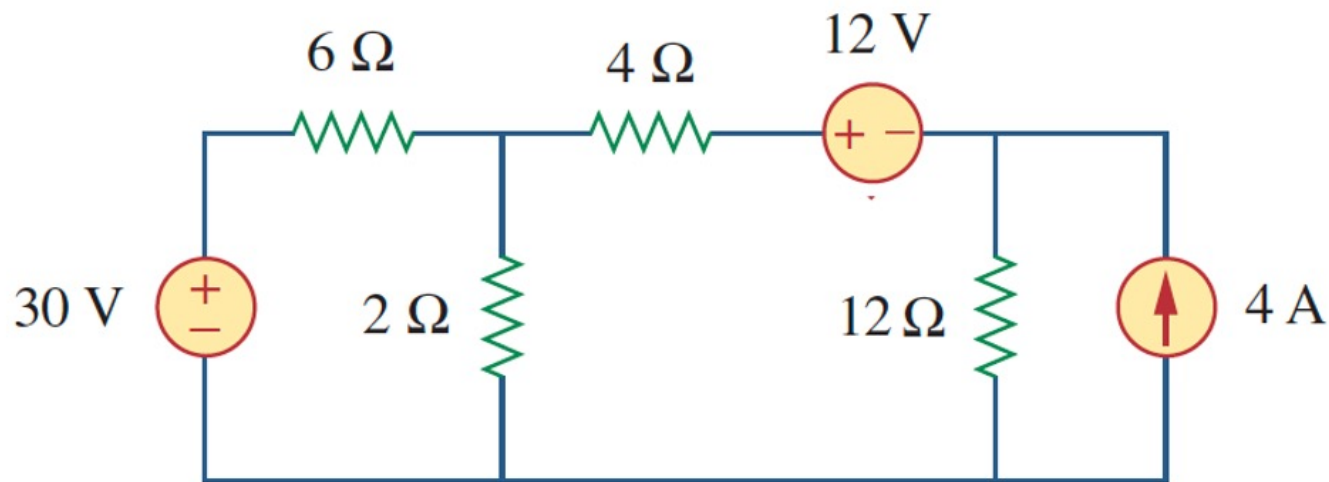

- Solution: Modify the Ohm's Law expression(s) for the individual branch current(s)

Example (solved on next slide)

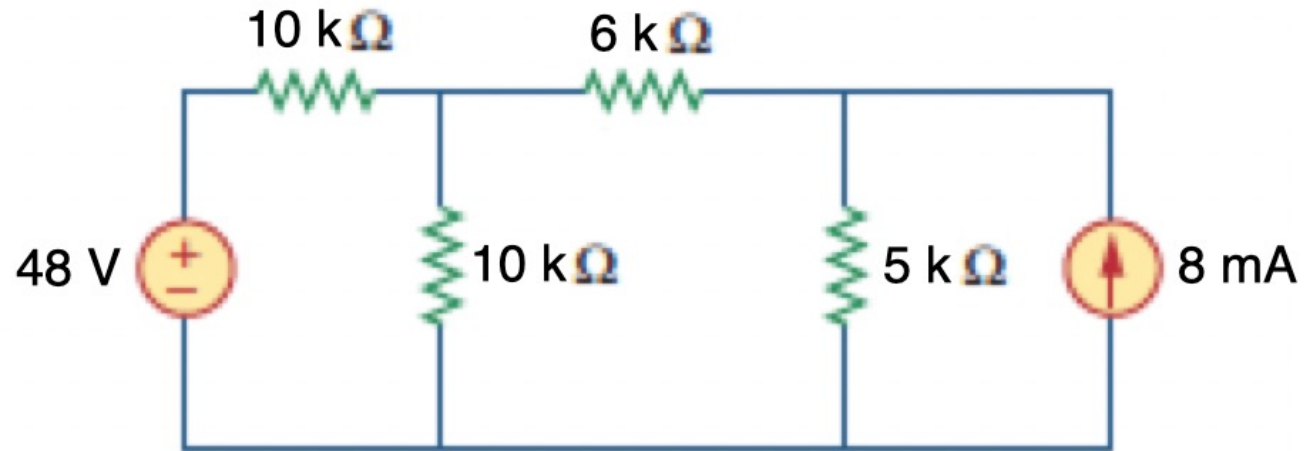

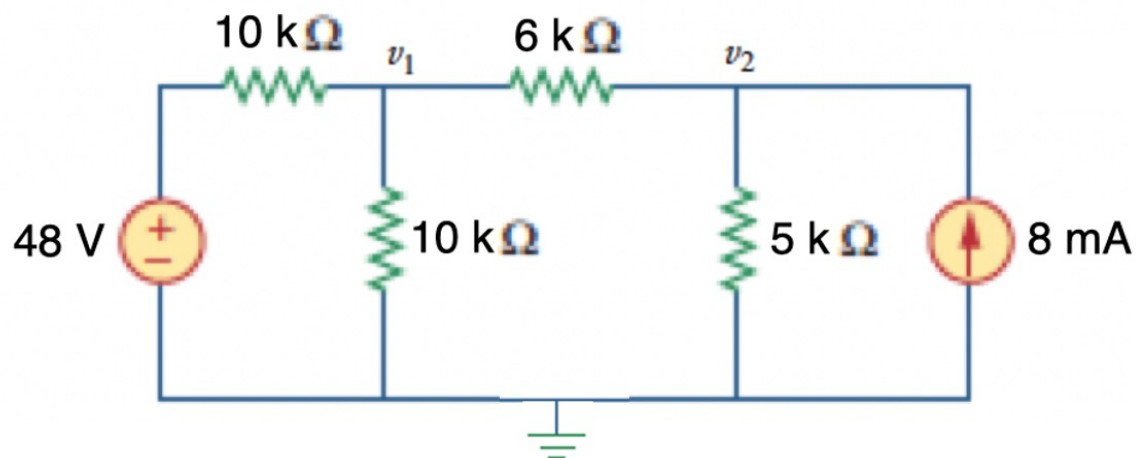


$$\frac{v_1}{10k} + \frac{v_1 - 48}{10k} + \frac{v_1 - v_2}{6k} = 0$$


$$\frac{v_2}{5k} + \frac{v_2 - v_1}{6k} - .008 = 0$$

$$\begin{aligned} 3v_1 + 3v_1 + 5v_1 - 5v_2 &= 144 \\ 6v_2 + 5v_2 - 5v_1 &= 240 \end{aligned}$$

$$\begin{aligned} 11v_1 - 5v_2 &= 288 \\ -5v_1 + 11v_2 &= 240 \end{aligned} \Rightarrow \begin{aligned} v_1 &= 29 \text{ V} \\ v_2 &= 35 \text{ V} \end{aligned}$$

Example

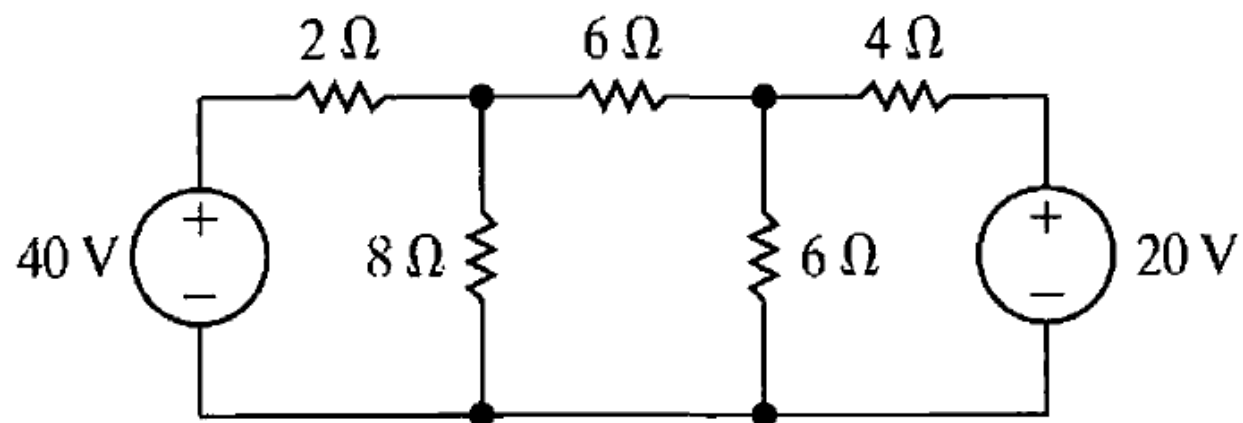

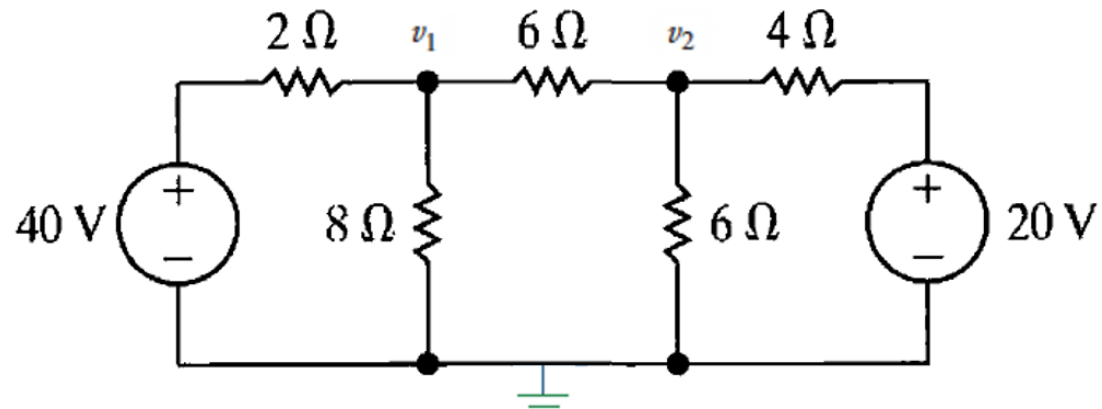

$$\frac{v_1}{8} + \frac{v_1 - 40}{2} + \frac{v_1 - v_2}{6} = 0$$

$$\frac{v_2}{6} + \frac{v_2 - v_1}{6} + \frac{v_2 - 20}{4} = 0$$


$$3v_1 + 12v_1 + 4v_1 - 4v_2 = 480$$


$$2v_2 + 2v_2 - 2v_1 + 3v_2 = 60$$

$$17v_1 - 4v_2 = 480 \Rightarrow v_1 = 27.5 \text{ V}$$

$$-2v_1 + 7v_2 = 60 \Rightarrow v_2 = 10.4 \text{ V}$$

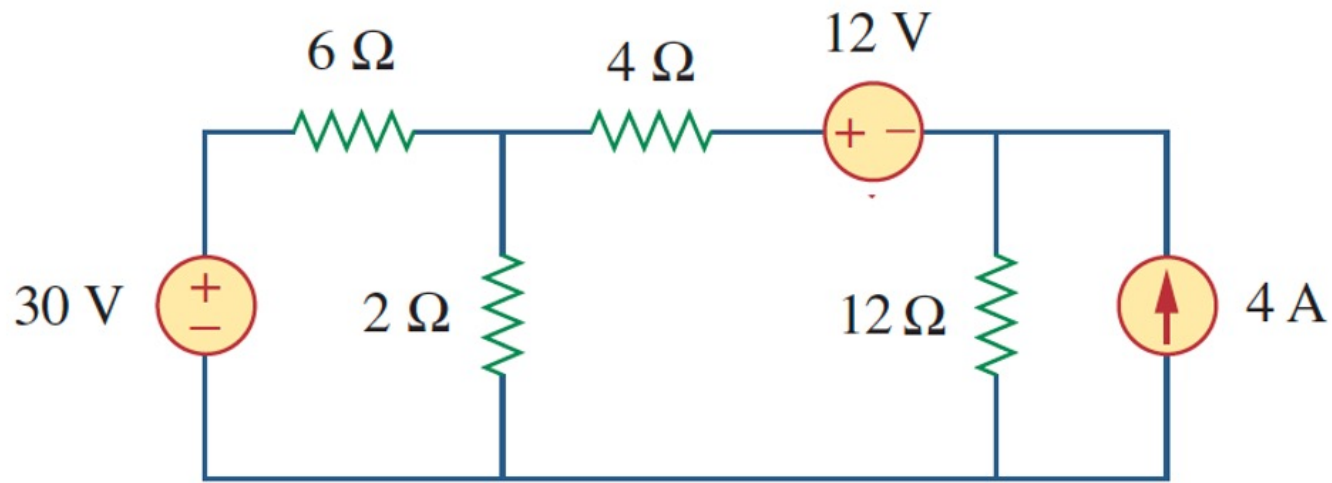Example: find the power of the current source



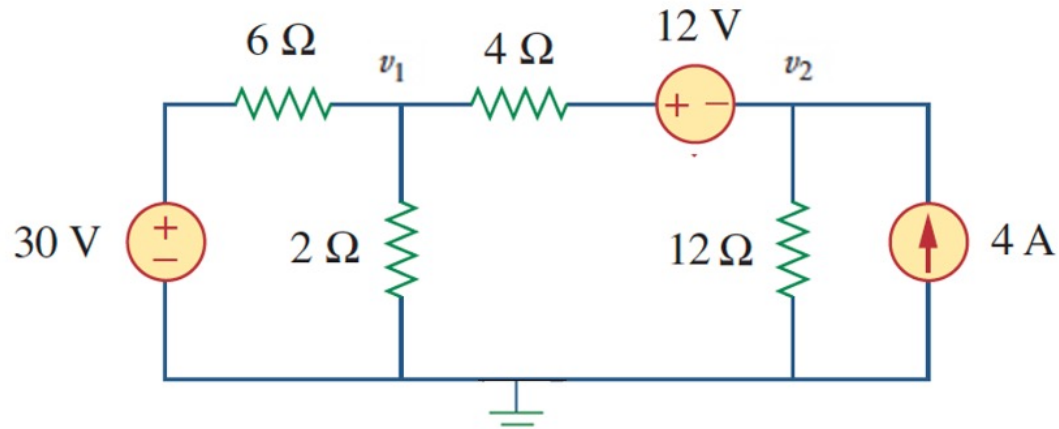

$$\frac{v_1}{2} + \frac{v_1 - 30}{6} + \frac{v_1 - v_2 - 12}{4} = 0$$

$$\frac{v_2}{12} + \frac{v_2 + 12 - v_1}{4} + 4 = 0$$


$$P = (-4 \text{ A}) * (12 \text{ V}) = -48 \text{ W}$$

$$\begin{aligned} 6v_1 + 2v_1 + 3v_1 - 3v_2 &= 60 + 36 \\ v_2 + 3v_2 - 3v_1 &= -36 - 48 \end{aligned}$$

$$\begin{aligned} 11v_1 - 3v_2 &= 96 \\ -3v_1 + 4v_2 &= -84 \end{aligned} \Rightarrow \begin{aligned} v_1 &= 12 \text{ V} \\ v_2 &= 12 \text{ V} \end{aligned}$$


15 V

Example: find v

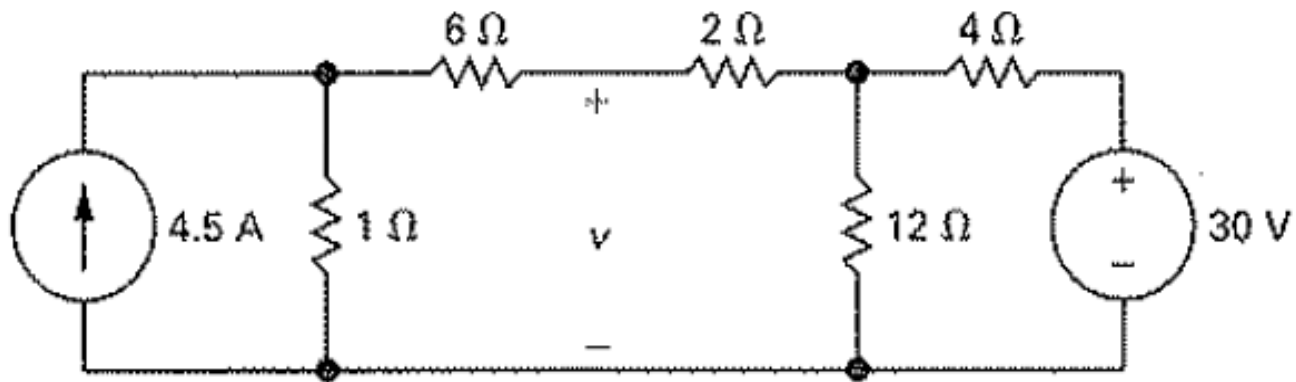


40 V

Practice problem: find V_o

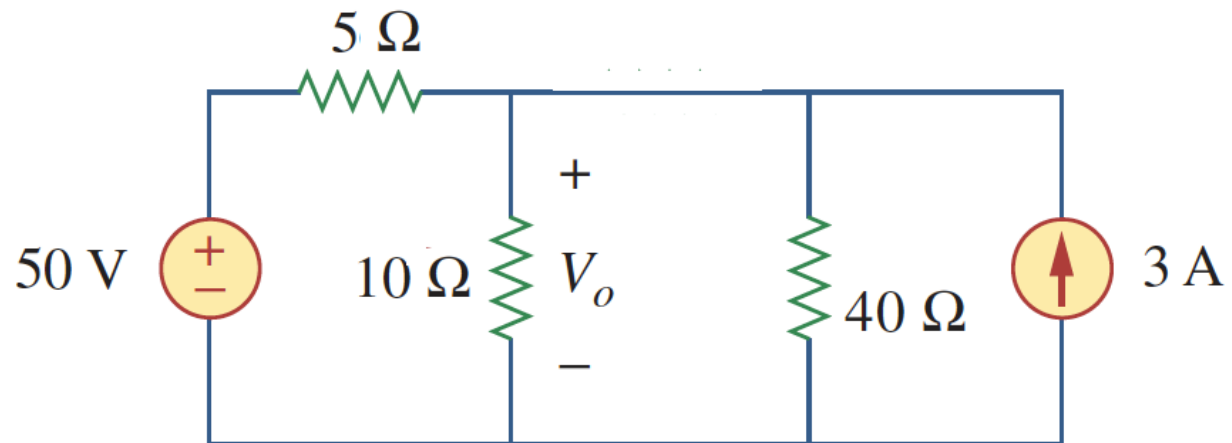

$$v_T = 40\text{ V}, v_M = 30\text{ V}$$

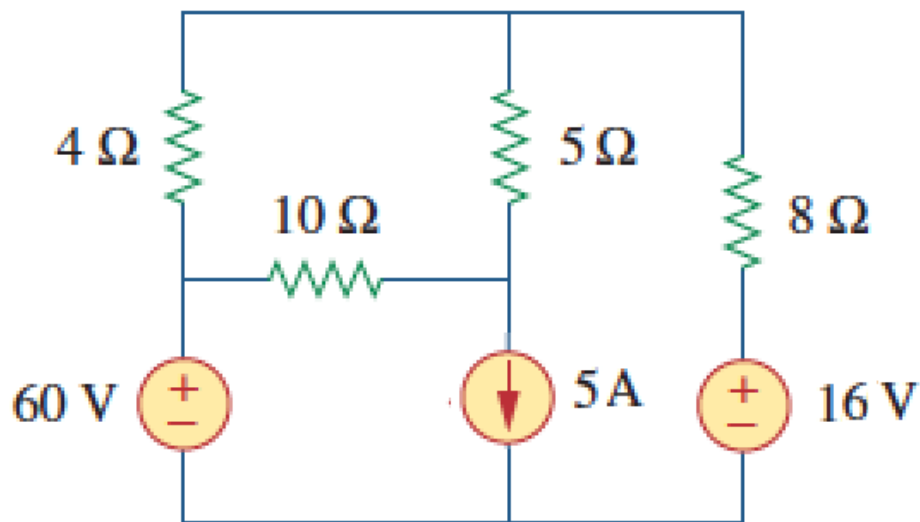Practice problem: find the node voltages to the top and bottom of the $5\ \Omega$ resistor relative to the bottom



-26 A

Practice problem: find i_o

