


Lecture 29


Theorems – 6 of 6

max power with phasors

Maximum AC Power

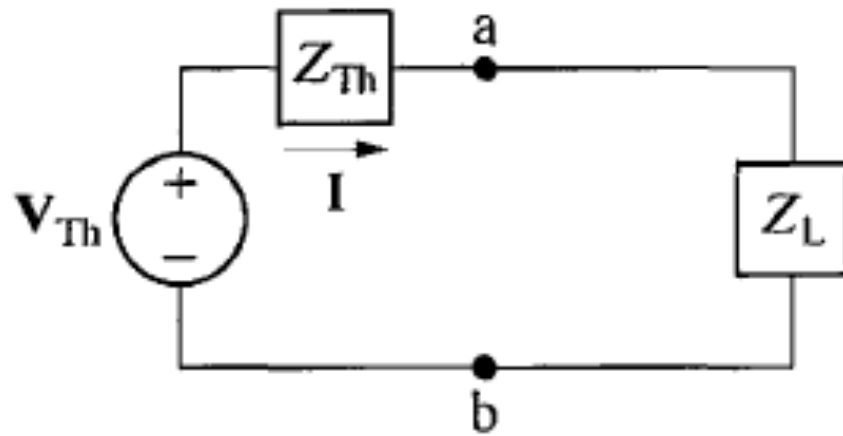- Given a phasor Thevenin model, how do we get maximum power to Z_L ?




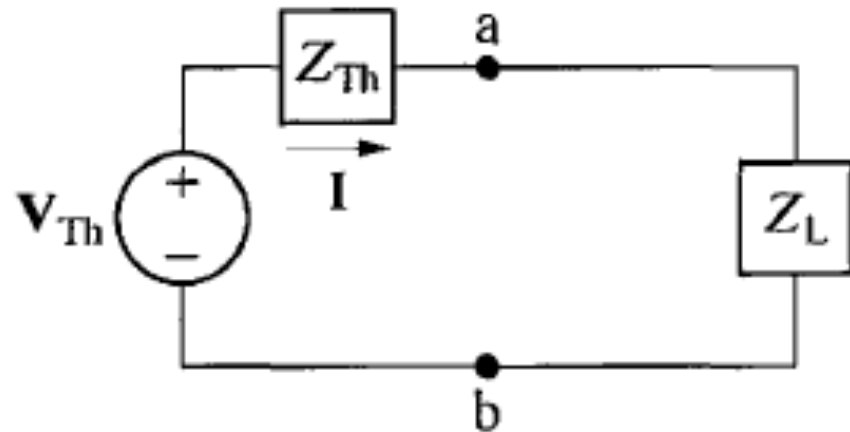

- As previously seen (lecture 21), for sinusoidal sources and RLC circuits, power is

Complex power
$$S = \frac{|\mathbf{I}|^2}{2} Z_L$$

Real power
$$P = \frac{|\mathbf{I}|^2}{2} R_L$$

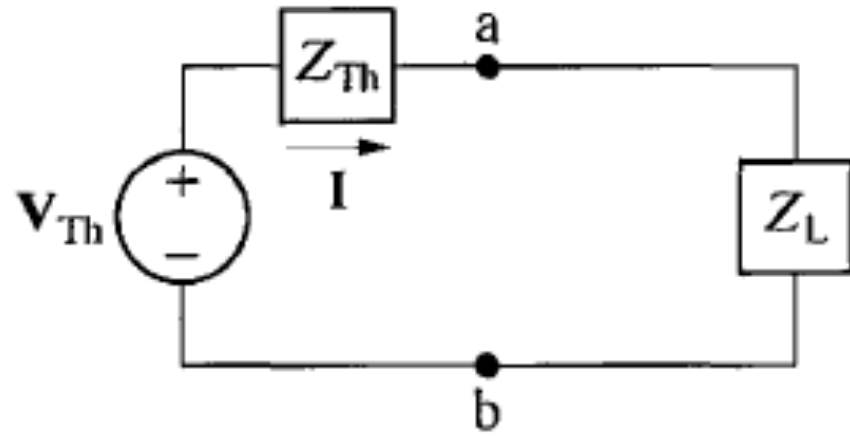

- For our problem

$$\mathbf{I} = \frac{\mathbf{V}_{Th}}{Z_{Th} + Z_L} = \frac{\mathbf{V}_{Th}}{(R_{Th} + R_L) + j(X_{Th} + X_L)}$$

- So

$$P = \frac{|\mathbf{I}|^2}{2} R_L = \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

$$P = \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

- We can optimize this using calculus
- How depends upon which parameters we can change

$$P = \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

- Case 1 (unusual): both R_L and X_L are free to choose

$$\frac{\partial P}{\partial X_L} = 0 \qquad \frac{\partial P}{\partial R_L} = 0$$

$$Z_L = Z_{Th}^*$$

$$P_{max} = \frac{|\mathbf{V}_{Th}|^2}{8R_{Th}}$$

$$P = \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

- Case 2: X_L is fixed, but R_L is free to choose

$$\frac{\partial P}{\partial R_L} = 0$$

$$R_L = \sqrt{R_{Th}^2 + (X_{Th} + X_L)^2}$$

$$P_{max} = \dots$$

$$P = \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

- Case 3: R_L is fixed, but X_L is free to choose

$$\frac{\partial P}{\partial X_L} = 0$$

$$X_L = -X_{Th}$$

$$P_{max} = \dots$$

$$P = \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

- Case 4: X_L is 0, but R_L is free to choose

$$\frac{\partial P}{\partial R_L} = 0$$


$$R_L = \sqrt{R_{Th}^2 + X_{Th}^2}$$

$$P_{max} = \dots$$


$$P = \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

- Other scenarios:
 - Fixed angle on Z_L
 - Limits on R_L and X_L

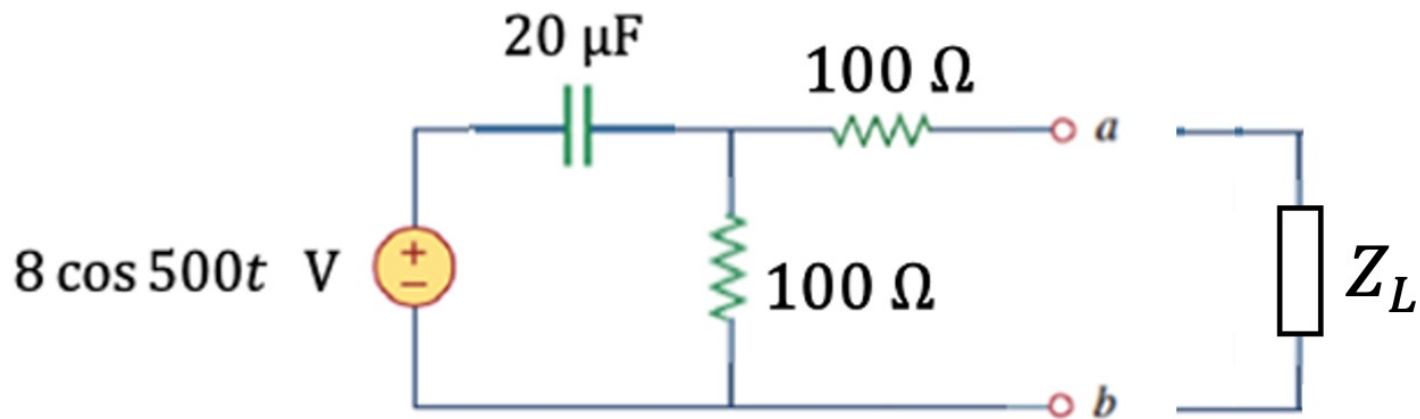
Example: find Z_L to maximize the power transfer



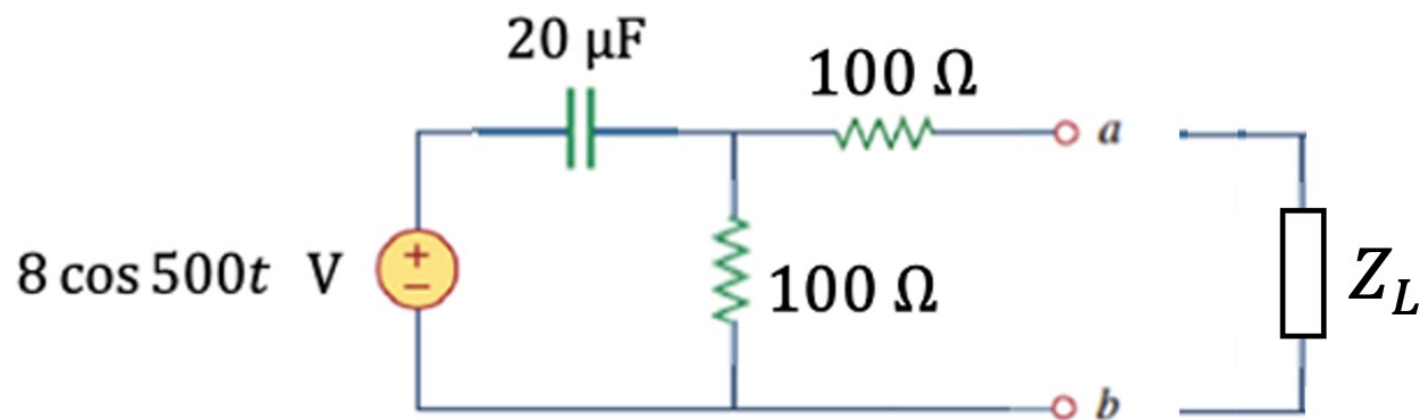If Z_L is free to choose or must be resistive only



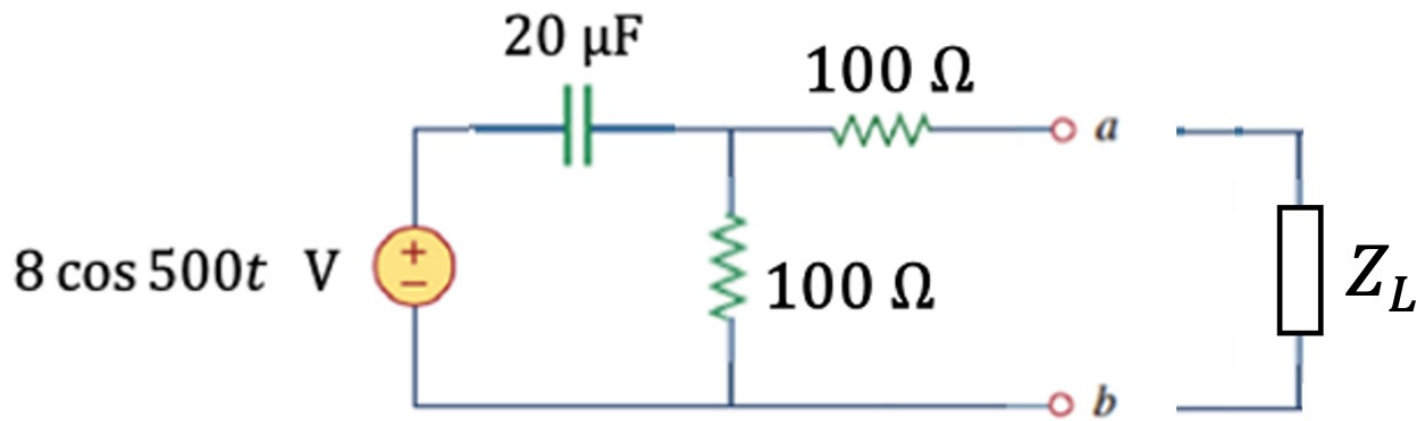
$$V_{Th} = 4\sqrt{2} \cos(500t + 45^\circ) \text{ V and } Z_{Th} = 150 - j50 \Omega,$$



- If $Z_L = R_L + jX_L$
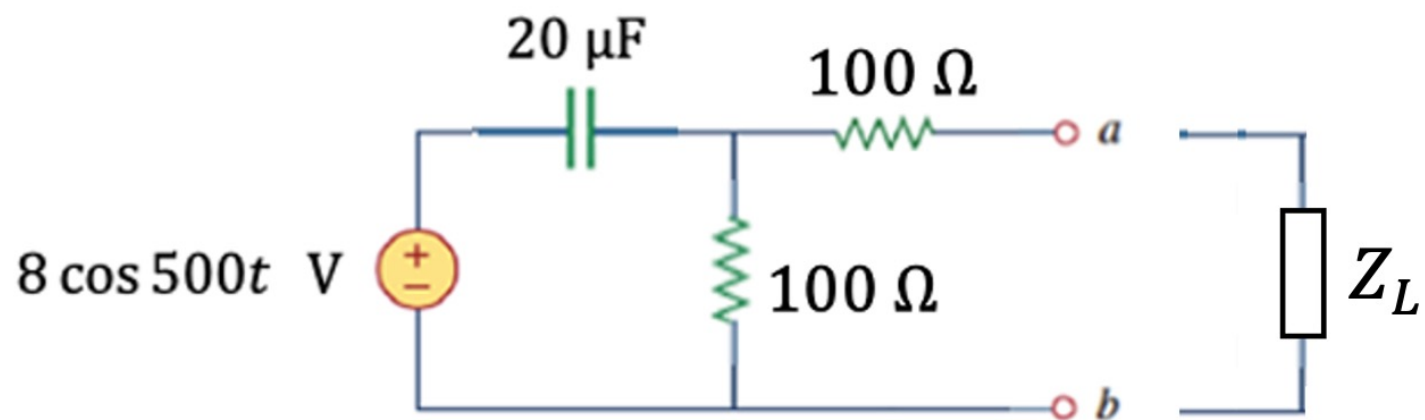
$$Z_L = 150 + j50 \Omega = 150 \Omega, 0.1 \text{ H}, \text{ and } P = 26.7 \text{ mW}$$



- If $Z_L = R_L$

$$Z_L = 158 \Omega \text{ and } P = 26.0 \text{ mW}$$