

# Lecture 18

## Phasors – 4 of 9

using phasors;  
variation with frequency

# Phasor Review

- Extend sinusoidal voltages/currents to phasors (complex)
- Convert components (R,L,C) to impedances
- Solve the problem using Ohm's Law, KVL/KCL, ...
- Convert back


$$V_s \cos(\omega t + \phi) \Rightarrow \mathbf{V} = V_s e^{j\phi}$$
$$I_s \cos(\omega t + \phi) \Rightarrow \mathbf{I} = I_s e^{j\phi}$$

$$Z = \begin{cases} R & \text{resistor} \\ j\omega L & \text{inductor} \\ \frac{1}{j\omega C} = -j \frac{1}{\omega C} & \text{capacitor} \end{cases}$$

$$B \angle \theta \Rightarrow B \cos(\omega t + \theta)$$

# Common Usage

- Find the voltage  $v(t)$

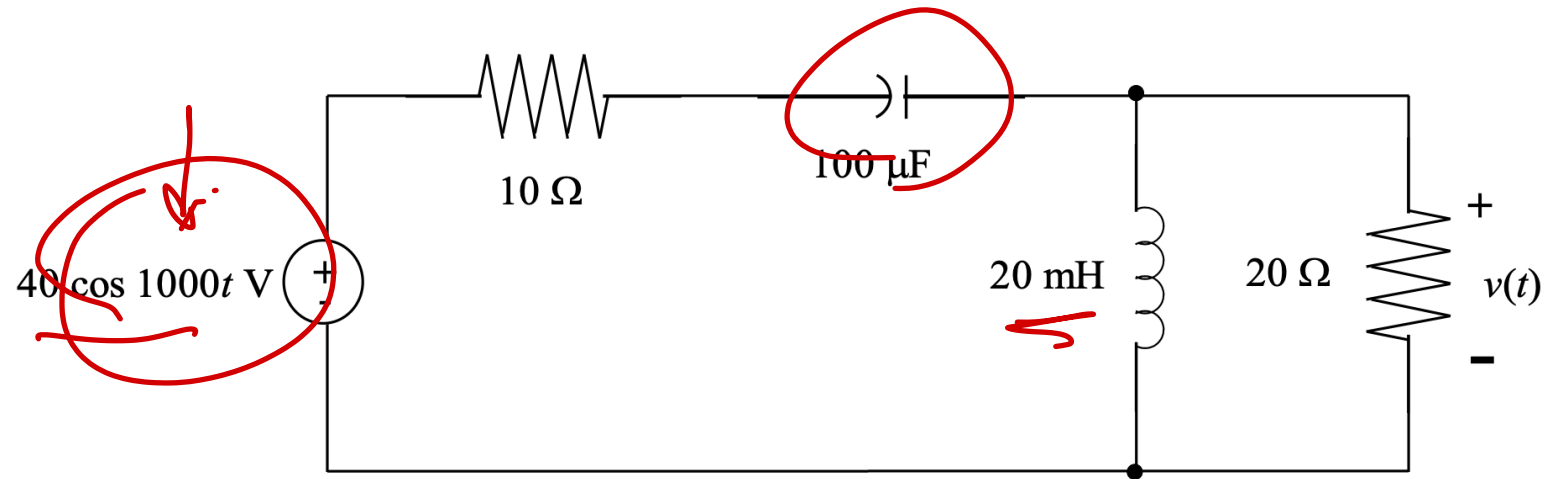


- Convert:

$$40 \cos 1000 t \rightarrow 40$$

$$20 \text{ mH} \rightarrow j\omega L = j20$$

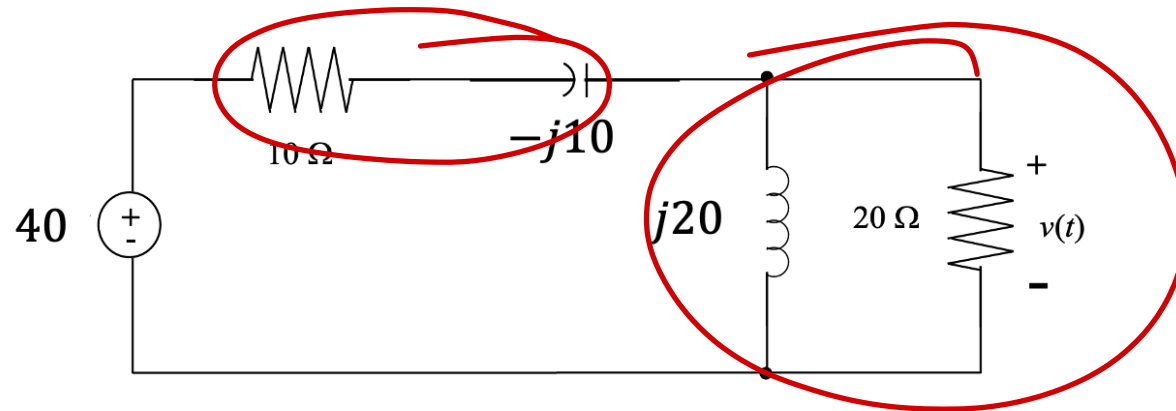
$$100 \mu\text{F} \rightarrow -j \frac{1}{\omega C} = -j10$$



- Solve: series/parallel combining, voltage division

$$Z_s = \underline{10 - j10} = 10(1 - j) \qquad Z_p = \frac{(20)(j20)}{\underline{20 + j20}} = \frac{j20}{1 + j}$$

$$V = 40 \frac{Z_p}{Z_s + Z_p}$$

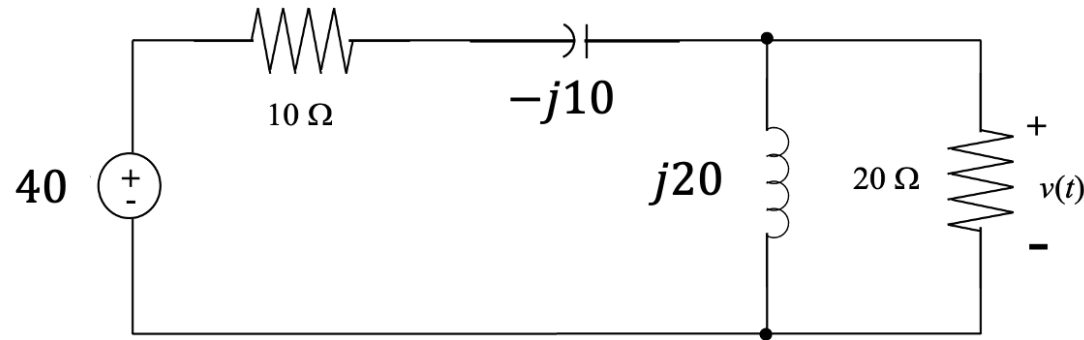

- Simplify and convert to polar form

$$V = 40 \frac{\frac{j20}{1+j}}{10(1-j) + \frac{j20}{1+j}} = \frac{40(1+j)}{2} = 28.3 \angle 45^\circ$$

- Convert to a time function

$$v(t) = 28.3 \cos(1000t + 45^\circ) V$$

- **Example:** find  $i(t)$

1- convert to phasor/input

$$Z_c = -j \frac{1}{\omega C} = -j \frac{10^6}{2000 \cdot 20}$$


$$= -j 25$$

2- node  $V = \frac{5}{1+j}$

3- Ohm's law

$$I = \frac{V}{-j 25}$$

$$= \frac{5}{(1+j)(-j 25)}$$

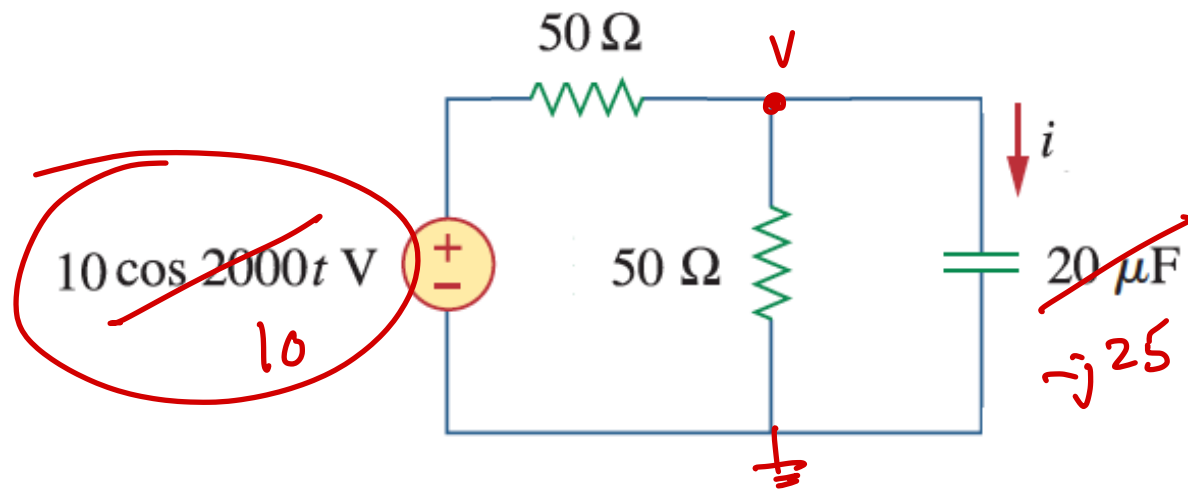

$$\sum \left( \frac{V-10}{50} + \frac{V}{50} + \frac{V}{-j 25} = 0 \right)$$

$$V-10+V+j 2V = 0$$

$$V(2+j 2) = 10$$

$$V = \frac{10}{2(1+j)} = \frac{5}{1+j}$$

$$\bar{I} = \frac{5}{(1+j)(-j25)}$$

$$= \frac{5 \angle 0^\circ}{\sqrt{2} \angle 45^\circ \quad 25 \angle -90^\circ}$$



$$= \frac{5}{25\sqrt{2}} \angle 0 - 45 + 90$$

$$= \frac{1}{5\sqrt{2}} \angle 45^\circ$$

$$\frac{\sqrt{2}}{10} = \frac{1.414}{10} = .141$$

$$\underline{\underline{141 \cos(2000t + 45^\circ) \text{ mA}}}$$

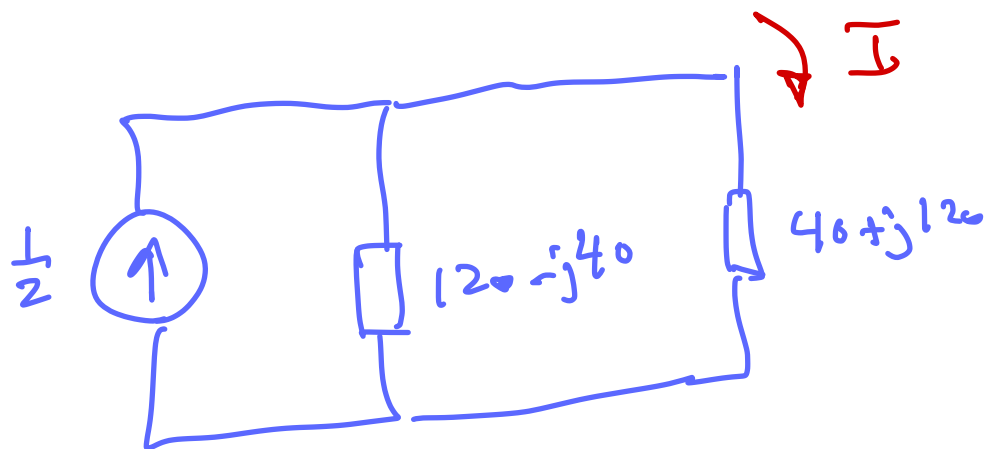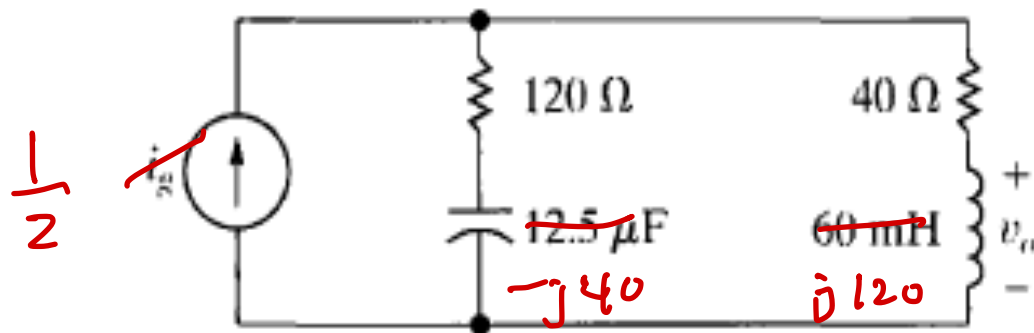**Example:** find  $v_o(t)$  if  $i_g(t) = 500 \cos 2000 t \text{ mA}$



1 - convert

$$Z_L = \frac{60}{1000} \cdot j^{2000} = j120$$

$$Z_C = -j \frac{10^6}{2000 \cdot 12.5} = -j40$$

2 - series comb.

3 - current div

$$I = \frac{1}{2} \cdot \frac{120 - j40}{160 + j80}$$

4 - ohm's law

$$v_o = j120 \cdot I$$



$$v_o = \underbrace{j120 \cdot \frac{1}{2}}_{60 \angle 90^\circ} \cdot \frac{120 - j40}{160 \angle 80^\circ}$$

$$\frac{126.5 \angle -18.43^\circ}{178.9 \angle 26.57^\circ}$$


$$\underbrace{\quad \quad \quad}_{42.4} \underbrace{\quad \quad \quad}_{\cos(2000t + 45^\circ)} \underbrace{\quad \quad \quad}_{V}$$

$$60 \cdot \frac{126.5}{178.9} = 42.4$$

$$90 + (-18.43) - (26.57) = 45$$

# Consider Variation with Frequency

Consider voltage division:



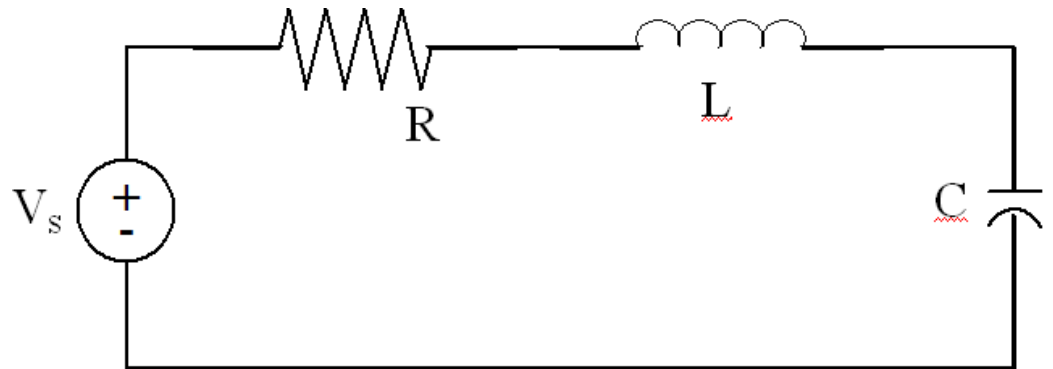


$$V_R = \frac{RV_s}{R + j\omega L + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 - \omega^2 LC + j\omega RC} V_s$$


Similarly

$$V_L = \frac{-\omega^2 LC}{1 - \omega^2 LC + j\omega RC} V_s$$
$$V_C = \frac{1}{1 - \omega^2 LC + j\omega RC} V_s$$

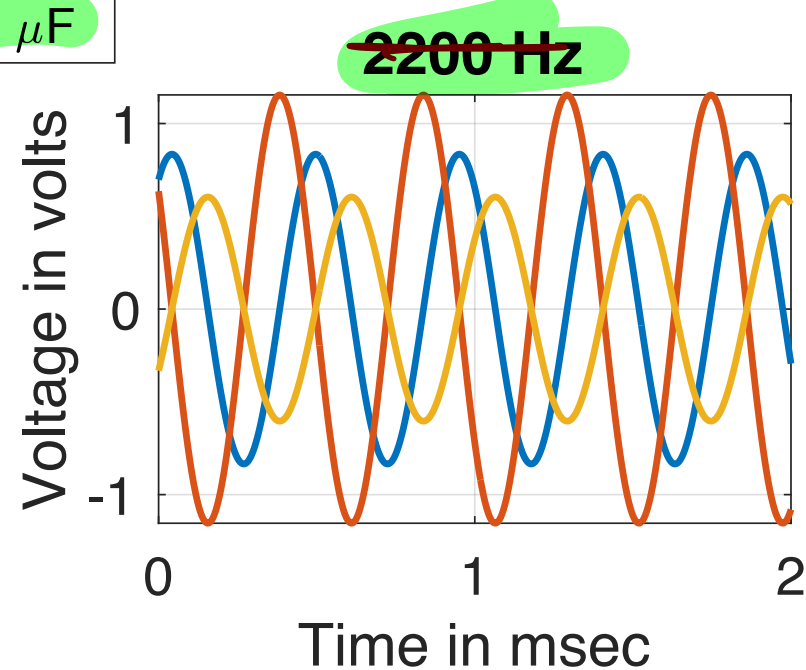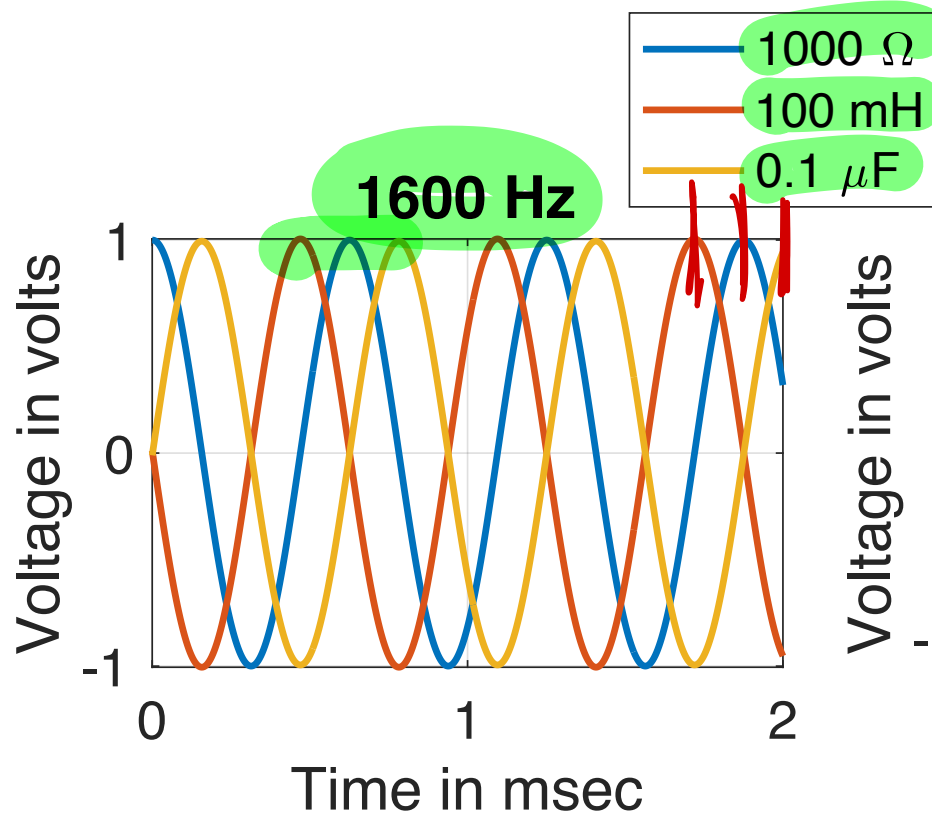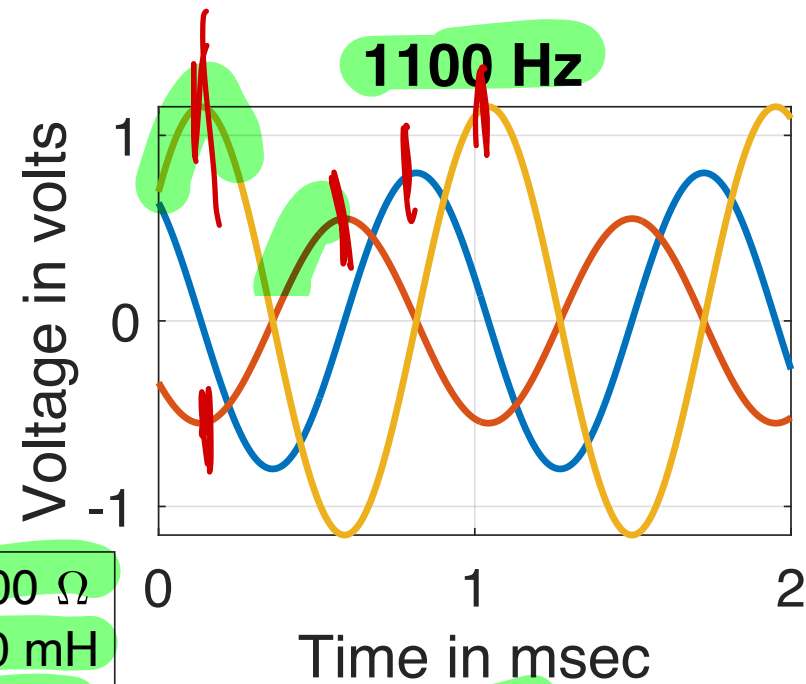- Comparison of the component voltages for different frequencies ( $V_s = 1$ )



Consider combined impedance variation

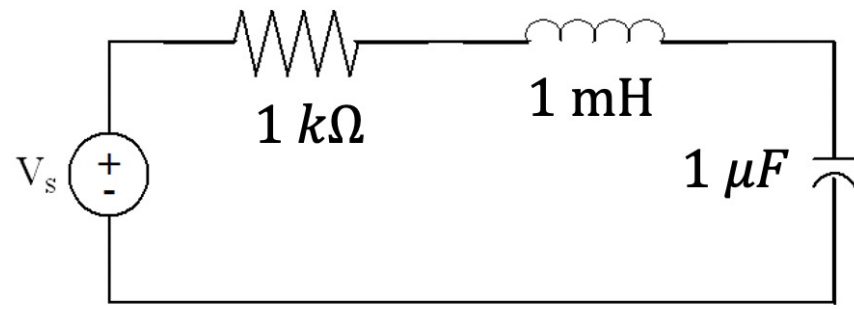


$$Z = R + j\omega L + \frac{1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$
$$= 1000 + j\left(\frac{\omega}{100} - \frac{10^6}{\omega}\right)$$

$$\omega = 10,000$$

Questions:

- At what frequency does this “appear” purely resistive?
- What happens at small frequency? Large frequency?

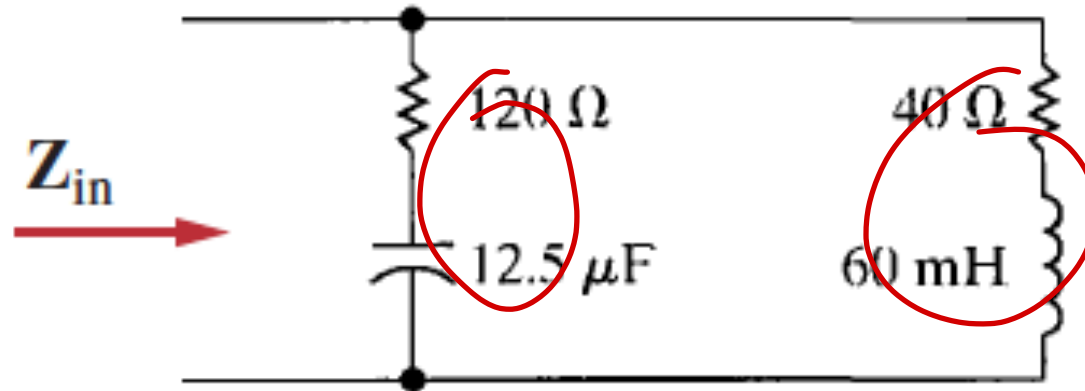
**Example:** find  $Z_{in}$  if  $\omega = \underline{2000}$  rad/sec



- Convert:

$$60\ \text{mH} \rightarrow j\omega L = \underline{j120}$$
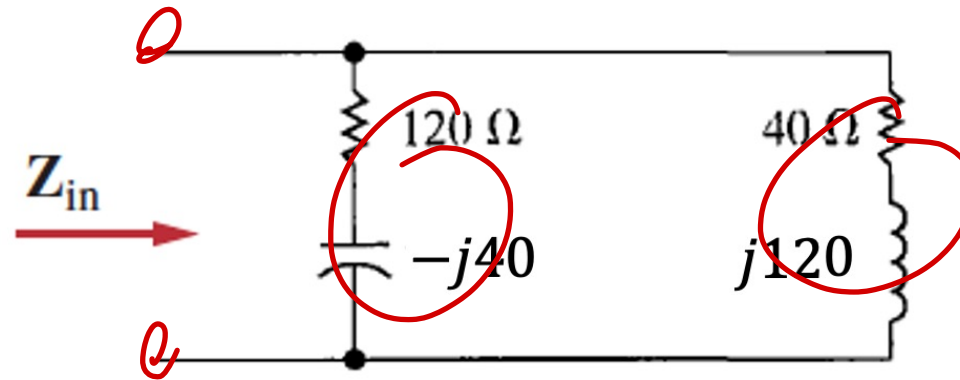
$$12.5\ \mu\text{F} \rightarrow -j\frac{1}{\omega C} = \underline{-j40}$$



- Solve: series/parallel combining

$$Z_{s,left} = 120 - j40 = 40(3 - j)$$

$$Z_{s,right} = 40 + j120 = 40(1 + j3)$$


$$Z_{in} = \frac{40(3 - j)40(1 + j3)}{40(3 - j) + 40(1 + j3)} = \frac{40(6 + j8)}{4 + j2} = \frac{40(3 + j4)}{2 + j}$$

$$= \frac{40(3 + j4)(2 - j)}{5} = 80 + j40$$

80 ohm resistor in series with 20 mH inductor !!

$\omega = 2000 \text{ rad/sec}$

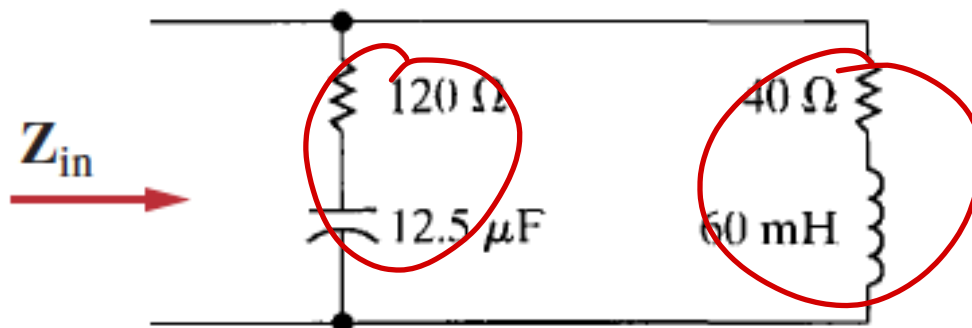
**Example:** How does  $Z_{in}$  vary with frequency? Is it ever purely real?




- Solve: series/parallel combining

$$Z_{s,left} = 120 - j \frac{80,000}{\omega} \quad Z_{s,right} = 40 + j60\omega$$
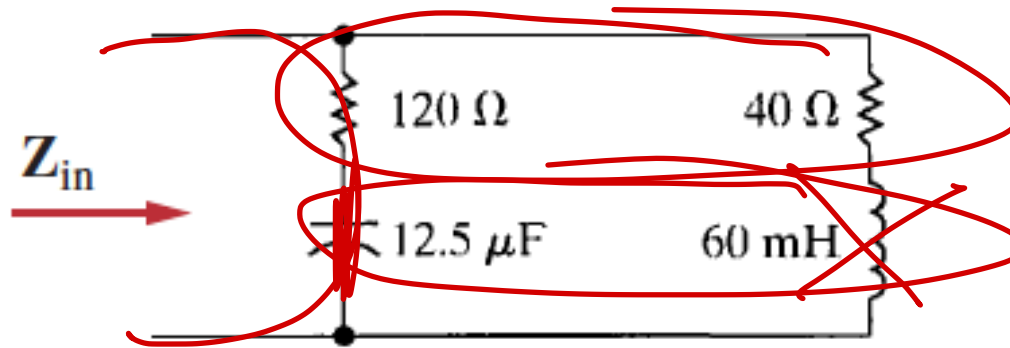
$$Z_{in} = \frac{Z_{s,left} \times Z_{s,right}}{Z_{s,left} + Z_{s,right}} = \frac{(120 - j \frac{80,000}{\omega})(40 + j60\omega)}{120 - j \frac{80,000}{\omega} + 40 + j60\omega} = \dots$$



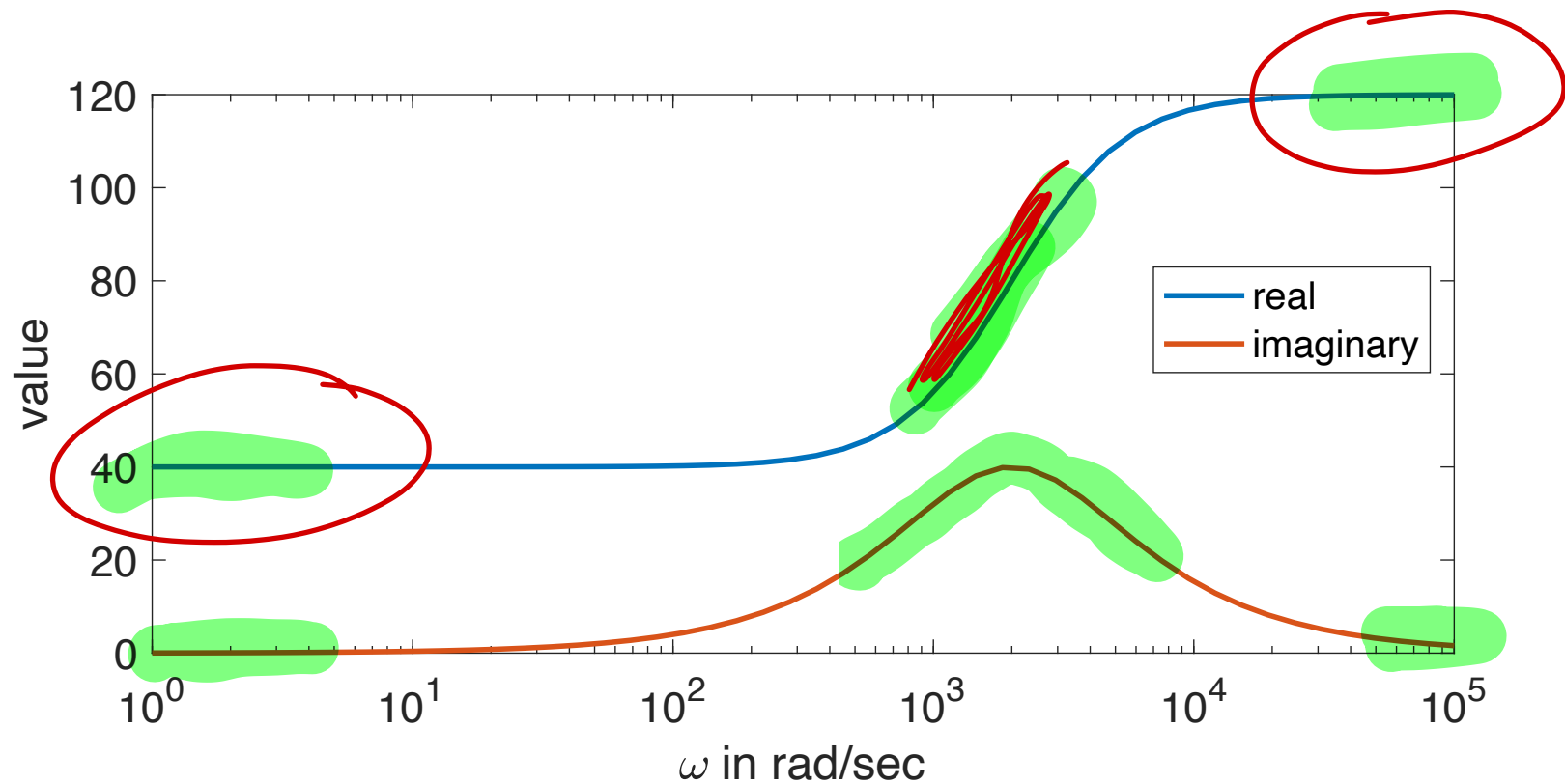
$$Z_{in} = \frac{120\omega^2 + 160 \times 10^6}{\omega^2 + 4 \times 10^6} + j \frac{160,000\omega}{\omega^2 + 4 \times 10^6}$$






**Practice problem:** find  $Z$
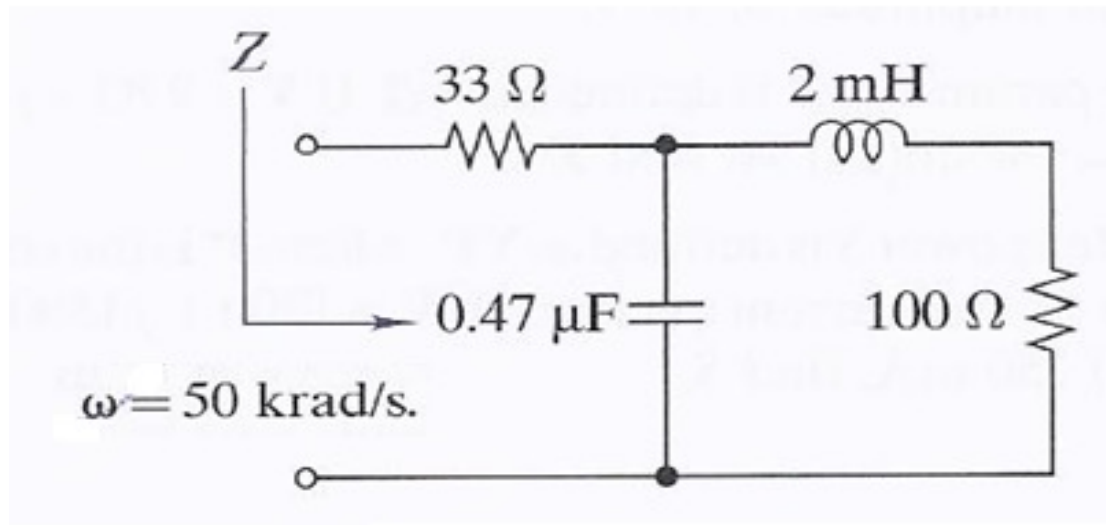
$$46.4 - j50.4;$$
$$46.4 \, \Omega \quad 0.397 \, \mu F$$




**Practice problem:** find  $Z$

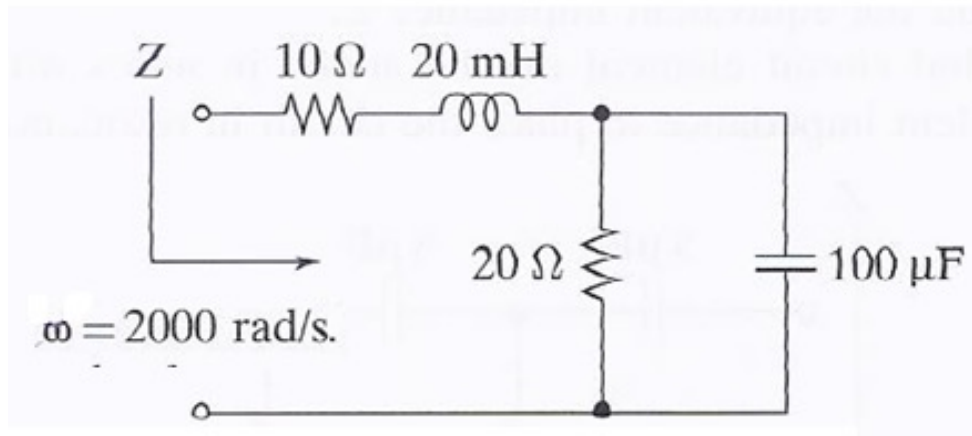$11.2 + j35.3$ ;  
 $11.2\ \Omega\ 17.6\text{ mH}$



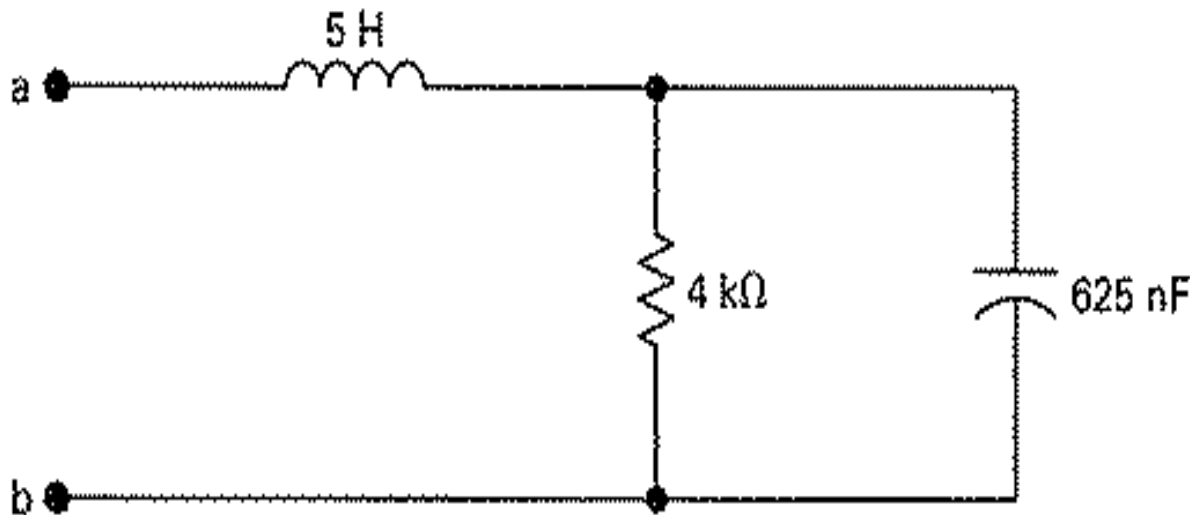**Practice problem:** at what frequency does this circuit seem purely resistive? What is the resistance?



$$400 \frac{\text{rad}}{\text{sec}}; 2 \text{ k}\Omega$$

- **Practice problem:** consider the parallel connection of a  $220\ \Omega$  resistor, a  $0.5\ \mu\text{F}$  capacitor, and a  $5\ \text{mH}$  inductor.
  - What is the equivalent impedance of this circuit at  $1000\ \text{Hz}$ ?
  - At  $5000\ \text{Hz}$ ?
  - At what frequency is the impedance purely real?

$11.6 + j49.2\ \Omega$ ;  $1.42 - j17.6\ \Omega$ ;  $1.59\ \text{kHz}$

**Practice problem:** Find the time expression for  $v_o(t)$ .

Note that  $\sin \omega t = \cos(\omega t - 90^\circ)$

$17.1 \cos 200t \text{ V}$

