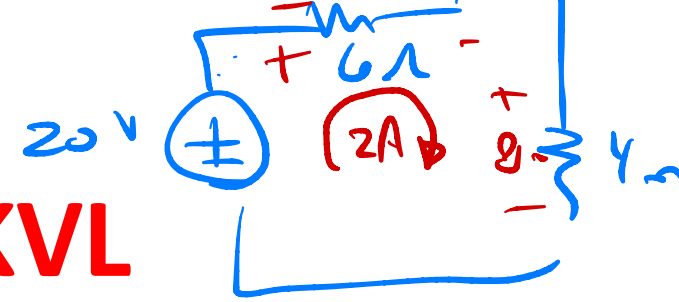


Lecture 4

Basics – 4 of 7


series/parallel resistance;
voltage/current division

Applying KCL and KVL




Consider:

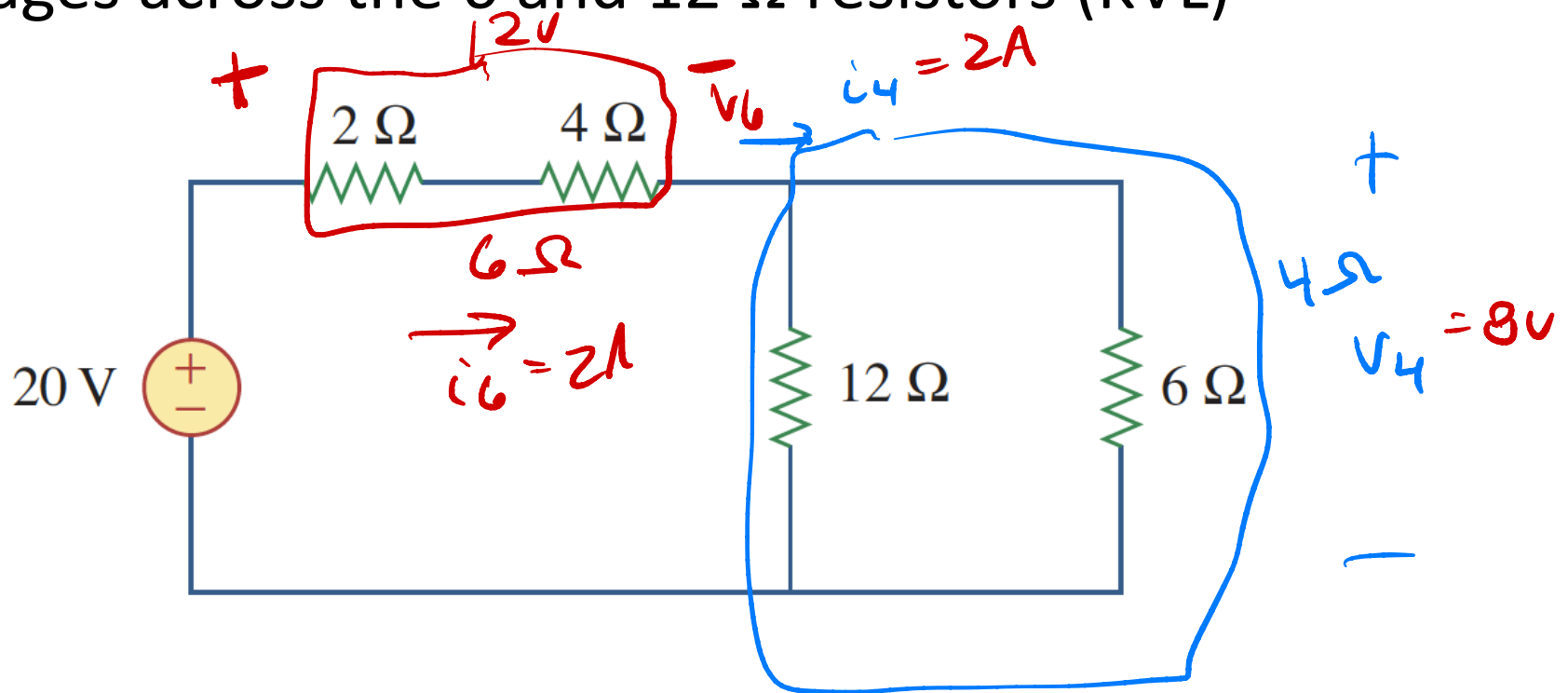- Currents in the 2 and 4 Ω resistors (KCL)
- Voltages across the 6 and 12 Ω resistors (KVL)



+ 10V -

Series Resistors & Voltage Division

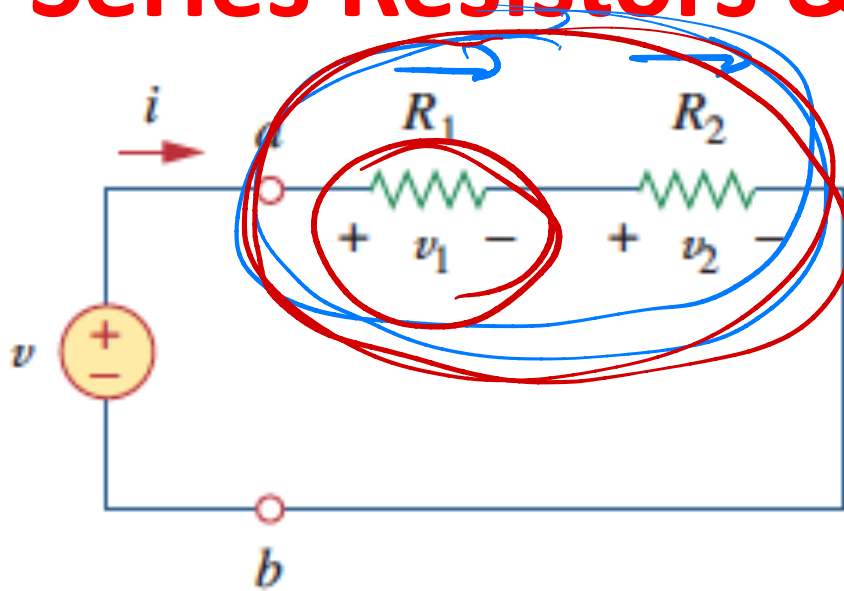

$R_1 + R_2$

— V —

$$V_1 = \frac{R_1}{R_1 + R_2} \cdot 10$$

$$V_2 = \frac{R_2}{R_1 + R_2} \cdot 10$$



$$V_1 = R_1 \cdot I$$

$$V_2 = R_2 \cdot I$$

$$V_1 + V_2 = R_1 I + R_2 I$$

$$V_{12} = (R_1 + R_2) I$$

Examples

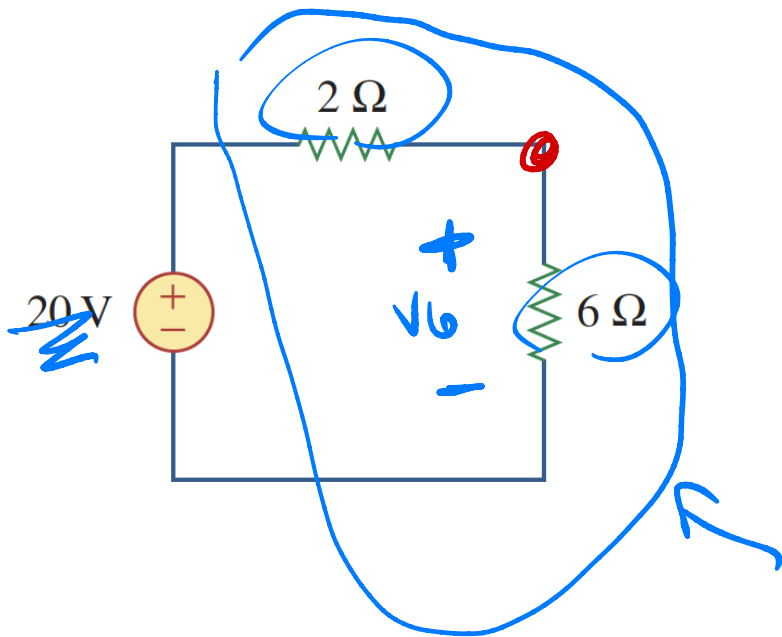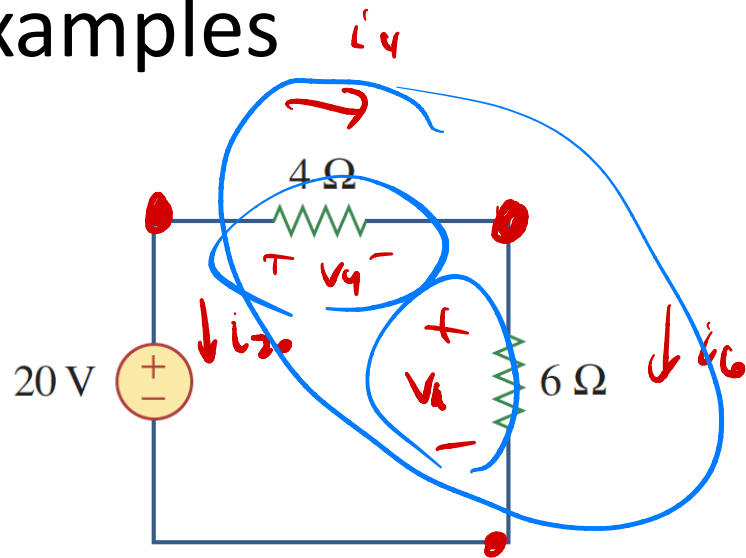

$$v_4 = 4 i_4$$

$$20 = v_4 + v_6$$


$$v_6 = 6 i_6$$

$$i_4 = i_6$$

$$20V$$

$$i_4 + i_{20} = 0$$

$$i_6 + i_{20} = 0$$

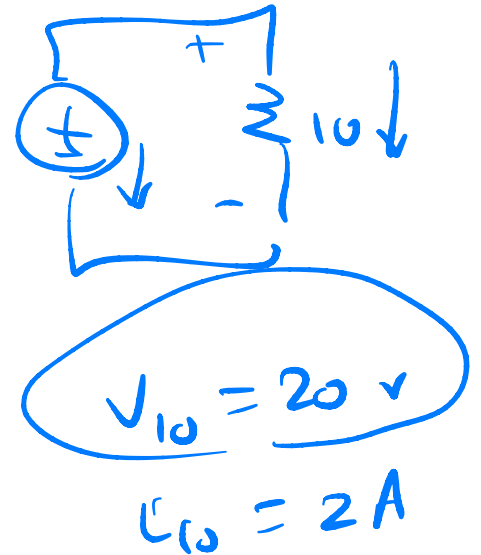

$$v_{10} = 20V$$

$$i_{10} = 2A$$


$$v_4 = \frac{4}{10} \cdot 20 = 8V$$

$$i_{20} = -2A$$

$$v_6 = \frac{6}{10} \cdot 20 = 12V$$

$$v_6 = 20 \cdot \frac{6}{6+2} = 15V$$


Example:

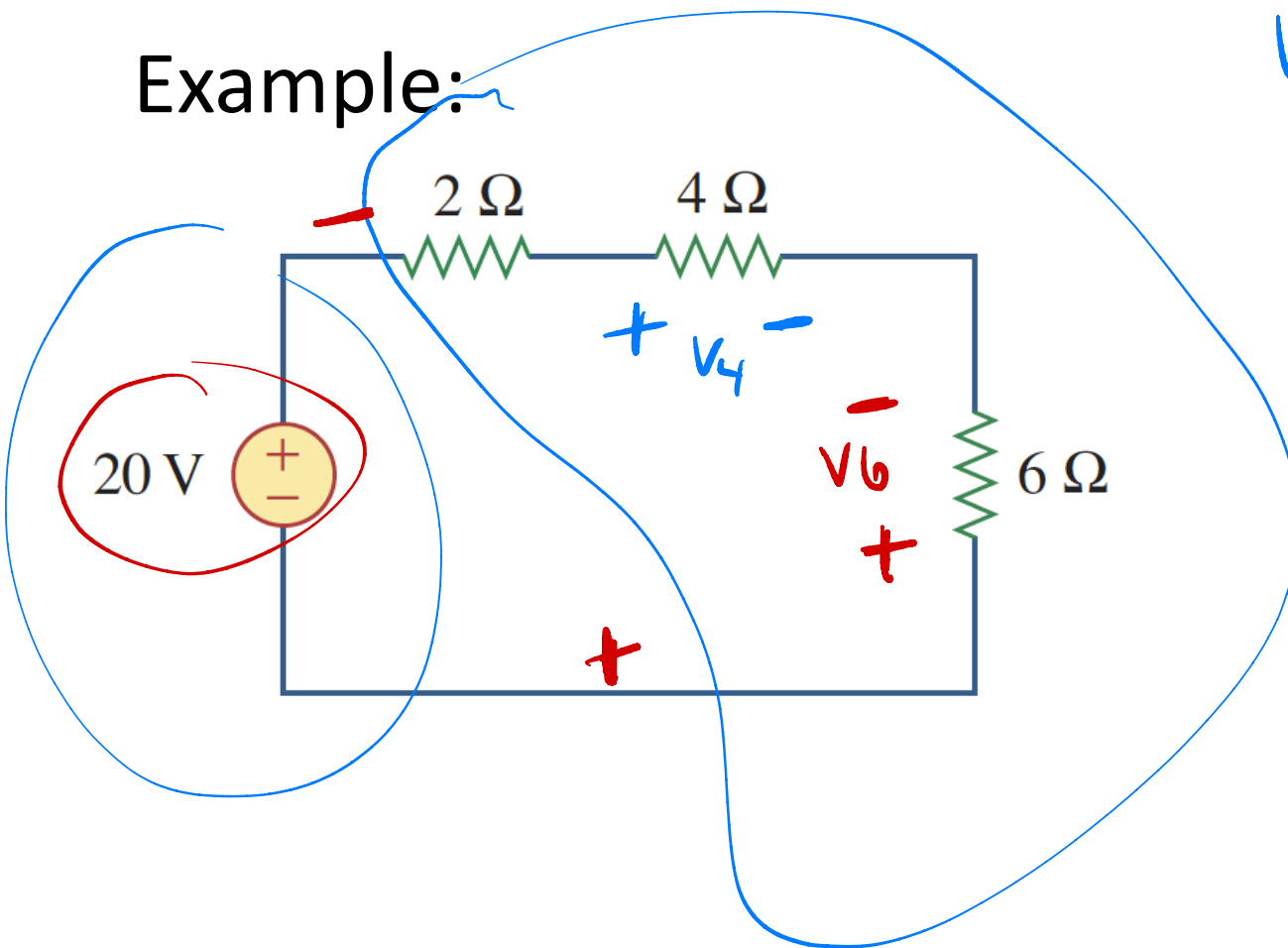

$$V_4 = \frac{4}{12} \cdot 20 = \frac{20}{3} \text{ V}$$

$$V_6 = \frac{6}{12} (-20) \\ = -10 \text{ V}$$

Parallel Resistors & Current Division

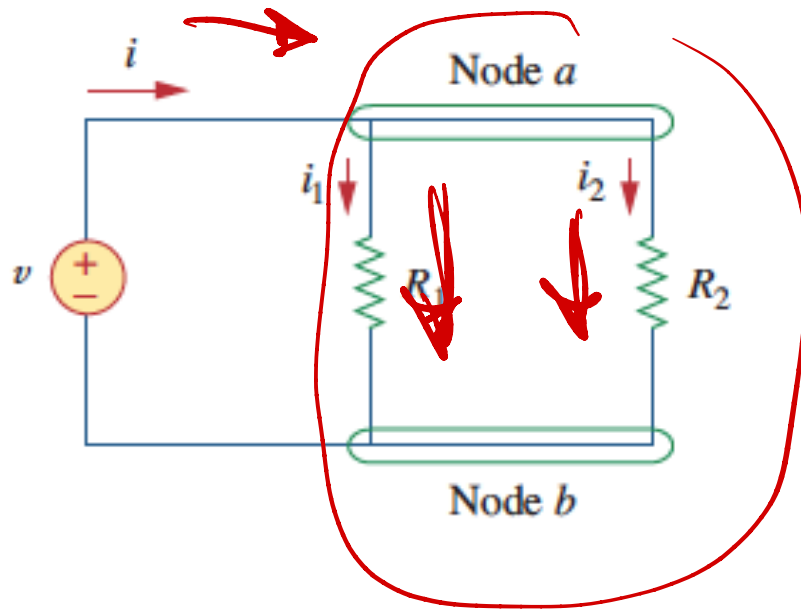


$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$
$$= \frac{R_1 \cdot R_2}{R_1 + R_2}$$


$$I_1 = \frac{R_2}{R_1 + R_2} \cdot I$$

$$I_2 = \frac{R_1}{R_1 + R_2} \cdot I$$

Examples:

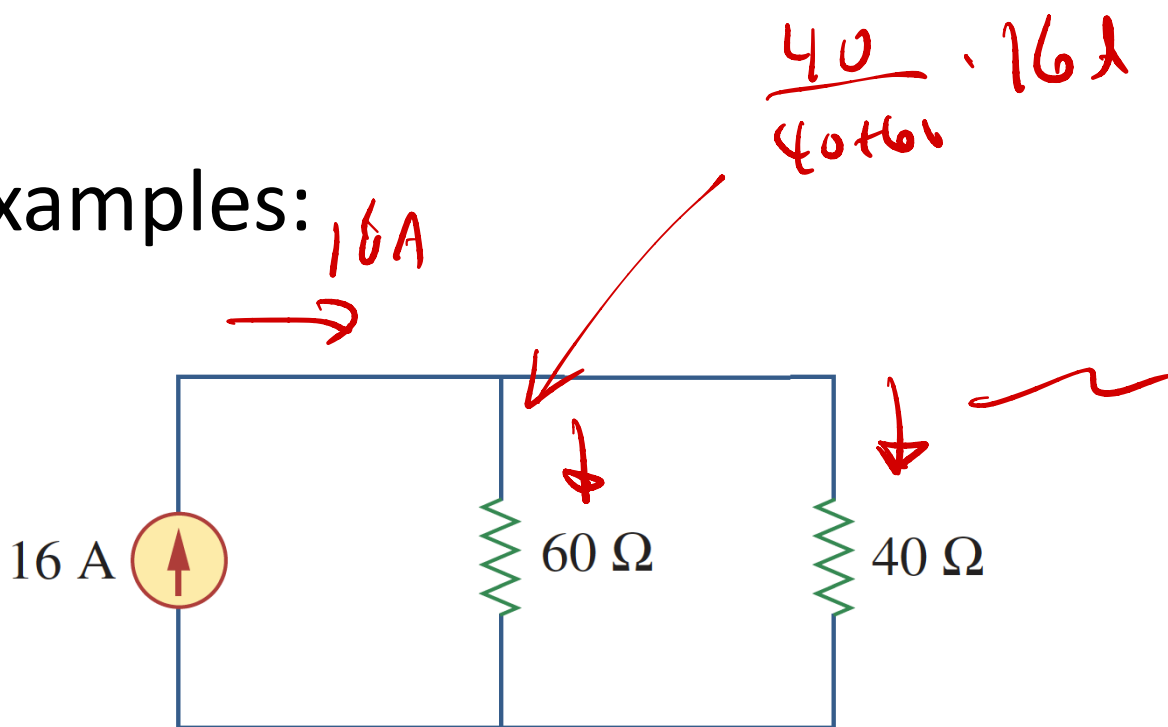


$$\frac{60}{100} \cdot 16 A$$

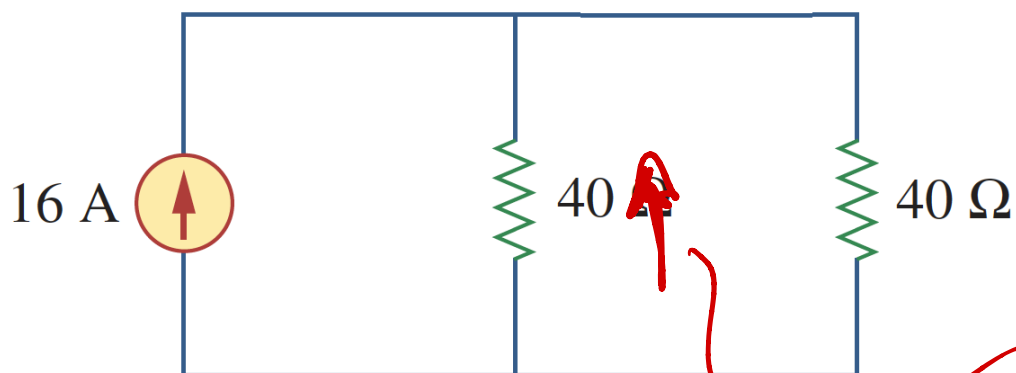

$$\frac{40}{40+40} \cdot (-16) A$$

Example:

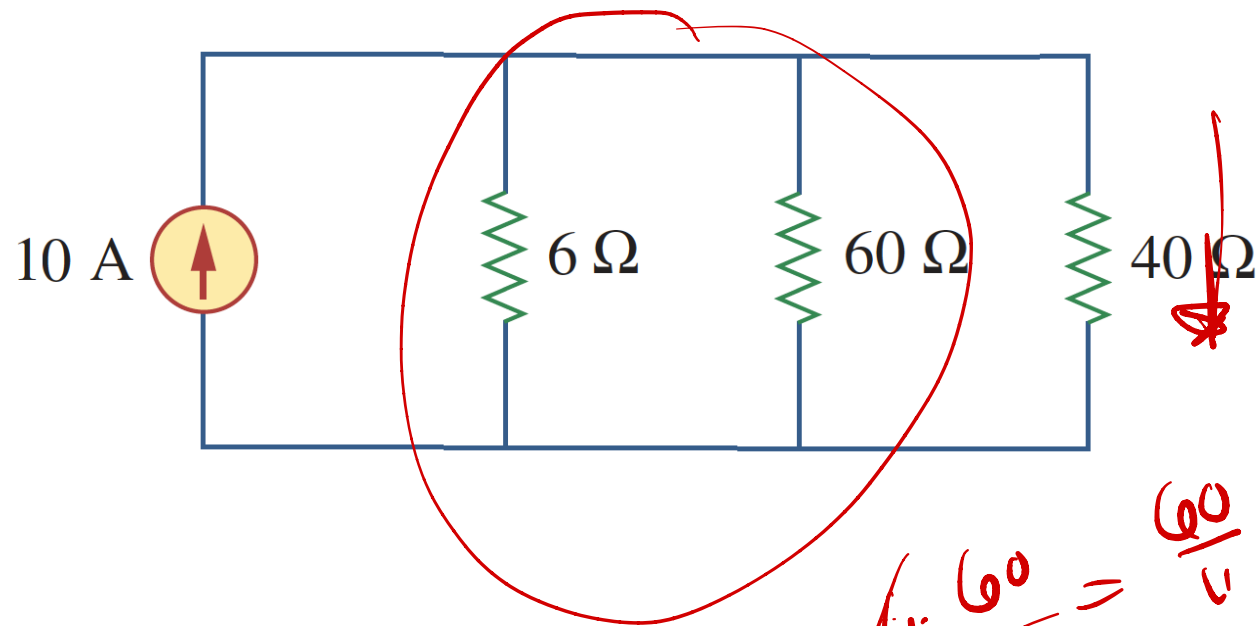

$$\frac{6 \cdot 60}{6 + 60}$$



$$\frac{6 \cdot 60}{66} = \frac{60}{11} \Omega$$

= ?

$$\frac{\frac{60}{11}}{40 + \frac{60}{11}} \cdot 10 \text{ A}$$


Series/Parallel Summary

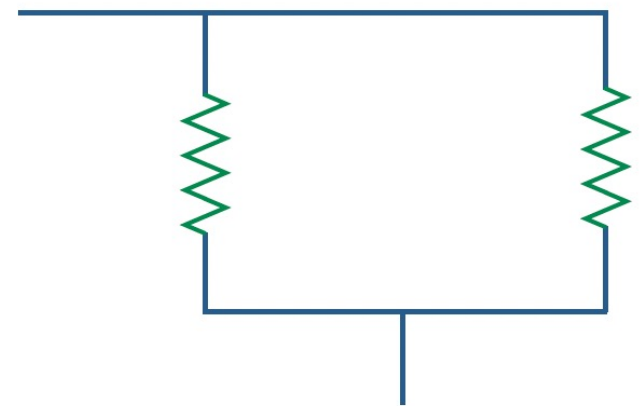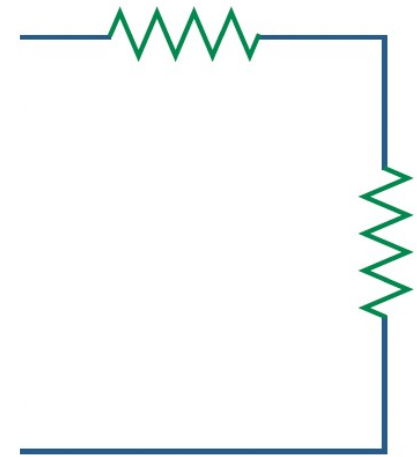- Series: resistances add
 - Nothing connected in the middle
 - **Same current (KCL)**
 - Voltage divides proportionally
- Parallel: resistances add inversely
 - Connected at both ends
 - **Same voltage (KVL)**
 - Current divides proportionally




-3.75 V

Example: find v

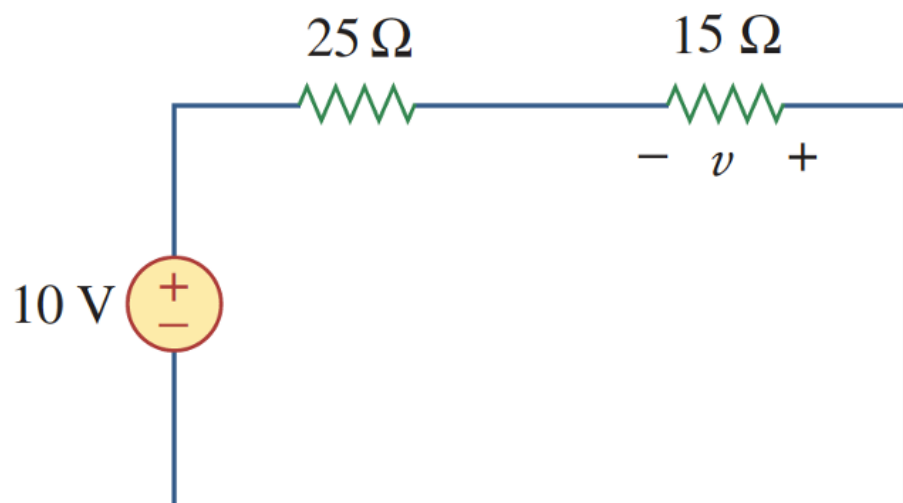


27 W

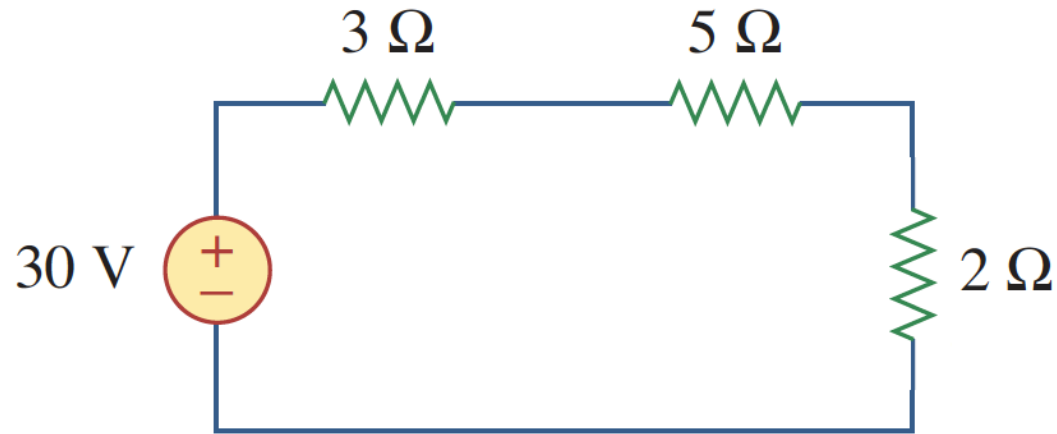Practice problem: find the power in the $3\ \Omega$ resistor



Practice problem: find v

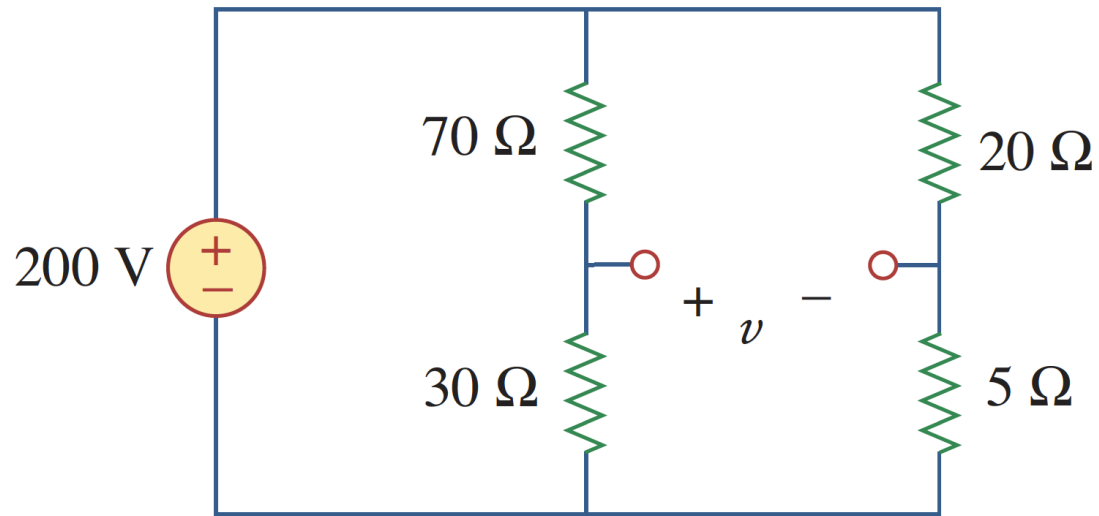

1152 W

Practice problem: find the power in the 50 Ω resistor

