

Lecture 4


Basics – 4 of 7

series/parallel resistance;
voltage/current division


Applying KCL and KVL

Consider:


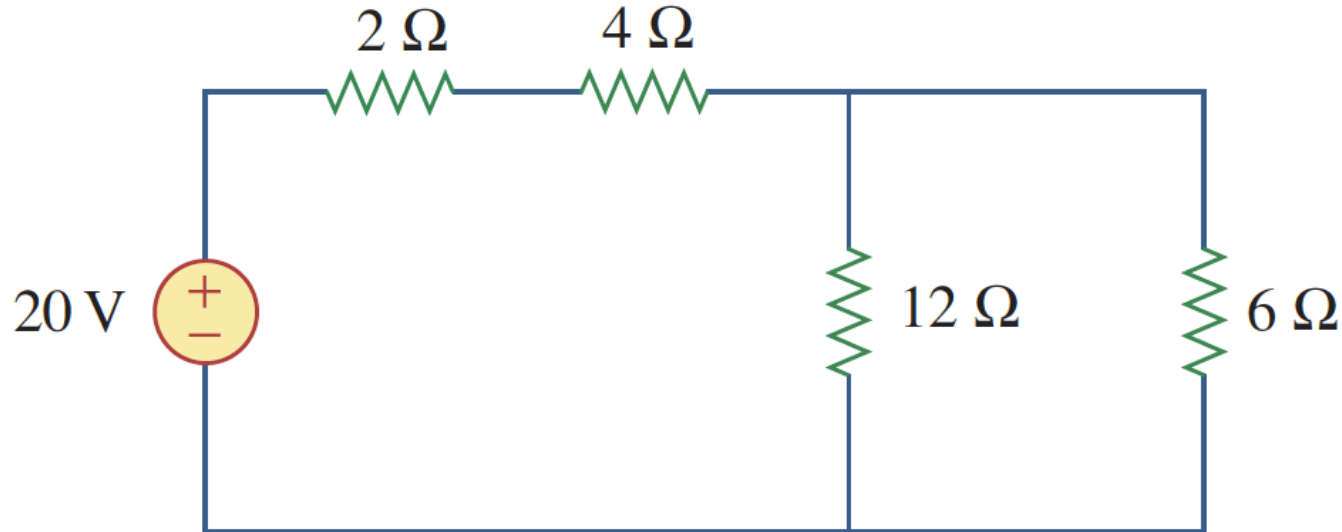
- Currents in the 2 Ω and 4 Ω resistors (KCL)
- Voltages across the 6 Ω and 12 Ω resistors (KVL)




Series Resistors & Voltage Division

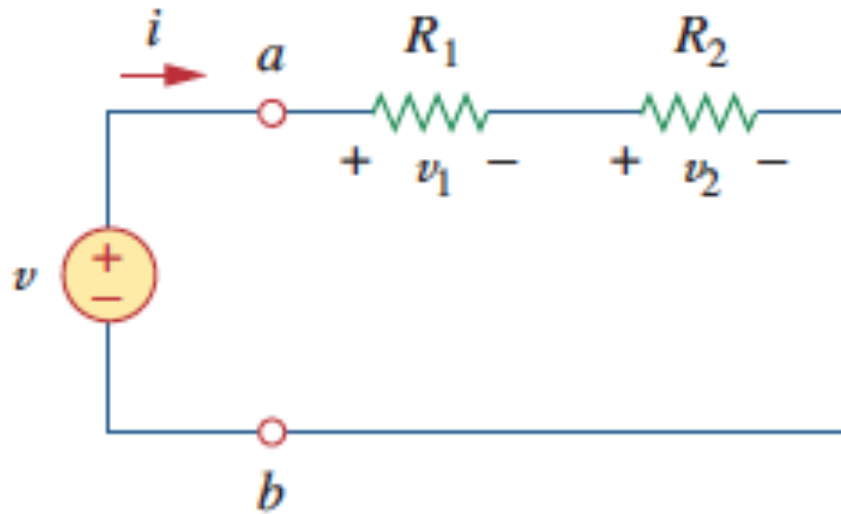


Examples

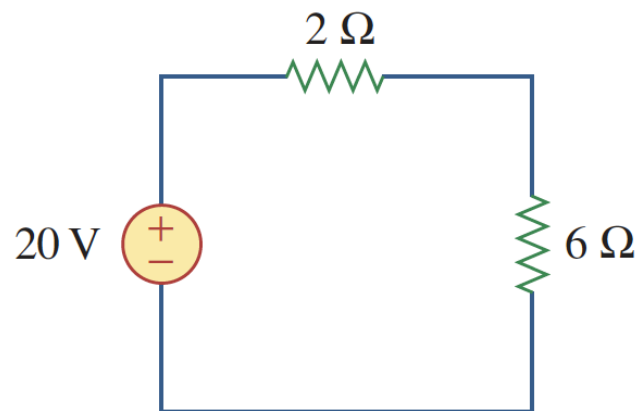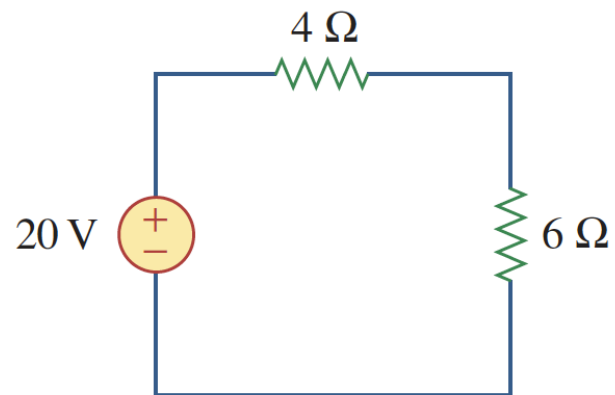



Example:

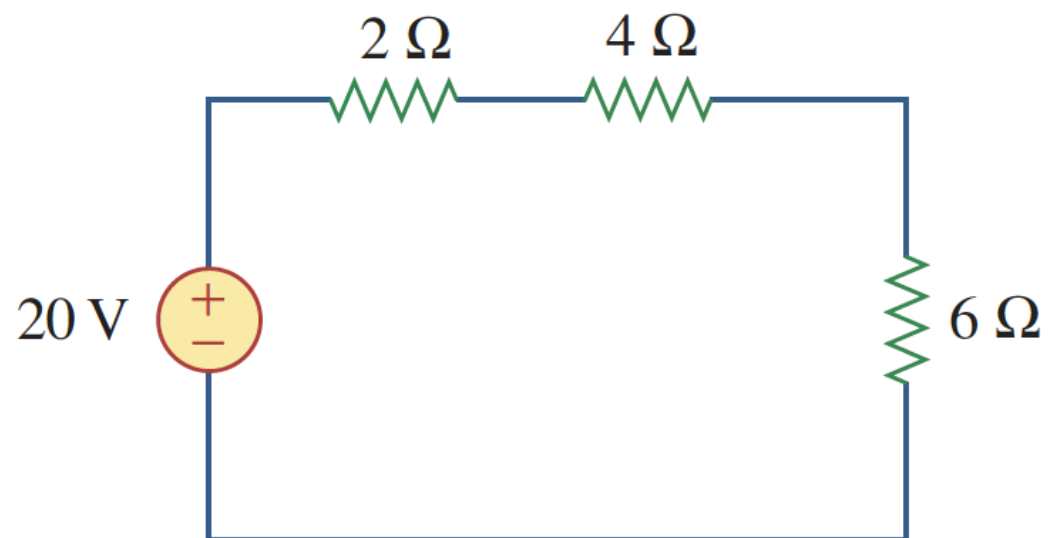


Parallel Resistors & Current Division

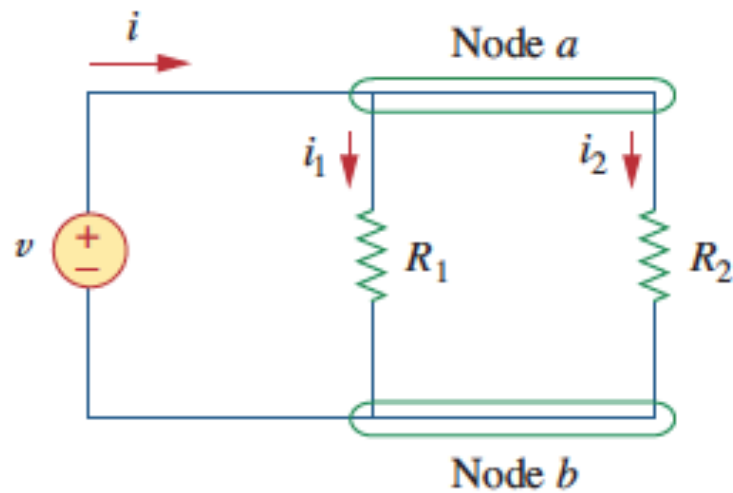

Examples:

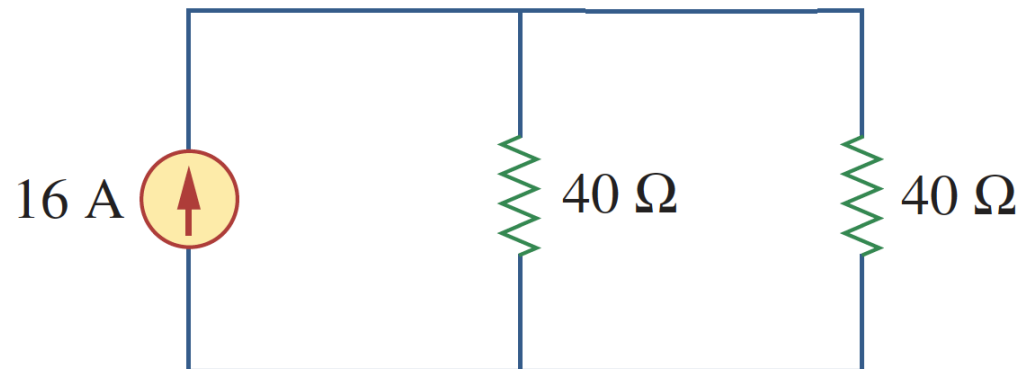
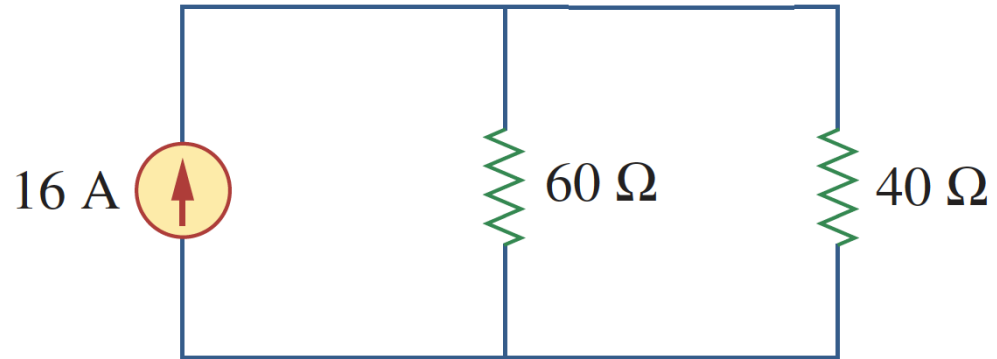


Example:

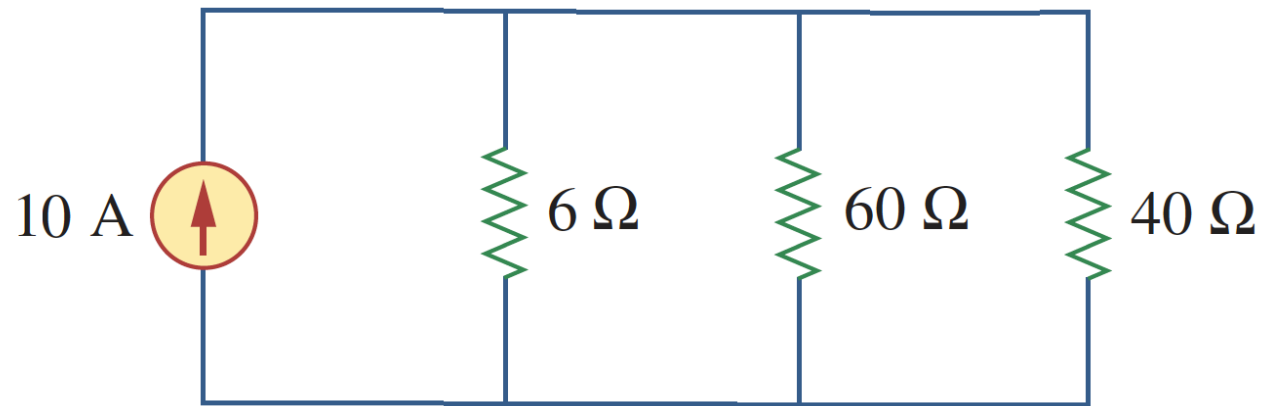


Series/Parallel Summary

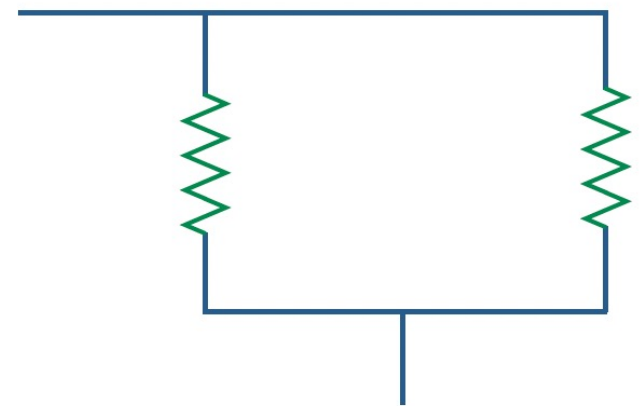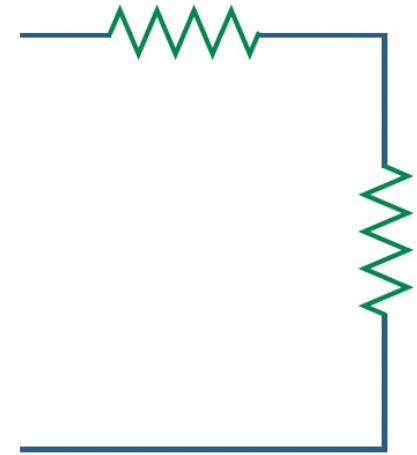- Series: resistances add
 - Nothing connected in the middle
 - **Same current (KCL)**
 - Voltage divides proportionally
- Parallel: resistances add inversely
 - Connected at both ends
 - **Same voltage (KVL)**
 - Current divides proportionally




-3.75 V

Example: find v

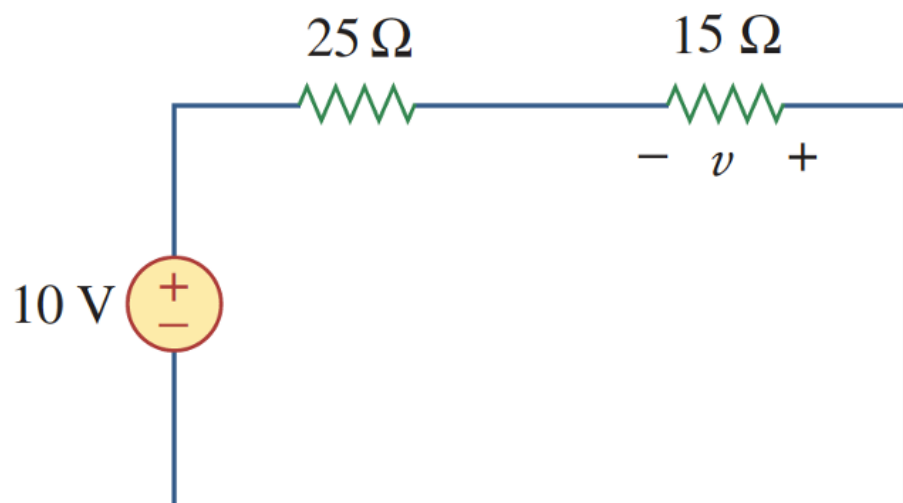


27 W

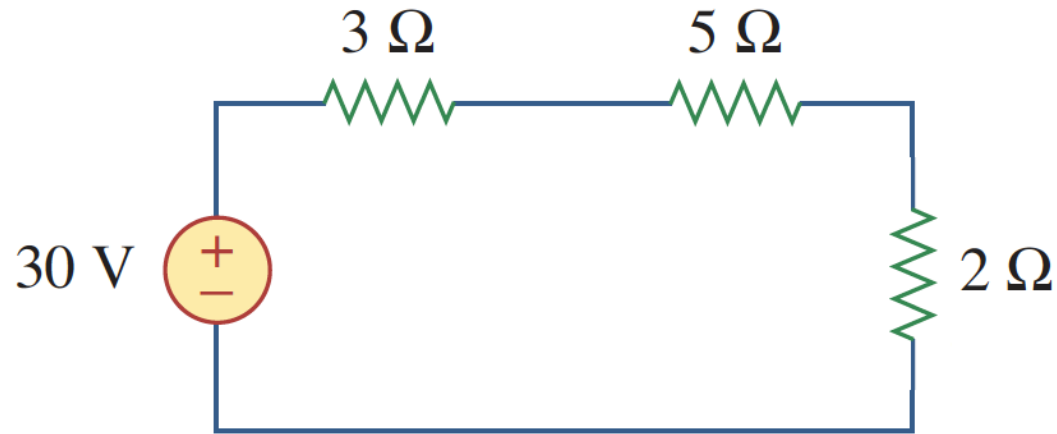Practice problem: find the power in the $3\ \Omega$ resistor



Practice problem: find v

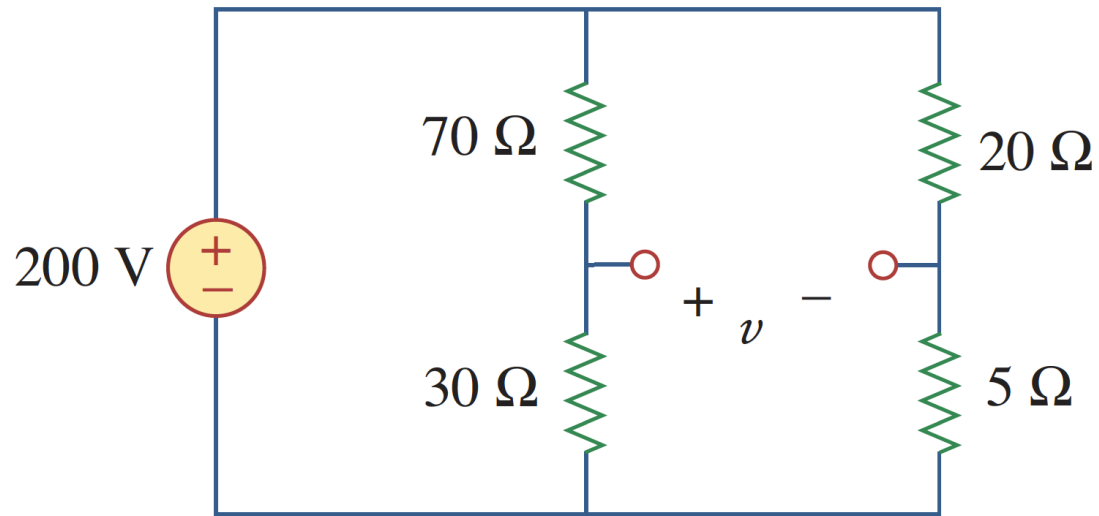

1152 W

Practice problem: find the power in the 50 Ω resistor

