

Lecture 9


Node Analysis – 2 of 7

more complex branches

$$A: \frac{A}{2} + \frac{A-30}{6} + \frac{A-(B+12)}{4} = 0$$

Extension #2 – V + R branches


- Consider:

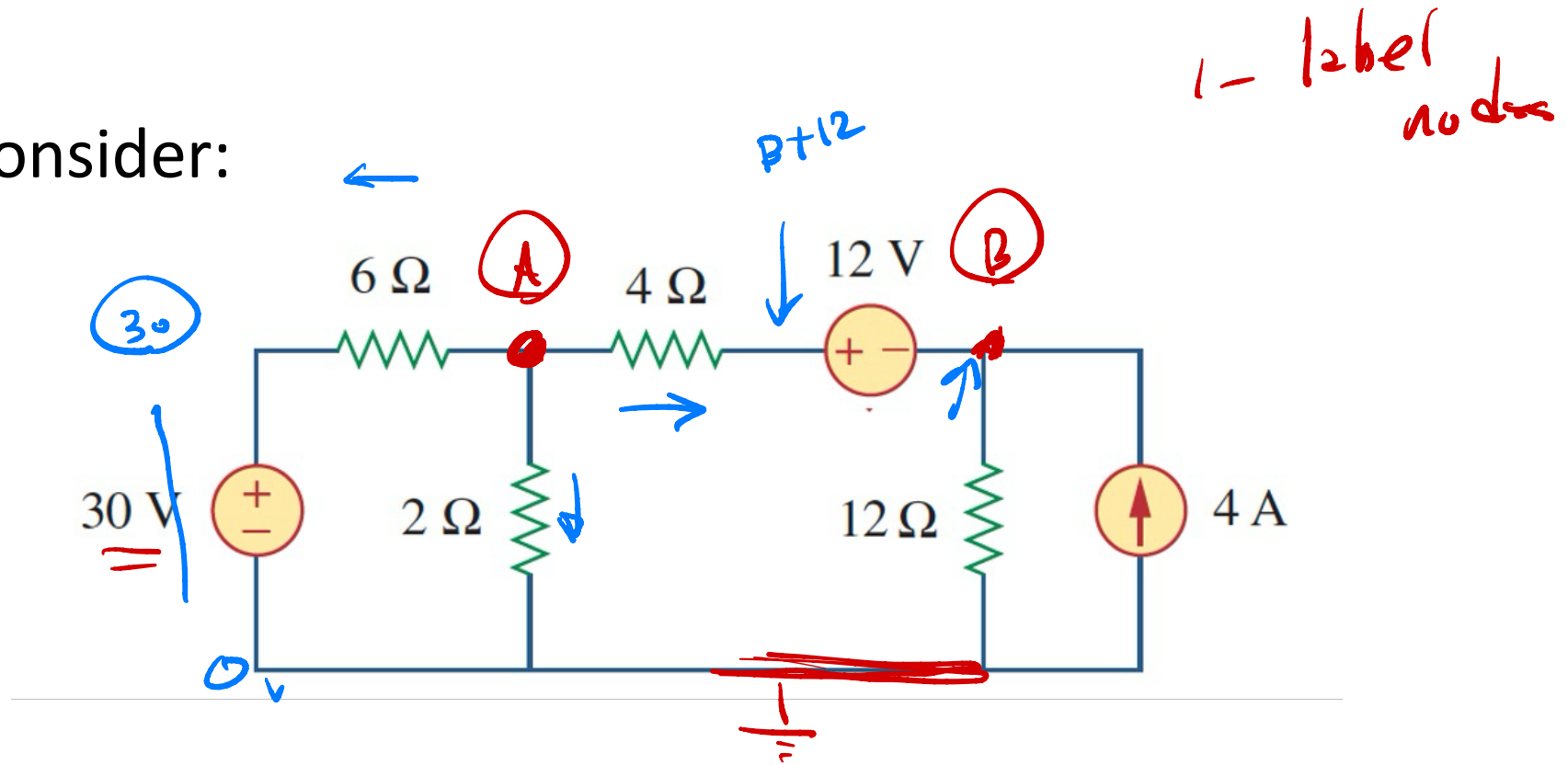

- Solution: Modify the Ohm's Law expression(s) for the individual branch current(s)

$$B: -4 + \frac{B}{12} + \frac{B+12-A}{4} = 0$$


Example (solved on next slide)

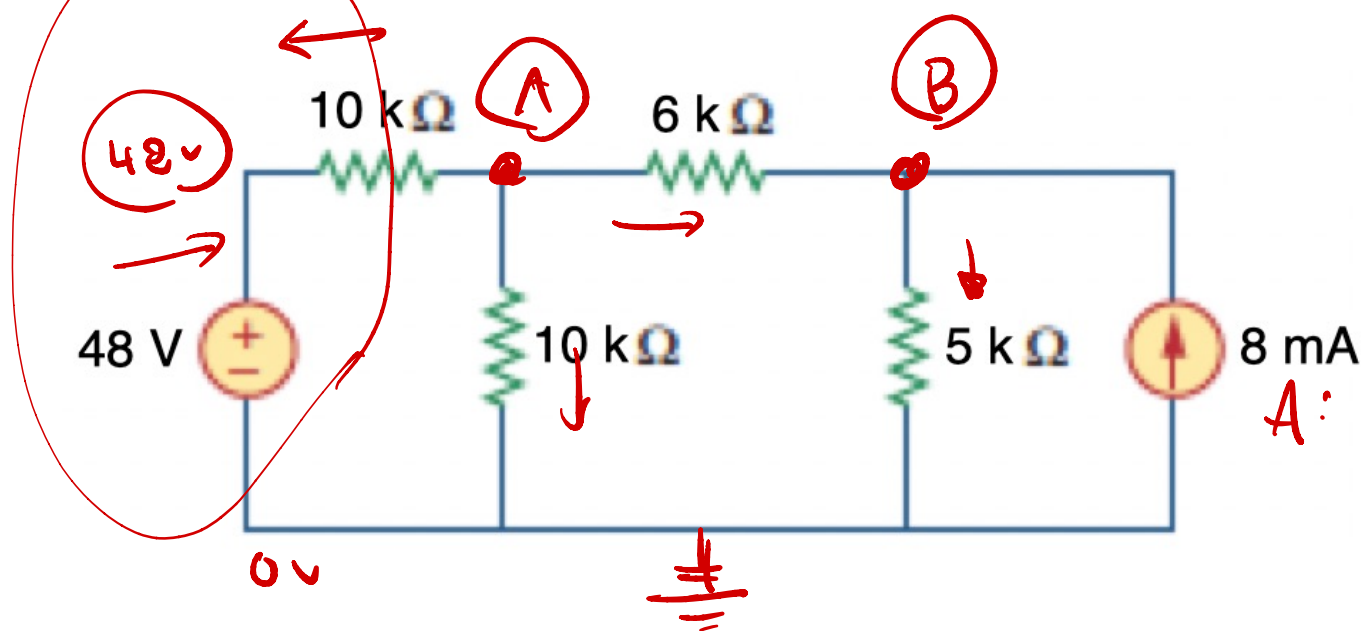

$$B: \frac{B}{5000} + \frac{B-A}{6000} - 0.008 = 0$$

$$A: \frac{A-B}{6000} + \frac{A}{10000}$$

$$\frac{A-48}{10000}$$

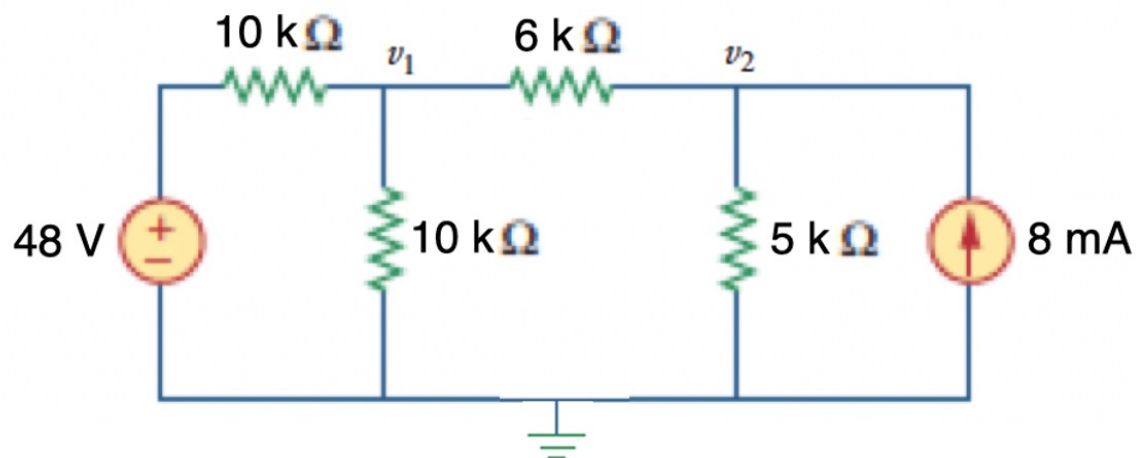

$$\frac{v_1}{10k} + \frac{v_1 - 48}{10k} + \frac{v_1 - v_2}{6k} = 0$$

$$\frac{v_2}{5k} + \frac{v_2 - v_1}{6k} - .008 = 0$$


$$3v_1 + 3v_1 + 5v_1 - 5v_2 = 144$$

$$6v_2 + 5v_2 - 5v_1 = 240$$

$$11v_1 - 5v_2 = 288 \Rightarrow v_1 = 29 V$$

$$-5v_1 + 11v_2 = 240 \Rightarrow v_2 = 35 V$$

Example

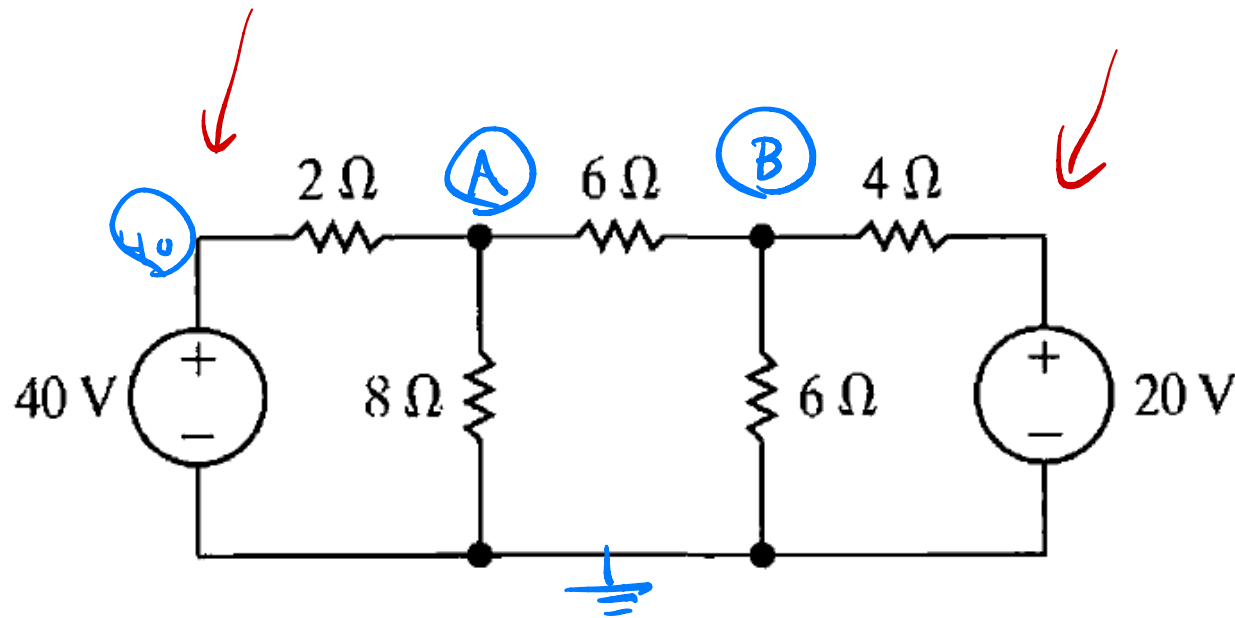

1 - 126el

2 - KCL

$$\begin{aligned} A: \quad \frac{A}{8} + \frac{A-B}{6} + \frac{A-40}{2} &= 0 \quad \left. \vphantom{\frac{A}{8} + \frac{A-B}{6} + \frac{A-40}{2}} \right\} 24 \\ B: \quad \frac{B}{6} + \frac{B-A}{6} + \frac{B-20}{4} &= 0 \quad \left. \vphantom{\frac{B}{6} + \frac{B-A}{6} + \frac{B-20}{4}} \right\} 12 \end{aligned}$$


$$3A + 4A - 4B + 12A - 480 = 0$$

$$19A - 4B = 480$$

$$2B + 2B - 2A + 3B - 60 = 0$$

$$-2A + 7B = 60$$
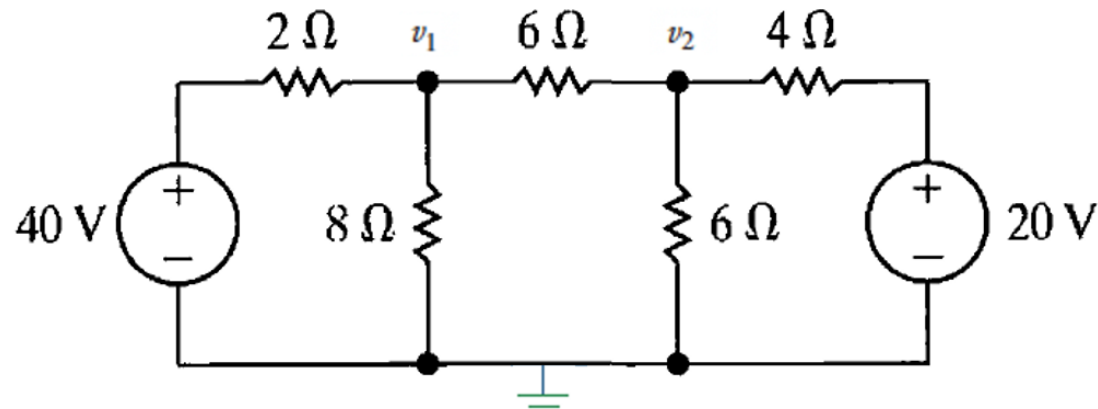
$$A = \frac{\begin{vmatrix} 480 & -4 \\ 60 & 7 \end{vmatrix}}{\begin{vmatrix} 19 & -4 \\ -2 & 7 \end{vmatrix}} = \frac{3600}{125} = 28.8$$



$$\frac{v_1}{8} + \frac{v_1 - 40}{2} + \frac{v_1 - v_2}{6} = 0$$

$$\frac{v_2}{6} + \frac{v_2 - v_1}{6} + \frac{v_2 - 20}{4} = 0$$

$$3v_1 + 12v_1 + 4v_1 - 4v_2 = 480$$


$$2v_2 + 2v_2 - 2v_1 + 3v_2 = 60$$


$$\begin{aligned} 19v_1 - 4v_2 &= 480 \\ -2v_1 + 7v_2 &= 60 \end{aligned} \Rightarrow \begin{aligned} v_1 &= 27.5 \text{ V} \\ v_2 &= 10.4 \text{ V} \end{aligned}$$

fixed

*28.8
16.8*

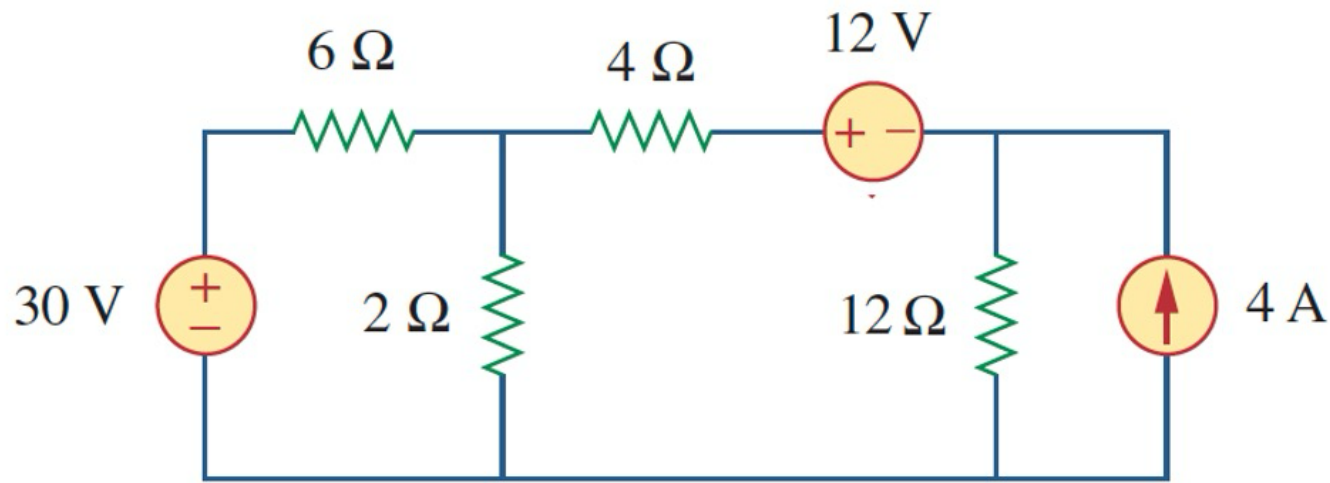Example: find the power of the current source



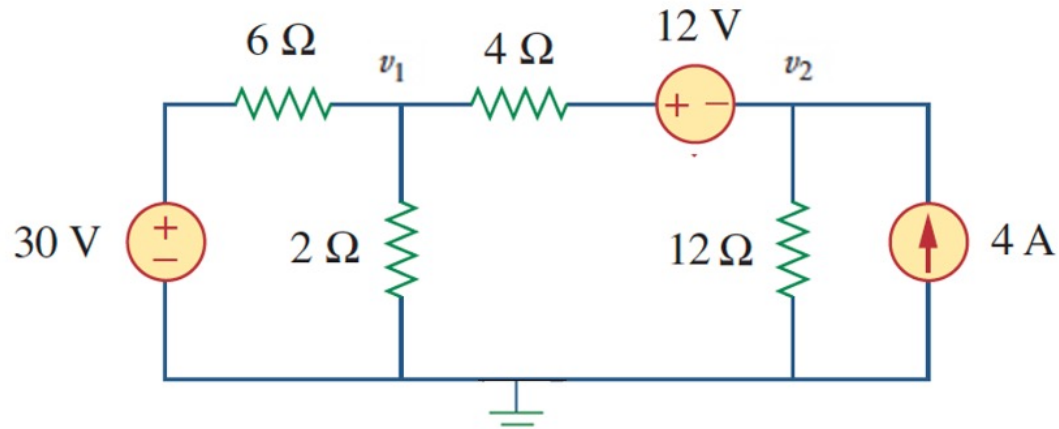

$$\frac{v_1}{2} + \frac{v_1 - 30}{6} + \frac{v_1 - v_2 - 12}{4} = 0$$

$$\frac{v_2}{12} + \frac{v_2 + 12 - v_1}{4} \text{ ~~12~~ } - 4 = 0$$


$$P = (-4 \text{ A}) * (12 \text{ V}) = -48 \text{ W}$$

$$\begin{aligned} 6v_1 + 2v_1 + 3v_1 - 3v_2 &= 60 + 36 \\ v_2 + 3v_2 - 3v_1 &= -36 \text{ } + 48 \end{aligned}$$

$$\begin{aligned} 11v_1 - 3v_2 &= 96 \\ -3v_1 + 4v_2 &= \text{~~-64~~ } 12 \end{aligned} \Rightarrow \begin{aligned} v_1 &= 12 \text{ V} \\ v_2 &= 12 \text{ V} \end{aligned}$$

15 V

Example: find v

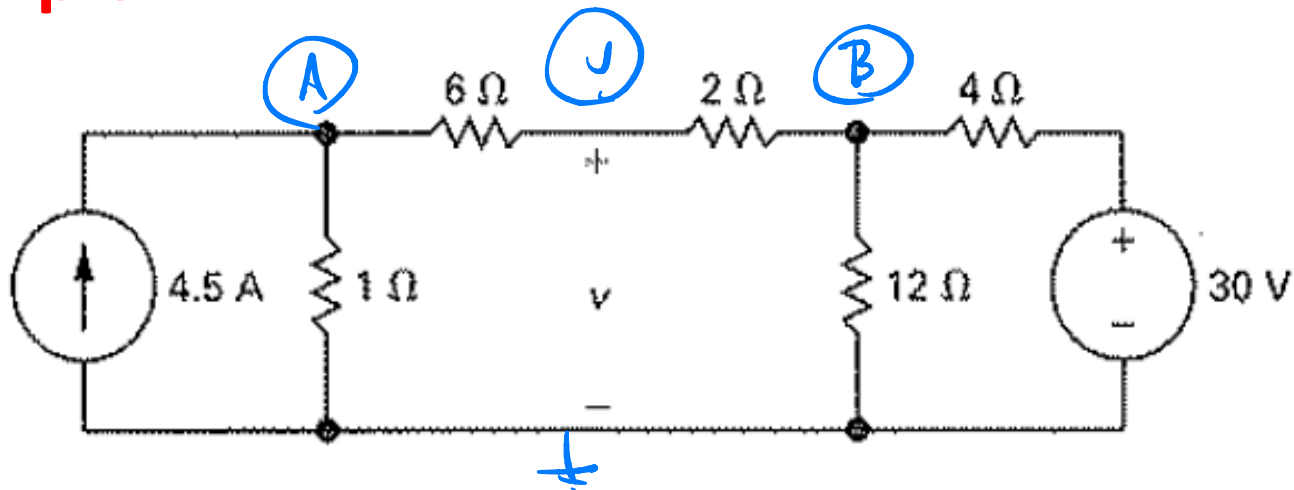

$$\frac{A}{1} - 4.5 + \frac{A-v}{6} = 0$$

$$\frac{B}{12} + \frac{B-30}{4} + \frac{B-v}{2} = 0$$


$$\frac{v-A}{6} + \frac{v-B}{2} = 0$$

$$A\left(\frac{7}{6}\right) - v\left(\frac{1}{6}\right) - 4.5 - v\left(\frac{1}{2}\right) B\left(\frac{1}{12} + \frac{1}{4} + \frac{1}{2}\right) = \frac{30}{4}$$

$$A\left(-\frac{1}{6}\right) + v\left(\frac{1}{6} + \frac{1}{2}\right) - B\left(\frac{1}{2}\right) = 0$$


40 V

Practice problem: find V_o

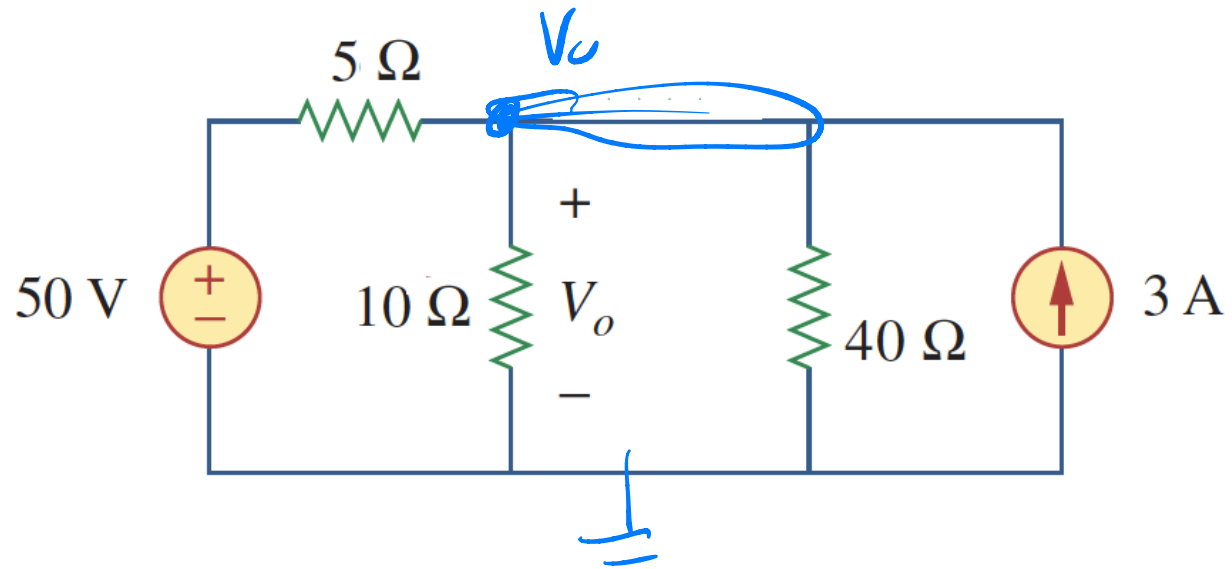


$$v_T = 40\text{ V}, v_M = 30\text{ V}$$

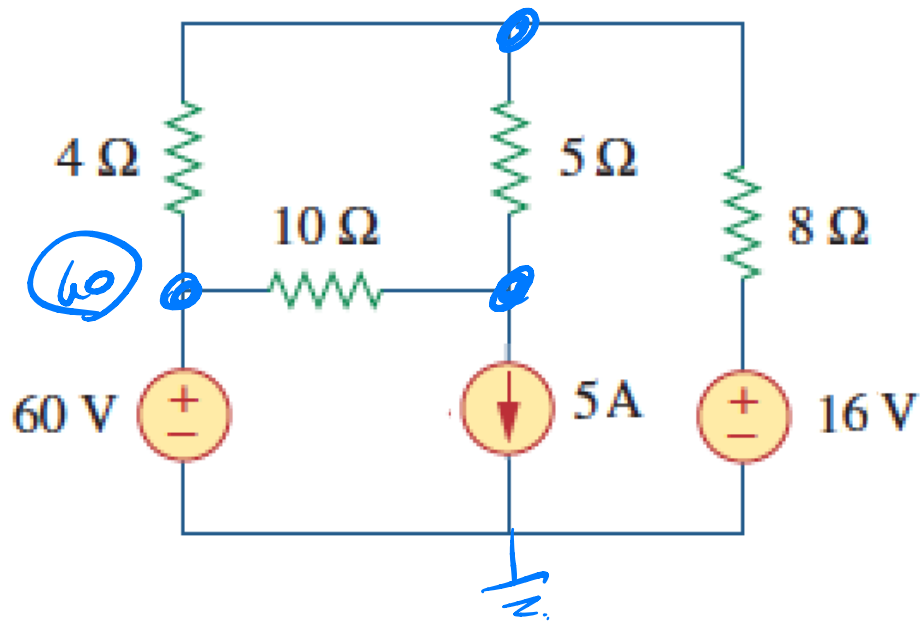Practice problem: find the node voltages to the top and bottom of the $5\ \Omega$ resistor relative to the bottom



-26 A

Practice problem: find i_o

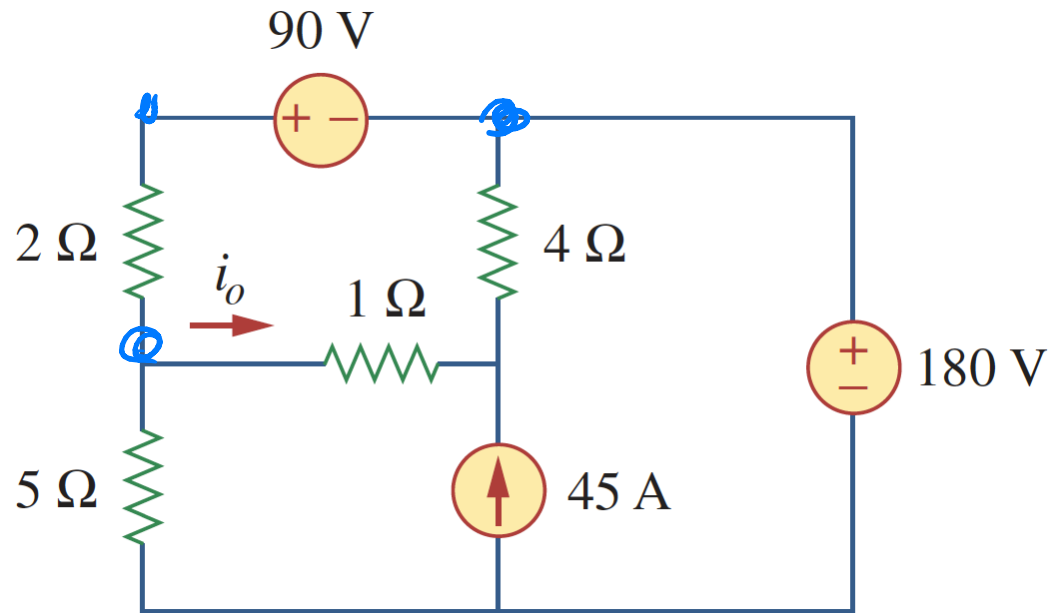

-26 A

Practice problem: find i_o

