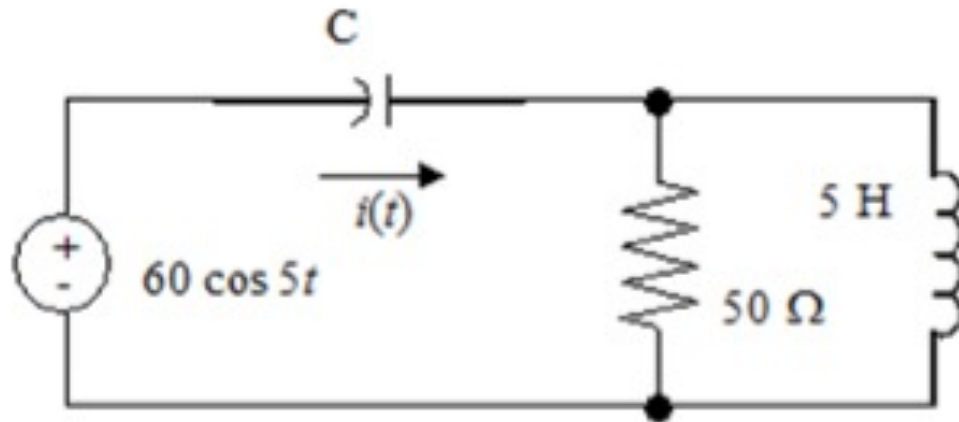


Lecture 23

Phasors – 9 of 9

design examples


Example: Find C so that the magnitude of $i(t)$ is 4 amps.





```

om = 5;
R = 50;
L = 5;
ZL = 1j*om*L;
C = logspace(-9,0,1000);
ZC = 1./(1j*om*C);
Z = ZC + 50*ZL/(50+ZL);
I = 60./Z;


```

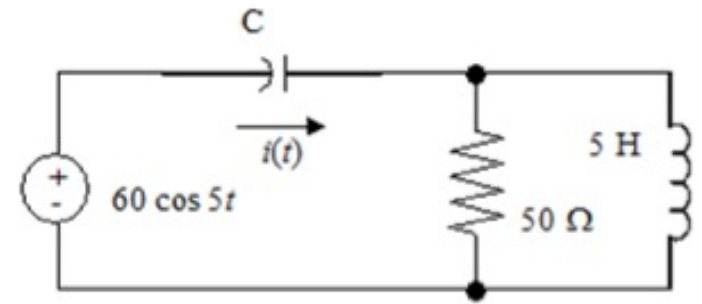

$|I| = 4$ occurs in two spots !!

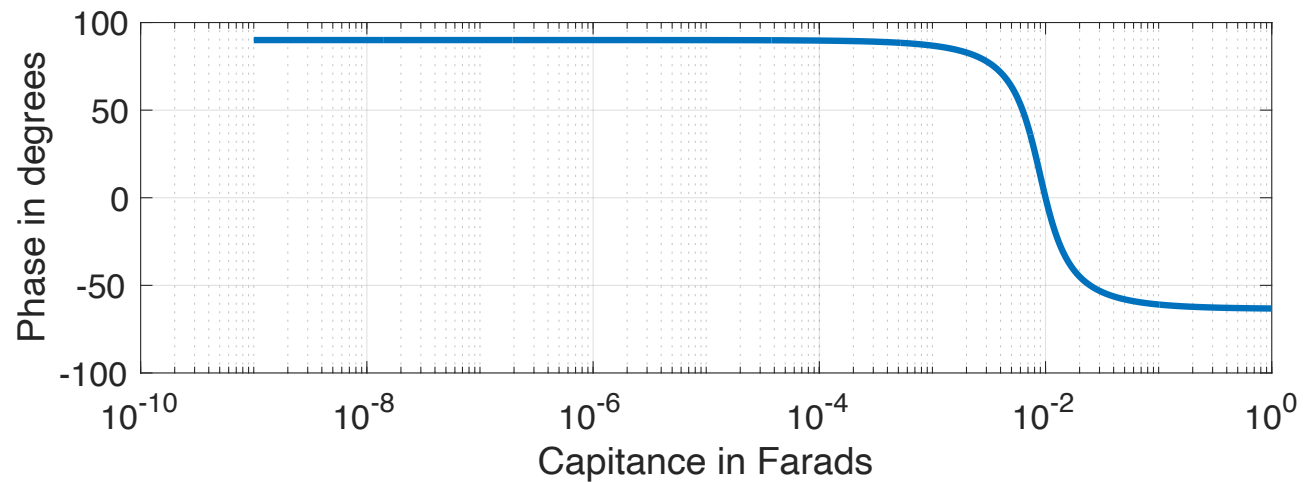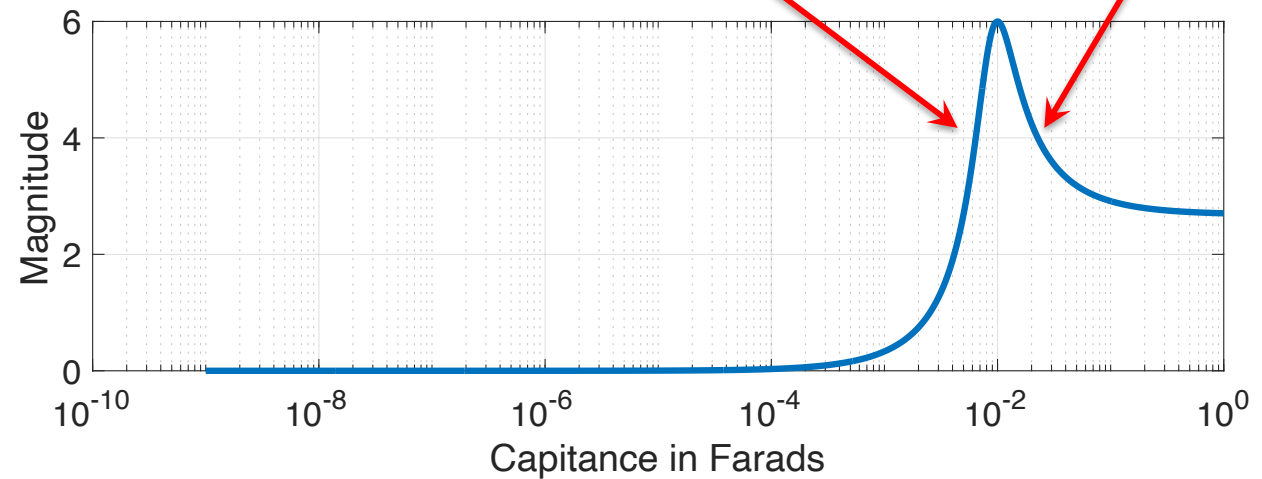



Let's actually solve for C

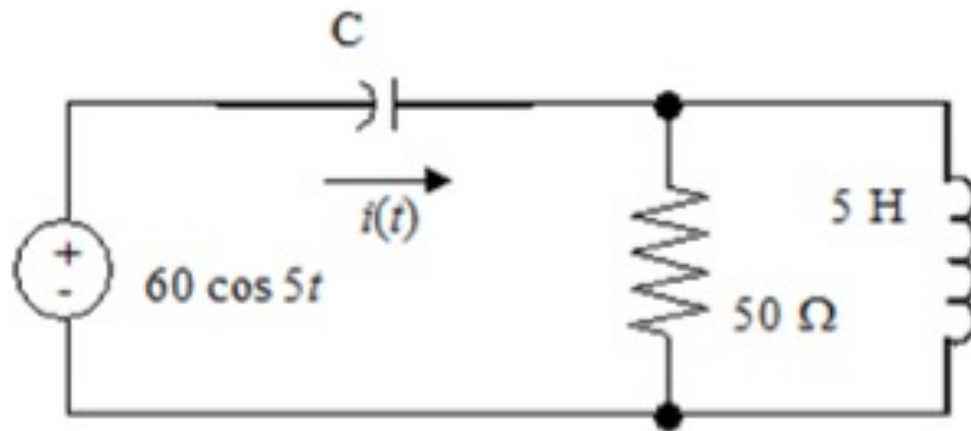

6.4 mF; 22.7 mF


Example: The circuit shown is a low pass filter meaning that it passes lower frequency sinusoids and attenuates higher frequency sinusoids. Find a value for the capacitor C so that all sinusoids above 1000 Hz in frequency are attenuated by at least 90% (i.e. their amplitude scaling, $|V_o/V_s|$, is at most 0.1). Using your result what happens to a 60 Hz signal? How is its amplitude changed? How is its phase angle changed?

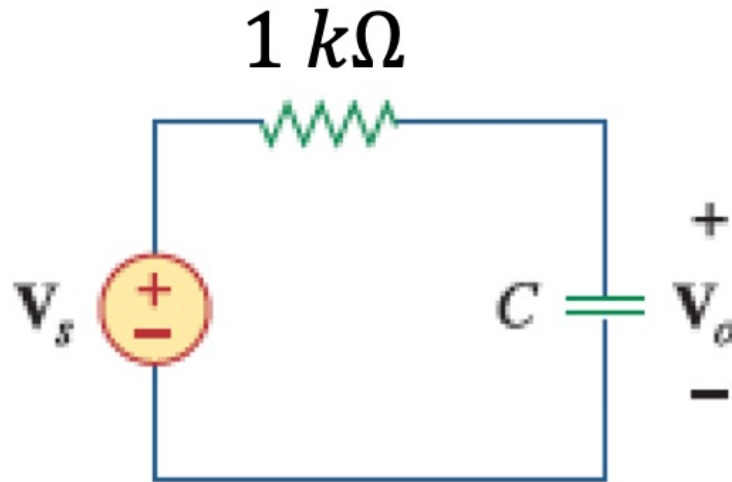

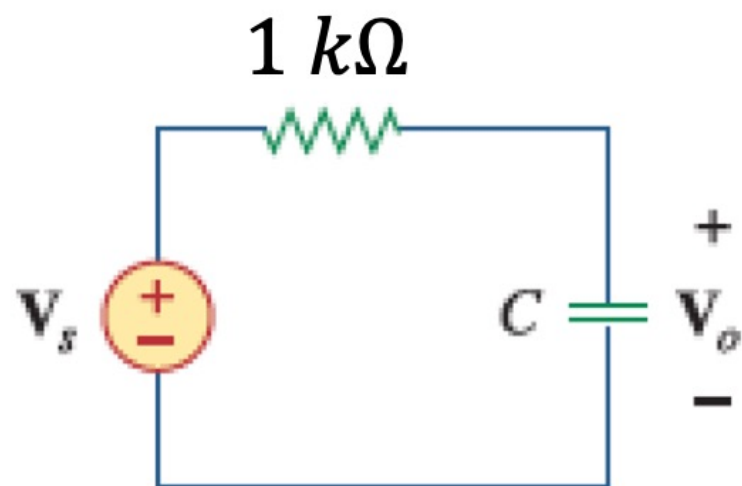


$1.58\text{ }\mu\text{F}; 85.9\text{ }%; -20.8^\circ$

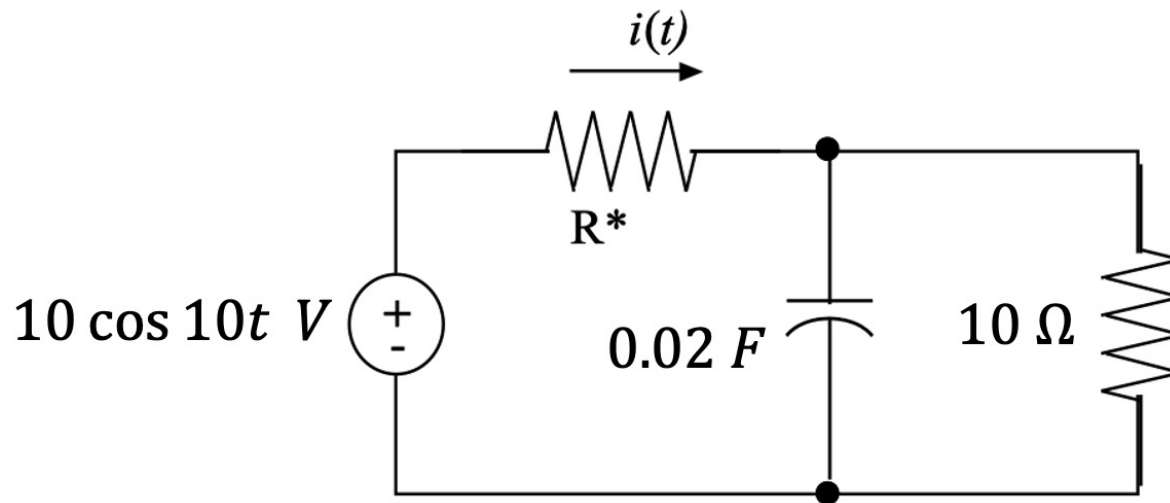Example: Find the resistor R^* so that the magnitude of the current $i(t)$ is 1 A.




97.9 Ω

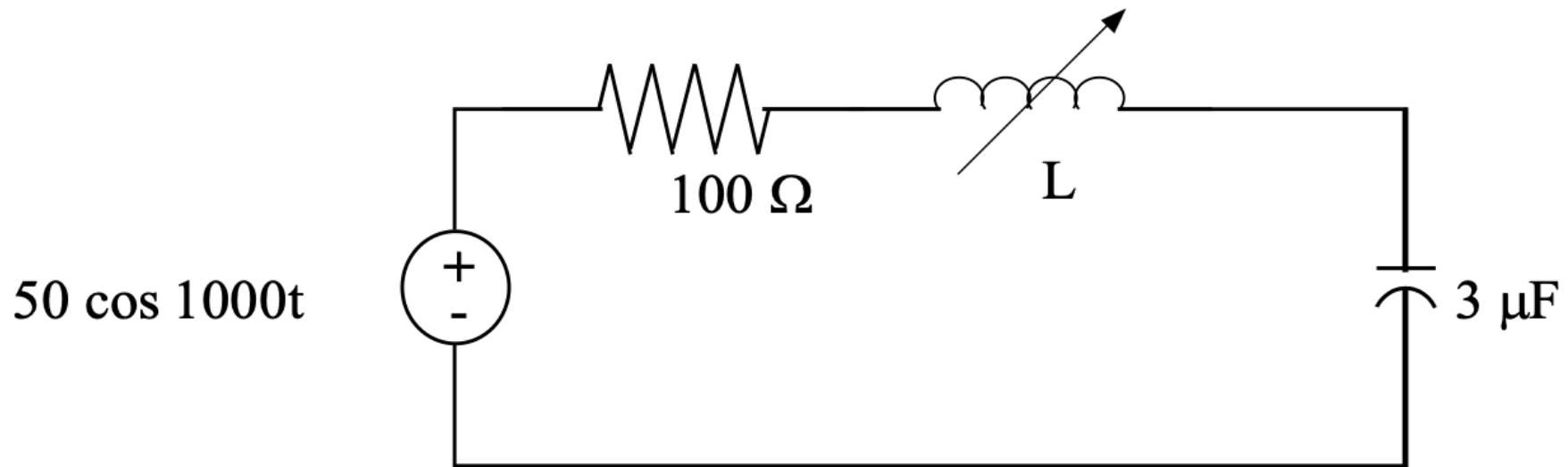Example: Find the inductor value to maximize the magnitude of the voltage appearing across the capacitor. What is that magnitude?



$$\frac{1}{3}H, \frac{10}{3}V$$

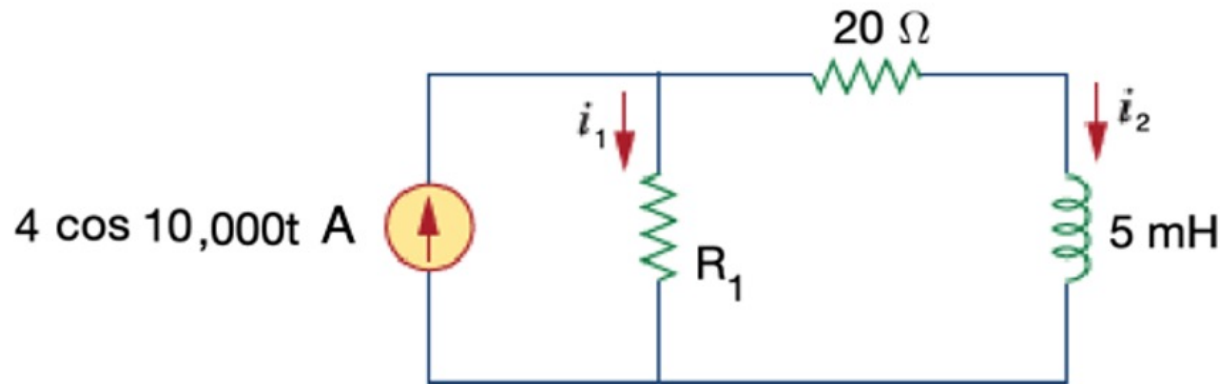
Example: what value for resistor R_1 results in the two currents, i_1 and i_2 , having the same magnitude (but might be different phase angles)? What is that magnitude?



53.9 Ω ; 2.42 A

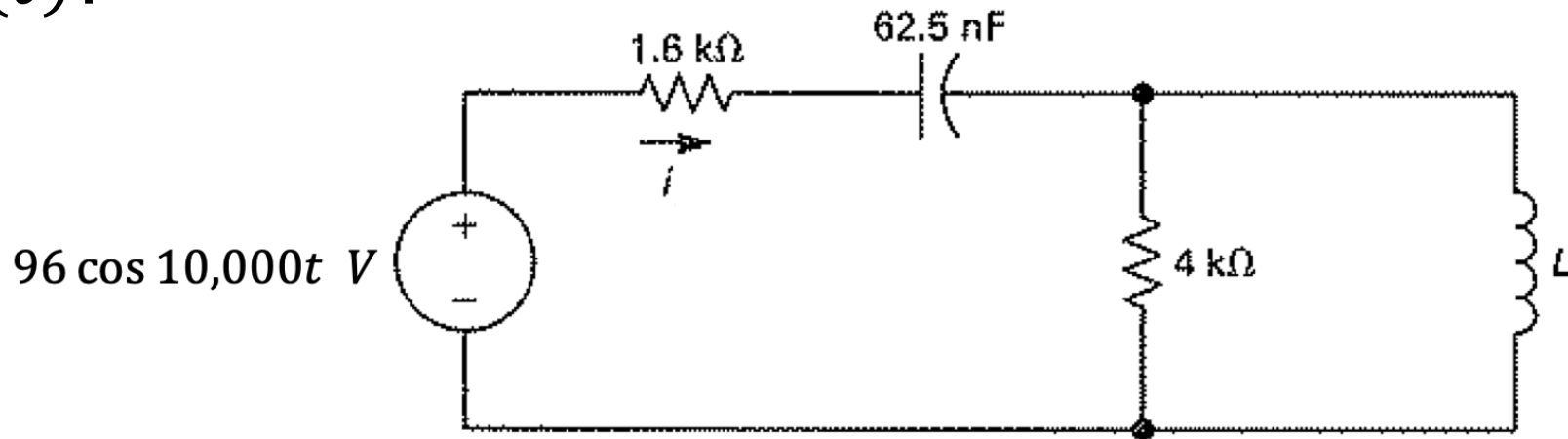
53.9 Ω ; 2.42 A

Practice problem: find the inductor value so that the current i is “in phase” with the voltage source. What is $i(t)$?




$0.8 \text{ H}, 20 \cos(10,000t) \text{ mA}; 0.2 \text{ H}, 405 \cos(10,000t) \text{ mA}$

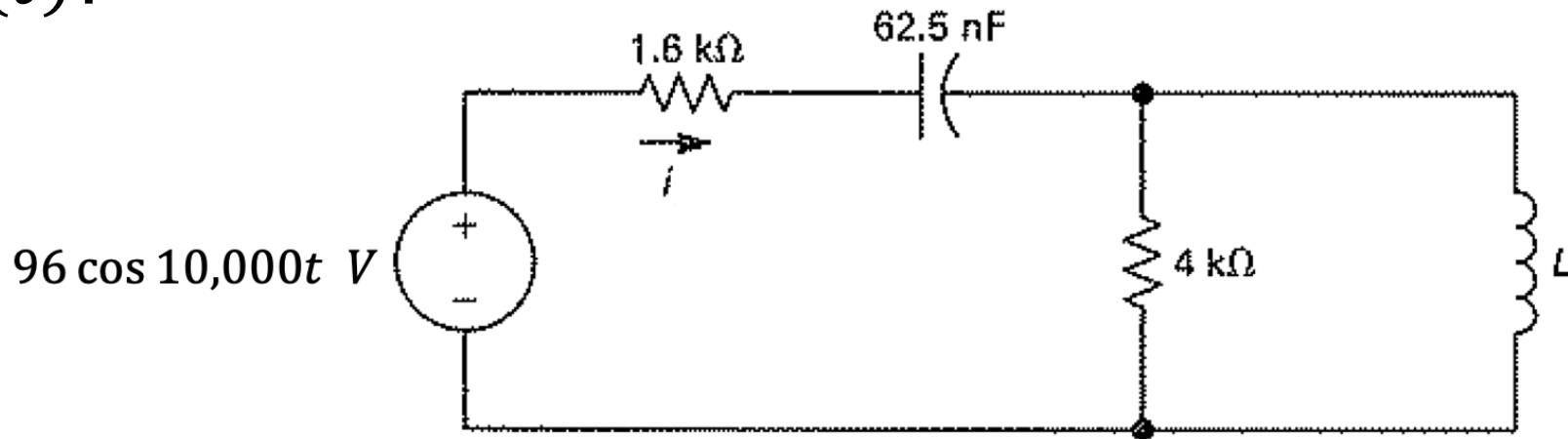Practice problem: find the inductor value so that the current i is “in phase” with the voltage source. What is $i(t)$?



$0.8 \text{ H}, 20 \cos(10,000t) \text{ mA}; 0.2 \text{ H}, 405 \cos(10,000t) \text{ mA}$

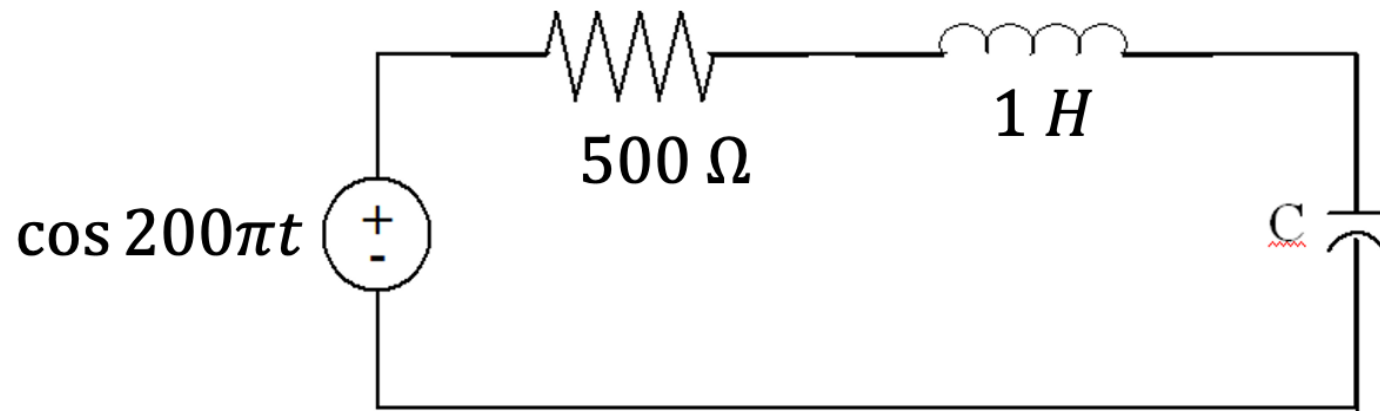Practice problem: find the capacitor value to maximize the magnitude of the voltage appearing across the capacitor. What is that magnitude?



$1.55\ \mu F, 1.61\ V$