



# Lecture 12

## Node Analysis – 5 of 7


supernodes

## Extension #4 – multiple V-only branches


- There might be an obvious solution

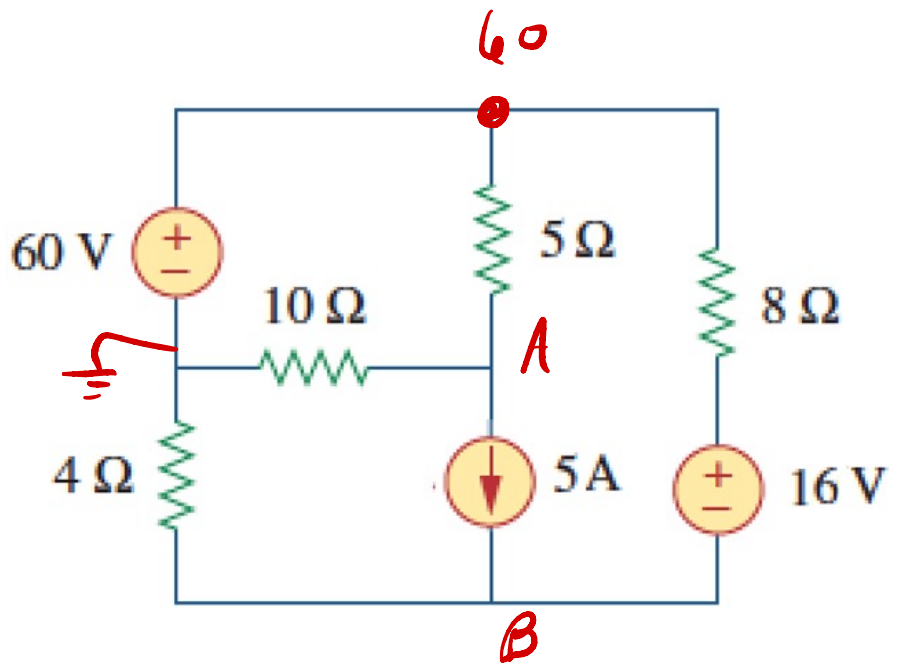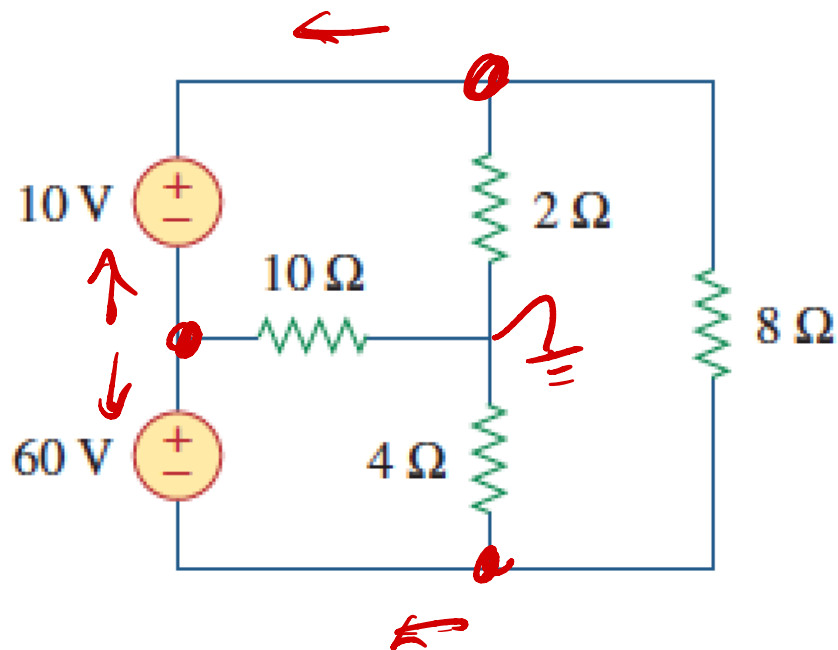


But sometimes ??

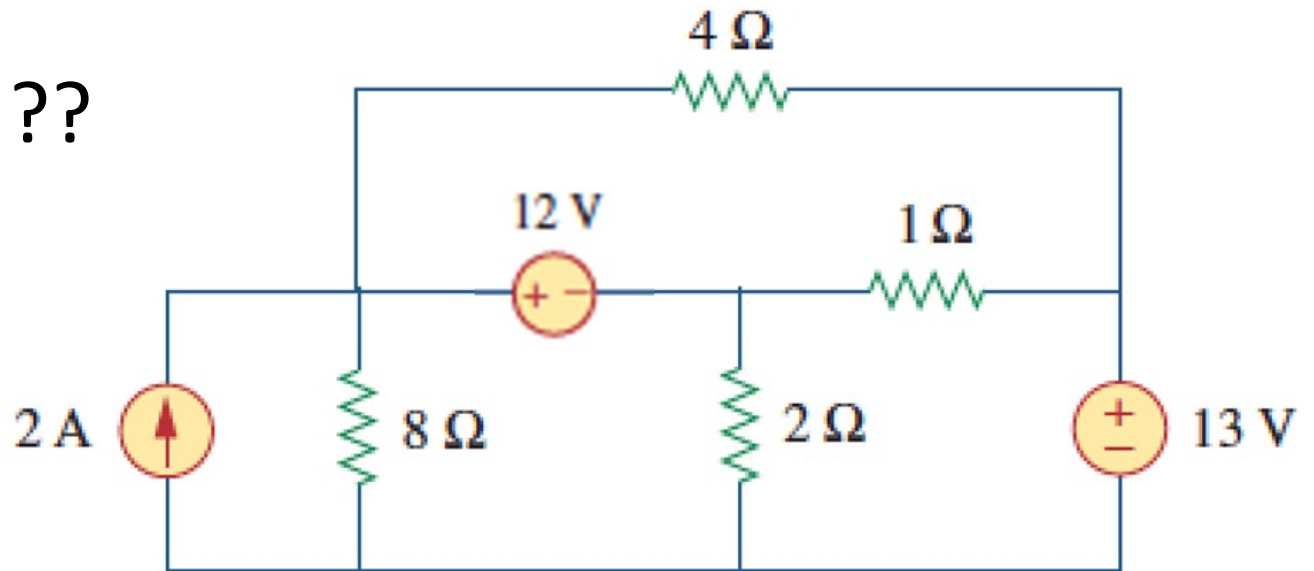

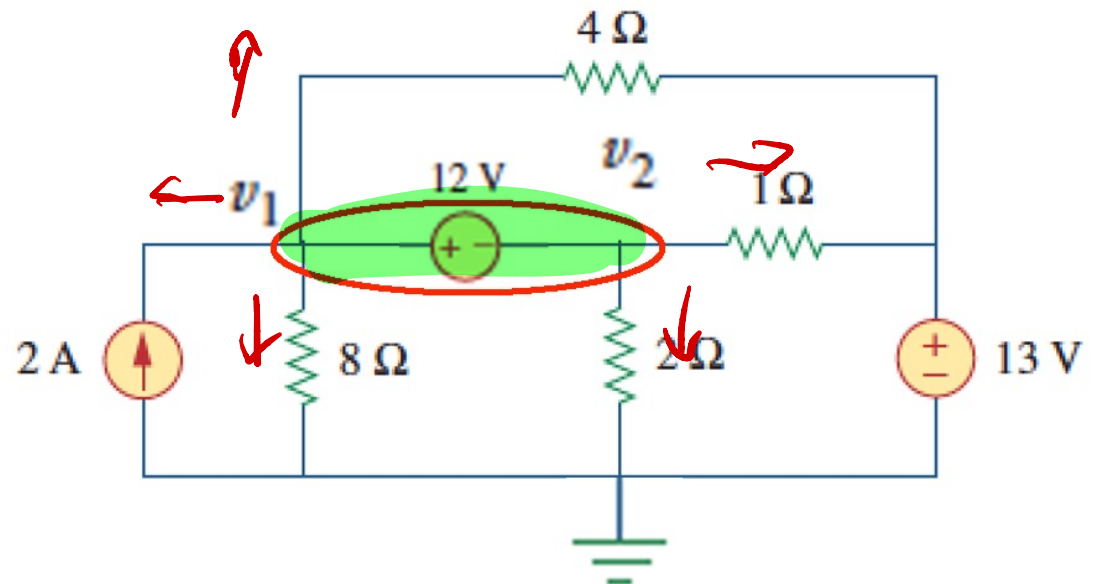
- Define a “supernode” (a cutset)
- Apply KCL on it
- Relate the voltages across it



Example (details on next slide)

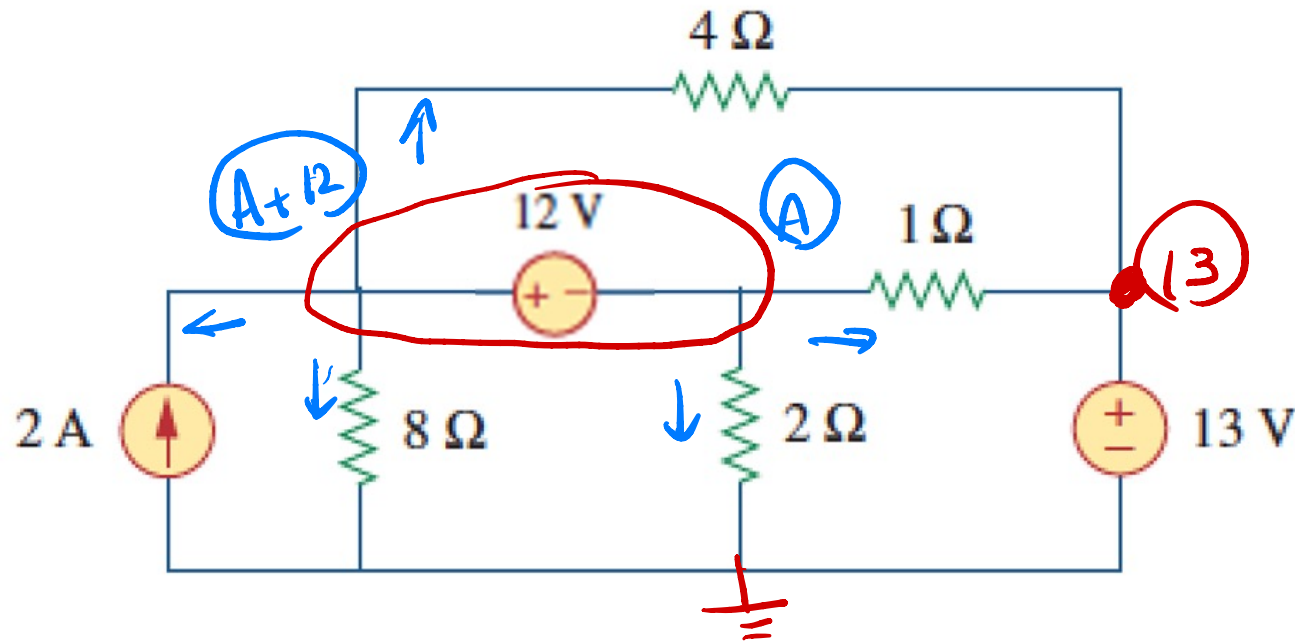
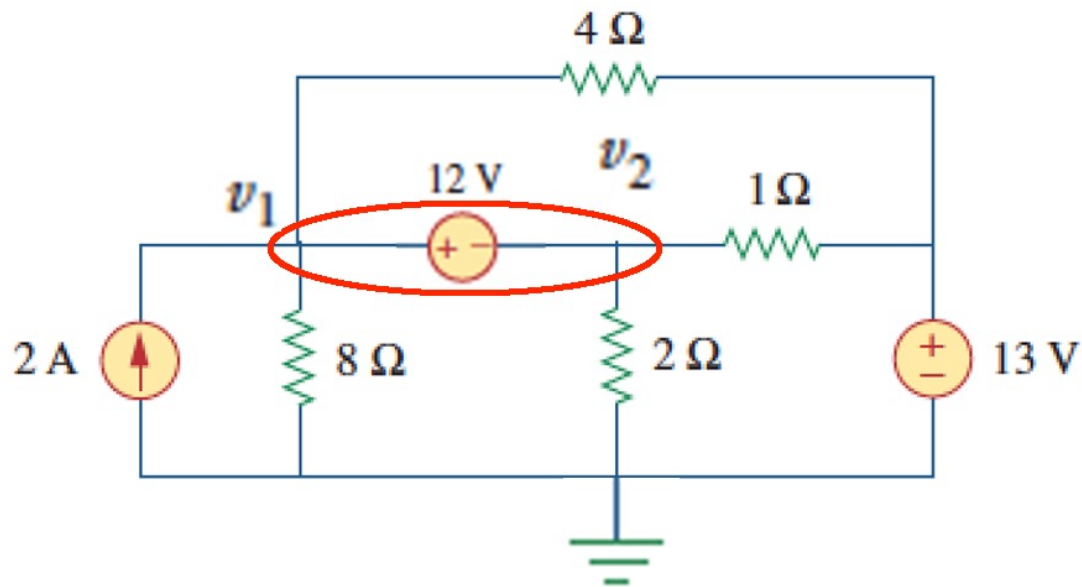
$$-2 + \frac{A+12}{8} + \frac{A}{2} + \frac{A-13}{1} + \frac{A+12-13}{4} = 0$$



Relate nodes:

$$v_2 = v_1 - 12$$

Node equation:

$$\frac{v_1}{8} - 2 + \frac{v_1 - 13}{4} + \frac{v_2 - 13}{1} + \frac{v_2}{2} = 0$$

$$3v_1 + 12(v_1 - 12) = 146$$

$$3v_1 + 12v_2 = 146$$

$$15v_1 = 290$$


$$v_1 = 19\frac{1}{3}$$

$$v_2 = 7\frac{1}{3}$$

**Example:** find  $i$

1- label

2- KCL

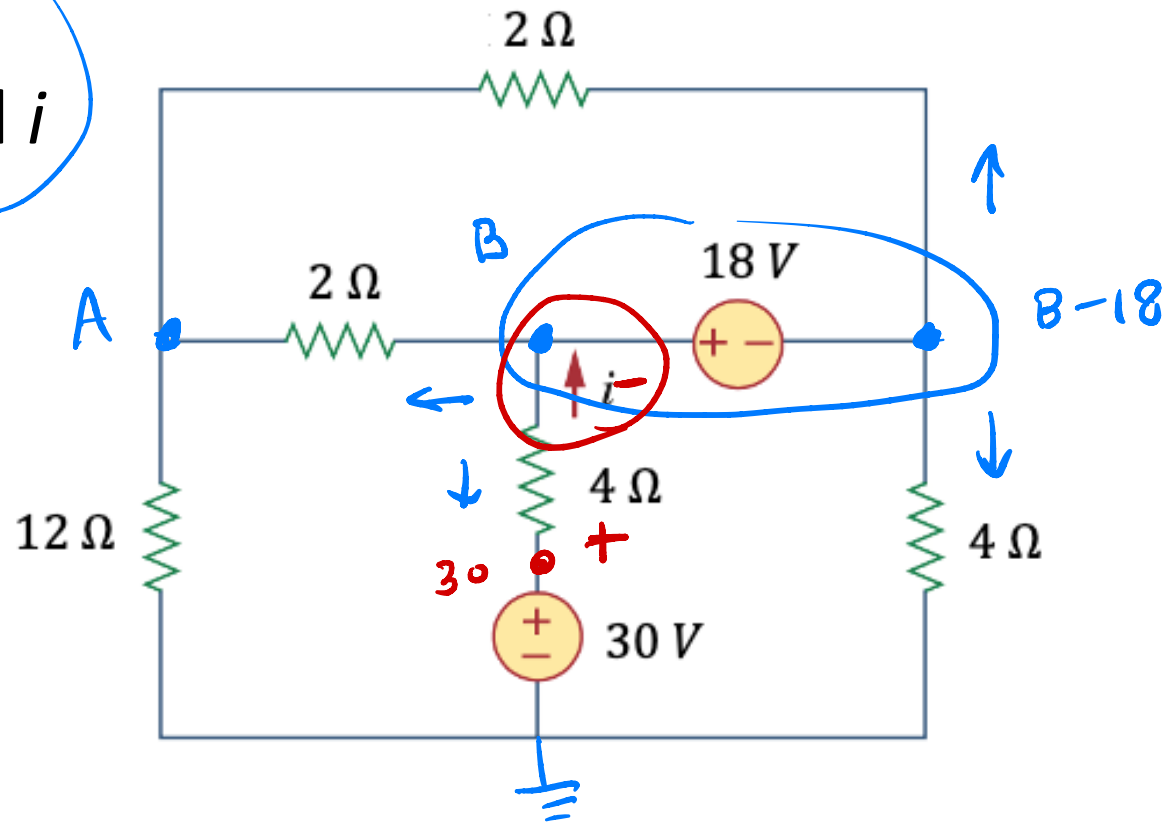


$$A: \frac{A}{12} + \frac{A-B}{2} + \frac{A-(B-18)}{2} = 0$$

$$\text{super node: } \frac{B-A}{2} + \frac{B-30}{4} + \frac{B-18-A}{2} + \frac{B-18}{4} = 0$$

3- solve for  $A, B$  ...

4-

$$i = \frac{30-B}{4}$$

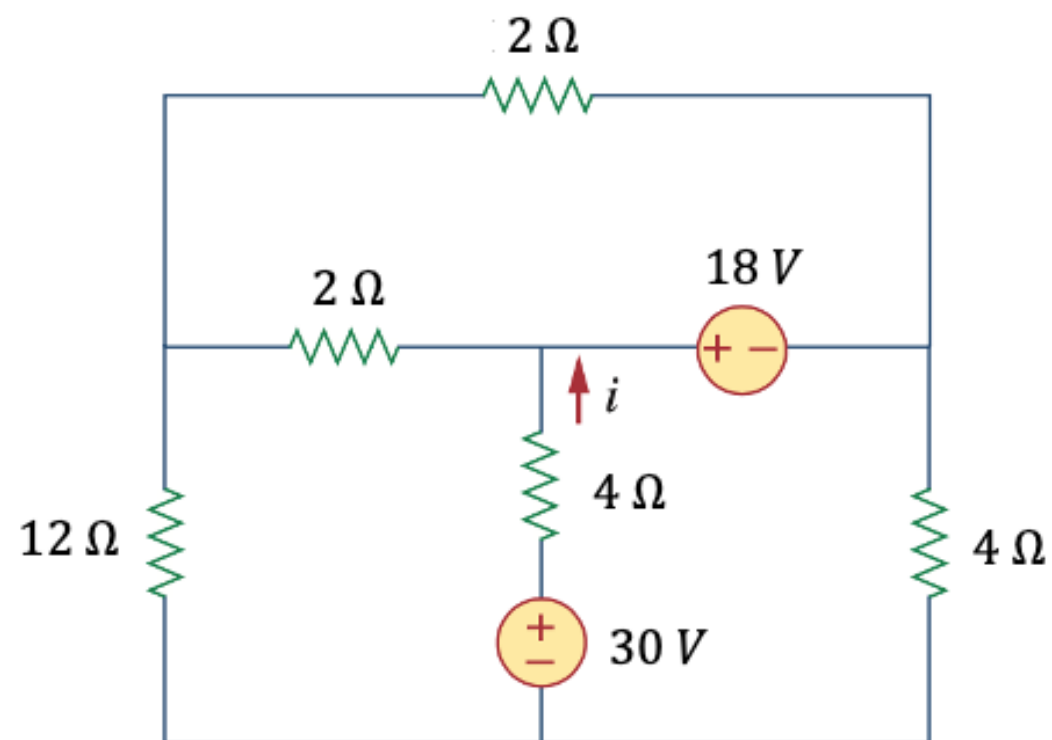

$$i = 2\text{ A}$$

**Example:** find  $v$

1- labelled


2- define  $i_0$

$$i_0 = \frac{70 - v}{4}$$


3- KCL on supernode

$$\frac{v - 2i_0 - 70}{20} + \frac{v - 2i_0}{2} + \frac{v + 50}{10} = 0$$

$$\frac{v - 70}{4} = 0$$

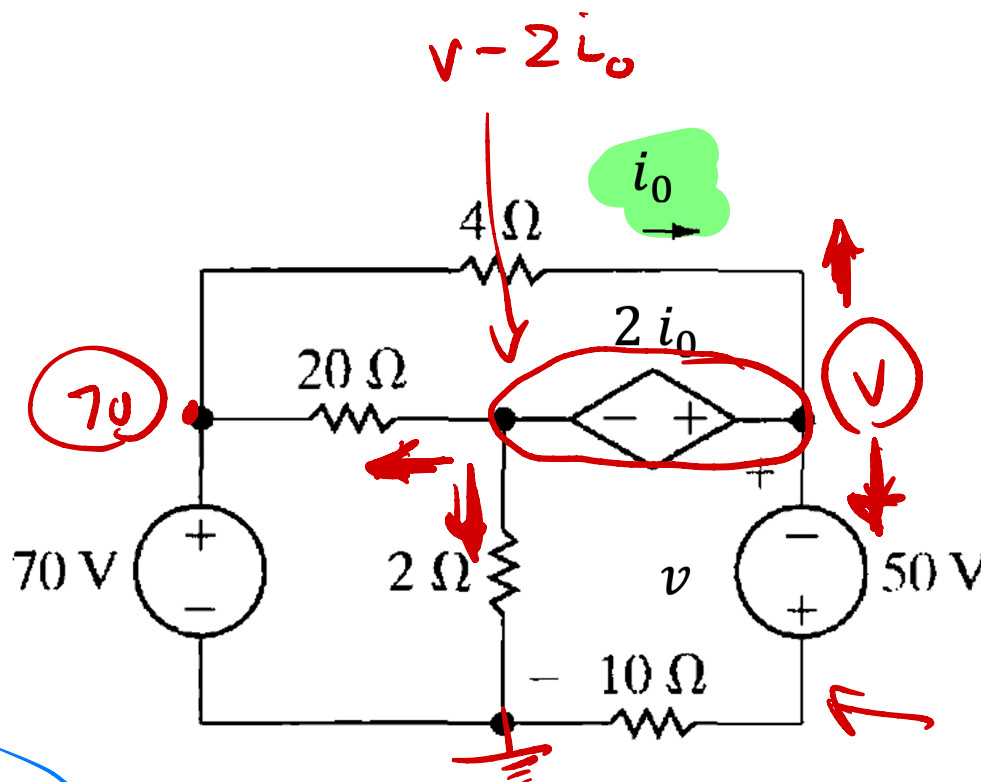



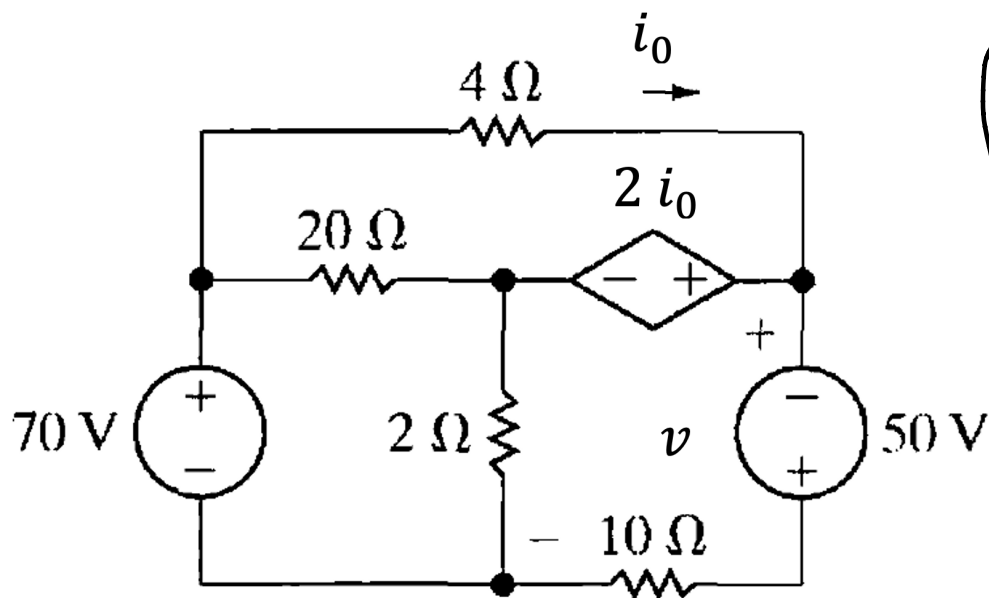

$$4i_0 + v = 70$$

$$-22i_0 + 18v = 320$$

$v = 30V$


4. solve Cramer

$$v = \frac{\begin{vmatrix} 4 & 70 \\ -22 & 320 \end{vmatrix}}{\begin{vmatrix} 4 & 1 \\ -22 & 18 \end{vmatrix}} = \frac{1280 + 1540}{72 + 22} = \frac{2820}{94}$$

$$v = \frac{2820}{94} = 30V$$


48 W

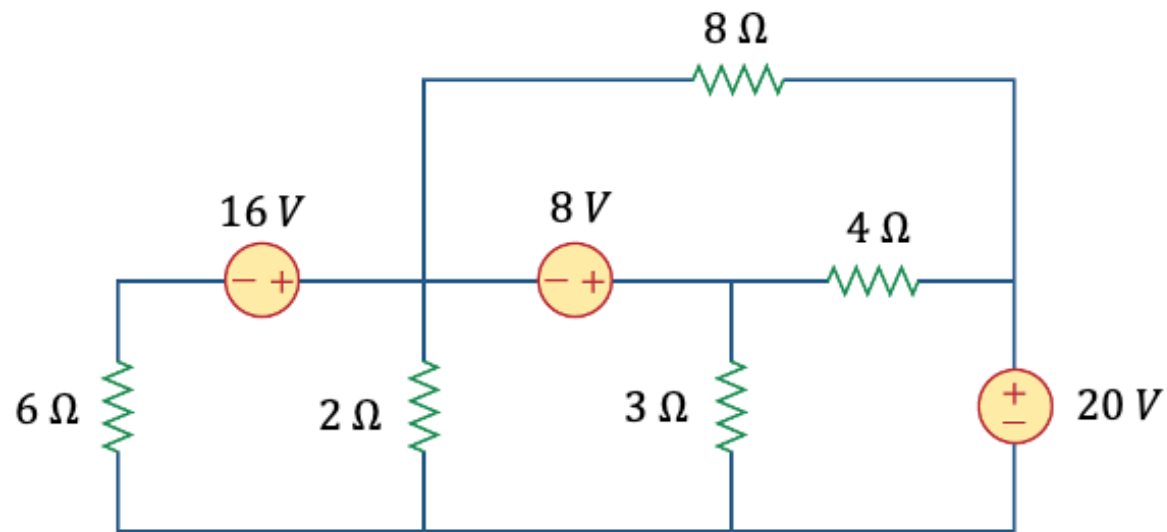**Practice problem:** find the power of the  $3\ \Omega$  resistor



$$v_o =$$

**Practice problem:** find  $v_o$

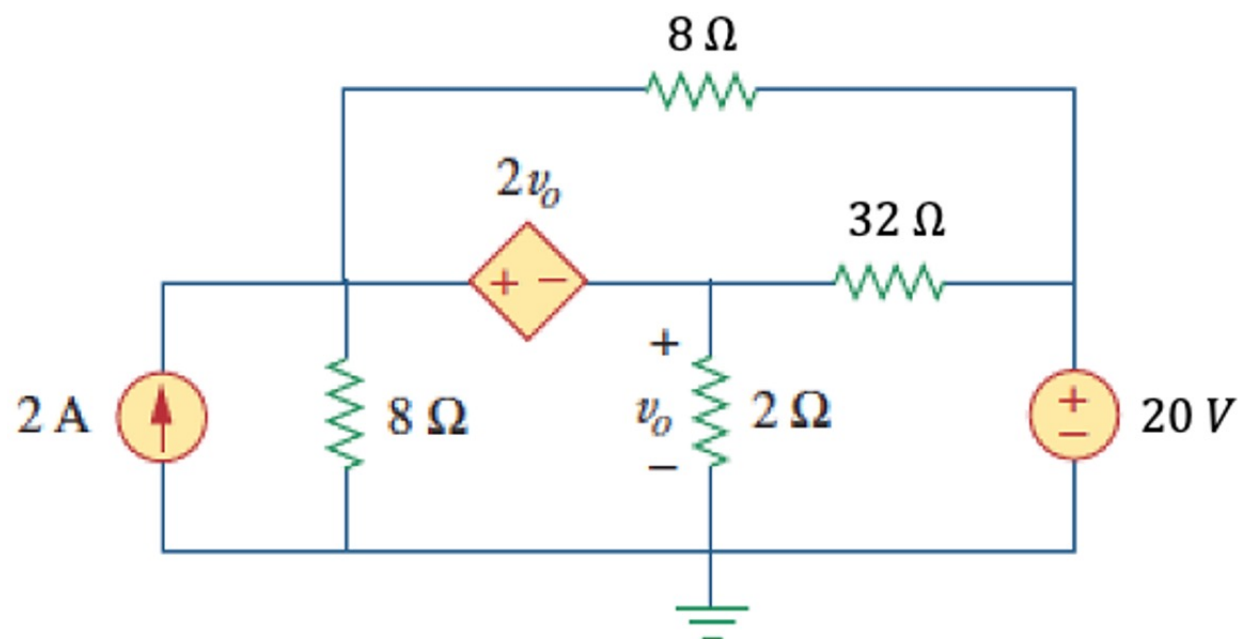

$$v_o =$$

**Practice problem :** find  $v_o$

