



Lecture 7

Basics – 7 of 7

odds and ends


Special Cases

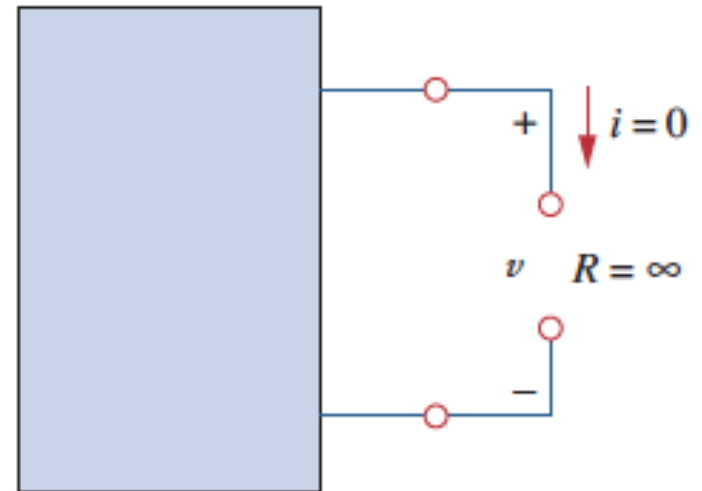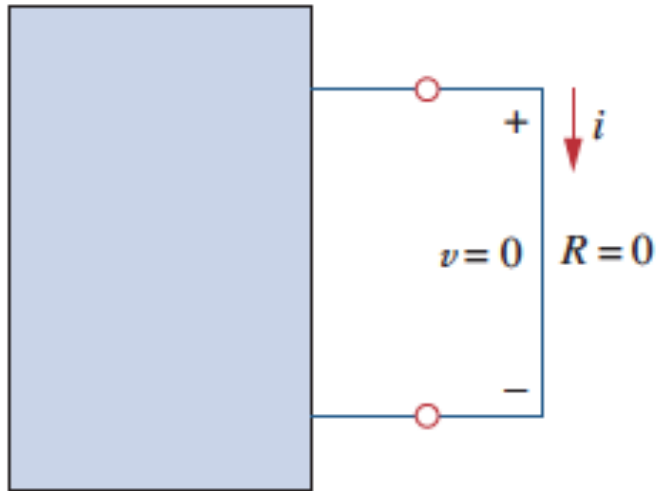- Short circuit ($R = 0$)
- Open circuit ($R = \text{infinity}$)




- Voltage division

$$v_1 = \frac{R_1}{R_1 + R_2} v$$

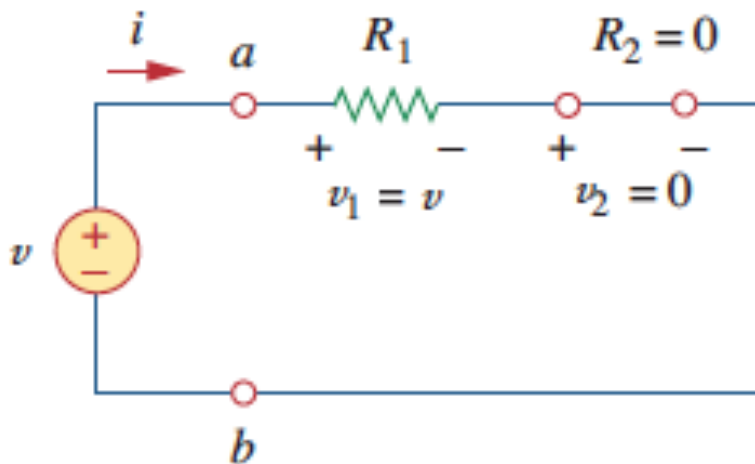



$$v_2 = \frac{R_2}{R_1 + R_2} v$$

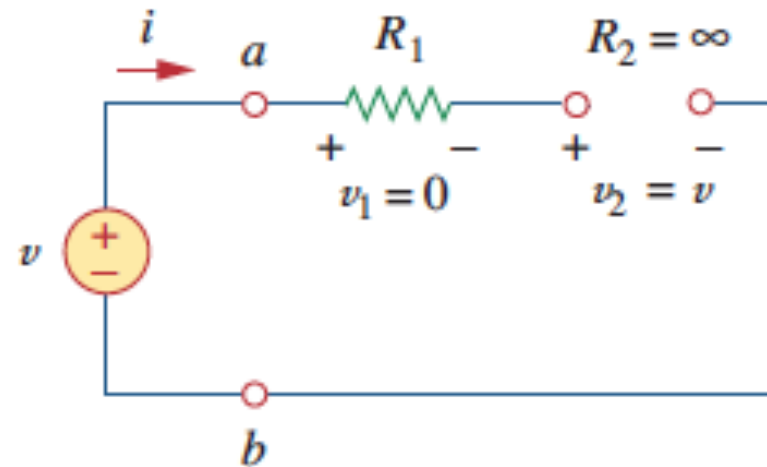

- Current division



$$i_1 = \frac{R_2}{R_1 + R_2} i$$

$$i_2 = \frac{R_1}{R_1 + R_2} i$$

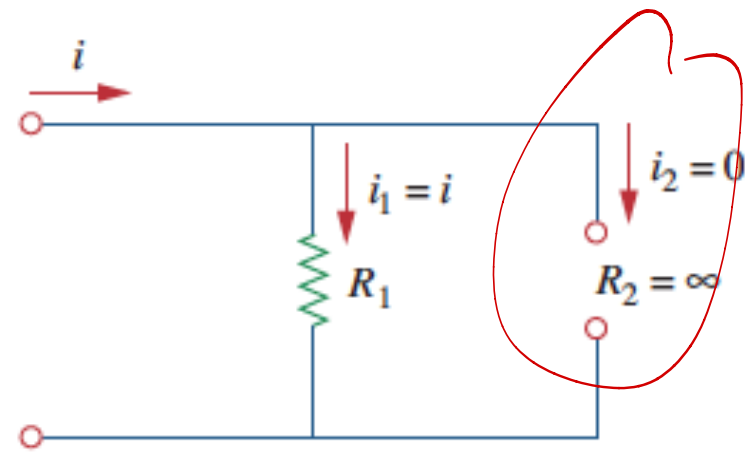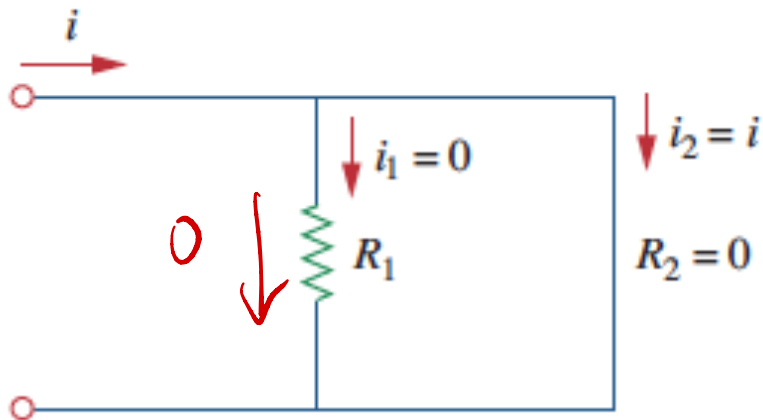


$$V_0 = -30 \text{ V}$$

Example:

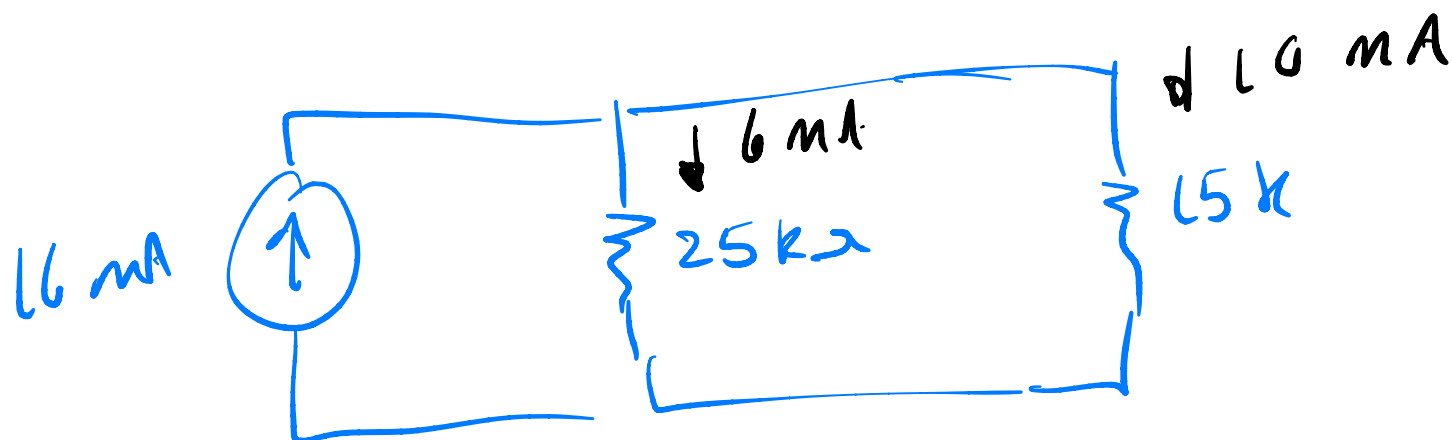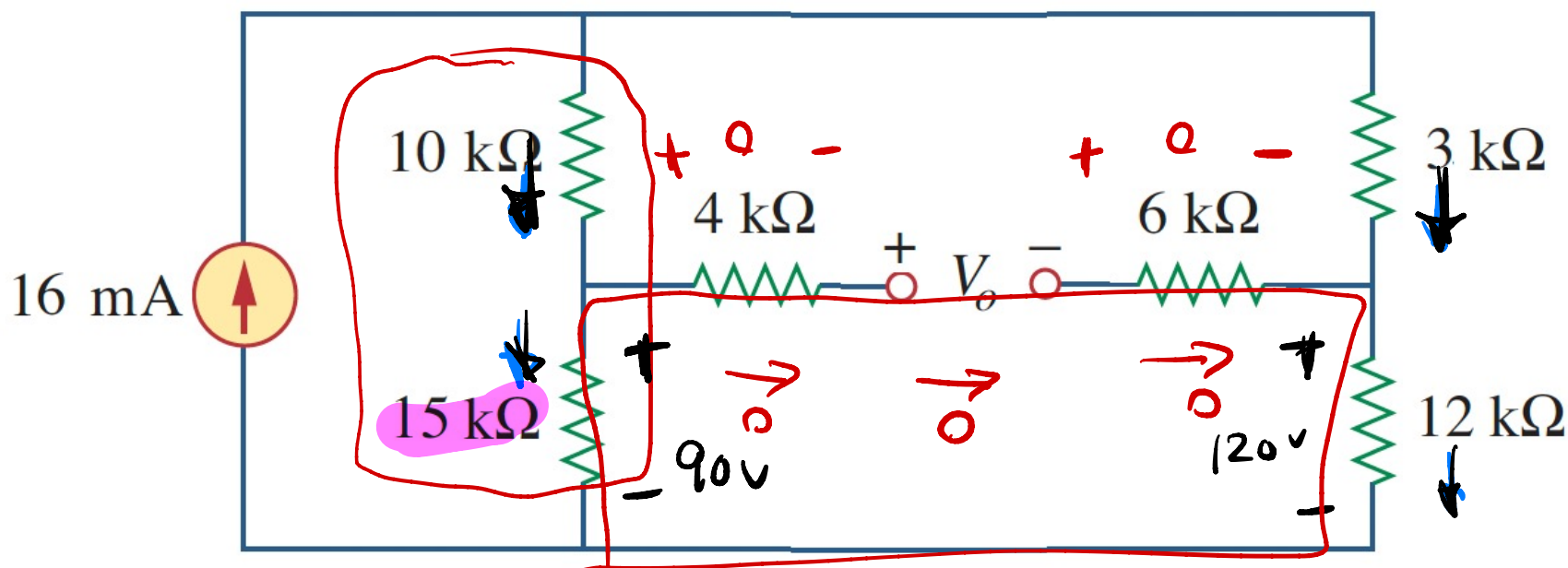

Example: find i and v

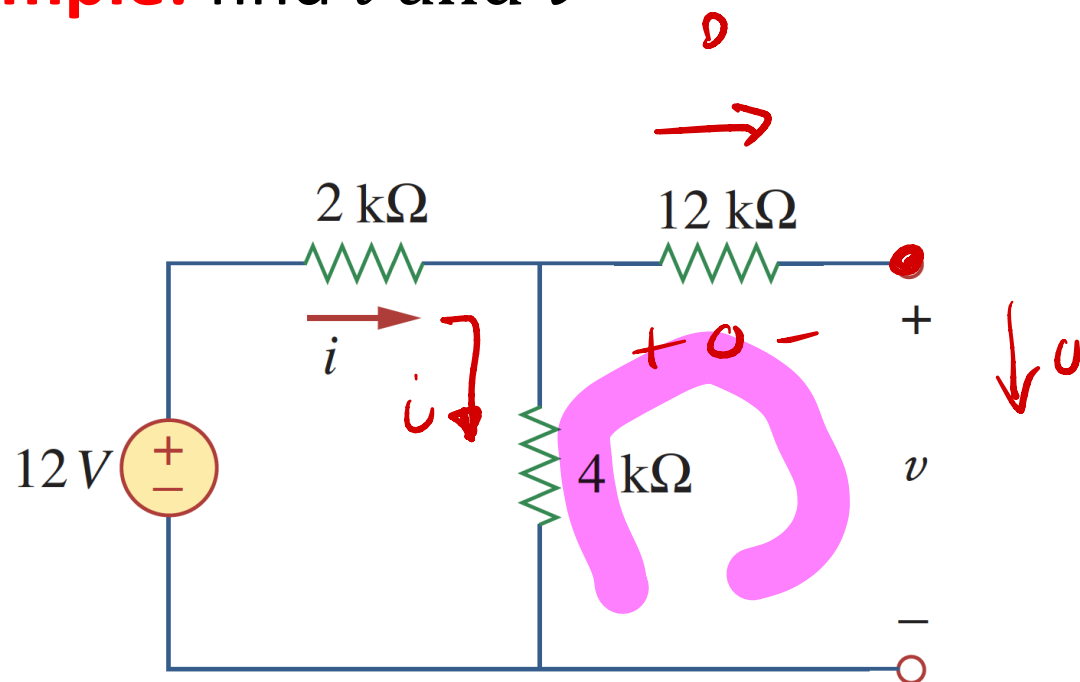


$$v = 8 \text{ V}$$

$$V_4 = \frac{4k}{4k + 2k} \cdot 12 \text{ V} = \boxed{8 \text{ V}}$$

$$i = \frac{8 \text{ V}}{4k} = \boxed{2 \text{ mA}}$$

Example: find i and v

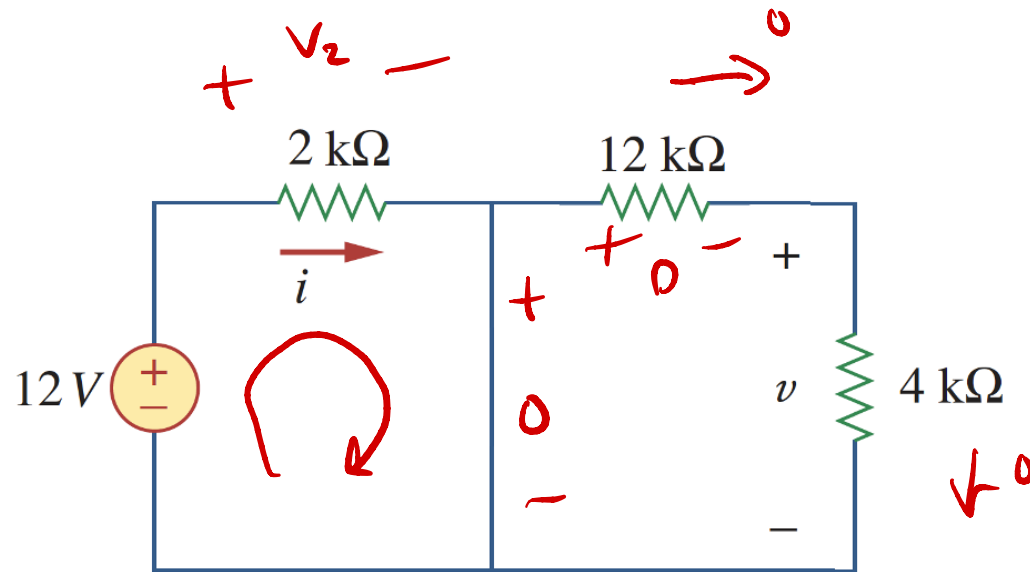

$$v = 0 \text{ volts}$$


$$v = 0$$

$$12 - V_2 - 0 = 0$$

$$12 = V_2$$




$$i = \frac{12}{2k} = 6 \text{ mA}$$

Do We Allow Series Sources?

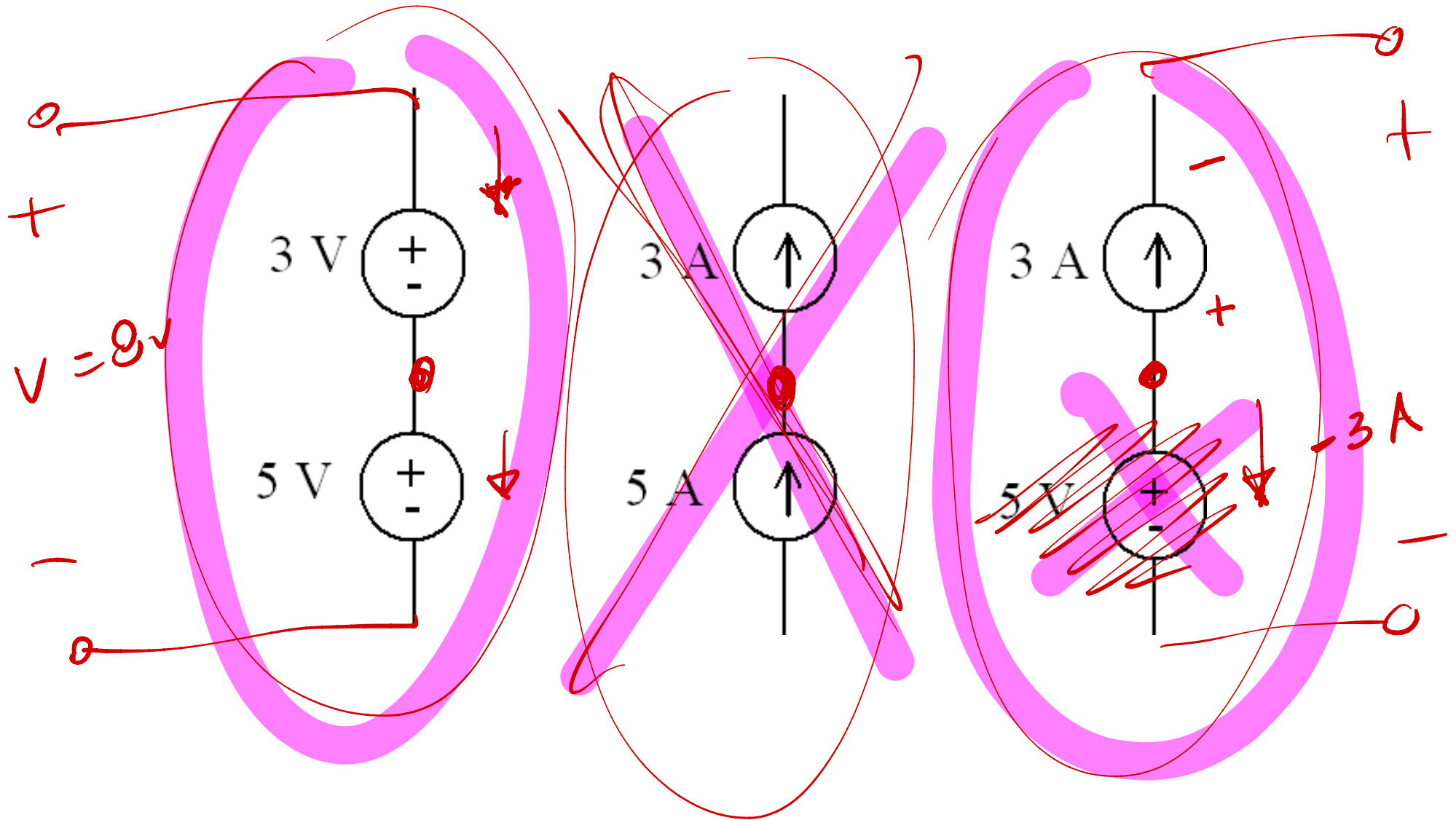



How about parallel sources?



\pm 5V

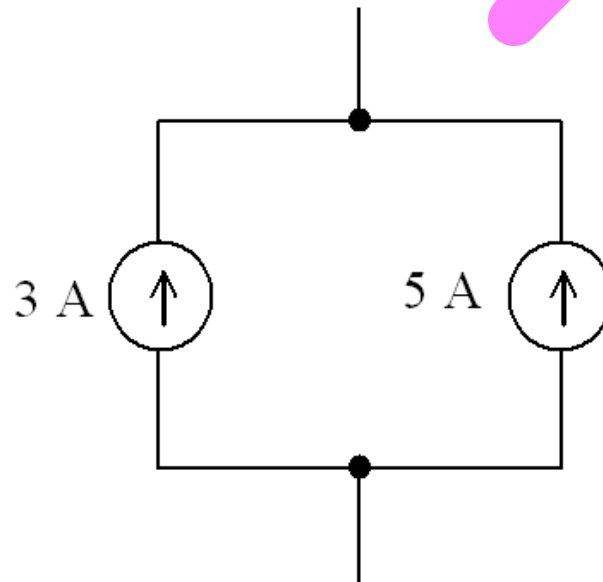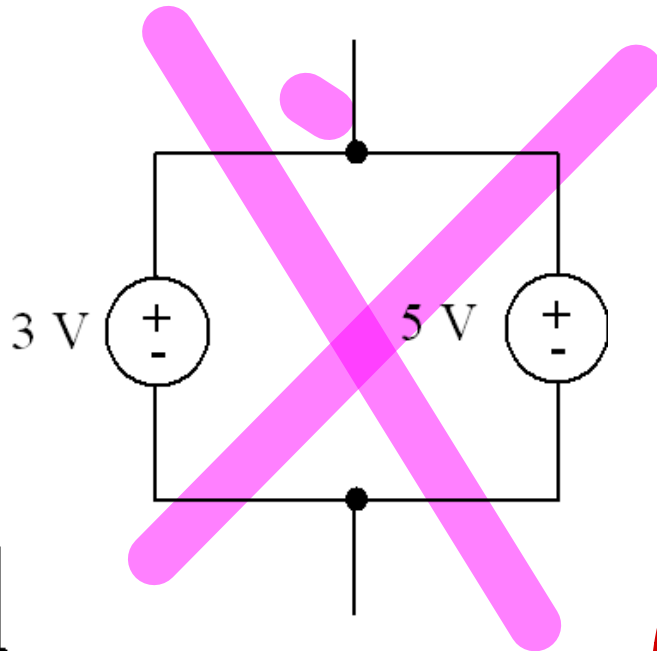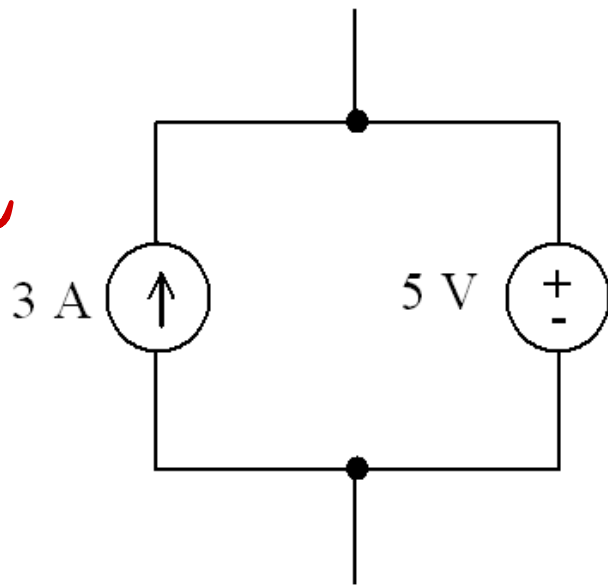


\uparrow 8A

How about resistors and sources?

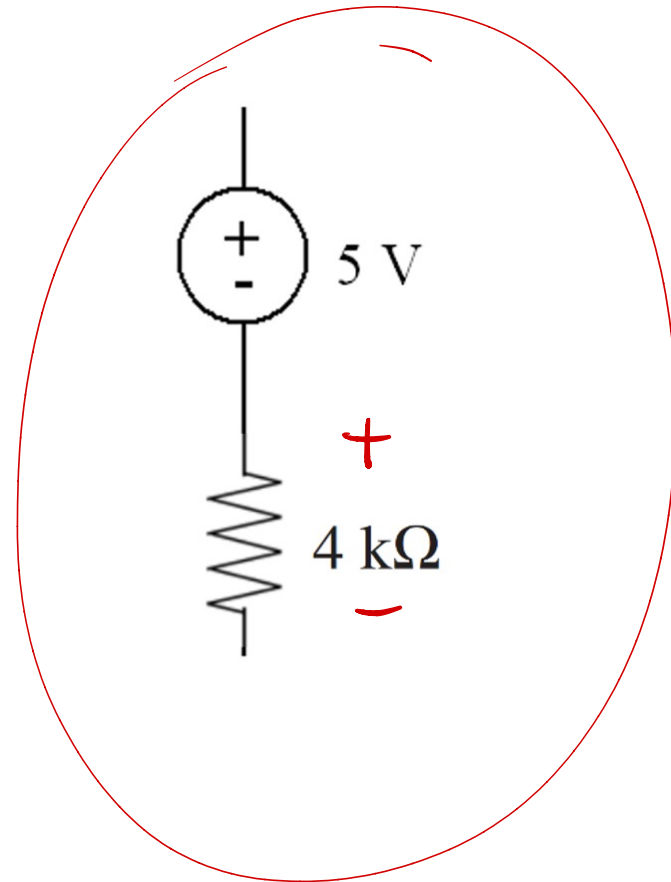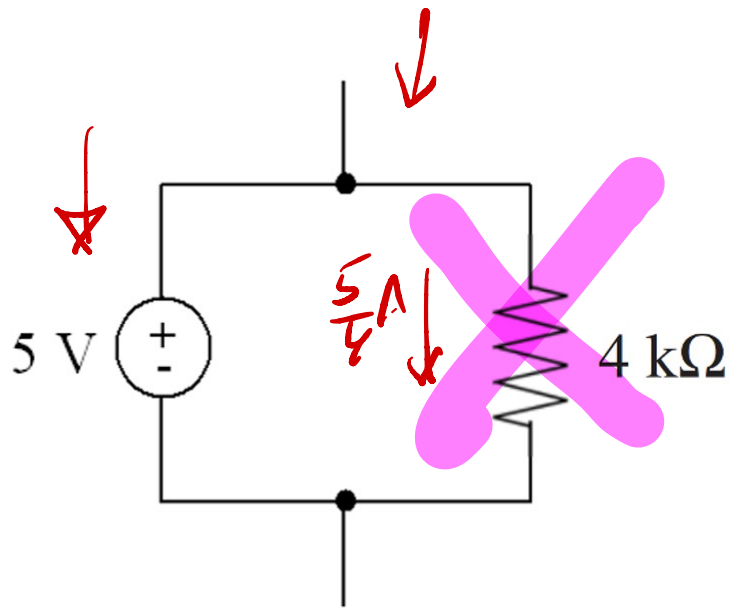


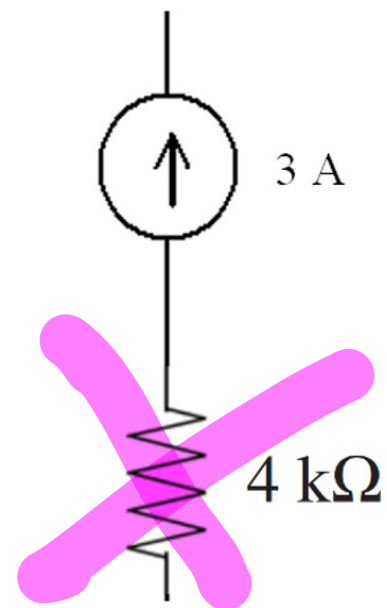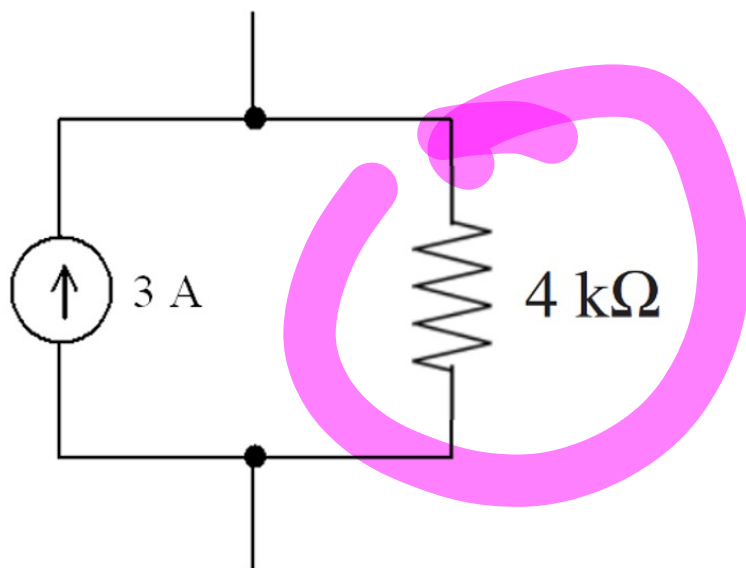

Example: find I

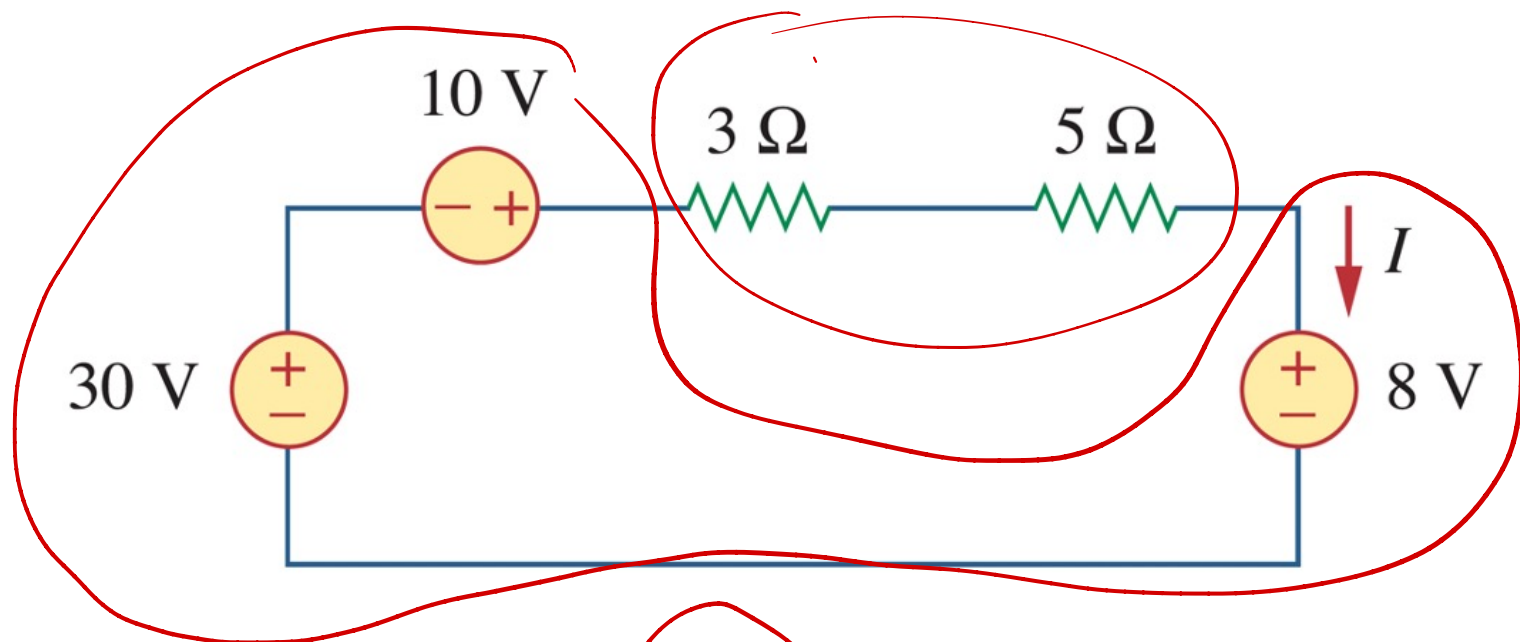


And now?

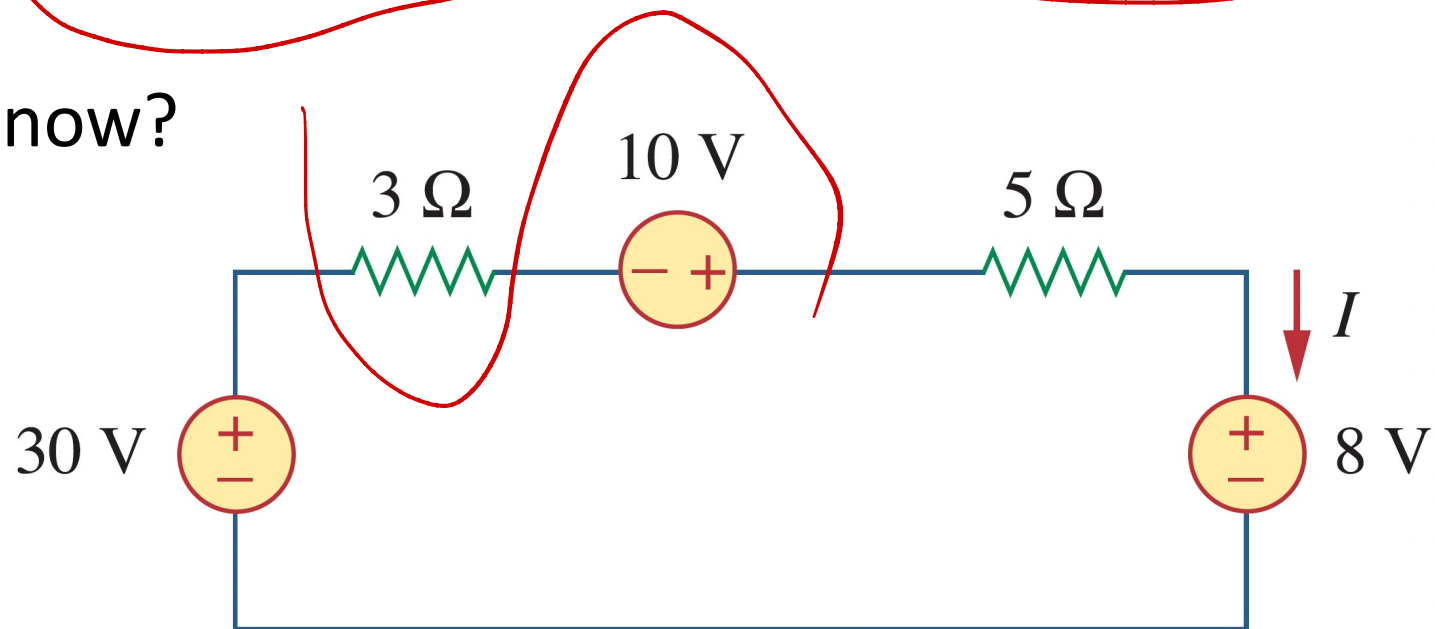

Time Varying Example

Consider this voltage division

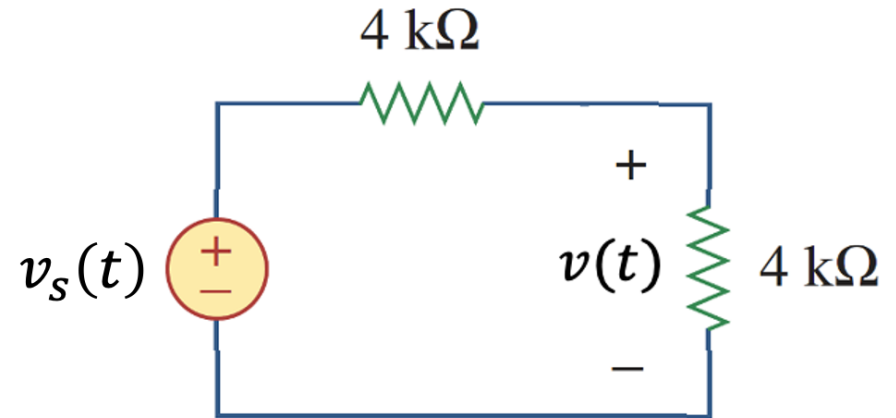

- $v_s(t) = 12\text{ V}$, then $v(t) = 6\text{ V}$
- If $v_s(t)$, then ???

